
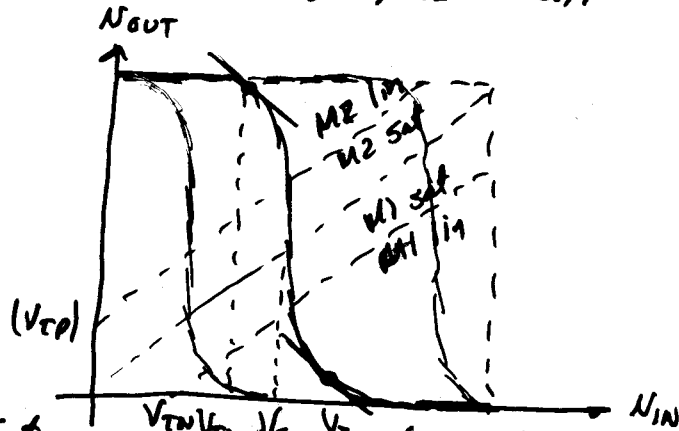


PROBLEM SESSION FOR EXAM 2

How can you determine whether a transistor is in saturation or the linear region when find V_{IH} , V_{IL} , V_{OL} and V_{OH} ?

CMOS Inverter -

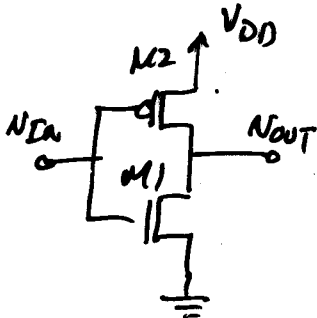

$N_{DS} > V_{DS}(sat) \Rightarrow Sat.$

$N_{DS} < V_{DS}(sat) \Rightarrow Lin.$

$N_{DS} = V_{DS}(sat)$

$V_{DS}(sat) = \frac{(V_{GS} - V_T) E_{CL}}{(V_{GS} - V_T) + E_{CL}}$

Short Channel

Long Channel $\leftarrow N_{DS}(sat) = V_{GS} - V_T$


$V_{IH} = ?$

V_{out} is low \leftarrow Assume that M1 is linear
 V_{in} is High $V_{GS} \cong V_{DD}$ M2 is sat

$V_{IL} = ?$

$V_{out} \cong V_{OL}$ $V_{in} = V_{GS} \cong 0 \leftarrow$ M1 is sat
 M2 is lin.

Ex. 4.7 Pseudo NMOS

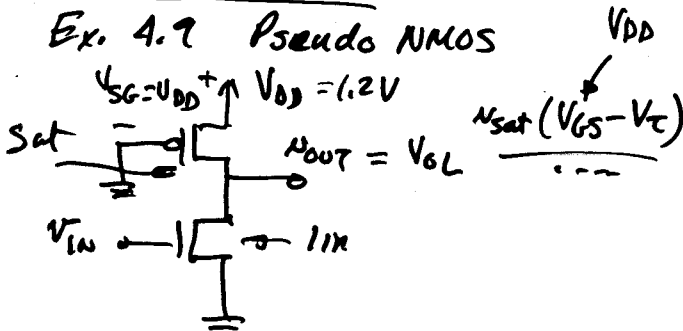

In Prob. 4.2a, the value of μ_e should be $270 \text{ cm}^2/\text{V}\cdot\text{s}$

No questions on flip-flops


Question on Exer. 5.4 (p. 220)

Why the "2" in

$$t_{PHL} = 0.7 (2 \times 125 \text{ k}\Omega / D) \frac{L}{W} (100 \text{ fF})$$

$$t_{PHL} = 0.7 R_{eff} C_L$$

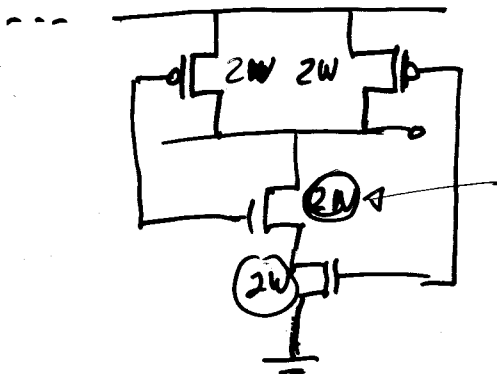Page 186, $R_{eqn} = 125 \text{ k}\Omega / \square \rightarrow R_n = R_{eqn} \times \frac{L}{W}$



Complex Logic Example

XOR $F = \bar{A}B + A\bar{B}$

NMOS Complex:

$$F = \overline{\bar{A}B + A\bar{B}} = \overline{\bar{A}B} \cdot \overline{A\bar{B}} \\ = (A + \bar{B}) \cdot (\bar{A} + B)$$



PMOS Complex:

Dual of F


$$= A\bar{B} + \bar{A}B$$

$$ab \Leftrightarrow a + b$$

$$(a+b)c \Leftrightarrow abc$$

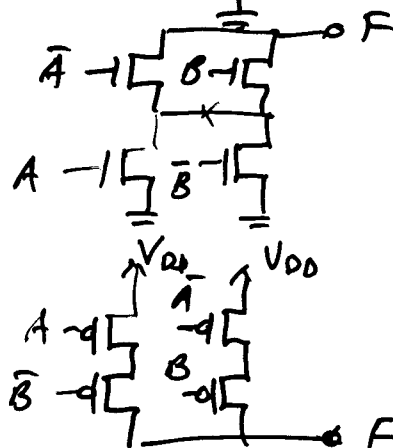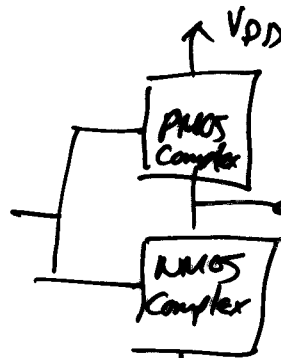

Example 5.1 - Sizing Transistors

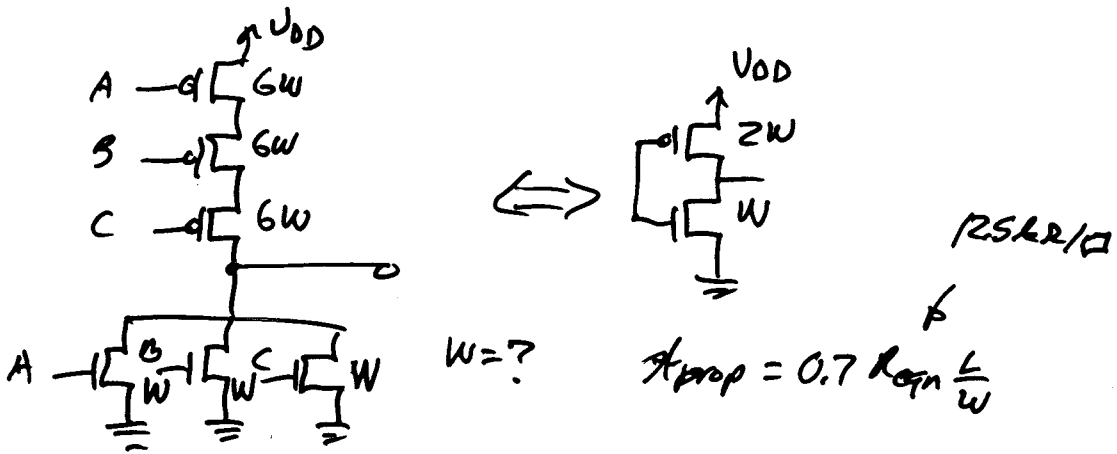

$W = ?$