

LECTURE 090 – MULTIPLE-STAGE FREQUENCY RESPONSE - I (READING: GHLM – 516-527)

Objective

The objective of this presentation is:

- 1.) Develop methods for the frequency analysis of multiple stage amplifiers
- 2.) Illustrate by examples

Outline

- Dominant Pole Approximation
- Zero-Value (Open-circuit) Time Constant Analysis
- Examples
- Short-Circuit Time Constants
- Examples
- Summary

Dominant Pole Approximation

If one of the poles is significantly closer to the origin of the complex frequency plane, its magnitude is a good approximation to the -3dB frequency.

Consider the following general transfer function:


$$A(s) = \frac{N(s)}{D(s)} = \frac{a_0 + a_1s + a_2s^2 + \dots + a_ms^m}{b_0 + b_1s + b_2s^2 + \dots + b_ns^n} = \frac{K}{\left(1 - \frac{s}{p_1}\right)\left(1 - \frac{s}{p_2}\right)\dots\left(1 - \frac{s}{p_n}\right)}$$

Equating denominator terms gives,

$$b_1 = -\frac{1}{p_1} - \frac{1}{p_2} \dots - \frac{1}{p_n} = \sum_{i=1}^n \left(-\frac{1}{p_i}\right)$$

If $|p_1| \ll |p_2|, |p_3|, \dots$ then $b_1 \approx -\frac{1}{p_1}$ and $\omega_{-3\text{dB}} \approx |p_1| = \frac{1}{b_1}$

Complex frequency plane:

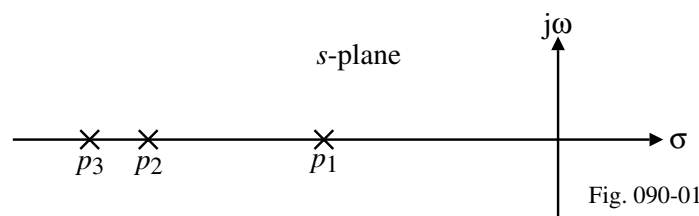

Open-Circuit Time Constant Analysis

This method is suitable for finding the dominant pole of a circuit with multiple capacitors.

Consider the following n -port network,

We may express the nodal equations as,

$$\begin{aligned} I_1 &= (g_{11} + sC_1)V_1 + g_{12}V_2 + g_{13}V_3 + \dots \\ I_2 &= g_{21}V_1 + (g_{22} + sC_2)V_2 + g_{23}V_3 + \dots \\ I_3 &= g_{31}V_1 + g_{32}V_2 + (g_{33} + sC_3)V_3 + \dots \\ &\vdots \\ &\vdots \end{aligned}$$

The determinant of the above can be expressed as

$$\Delta(s) = K_0 + K_1s + K_2s^2 + K_3s^3 = K_0(1 + b_1s + b_2s^2 + b_3s^3)$$

where $K_0 = \Delta(C_i = 0)$ for all $i \equiv \Delta_0$

Consider now the K_1 which involves a single capacitor and is given as

$$K_1 = h_1sC_1 + h_2sC_2 + h_3sC_3$$

The h_i terms can be evaluated by expanding the determinant about each row:

First row: $\Delta(s) = (g_{11} + sC_1)\Delta_{11} + g_{12}\Delta_{12} + g_{13}\Delta_{13} \Rightarrow h_1 = \Delta_{11}(C_i=0, i \neq 1)$

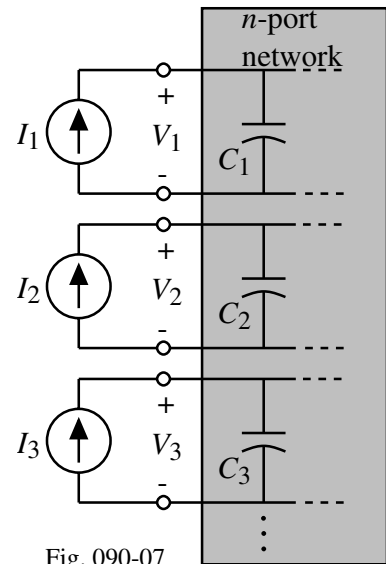


Fig. 090-07

Open-Circuit Time Constant Analysis - Continued

Second row: $\Delta(s) = g_{21}\Delta_{12} + (g_{22} + sC_2)\Delta_{22} + g_{23}\Delta_{23} \Rightarrow h_2 = \Delta_{22}(C_i=0, i \neq 2)$

Third row: $\Delta(s) = g_{31}\Delta_{31} + g_{32}\Delta_{32} + (g_{33} + sC_3)\Delta_{33} \Rightarrow h_3 = \Delta_{33}(C_i=0, i \neq 3)$

$\therefore K_1 = C_1\Delta_{11}(C_i=0, i \neq 1) + C_2\Delta_{22}(C_i=0, i \neq 2) + C_3\Delta_{33}(C_i=0, i \neq 3)$

Finally,

$$b_1 = \frac{K_1}{K_0} = \frac{\Delta_{11}(C_i=0, i \neq 1)}{\Delta_0} C_1 + \frac{\Delta_{22}(C_i=0, i \neq 2)}{\Delta_0} C_2 + \frac{\Delta_{33}(C_i=0, i \neq 3)}{\Delta_0} C_3$$

If we realize that the driving-point impedance of the i -th port are expressed as $\frac{V_i}{I_i} = \frac{\Delta_{11}}{\Delta(s)}$

then $R_{1o} = \frac{\Delta_{11}(C_i=0, i \neq 1)}{\Delta_0}$, $R_{2o} = \frac{\Delta_{22}(C_i=0, i \neq 2)}{\Delta_0}$, $R_{3o} = \frac{\Delta_{33}(C_i=0, i \neq 3)}{\Delta_0}$, ...

are the driving-point impedances at ports 1, 2, 3, ... with all capacitors set equal to zero.

$\therefore b_1 = R_{1o}C_1 + R_{2o}C_2 + R_{3o}C_3 + \dots$

where $R_{io}C_i$ are called the *open-circuit time constants*.

If there are no dominant zeros, then the dominant pole, p_1 , is given as

$$\omega_{-3dB} \approx |p_1| = \frac{1}{b_1} = \frac{1}{R_{1o}C_1 + R_{2o}C_2 + R_{3o}C_3 + \dots} = \frac{1}{\sum_{i=1}^n (R_{io}C_i)}$$

Example 1

A more exact model of the common-emitter BJT is shown below. Using the open-circuit time constant approach, find an expression for the -3dB frequency.

Solution

The procedure involves finding the open-circuit time constants.

R_{io} (Corresponds to C_i):

$$\therefore R_{io} = r_{\pi} \parallel (r_b + R_I)$$

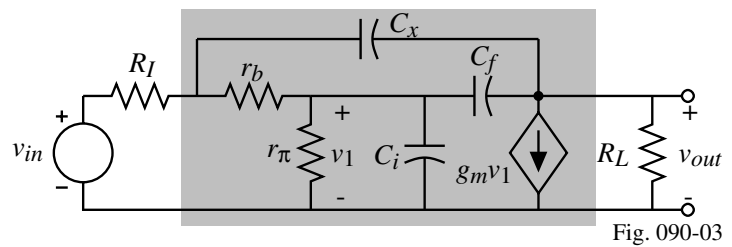


Fig. 090-03

R_{fo} (Corresponds to C_f):

$$V_t = I_t r_{\pi} \parallel (r_b + R_I) + (I_t + g_m V_1) R_L$$

$$V_1 = I_t r_{\pi} \parallel (r_b + R_I) = I_t R_{io}$$

$$\therefore V_t = I_t R_{io} + I_t R_L + I_t g_m R_{io} R_L$$

$$R_{fo} = R_{io} + R_L + g_m R_{io} R_L$$

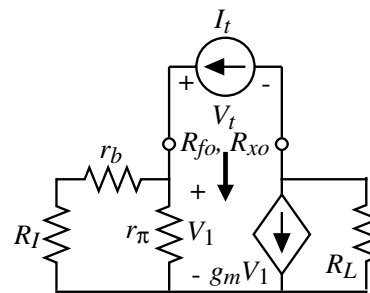
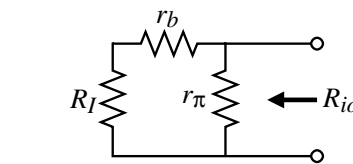


Fig. 090-04

Example 1 - Continued

R_{xo} (Corresponds to C_x):

$$V_t = I_t (r_{\pi} + r_b) \parallel R_I + (I_t + g_m V_1) R_L$$

$$V_1 = I_t [R_I r_{\pi} / (R_I + r_b + r_{\pi})]$$

$$\therefore V_t = I_t (r_{\pi} + r_b) \parallel R_I + I_t R_L + I_t g_m R_L [(r_{\pi} + r_b) \parallel R_I]$$

$$R_{xo} = (r_{\pi} + r_b) \parallel R_I + R_L + g_m [R_I r_{\pi} / (R_I + r_b + r_{\pi})] R_L$$

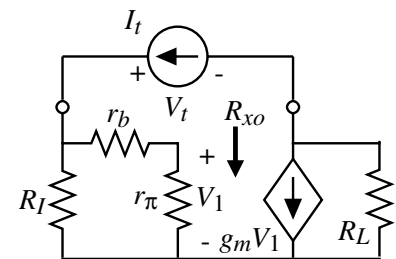


Fig. 090-05

$$\omega_{-3\text{dB}} \approx \frac{1}{R_{io} C_i + R_{fo} C_f + R_{xo} C_x}$$

$$\omega_{-3\text{dB}} = \frac{1}{r_{\pi} \parallel (r_b + R_I) C_i + (R_{io} + R_L + g_m R_{io} R_L) C_f + \{(r_{\pi} + r_b) \parallel R_I + R_L + g_m R_L [R_I r_{\pi} / (R_I + r_b + r_{\pi})]\} C_x}$$

$$\omega_{-3\text{dB}} \approx \frac{1}{r_{\pi} \parallel (r_b + R_I) C_i + [g_m R_L (r_{\pi} \parallel R_I)] (C_f + C_x)} \quad \text{if } r_b \rightarrow 0$$

Let $R_I = 1\text{k}\Omega$, $r_b = 200\Omega$, $I_C = 1\text{mA}$, $\beta_o = 100$, $f_T = 400\text{MHz}$ ($I_C = 1\text{mA}$), $C_{\mu} = 0.5\text{pF}$, $C_x = 0$, $R_L = 5\text{k}\Omega$, and find the -3dB frequency.

$$r_{\pi} = \frac{\beta_o}{g_m} = 100(26) = 2.6\text{k}\Omega, \quad \tau_T = \frac{1}{2\pi f_T} = 398\text{ps} \Rightarrow C_{\pi} = g_m \tau_T - C_{\mu} = 15.3\text{pF} - 0.5\text{pF} = 14.8\text{pF}$$

$$\therefore \omega_{-3\text{dB}} \approx \frac{10^{-9}}{2.6 \parallel 1.2(14.8) + (5000/26)(2.6 \parallel 1)0.5} = \frac{10^{-9}}{12.2 + 69.4} = 12.3 \times 10^6 \text{ rad/s (1.95MHz)}$$

Example 2 - Cascade Voltage-Amplifier Frequency Response

Calculate the -3dB frequency of the cascade voltage amplifier shown which has the following parameters:

$$R_I = 10\text{k}\Omega$$

$$R_{L1} = 10\text{k}\Omega$$

$$R_{L2} = 5\text{k}\Omega$$

$$C_{gs1} = 5\text{pF}$$

$$C_{gs2} = 10\text{pF}$$

$$C_{gd1} = C_{gd2} = 1\text{pF}$$

$$C_{bd1} = C_{bd2} = 2\text{pF}$$

$$g_{m1} = 3\text{mA/V}$$

$$g_{m2} = 6\text{mA/V}$$

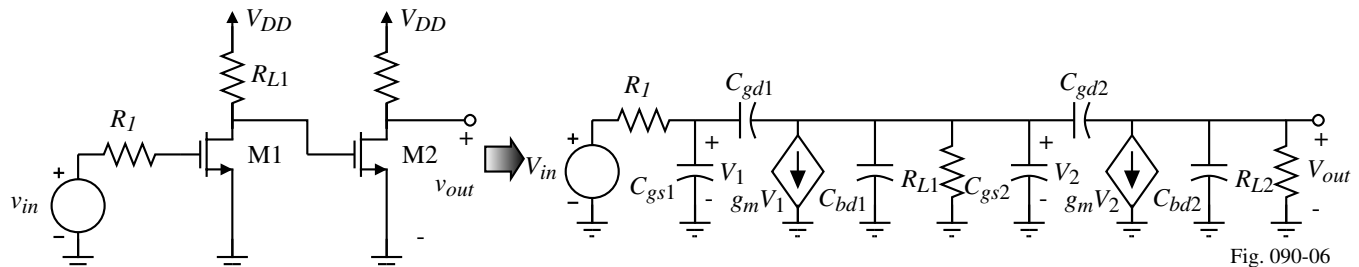


Fig. 090-06

Finding the open-circuit time constants:

$$C_{gs1}: R_{gs01} = R_I = 10\text{k}\Omega$$

$$C_{gs2}: R_{gs02} = R_{L1} = 10\text{k}\Omega$$

C_{gd1} : (Use the model to the right)

$$V_t = I_t R_I + (I_t + g_{m1} V_1) R_{L1} = I_t R_I + (I_t + g_{m1} I_t R_I) R_{L1}$$

$$\therefore R_{gd01} = \frac{V_t}{I_t} = R_I + R_{L1} + g_{m1} R_I R_{L1} = 20\text{k}\Omega + 300\text{k}\Omega = 320\text{k}\Omega$$

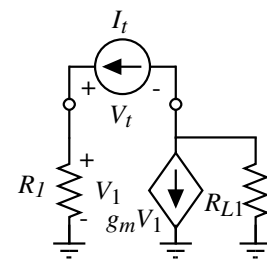


Fig. 090-07

Example 2 – Continued

C_{gd2} : (Can use the results of C_{gd1})

$$\therefore R_{gd02} = R_{L1} + R_{L2} + g_{m2} R_{L1} R_{L2} = 10\text{k}\Omega + 5\text{k}\Omega + 300\text{k}\Omega = 315\text{k}\Omega$$

$$C_{bd1}: R_{bd01} = R_{L1} = 10\text{k}\Omega$$

$$C_{bd2}: R_{bd02} = R_{L2} = 5\text{k}\Omega$$

$$\omega_{-3\text{dB}} \approx \frac{1}{\sum T_0} = \frac{1}{R_{gs01} C_{gs1} + R_{gs02} C_{gs2} + R_{gd01} C_{gd1} + R_{gd02} C_{gd2} + R_{bd01} C_{bd1} + R_{bd02} C_{bd2}}$$

$$= \frac{10^9}{10 \cdot 5 + 10 \cdot 10 + 320 \cdot 1 + 315 \cdot 1 + 10 \cdot 2 + 5 \cdot 2} = \frac{10^9}{815} = 1.227 \times 10^6 \text{ rad/s} \rightarrow f_{-3\text{dB}} = 195\text{kHz}$$

- Computer simulation gives poles at -205kHz , -4.02MHz , and -39.98MHz and two zeros at $+477\text{MHz}$ and $+955\text{MHz}$.
- How important is it for the circuit to have a dominant pole for the open-circuit time constant approach?

For a circuit with two identical poles, the -3dB frequency is

$$\omega_{-3\text{dB}} = \omega_x \sqrt{\sqrt{2} - 1} = 0.64 \omega_x$$

The open-circuit time constant approach gives

$$\omega_{-3\text{dB}} = \omega_x / 2 = 0.5 \omega_x \rightarrow 22\% \text{ error and is pessimistic}$$


Example 3 - Cascode Voltage-Amplifier Frequency Response

Calculate the -3dB frequency of the cascode voltage amplifier shown which has the following parameters:

$$\begin{aligned} R_I &= 10\text{k}\Omega \\ C_{gs2} &= 10\text{pF} \\ g_{m1} &= 3\text{mA/V} \end{aligned}$$

$$\begin{aligned} R_{L2} &= 10\text{k}\Omega \\ C_{gd1} &= C_{gd2} = 1\text{pF} \\ g_{m2} &= 6\text{mA/V} \end{aligned}$$
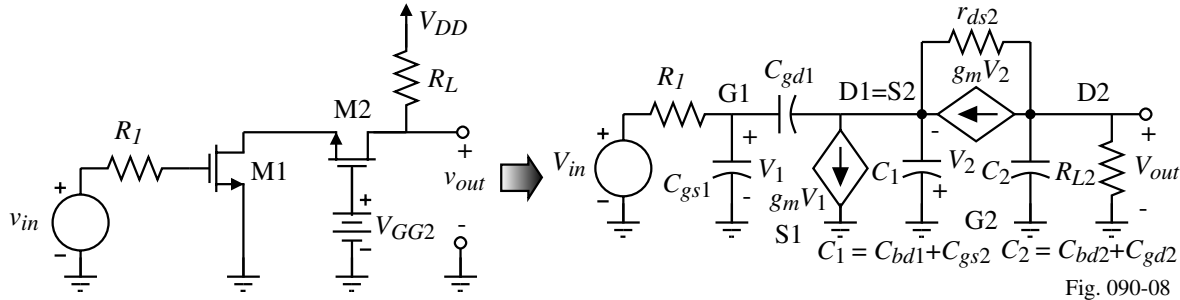
$$\begin{aligned} C_{gs1} &= 5\text{pF} \\ C_{bd1} &= C_{bd2} = 2\text{pF} \\ r_{ds2} &= 50\text{k}\Omega \end{aligned}$$




Finding the open-circuit time constants:

$$C_{gs1}: R_{gs01} = R_I = 10\text{k}\Omega$$

$$C_{gd1}: R_{gd01} = ?$$

$$V_t = I_t R_I + (I_t + g_{m1} V_1) R_{S2} = I_t R_I + (I_t + g_{m1} I_t R_I) R_{S2}$$

$$\therefore R_{gd01} = \frac{V_t}{I_t} = R_I + R_{S2} + g_{m1} R_I R_{S2} = R_I + R_{S2} (1 + g_{m1} R_I)$$

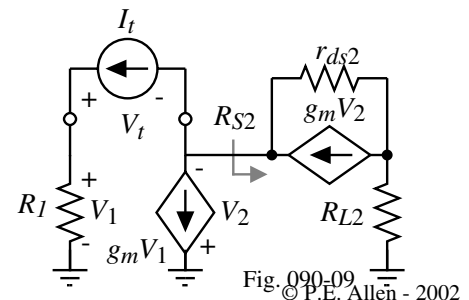

ECE 6412 - Analog Integrated Circuits and Systems II

Fig. 090-09 © P.E. Allen - 2002

Example 3 – Continued

But what is R_{S2} ?

Using the model shown, we see that

$$I_t = g_{m2} V_t \left(\frac{r_{ds2}}{r_{ds2} + R_{L2}} \right) \Rightarrow R_{S2} = \frac{V_t}{I_t} = \frac{r_{ds2} + R_{L2}}{g_{m2} r_{ds2}}$$

Note that unless $r_{ds2} \gg R_{L2}$ that R_{S2} is greater than $1/g_{m1}$.

$$\therefore R_{gd01} = R_I + (1 + g_{m1} R_I) \left(\frac{r_{ds2} + R_{L2}}{g_{m2} r_{ds2}} \right) = 10\text{k}\Omega + 31 \cdot 0.2\text{k}\Omega = 16.2\text{k}\Omega$$

$$C_1: R_{01} = R_{S2} = \frac{r_{ds2} + R_{L2}}{g_{m2} r_{ds2}} = 0.2\text{k}\Omega \quad C_2: R_{01} = R_{L2} = 10\text{k}\Omega$$

$$\omega_{-3\text{dB}} \approx \frac{1}{\sum T_0} = \frac{1}{R_{gs01} C_{gs1} + R_{gd01} C_{gd1} + R_{01} C_1 + R_{02} C_2}$$

$$= \frac{1}{R_{gs01} C_{gs1} + R_{gd01} C_{gd1} + R_{01} (C_{bd1} + C_{gs2}) + R_{02} (C_{bd2} + C_{gd2})}$$

$$= \frac{10^9}{10 \cdot 5 + 16.2 \cdot 1 + 0.2 \cdot 12 + 10 \cdot 3} = \frac{10^9}{64.8} = 15.43 \times 10^6 \text{ rad/s} \rightarrow f_{-3\text{dB}} = 2.46\text{MHz}$$

Note that the Miller effect, R_{gd01} , is less in the cascode amplifier ($16.2\text{k}\Omega$ compared with $320\text{k}\Omega$).

SUMMARY

- Developed the background for the open-circuit time constant analysis
 - Good for amplifiers with multiple capacitors
 - Works well if one of the poles is dominant, okay if not (pessimistic approx.)
- Illustrated the open-circuit time constant analysis
 - Cascaded MOSFET amplifier
 - Cascode MOSFET amplifier
- The input impedance to the cascoding stage depends on what is connected to the output of the cascoding stage.

$$R_{S2} = \frac{V_t}{I_t} = \frac{r_{ds2} + R_{L2}}{g_{m2} r_{ds2}}$$

We will continue the multiple amplifier analysis techniques in the following lecture.