

## LECTURE 100 – MULTIPLE-STAGE FREQUENCY RESPONSE - II (READING: GHLM – 527-537)

### Objective

The objective of this presentation is:

- 1.) Develop methods for the frequency analysis of multiple stage amplifiers
- 2.) Illustrate by examples

### Outline

- Dominant Pole Approximation
- Zero-Value (Open-circuit) Time Constant Analysis
- Examples
- Short-Circuit Time Constants
- Examples
- Summary

### Example 1 – Cascode Differential Amplifier

Calculate the low-frequency, small-signal voltage gain and the  $-3\text{dB}$  frequency of the circuit shown using the following data:

$$R_I = 1\text{k}\Omega$$

$$R_E = 75\Omega$$

$$R_3 = 4\text{k}\Omega$$

$$R_L = 1\text{k}\Omega$$

$$R_1 = 4\text{k}\Omega$$

$$R_2 = 10\text{k}\Omega$$

$$V_{CC} = -V_{EE} = 10\text{V}$$

$$\beta = 200$$

$$V_{BE(\text{on})} = 0.7\text{V}$$

$$\tau_F = 0.25\text{ns}$$

$$r_b = 200\Omega$$

$$r_c(\text{active}) = 150\Omega$$

$$C_{je0} = 1.3\text{pF}$$

$$C_{\mu0} = 0.6\text{pF}$$

$$\psi_{0c} = 0.6\text{V}$$

$$C_{cs0} = 2\text{pF}$$

$$\psi_{0s} = 0.58\text{V}$$

$$n_s = 0.5$$

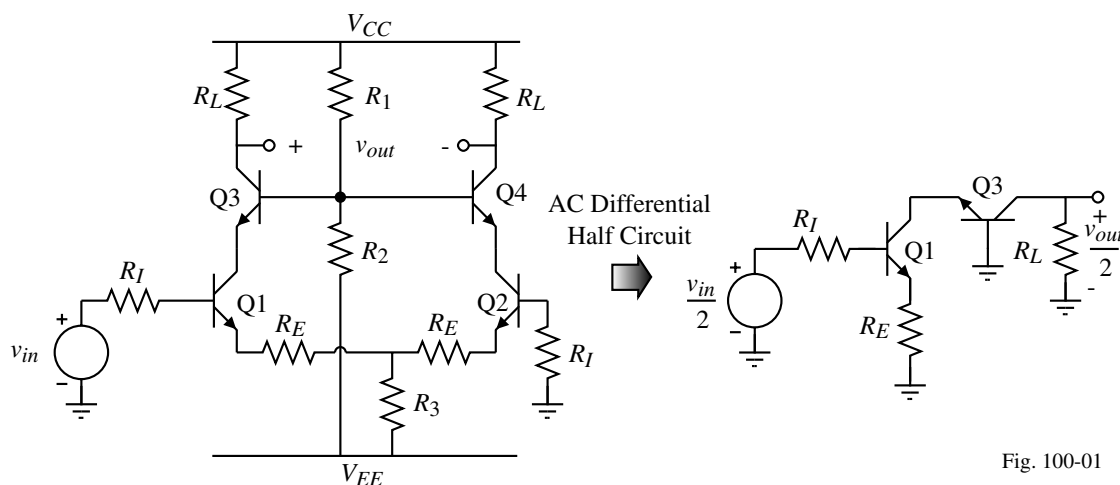


Fig. 100-01

**Example 1 – Continued**

DC Calculations:

$$V_{B3} = V_{CC} - \frac{R_1}{R_1 + R_2} (V_{CC} - V_{EE}) = 10 - \frac{4}{14} (20) = 4.3\text{V}$$

$$V_{C1} = V_{B3} - V_{BE3(\text{on})} = 3.6\text{V}$$

Assume the bases of Q1 and Q2 are at 0V,

$$I_{C1} = \frac{V_{EE} - V_{BE1(\text{on})}}{R_E + 2R_3} = \frac{10 - 0.7}{8.075} \text{ mA} = 1.15\text{mA}$$

$$V_{C3} = V_{CC} - I_{C1}R_L = 10\text{V} - 1.15\text{V} = 8.85\text{V}$$

Small-signal model:

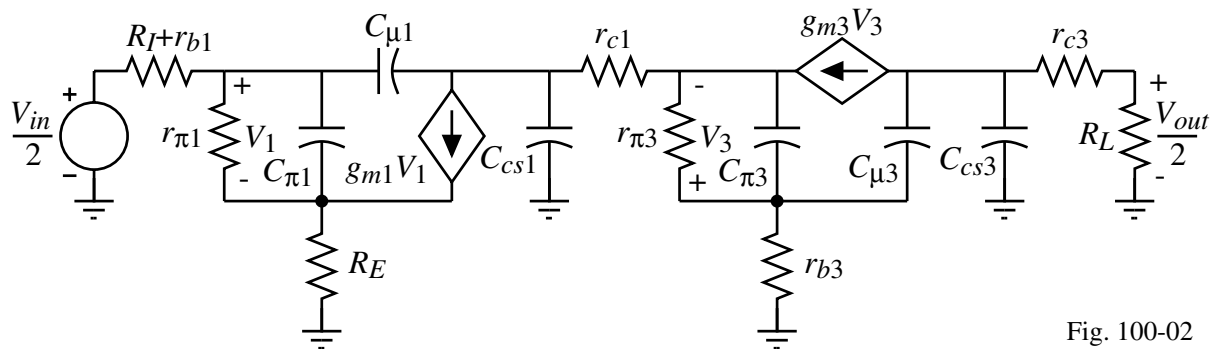


Fig. 100-02

**Example 1 – Continued**

The low-frequency gain is found as,

$$\frac{V_{out}}{V_{in}} \approx -\frac{R_{i1}}{R_{i1} + R_I} \frac{g_{m1} R_L}{1 + g_{m1} R_E} \quad \text{where } R_{i1} = r_{\pi 1} + (1 + \beta) R_E$$

$$g_{m1} = g_{m3} = \frac{1.15\text{mA}}{26\text{mV}} = 44.2\text{mA/V} \quad \text{and} \quad r_{\pi 1} = r_{\pi 3} = \frac{\beta}{g_m} = \frac{200}{44.2} \text{ k}\Omega = 4525\Omega$$

Thus,  $R_{i1} = 4.525\text{k}\Omega + 201(75\Omega) = 19.6\text{k}\Omega$ 

$$\therefore \frac{V_{out}}{V_{in}} \approx -\frac{19.6}{19.6 + 1.2} \frac{0.0442 \cdot 1000}{1 + 0.0442 \cdot 75} = -0.942 \cdot 10.24 = -9.65\text{V/V}$$

-3dB frequency:

First calculate the capacitances-

$$C_{je} \approx 2C_{je0} = 2.6\text{pF}, \quad C_{b1} = \tau_F g_m = 0.25 \times 10^{-9} \cdot 44.2 \times 10^{-3} = 11.1\text{pF}, \quad \therefore C_{\pi 1} = C_{b1} + C_{je1} = 13.7\text{pF}$$

Also,  $C_{\pi 3} = C_{\pi 1} = 13.7\text{pF}$  because the collector currents are equal.

$$C_{\mu 1}(V_{CB1} = 3.6\text{V}) = \frac{C_{\mu 0}}{\sqrt{1 + (V_{CB1}/\psi_{0c})}} = \frac{0.6}{\sqrt{1 + (3.6/0.6)}} \text{ pF} = 0.23\text{pF}$$

$$C_{cs1}(V_{CS1} = 13.6\text{V}) = \frac{C_{cs0}}{\sqrt{1 + (V_{CS1}/\psi_{0s})}} = \frac{2}{\sqrt{1 + (13.6/0.58)}} \text{ pF} = 0.40\text{pF}$$

**Example 1 – Continued**

$$C_{\mu 3}(V_{CB3}=8.85-4.3=4.55\text{V}) = \frac{C_{\mu 0}}{\sqrt{1+(V_{CB3}/\psi_{0c})}} = \frac{0.6}{\sqrt{1+(4.55/0.6)}} \text{ pF} = 0.20\text{pF}$$

$$C_{cs3}(V_{CS3}=18.85\text{V}) = \frac{C_{cs0}}{\sqrt{1+(V_{CS3}/\psi_{0s})}} = \frac{2}{\sqrt{1+(18.85/0.58)}} \text{ pF} = 0.35\text{pF}$$

Next, the O.C. time constants-

$R_{\pi 01}$ : Using the model shown, we get

$$I_t = \frac{V_t}{r_{\pi 1}} + \frac{V_t + V_E}{R_I + r_{b1}}$$

and 
$$I_t + \frac{V_E}{R_E} = \frac{V_t}{r_{\pi 1}} + g_{m1}V_t \rightarrow V_E = R_E \left( \frac{V_t}{r_{\pi 1}} + g_{m1}V_t - I_t \right)$$

Combining equations gives,

$$I_t \left( 1 + \frac{R_E}{R_I + r_{b1}} \right) = V_t \left( \frac{1}{r_{\pi 1}} + \frac{1}{R_I + r_{b1}} + \frac{R_E}{r_{\pi 1}(R_I + r_{b1})} + \frac{g_{m1}R_E}{R_I + r_{b1}} \right)$$


Multiplying through by  $r_{\pi 1}(R_I + r_{b1})$  gives,

$$I_t [r_{\pi 1}(R_I + r_{b1}) + r_{\pi 1}R_E] = V_t [R_I + r_{b1} + r_{\pi 1} + R_E + g_{m1}r_{\pi 1}R_E]$$

or

$$R_{\pi 01} = \frac{V_t}{I_t} = \frac{r_{\pi 1}(R_I + r_{b1} + R_E)}{R_I + r_{b1} + r_{\pi 1} + R_E(1 + \beta_1)} = \frac{4525(1000 + 200 + 75)}{1000 + 200 + 4525 + 75(1 + 200)} = 277\Omega$$

$$\therefore R_{\pi 01}C_{\pi 1} = 13.7 \cdot 0.277 \text{ ns} = 3.79\text{ns}$$

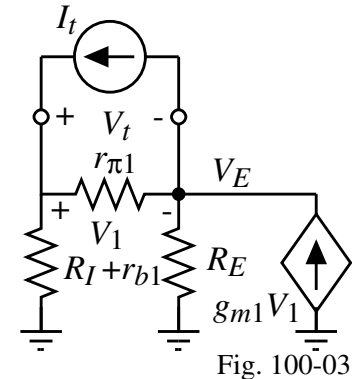
**Example 1 – Continued**

$R_{cs01}$ : This resistance is simply  $r_{c1}$  plus the input resistance to the CB stage,  $R_{i3}$ .

$$R_{i3} = \frac{1}{g_{m3}} + \frac{r_{b3}}{1 + \beta} = \frac{1}{0.0442} + \frac{200}{1 + 200} = 23.6\Omega \rightarrow R_{cs01} = 23.6 + 150 = 174\Omega$$

$$\therefore R_{cs01}C_{cs1} = 0.4 \cdot 0.174\text{ns} = 0.07\text{ns}$$

$R_{\mu 01}$ : Use the model shown.

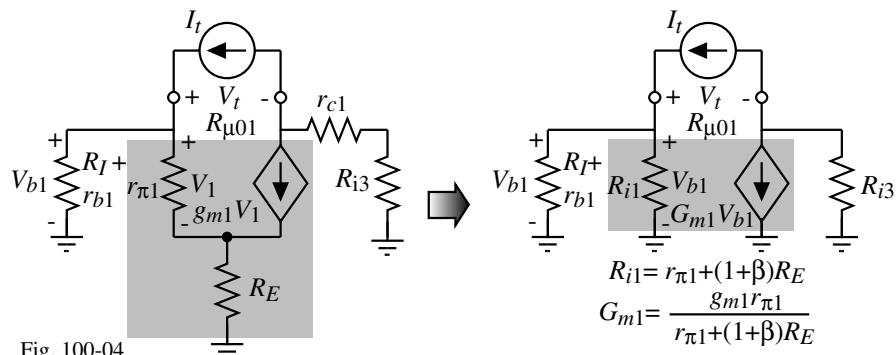

From previous work, we can write,

$$V_t = I_t R_{i1} \parallel (r_{b1} + R_I) + (I_t + G_{m1} V_{b1}) R_{cs01} \quad \text{and} \quad V_{b1} = I_t R_{i1} \parallel (r_{b1} + R_I)$$

$$\therefore V_t = I_t R_{i1} \parallel (r_{b1} + R_I) + I_t R_{cs01} + I_t G_{m1} [R_{i1} \parallel (r_{b1} + R_I)] R_{cs01}$$

$$R_{\mu 01} = R_{i1} \parallel (r_{b1} + R_I) + R_{cs01} + G_{m1} R_{cs01} [R_{i1} \parallel (r_{b1} + R_I)]$$

$$= 1131\Omega + 174\Omega + 0.0102 \cdot 174 \cdot 1131\Omega = 3.31\text{k}\Omega$$

$$\therefore R_{\mu 01}C_{\mu 1} = 0.23 \cdot 3.31\text{ns} = 0.76\text{ns}$$

**Example 1 – Continued**

$R_{\pi 03}$ : Use the model shown.

$$V_t = (I_t + g_{m3}V_3)r_{\pi 3} = I_t r_{\pi 3} + g_{m3}(-V_t)r_{\pi 3}$$

$$V_t(1 + g_{m3}r_{\pi 3}) = I_t r_{\pi 3}$$

$$R_{\pi 03} = \frac{V_t}{I_t} = \frac{r_{\pi 3}}{1 + \beta} = 22.5\Omega$$

$$\therefore R_{\pi 03}C_{\pi 3} = 13.7 \cdot 0.0023\text{ns} = 0.32\text{ns}$$

$R_{\mu 03}$ :

$$R_{\mu 03} = r_{b3} + r_{c3} + R_L = 200 + 150 + 1000 = 1350\Omega \rightarrow R_{\mu 03}C_{\mu 3} = 0.2 \cdot 1.35\text{ns} = 0.27\text{ns}$$

$R_{cs03}$ :

$$R_{cs03} = r_{c3} + R_L = 150 + 1000 = 1150\Omega \rightarrow R_{cs03}C_{cs3} = 0.35 \cdot 1.15\text{ns} = 0.4\text{ns}$$

Finally,

$$\Sigma T_0 = (3.79 + 0.07 + 0.76 + 0.32 + 0.27 + 0.4)\text{ns} = 5.61\text{ns} \quad (C_{\pi 1} \text{ is the limitation})$$

$$\omega_{-3\text{dB}} \approx \frac{1}{\Sigma T_0} = \frac{1000 \times 10^6}{5.61} = 178.25 \times 10^6 \rightarrow f_{-3\text{dB}} = 28.4\text{MHz}$$

(Computer simulation shows 6 poles with the lowest two of  $-35.8\text{MHz}$  and  $-253\text{MHz}$  resulting in a  $f_{-3\text{dB}} = 34.7\text{MHz}$ )

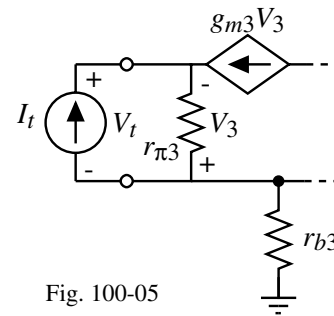


Fig. 100-05

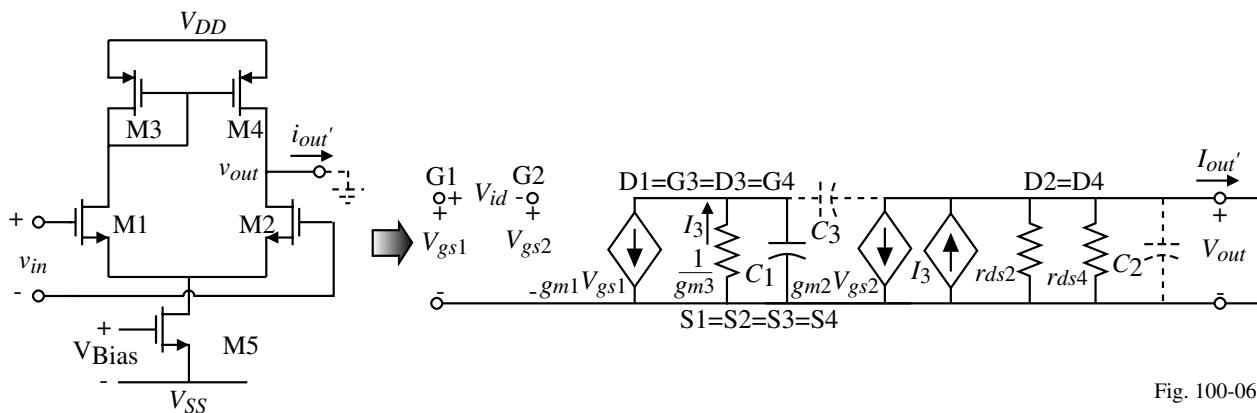
**Frequency Response of Current-Mirror Load Differential Amplifier**

Fig. 100-06

$$I_{out}' = I_3 - g_{m2}V_{gs2} = -\left(\frac{1}{sC_1}\right)g_{m1}V_{gs1} - g_{m2}V_{gs2} = -\left(\frac{1}{\frac{C_1}{s g_{m3}} + 1}\right)g_{m1}\frac{V_{in}}{2} - g_{m2}\frac{V_{in}}{2}$$

$$I_{out}' = -g_{md}\left(\frac{\frac{C_1}{s g_{m3}} + 2}{\frac{C_1}{s g_{m3}} + 1}\right)\frac{V_{in}}{2} = -g_{md}\left(\frac{s2g_{m3} + 2}{\frac{C_1}{s g_{m3}} + 1}\right)V_{in} \quad \text{where } g_{m1} = g_{m2} = g_{md}$$

The circuit has a zero at  $-2g_{m3}/C_1$  and a pole at  $-g_{m3}/C_1$ .

(These roots are not dominant,  $C_2$  will cause the  $-3\text{dB}$  frequency.)

## Short-Circuit Time Constants

- Short-circuit time constants are used to identify the *largest* pole of a multipole system
- The short-circuit time constant approach is not very useful for IC circuits because they are dc-coupled (lowest root is most important).
- The short-circuit time constant approach is useful for larger of a two-pole system.

Derivation:

Based on,

$$\begin{aligned} I_1 &= (g_{11} + sC_1)V_1 + g_{12}V_2 + g_{13}V_3 + \dots \\ I_2 &= g_{21}V_1 + (g_{22} + sC_2)V_2 + g_{23}V_3 + \dots \\ I_3 &= g_{31}V_1 + g_{32}V_2 + (g_{33} + sC_3)V_3 + \dots \\ &\vdots \\ &\vdots \end{aligned}$$

The determinant can be expressed as,

$$\begin{aligned} \Delta(s) &= K_0 + K_1s + K_2s^2 + K_3s^3 = K_3 \left( s^3 + \frac{K_2}{K_3}s^2 + \frac{K_1}{K_3}s + \frac{K_0}{K_3} \right) \\ \Delta(s) &= K_3(s-p_1)(s-p_2)(s-p_3) = K_3[s^3 - s^2(p_1+p_2+p_3) + s(p_1p_3 + p_2p_3) - p_1p_2p_3] \\ \therefore \frac{K_2}{K_3} &= -(p_1+p_2+p_3) = -\sum_{i=1}^3 p_i \end{aligned}$$

## Short-Circuit Time Constants – Continued

We know that,  $K_3 = C_1C_2C_3$  and  $K_2 = g_{11}C_2C_3 + g_{22}C_1C_3 + g_{33}C_1C_2$

$$\therefore \frac{K_2}{K_3} = \frac{g_{11}}{C_1} + \frac{g_{22}}{C_2} + \frac{g_{33}}{C_3} = \frac{1}{r_{11}C_1} + \frac{1}{r_{22}C_2} + \frac{1}{r_{33}C_3}$$

where  $r_{ii}C_i = \tau_{si}$  ( $i = 1, 2, 3$ ) are called the *short-circuit time constants* and  $r_{ii}$  is given as,

$$r_{11} = \frac{1}{g_{11}} = \frac{V_1}{I_1} \Big|_{V_2=V_3=0, C_1=0}, \quad r_{22} = \frac{1}{g_{22}} = \frac{V_2}{I_2} \Big|_{V_1=V_3=0, C_2=0}, \quad \text{and} \quad r_{33} = \frac{1}{g_{33}} = \frac{V_3}{I_3} \Big|_{V_1=V_2=0, C_3=0}$$

Therefore, if a circuit has  $n$  poles and  $|p_n| > |p_1|$ ,  $|p_n| > |p_2|$ ,  $|p_n| > |p_3|$ , ... then

$$p_n \approx \sum_{i=1}^n p_i = -\sum_{i=1}^n \frac{1}{\tau_{si}} = -\sum_{i=1}^n \frac{1}{r_{ii}C_i}$$

The most useful application of this idea is to find  $p_2$  where  $|p_2| > |p_1|$ .

**Example 2**

Consider the circuit shown below where  $R_I = 10\text{k}\Omega$ ,  $R_L = 10\text{k}\Omega$ ,  $g_m = 3\text{mS}$ ,  $C_i = 1\text{pF}$ , and  $C_f = 20\text{pF}$ .

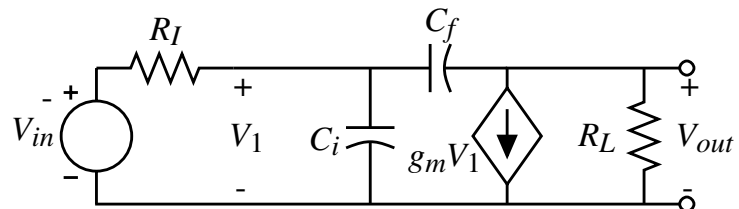


Fig. 100-07

The open-circuit time constants are:

$$\tau_{of} = C_f R_{fo} = C_f (R_I + R_L + g_m R_L R_I) = 20\text{pf}(10+10+30 \cdot 10)\text{k}\Omega = 6.4\mu\text{s}$$

$$\tau_{oi} = C_i R_{io} = C_i R_I = 1\text{pF}(10\text{k}\Omega) = 10\text{ns}$$

$$\therefore p_1 \approx \frac{-1}{6.4\mu\text{s} + 0.01\mu\text{s}} = -156\text{krad/s}$$

The short-circuit time constants are:

$$\tau_{sf} = C_f R_L = 20\text{pf}(10\text{k}\Omega) = 200\text{ns}$$

$$\tau_{si} = C_i [R_I \parallel (1/g_m) \parallel R_L] = 1\text{pf}(10 \parallel 0.33 \parallel 10) = 0.312\text{ns}$$

$$\therefore p_2 \approx -\left(\frac{1}{200\text{ns}} + \frac{1}{0.312\text{ns}}\right) = -3.21\text{Grad/s}$$

Exact analysis gives  $p_1 = -156\text{krad/s}$  and  $p_2 = -3.20\text{Grad/s}$

**SUMMARY**

- Exact methods of finding the poles of a circuit include:
  - Matrix methods
  - Simulation
- Approximate methods of finding the poles of a circuit include:
  - Miller approximation
  - Dominant pole approximation, good for  $-3\text{dB}$  frequency
  - Open-circuit time constants, good for finding the smallest pole of a multi-pole circuit
  - Short-circuit time constants, good for finding the largest pole of a multi-pole circuit

For these methods to work well, the poles should not be closely spaced
- Probably the most important result is the information the above methods provide for the design of the circuit to achieve a given frequency performance
- We will come back to the frequency analysis of the 741 later