

LECTURE 110 – INTRODUCTION AND CHARACTERIZATION OF THE OP AMP

(READING: GHLM – 404-424, AH – 243-249)

Objective

The objective of this presentation is:

- 1.) Introduce and characterize the op amp

Outline

- Static characteristics of the op amp
- Dynamic characteristics of the op amp
- Op amp architecture
 - Two stage
 - Folded-cascode
- Summary

INTRODUCTION AND CHARACTERIZATION OF OP AMPS

High-Level Viewpoint of an Op Amp

Block diagram of a general, two-stage op amp:

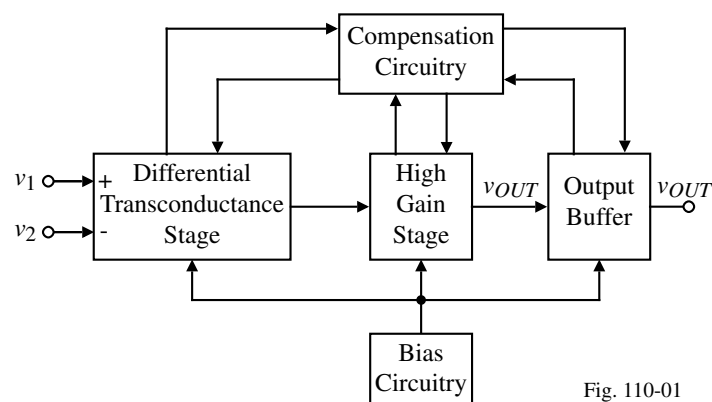


Fig. 110-01

- **Differential transconductance stage:**
Forms the input and sometimes provides the differential-to-single ended conversion.
- **High gain stage:**
Provides the voltage gain required by the op amp together with the input stage.
- **Output buffer:**
Used if the op amp must drive a low resistance.
- **Compensation:**
Necessary to keep the op amp stable when resistive negative feedback is applied.

Ideal Op Amp

Symbol:

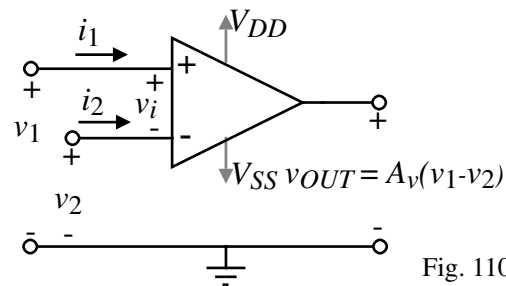


Fig. 110-02

Null port:

If the differential gain of the op amp is large enough then input terminal pair becomes a null port.

A null port is a pair of terminals where the voltage is zero and the current is zero.

I.e.,

$$v_1 - v_2 = v_i = 0$$

and

$$i_1 = 0 \text{ and } i_2 = 0$$

Therefore, ideal op amps can be analyzed by assuming the differential input voltage is zero and that no current flows into or out of the differential inputs.

General Configuration of the Op Amp as a Voltage Amplifier

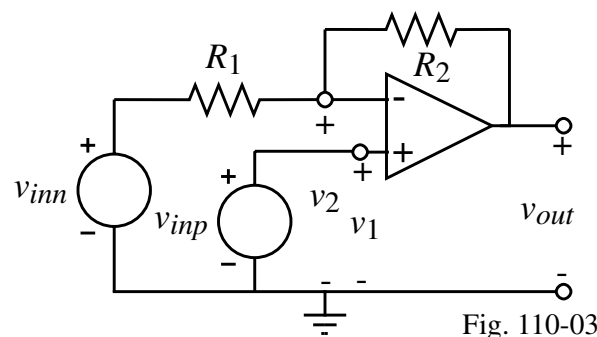


Fig. 110-03

Noninverting voltage amplifier:


$$v_{inn} = 0 \quad \Rightarrow \quad v_{out} = \left(\frac{R_1 + R_2}{R_1} \right) v_{inp}$$

Inverting voltage amplifier:

$$v_{inp} = 0 \quad \Rightarrow \quad v_{out} = - \left(\frac{R_2}{R_1} \right) v_{inn}$$

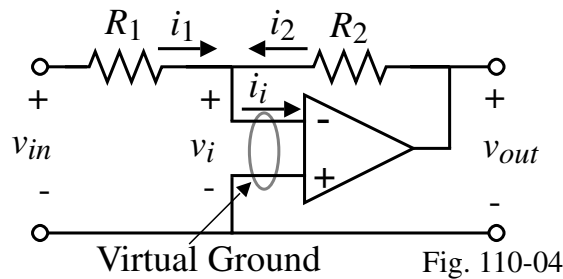Example 1 - Simplified Analysis of an Op Amp Circuit

The circuit shown below is an inverting voltage amplifier using an op amp. Find the voltage transfer function, v_{out}/v_{in} .



Solution

If $A_v \rightarrow \infty$, then $v_i \rightarrow 0$ because of the negative feedback path through R_2 .

(The op amp with $-fb.$ makes its input terminal voltages equal.)

$$v_i = 0 \text{ and } i_i = 0$$

Note that the null port becomes the familiar *virtual ground* if one of the op amp input terminals is on ground. If this is the case, then we can write that

$$i_1 = \frac{v_{in}}{R_1} \quad \text{and} \quad i_2 = \frac{v_{out}}{R_2}$$

Since, $i_i = 0$, then $i_1 + i_2 = 0$ giving the desired result as $\frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1}$.

Linear and Static Characterization of the Op Amp

A model for a nonideal op amp that includes some of the linear, static nonidealities:

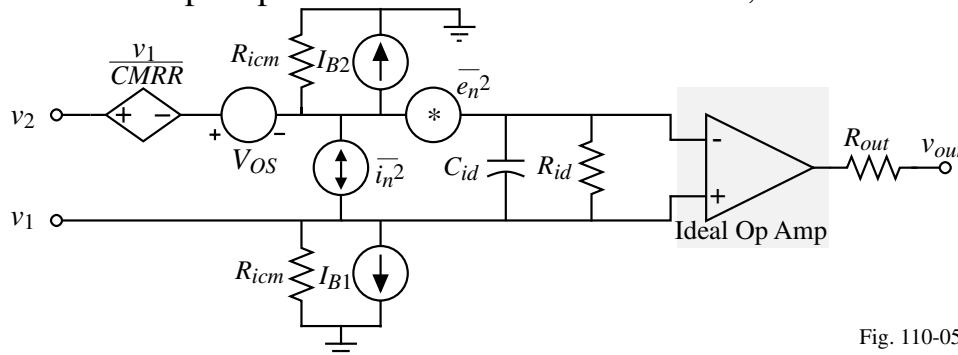


Fig. 110-05

where

R_{id} = differential input resistance

C_{id} = differential input capacitance

R_{icm} = common mode input resistance

V_{OS} = input-offset voltage

I_{B1} and I_{B2} = differential input-bias currents

I_{OS} = input-offset current ($I_{OS} = I_{B1} - I_{B2}$)

$CMRR$ = common-mode rejection ratio

e_n^2 = voltage-noise spectral density (mean-square volts/Hertz)

i_n^2 = current-noise spectral density (mean-square amps/Hertz)

Linear and Dynamic Characteristics of the Op Amp

Differential and common-mode frequency response:

$$V_{out}(s) = A_v(s)[V_1(s) - V_2(s)] \pm A_c(s) \left(\frac{V_1(s) + V_2(s)}{2} \right)$$

Differential-frequency response:

$$A_v(s) = \frac{A_{v0}}{\left(\frac{s}{p_1} - 1 \right) \left(\frac{s}{p_2} - 1 \right) \left(\frac{s}{p_3} - 1 \right) \dots} = \frac{A_{v0} p_1 p_2 p_3 \dots}{(s - p_1)(s - p_2)(s - p_3) \dots}$$

where p_1, p_2, p_3, \dots are the poles of the differential-frequency response (ignoring zeros).

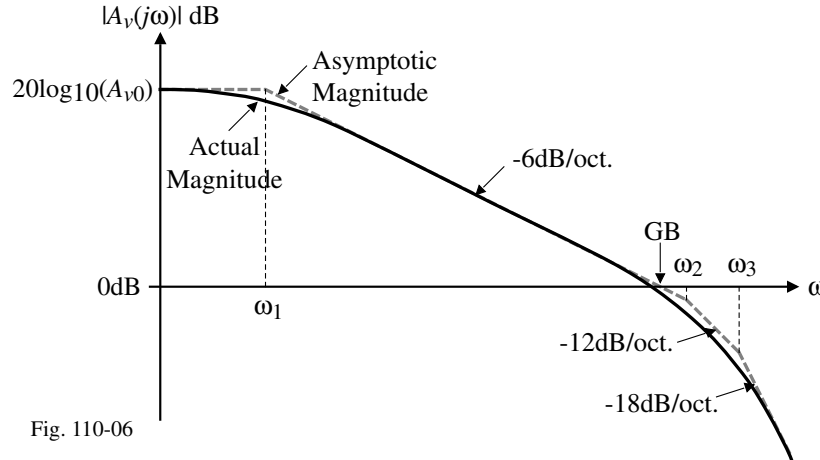


Fig. 110-06

Other Characteristics of the Op Amp

Power supply rejection ratio (*PSRR*):

$$PSRR = \frac{\Delta V_{DD}}{\Delta V_{OUT}} A_v(s) = \frac{V_o/V_{in} (V_{dd} = 0)}{V_o/V_{dd} (V_{in} = 0)}$$

Input common mode range (*ICMR*):

ICMR = the voltage range over which the input common-mode signal can vary without influence the differential performance

Slew rate (*SR*):

SR = output voltage rate limit of the op amp

Settling time (T_s):

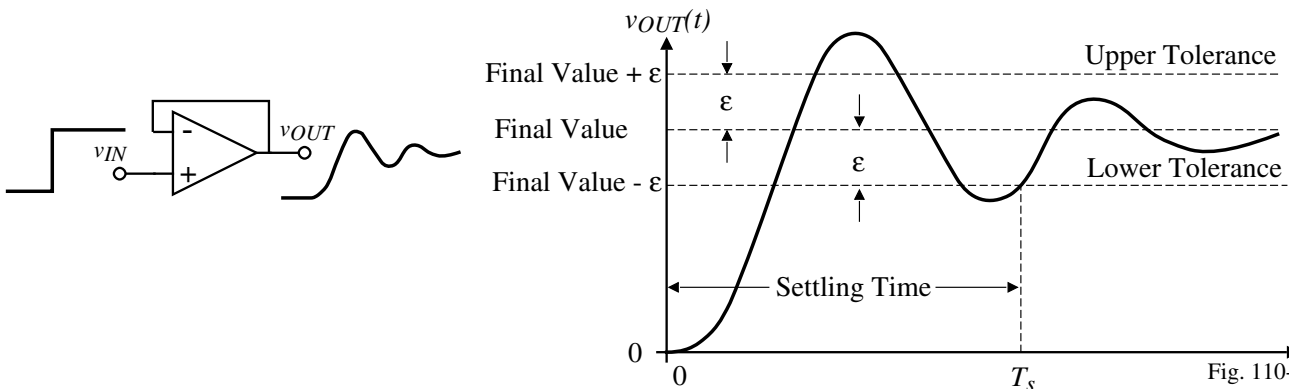


Fig. 110-07

Classification of CMOS Op Amps

Categorization of op amps:

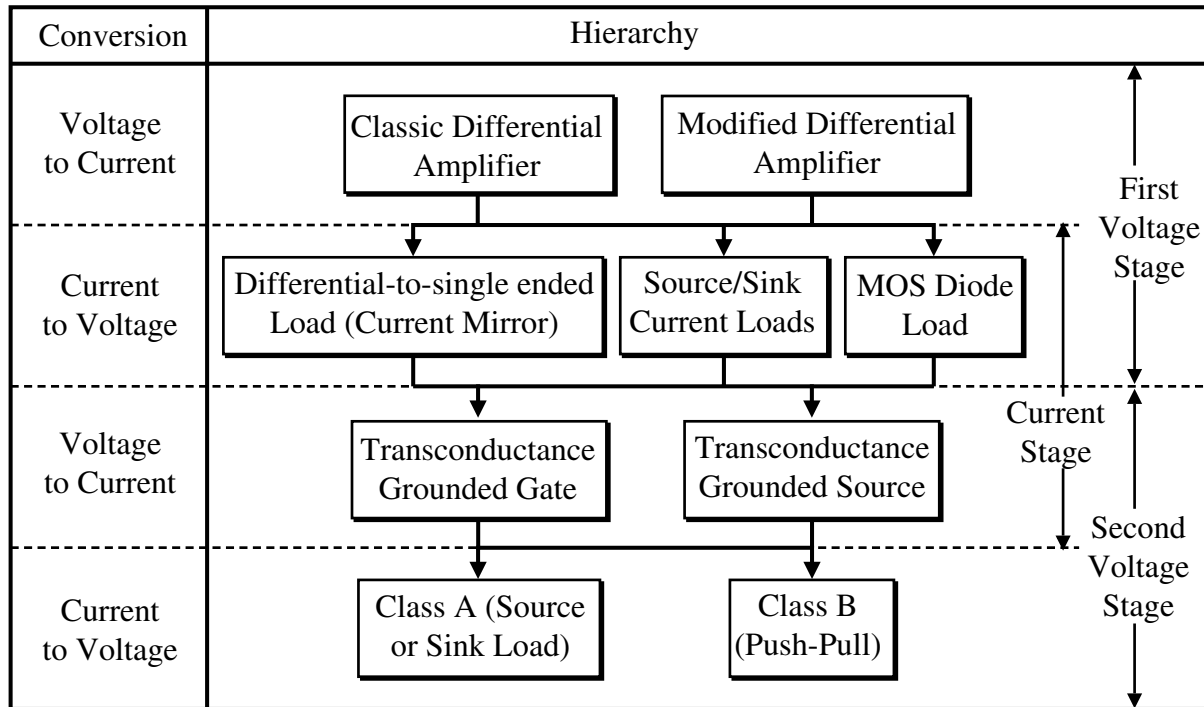


Table 110-01

Two-Stage Op Amp Architecture

Simple two-stage op amp broken into voltage-to-current and current-to-voltage stages:


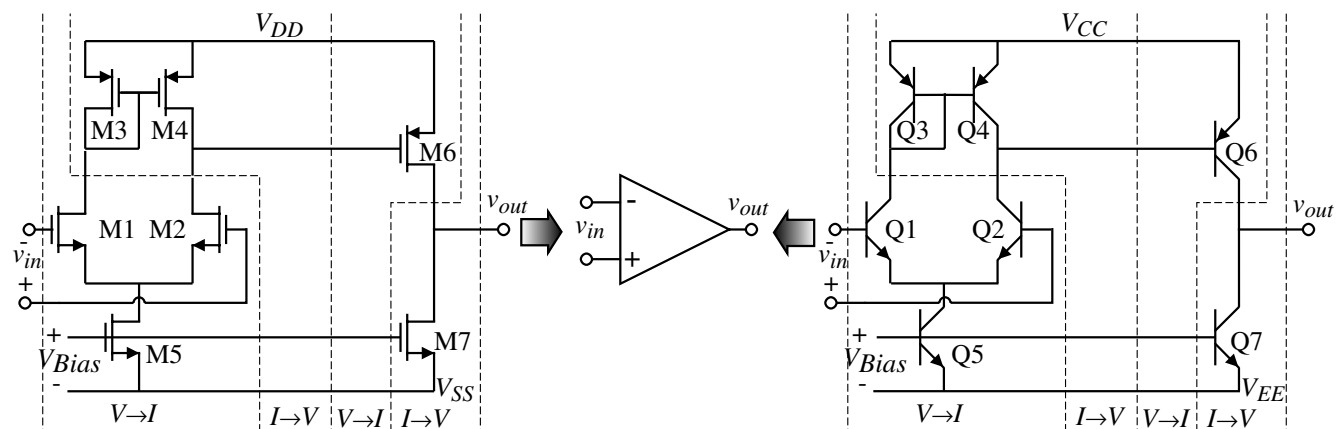


Fig. 110-08

Folded-Cascode Op Amp Architecture

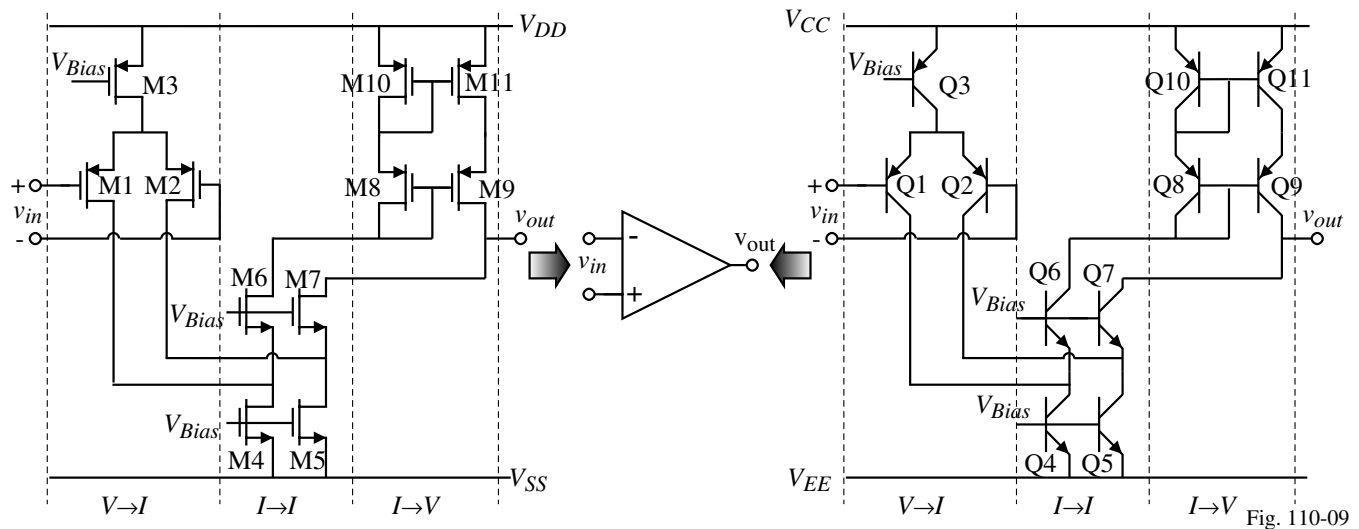Simple folded-cascode op amp broken into voltage-to-current and current-to-voltage stages:



SUMMARY

- The op amp is an amplifier whose gain approaches ∞
 - The input is a null port which is useful for analysis
 - Two classical op amp configurations – noninverting and inverting amplifier
- Static characteristics include offsets, bias currents, finite resistance, and noise
- Dynamic characteristics include frequency, slew rate, transient response, etc.
- Basic op amp architectures are,
 - Two-stage
 - Cascode and folded-cascode