

# LECTURE 170 – INTUITIVE ANALYSIS OF ANALOG CIRCUITS

**(READING: AH – 191-193)**

## **Objective**

The objective of this presentation is:

- 1.) Illustrate how to perform a small-signal, midband analysis from the schematic
- 2.) Introduce the Miller technique and the approximate method of solving for two poles

## **Outline**

- Key concepts in CMOS analog IC circuit analysis
- Intuitive approach
- Examples
- Summary

## **IMPORTANT RELATIONSHIPS FOR CMOS ANALOG IC DESIGN**

- 1.) Square law relationship:

$$i_D = \frac{K'W}{2L} (v_{GS} - V_T)^2$$

- 2.) Small-signal transconductance formula:

$$g_m = \sqrt{\frac{2K'WI_D}{L}}$$

- 3.) Small-signal simplification:

$$g_m \approx 10g_{mbs} \approx 100g_{ds}$$

- 4.) Saturation relationship:

$$V_{DS(\text{sat})} = \sqrt{\frac{2I_D}{K'(W/L)}}$$

## An Intuitive Method of Small Signal Analysis

Small signal analysis is used so often in analog circuit design that it becomes desirable to find faster ways of performing this important analysis.

### Intuitive Analysis (or Schematic Analysis)

Technique:

- 1.) Identify the transistor(s) that convert the input voltage to current (these transistors are called *transconductance transistors*).
- 2.) Trace the currents to where they flow into an equivalent resistance to ground.
- 3.) Multiply this resistance by the current to get the voltage at this node to ground.
- 4.) Repeat this process until the output is reached.

Simple Example:

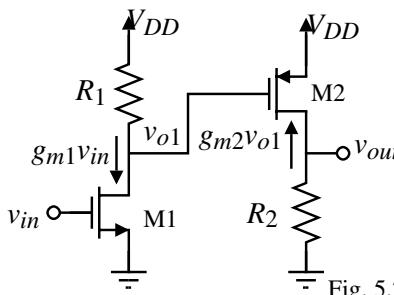


Fig. 5.2-10C

$$v_{o1} = -(g_m1 v_{in}) R_1 \rightarrow v_{out} = -(g_m2 v_{o1}) R_2 \rightarrow v_{out} = (g_m1 R_1 g_m2 R_2) v_{in}$$

## Intuitive Analysis of the Current-Mirror Load Differential Amplifier

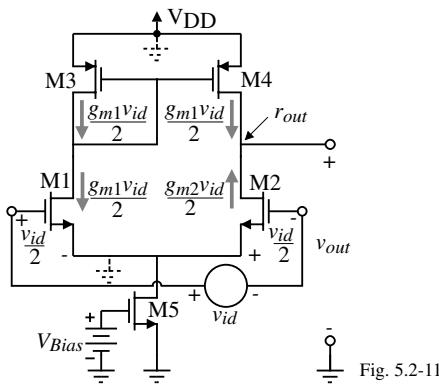


Fig. 5.2-11

- 1.)  $i_1 = 0.5g_m1v_{id}$  and  $i_2 = -0.5g_m2v_{id}$
- 2.)  $i_3 = i_1 = 0.5g_m1v_{id}$
- 3.)  $i_4 = i_3 = 0.5g_m1v_{id}$
- 4.) The resistance at the output node,  $r_{out}$ , is  $r_{ds2}||r_{ds4}$  or  $\frac{1}{g_{ds2} + g_{ds4}}$
- 5.)  $\therefore v_{out} = (0.5g_m1v_{id} + 0.5g_m2v_{id})r_{out} = \frac{g_m1v_{in}}{g_{ds2} + g_{ds4}} = \frac{g_m2v_{in}}{g_{ds2} + g_{ds4}} \Rightarrow \frac{v_{out}}{v_{in}} = \frac{g_m1}{g_{ds2} + g_{ds4}}$

## Some Concepts to Help Extend the Intuitive Method of Small-Signal Analysis

- 1.) Approximate the output resistance of any cascode circuit as

$$R_{out} \approx (g_m r_{ds2}) r_{ds1}$$

where M1 is a transistor cascoded by M2.

- 2.) If there is a resistance,  $R$ , in series with the source of the transconductance transistor, let the effective transconductance be

$$g_m(eff) = \frac{g_m}{1+g_m R}$$

Proof:

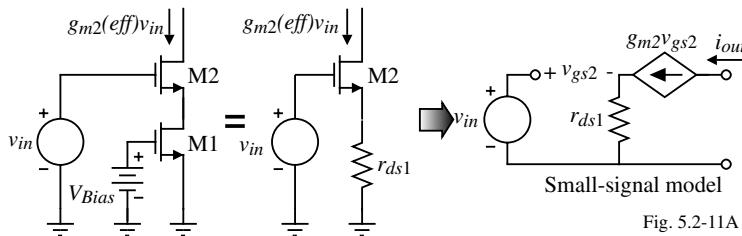


Fig. 5.2-11A

$$\therefore v_{gs2} = v_{g2} - v_{s2} = v_{in} - (g_m r_{ds1}) v_{gs2} \Rightarrow v_{gs2} = \frac{v_{in}}{1 + g_m r_{ds1}}$$

$$\text{Thus, } i_{out} = \frac{g_m v_{in}}{1 + g_m r_{ds1}} = g_m(eff) v_{in}$$

## Miller Two-Stage Op Amp

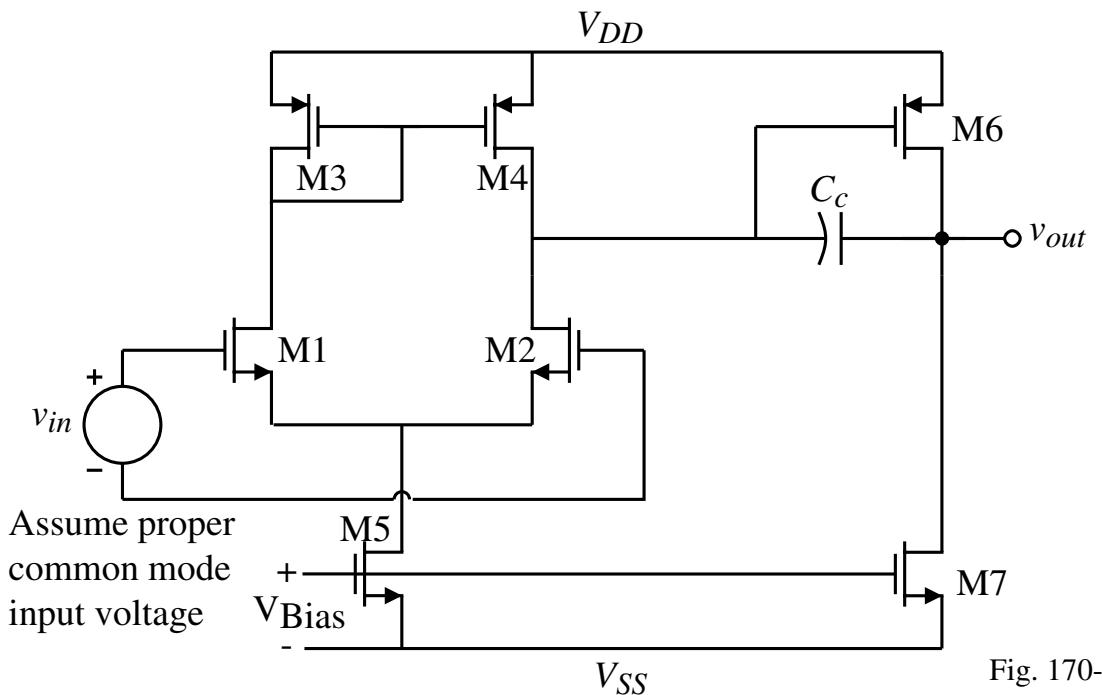


Fig. 170-01

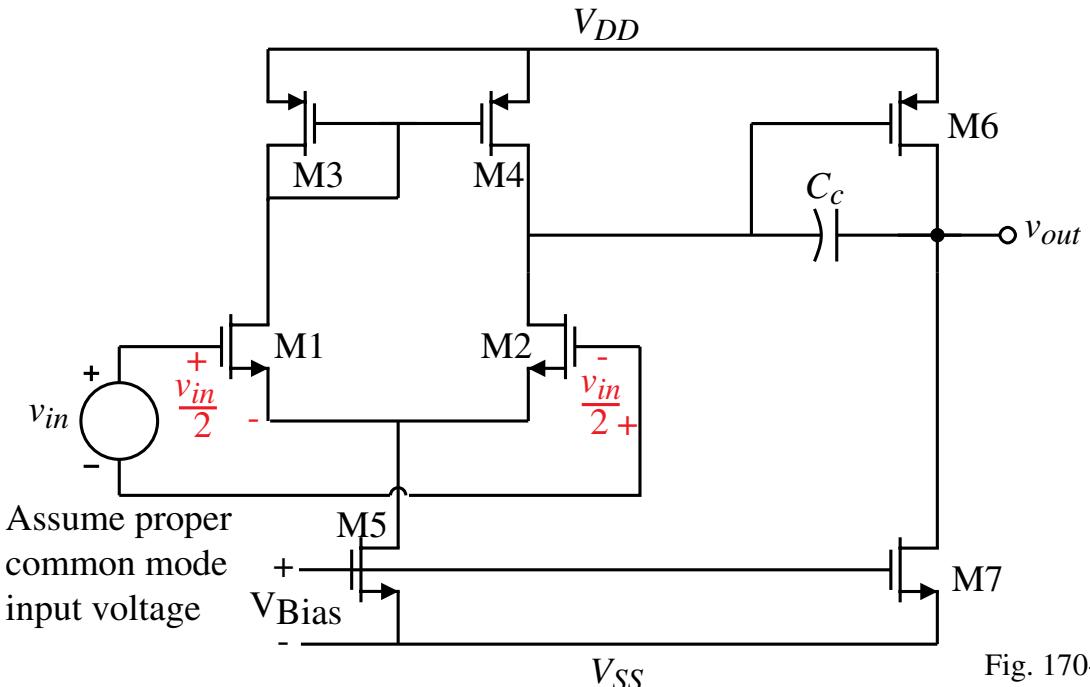
**Miller Two-Stage Op Amp**

Fig. 170-01

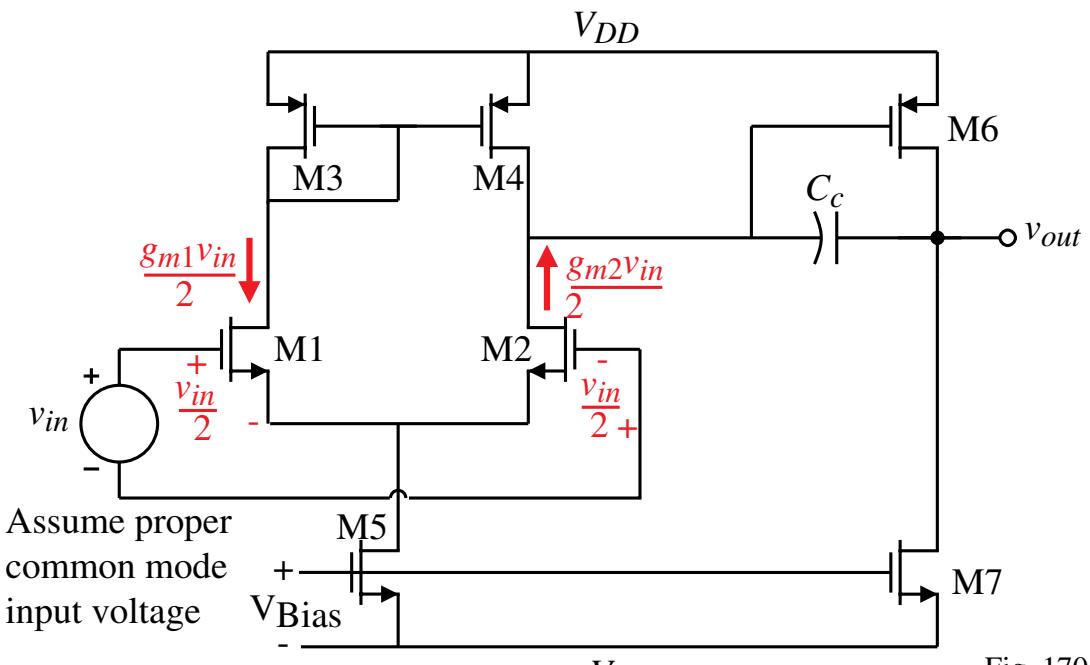
**Miller Two-Stage Op Amp**

Fig. 170-01

## Miller Two-Stage Op Amp

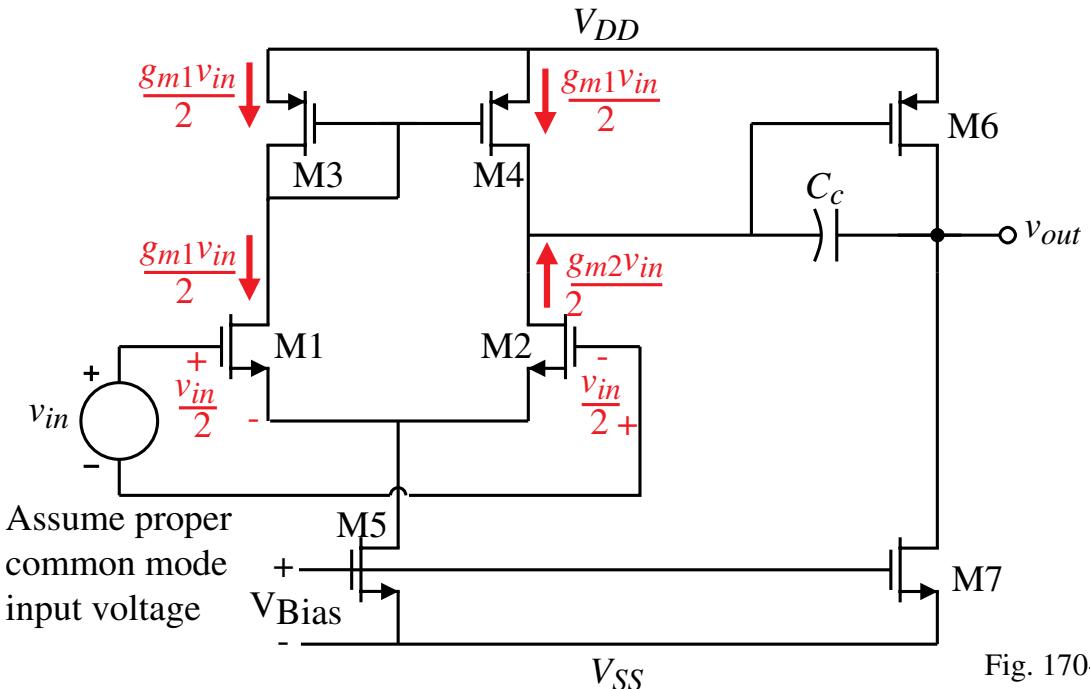


Fig. 170-01

## Miller Two-Stage Op Amp

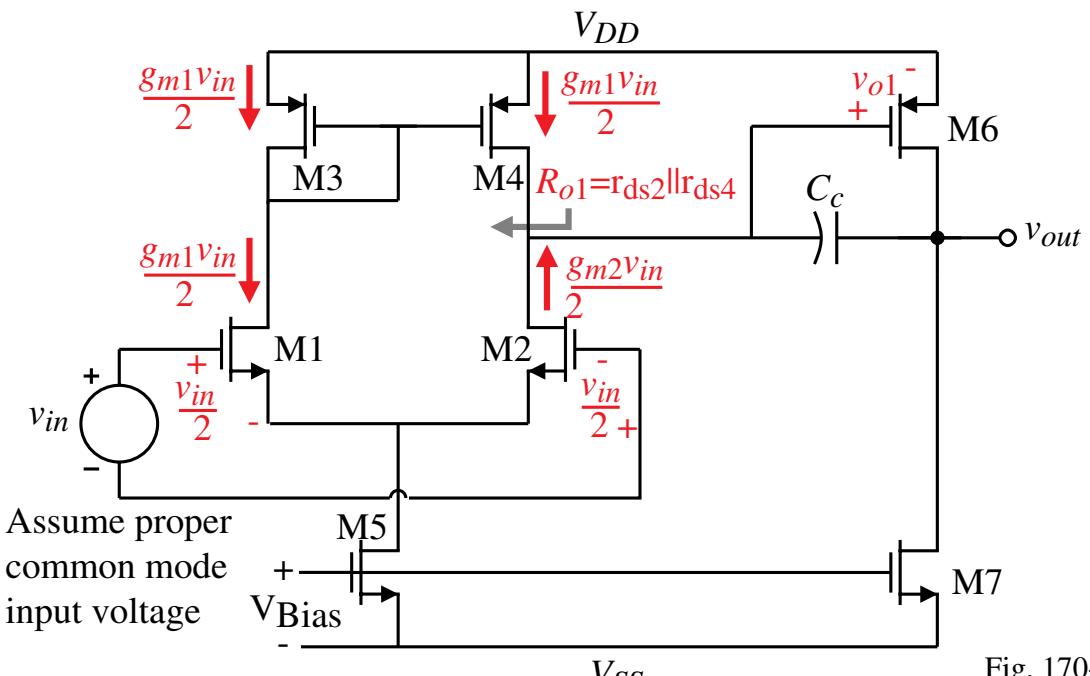


Fig. 170-01

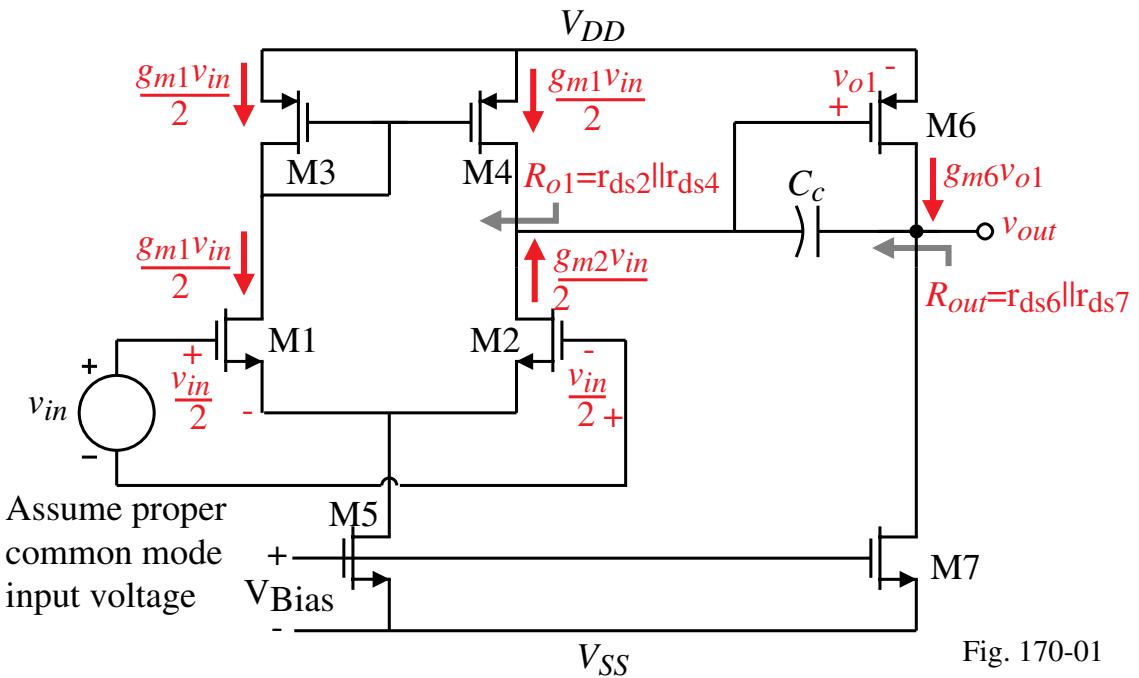
**Miller Two-Stage Op Amp**

Fig. 170-01

$$\frac{v_{out}}{v_{in}} = \left( \frac{-g_{m1}}{g_{ds2} + g_{ds4}} \right) \left( \frac{-g_{m6}}{g_{ds6} + g_{ds7}} \right) = \frac{-g_{m1} g_{m6}}{(g_{ds2} + g_{ds4})(g_{ds6} + g_{ds7})}$$

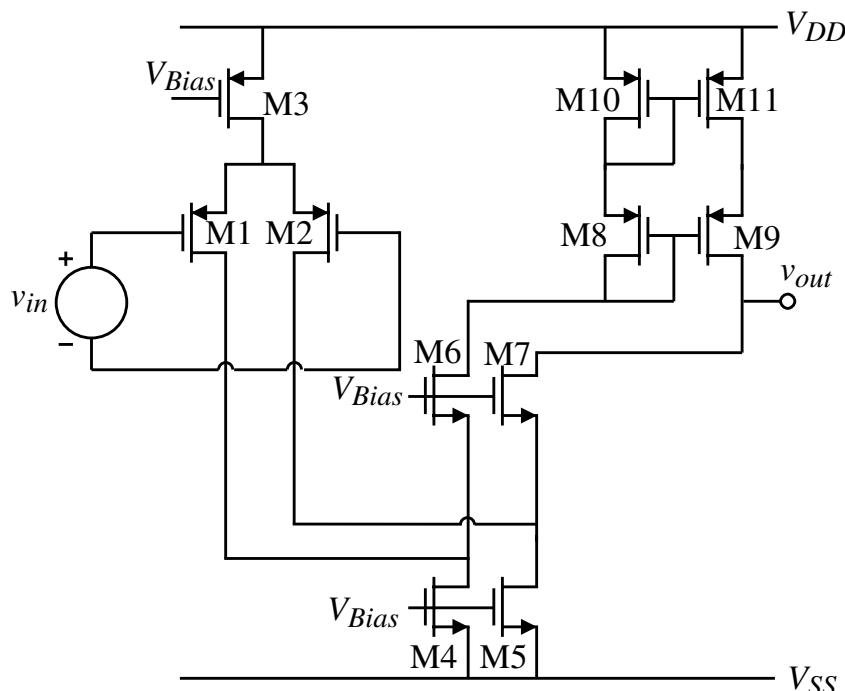
**Folded-Cascode Op Amp**

Fig. 170-02

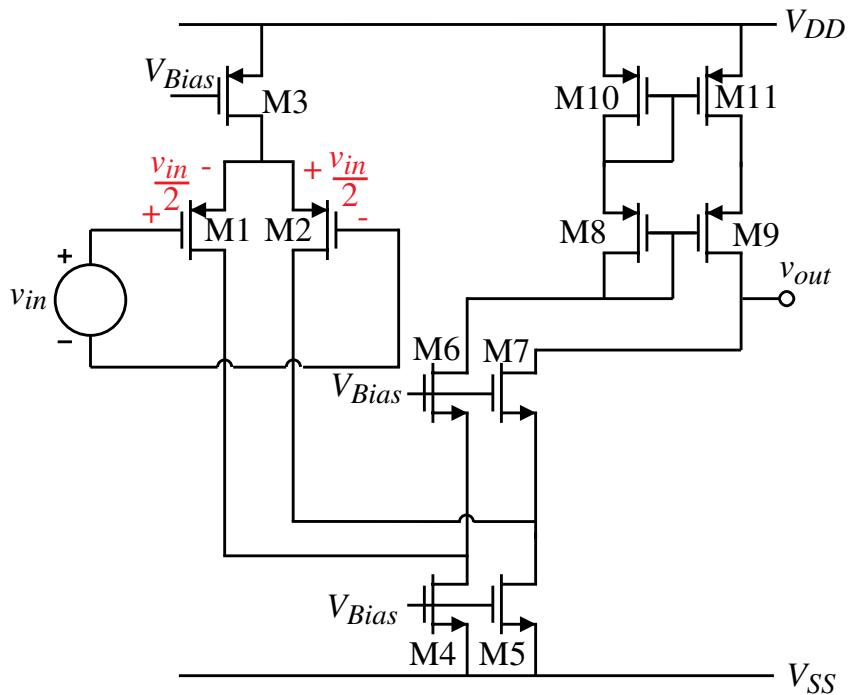
**Folded-Cascode Op Amp**

Fig. 170-02

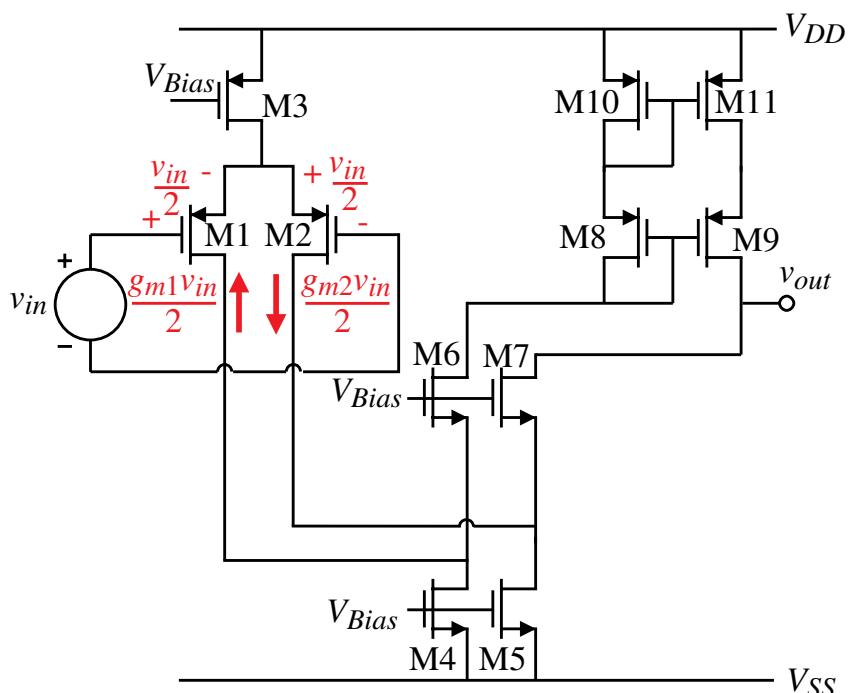
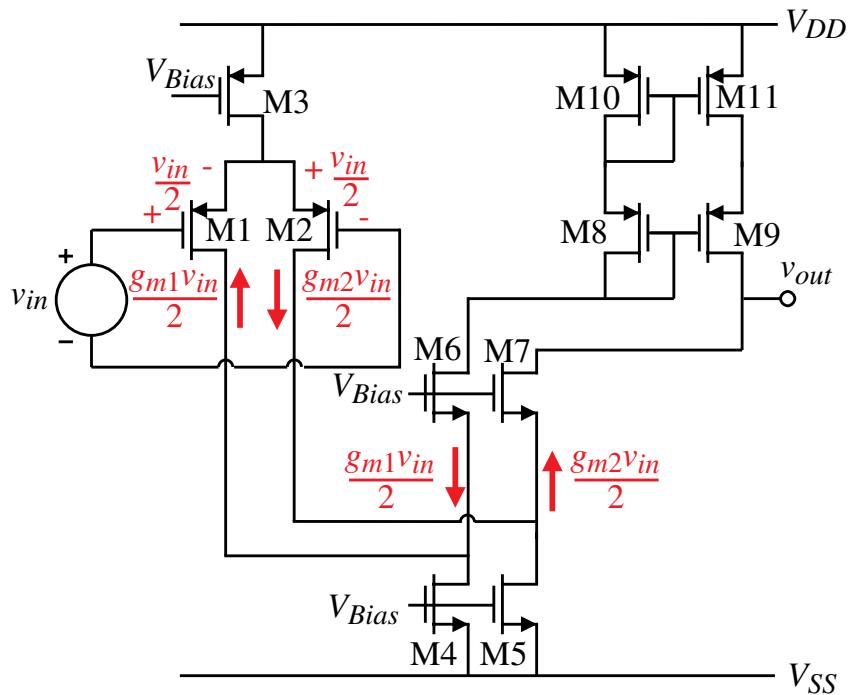
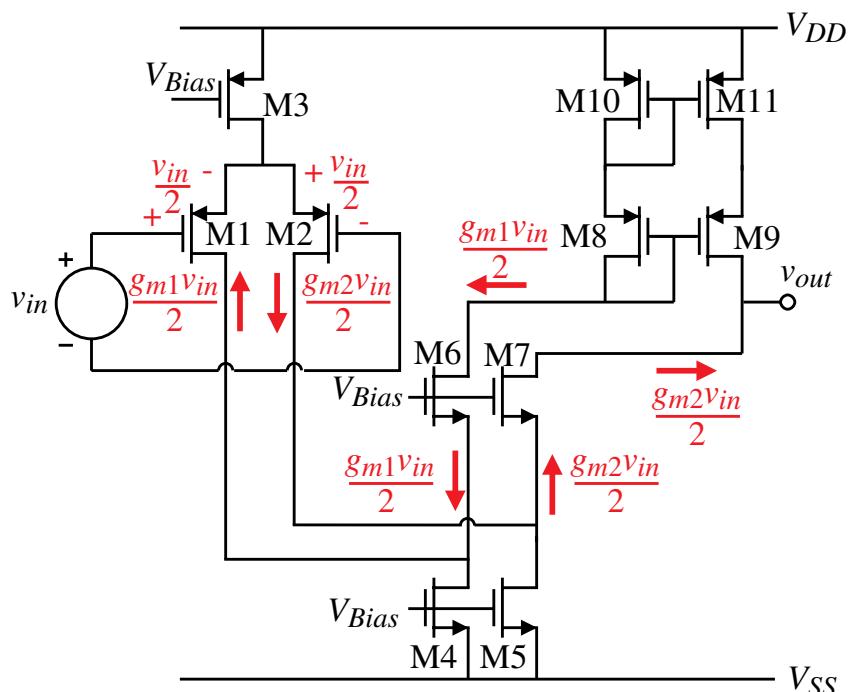
**Folded-Cascode Op Amp**

Fig. 170-02

**Folded-Cascode Op Amp****Folded-Cascode Op Amp**

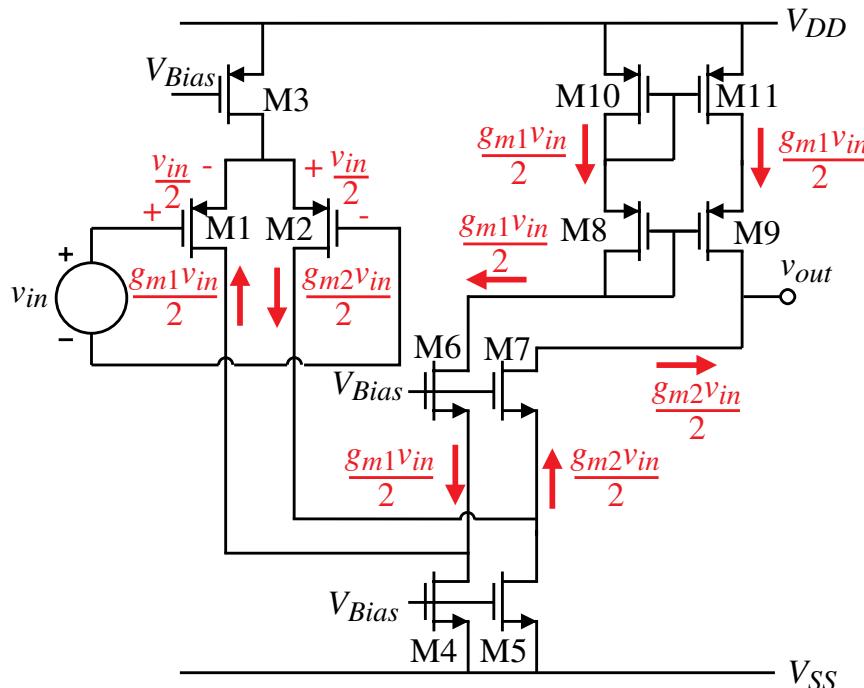
**Folded-Cascode Op Amp**

Fig. 170-02

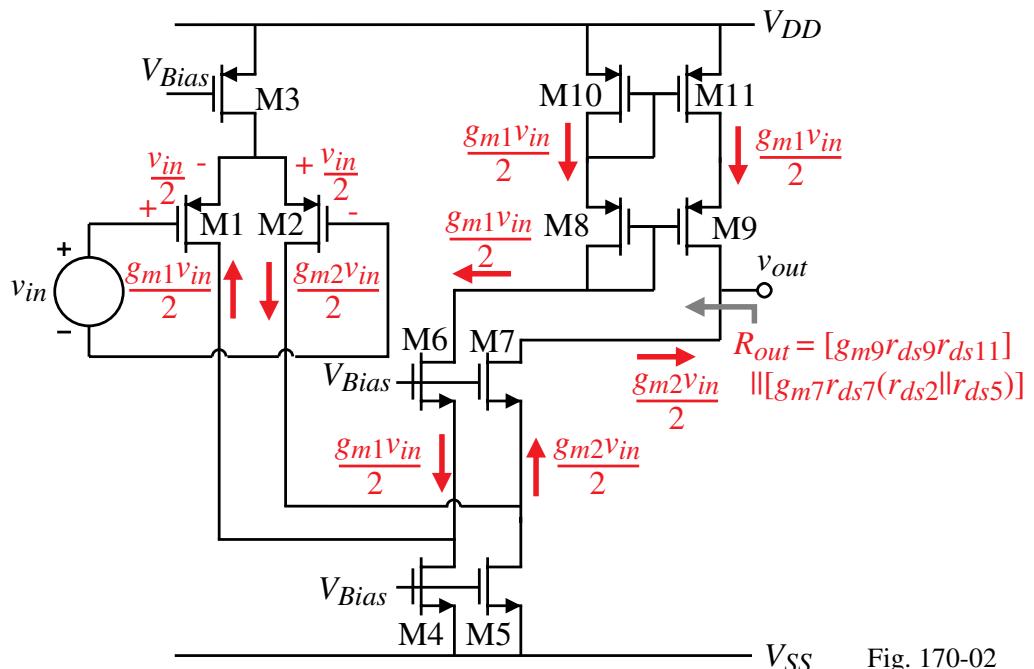
**Folded-Cascode Op Amp**

Fig. 170-02

$$\frac{v_{out}}{v_{in}} = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \right) R_{out} = g_{m1} \{ (g_{m9} r_{ds9} r_{ds11}) \parallel [g_{m7} r_{ds7} (r_{ds2} \parallel r_{ds5})] \}$$

## **SUMMARY**

- Intuitive method is quick and simple
- Intuitive method is approximate (misses the unbalance of the folded cascode)
- Intuitive method does not give any information about frequency response
- The intuitive method can be used with BJT circuits assuming  $\beta \gg 1$  and including  $r_\pi$  in the resistance calculations