

## LECTURE 190 – CASCODE OP AMPS I (READING: GHLM – 443-453, AH – 293-309)

### Objective

The objective of this presentation is:

- 1.) Develop cascode op amp architectures
- 2.) Show how to design with the cascode op amps

### Outline

- Op amps with cascoding in the first stage
- Op amps with cascoding in the second stage
- Folded cascode op amp
- Summary

### Why Cascode Op Amps?

- Control of the frequency behavior
- Can get more gain by increasing the output resistance of a stage
- In the past section,  $PSRR$  of the two-stage op amp was insufficient for many applications
- A two-stage op amp can become unstable for large load capacitors (if nulling resistor is not used)
- We will see in future sections that the cascode op amp leads to wider  $ICMR$  and/or smaller power supply requirements

### Where Should the Cascode Technique be Used?

- First stage -
  - Good noise performance
  - Requires level translation to second stage
  - Degrades the Miller compensation
- Second stage -
  - Self compensating
  - Increases the efficiency of the Miller compensation
  - Increases  $PSRR$

## Use of Cascoding in the First Stage of the Two-Stage Op Amp

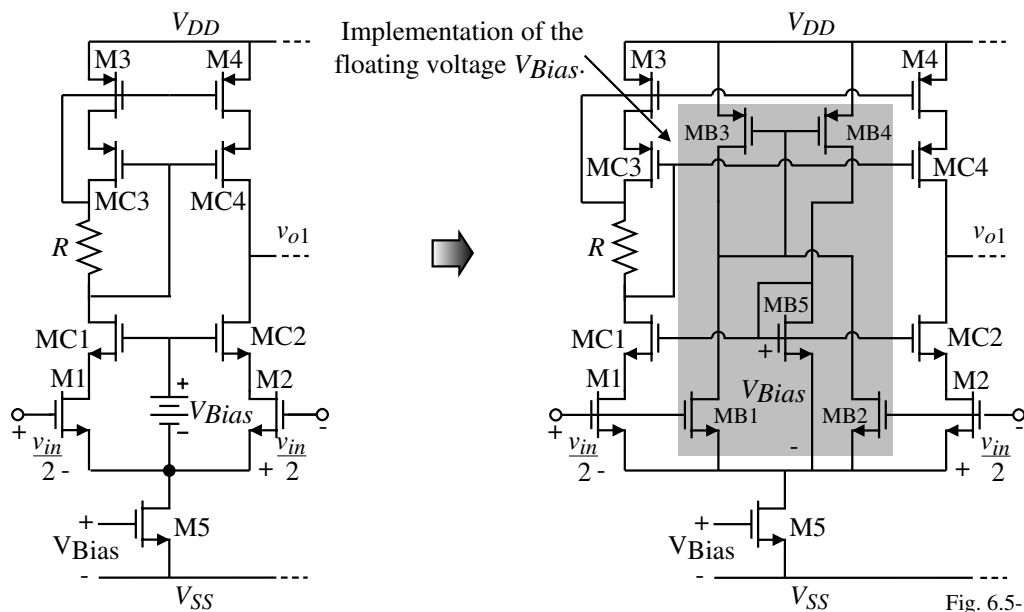


Fig. 6.5-1

$R_{out}$  of the first stage is  $R_I \approx (g_{mC2}r_{dsC2}r_{ds2}) \parallel (g_{mC4}r_{dsC4}r_{ds4})$

Voltage gain =  $\frac{v_{o1}}{v_{in}} = g_{m1}R_I$  [The gain is increased by approximately  $0.5(g_{mC}r_{ds}C)$ ]

As a single stage op amp, the compensation capacitor becomes the load capacitor.

### Example 1 Single-Stage, Cascode Op Amp Performance

Assume that all  $W/L$  ratios are  $10 \mu\text{m}/1 \mu\text{m}$ , and that  $I_{DS1} = I_{DS2} = 50 \mu\text{A}$  of single stage op amp. Find the voltage gain of this op amp and the value of  $C_I$  if  $GB = 10 \text{ MHz}$ . Use the model parameters of Table 3.1-2.

#### Solution

The device transconductances are

$$g_{m1} = g_{m2} = g_{mI} = 331.7 \mu\text{S}$$

$$g_{mC2} = 331.7 \mu\text{S}$$

$$g_{mC4} = 223.6 \mu\text{S}.$$

The output resistance of the NMOS and PMOS devices is  $0.5 \text{ M}\Omega$  and  $0.4 \text{ M}\Omega$ , respectively.

$$\therefore R_I = 25 \text{ M}\Omega$$

$$A_v(0) = 8290 \text{ V/V}.$$

For a unity-gain bandwidth of  $10 \text{ MHz}$ , the value of  $C_I$  is  $5.28 \text{ pF}$ .

What happens if a  $100 \text{ pF}$  capacitor is attached to this op amp?

$GB$  goes from  $10 \text{ MHz}$  to  $0.53 \text{ MHz}$ .

### Two-Stage Op Amp with a Cascoded First-Stage

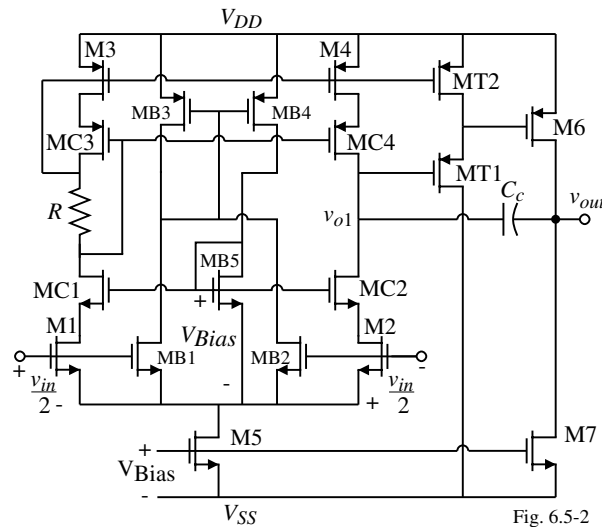


Fig. 6.5-2

- MT1 and MT2 are required for level shifting from the first-stage to the second.
- The  $PSRR^+$  is improved by the presence of MT1
- Internal loop pole at the gate of M6 may cause the Miller compensation to fail.
- The voltage gain of this op amp could easily be 100,000V/V

 


Fig. 6.5-2

### Two-Stage Op Amp with a Cascode Second-Stage

 


Fig. 6.5-3

$$A_v = g_{mI} g_{mII} R_I R_{II} \quad \text{where} \quad g_{mI} = g_{m1} = g_{m2}, \quad g_{mII} = g_{m6},$$

$$R_I = \frac{1}{g_{ds2} + g_{ds4}} = \frac{2}{(\lambda_2 + \lambda_4) I_{D5}} \quad \text{and} \quad R_{II} = (g_{mC6} r_{dsC6} r_{ds6}) \parallel (g_{mC7} r_{dsC7} r_{ds7})$$

Comments:

- The second-stage gain has greatly increased improving the Miller compensation
- The overall gain is approximately  $(g_m r_{ds})^3$  or very large
- Output pole,  $p_2$ , is approximately the same if  $C_c$  is constant
- The RHP is the same if  $C_c$  is constant

## A Balanced, Two-Stage Op Amp using a Cascode Output Stage

 


Fig. 6.5-4

$$v_{out} = \left( \frac{g_{m1}g_{m8}}{g_{m3}} \frac{v_{in}}{2} + \frac{g_{m2}g_{m6}}{g_{m4}} \frac{v_{in}}{2} \right) R_{II}$$

$$= \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \right) k v_{in} R_{II} = g_{m1} \cdot k \cdot R_{II} v_{in}$$

where

$$R_{II} = (g_{m7}r_{ds7}r_{ds6}) \parallel (g_{m12}r_{ds12}r_{ds11})$$

and

$$k = \frac{g_{m8}}{g_{m3}} = \frac{g_{m6}}{g_{m4}}$$

Note that this op amp is balanced because the drain-to-ground loads for M1 and M2 are identical.

### TABLE 1 - Pertinent Design Relationships for Balanced, Cascode Output Stage Op Amp.

$$\text{Slew rate} = \frac{I_{out}}{C_L}$$

$$GB = \frac{g_{m1}g_{m8}}{g_{m3}C_L}$$

$$A_v = \frac{1}{2} \left( \frac{g_{m1}g_{m8}}{g_{m3}} + \frac{g_{m2}g_{m6}}{g_{m4}} \right) R_{II}$$

$$V_{in}(\text{max}) = V_{DD} - \left[ \frac{I_5}{\beta_3} \right]^{1/2} - |V_{TO3}|(\text{max}) + V_{T1}(\text{min})$$

$$V_{in}(\text{min}) = V_{SS} + V_{DS5} + \left[ \frac{I_5}{\beta_1} \right]^{1/2} + V_{T1}(\text{min})$$

### Example 2 - Design of Balanced, Cascoded Output Stage Op Amp

The balanced, cascoded output stage op amp is a useful alternative to the two-stage op amp. Its design will be illustrated by this example. The pertinent design equations for the op amp were given above. The specifications of the design are as follows:

$$V_{DD} = -V_{SS} = 2.5 \text{ V}$$

$$\text{Slew rate} = 5 \text{ V}/\mu\text{s} \text{ with a } 50 \text{ pF load}$$

$$GB = 10 \text{ MHz with a } 10 \text{ pF load}$$

$$A_v \geq 5000$$

$$\text{Input CMR} = -1 \text{ V to } +1.5 \text{ V}$$

$$\text{Output swing} = \pm 1.5 \text{ V}$$

Use the parameters of Table 3.1-2 and let all device lengths be  $1 \mu\text{m}$ .

#### Solution

While numerous approaches can be taken, we shall follow one based on the above specifications. The steps will be numbered to help illustrate the procedure.

1.) The first step will be to find the maximum source/sink current. This is found from the slew rate.

$$I_{source}/I_{sink} = C_L \times \text{slew rate} = 50 \text{ pF}(5 \text{ V}/\mu\text{s}) = 250 \mu\text{A}$$

2.) Next some  $W/L$  constraints based on the maximum output source/sink current are developed. Under dynamic conditions, all of  $I_5$  will flow in M4; thus we can write

$$\text{Max. } I_{out}(\text{source}) = (S_6/S_4)I_5 \quad \text{and} \quad \text{Max. } I_{out}(\text{sink}) = (S_8/S_3)I_5$$

The maximum output sinking current is equal to the maximum output sourcing current if

$$S_3 = S_4, \quad S_6 = S_8, \quad \text{and} \quad S_{10} = S_{11}$$

**Example 2 - Continued**

3.) Choose  $I_5$  as  $100 \mu\text{A}$ . This current (which can be changed later) gives

$$S_6 = 2.5S_4 \text{ and } S_8 = 2.5S_3$$

Note that  $S_8$  could equal  $S_3$  if  $S_{11} = 2.5S_{10}$ . This would minimize the power dissipation.

4.) Next design for  $\pm 1.5 \text{ V}$  output capability. We shall assume that the output must source or sink the  $250 \mu\text{A}$  at the peak values of output. First consider the negative output peak. Since there is  $1 \text{ V}$  difference between  $V_{SS}$  and the minimum output, let  $V_{DS11}(\text{sat}) = V_{DS12}(\text{sat}) = 0.5 \text{ V}$  (we continue to ignore the bulk effects). Under the maximum negative peak assume that  $I_{11} = I_{12} = 250 \mu\text{A}$ . Therefore

$$0.5 = \sqrt{\frac{2I_{11}}{K'_N S_{11}}} = \sqrt{\frac{2I_{12}}{K'_N S_{12}}} = \sqrt{\frac{500 \mu\text{A}}{(110 \mu\text{A}/\text{V}^2)S_{11}}}$$

which gives  $S_{11} = S_{12} = 18.2$  and  $S_9 = S_{10} = 18.2$ . For the positive peak, we get

$$0.5 = \sqrt{\frac{2I_6}{K'_P S_6}} = \sqrt{\frac{2I_7}{K'_P S_7}} = \sqrt{\frac{500 \mu\text{A}}{(50 \mu\text{A}/\text{V}^2)S_6}}$$

which gives  $S_6 = S_7 = S_8 = 40$  and  $S_3 = S_4 = (40/2.5) = 16$ .

5.) Next the values of  $R_1$  and  $R_2$  are designed. For the resistor of the self-biased cascode we can write  $R_1 = V_{DS12}(\text{sat})/250 \mu\text{A} = 2 \text{ k}\Omega$  and  $R_2 = V_{SD7}(\text{sat})/250 \mu\text{A} = 2 \text{ k}\Omega$

**Example 2 - Continued**

Using this value of  $R_1$  ( $R_2$ ) will cause M11 to slightly be in the active region under quiescent conditions. One could redesign  $R_1$  to avoid this but the minimum output voltage under maximum sinking current would not be realized.

6.) Now we must consider the possibility of conflict among the specifications.

First consider the input CMR.  $S_3$  has already been designed as 16. Using ICMR relationship, we find that  $S_3$  should be at least 4.1. A larger value of  $S_3$  will give a higher value of  $V_{in}(\text{max})$  so that we continue to use  $S_3 = 16$  which gives  $V_{in}(\text{max}) = 1.95 \text{ V}$ .

Next, check to see if the larger W/L causes a pole below the gainbandwidth. Assuming a  $C_{ox}$  of  $0.4 \text{ fF}/\mu\text{m}^2$  gives the first-stage pole of

$$p_3 = \frac{-g_{m3}}{C_{gs3} + C_{gs8}} = \frac{-\sqrt{2K'_P S_3 I_3}}{(0.667)(W_3 L_3 + W_8 L_8) C_{ox}} = 33.15 \times 10^9 \text{ rads/sec or } 5.275 \text{ GHz}$$

which is much greater than  $10 \text{ GB}$ .

7.) Next we find  $g_{m1}$  ( $g_{m2}$ ). There are two ways of calculating  $g_{m1}$ .

(a.) The first is from the  $A_v$  specification. The gain is

$$A_v = (g_{m1}/2g_{m4})(g_{m6} + g_{m8}) R_{II}$$

Note, a current gain of  $k$  could be introduced by making  $S_6/S_4$  ( $S_8/S_3 = S_{11}/S_3$ ) equal to  $k$ .

$$\frac{g_{m6}}{g_{m4}} = \frac{g_{m11}}{g_{m3}} = \sqrt{\frac{2K'_P \cdot S_6 \cdot I_6}{2K'_P \cdot S_4 \cdot I_4}} = k$$

**Example 2 - Continued**

Calculating the various transconductances we get  $g_{m4} = 282.4 \mu\text{S}$ ,  $g_{m6} = g_{m7} = g_{m8} = 707 \mu\text{S}$ ,  $g_{m11} = g_{m12} = 707 \mu\text{S}$ ,  $r_{ds6} = r_{d7} = 0.16 \text{ M}\Omega$ , and  $r_{ds11} = r_{ds12} = 0.2 \text{ M}\Omega$ . Assuming that the gain  $A_v$  must be greater than 5000 and  $k = 2.5$  gives  $g_{m1} > 72.43 \mu\text{S}$ .

(b.) The second method of finding  $g_{m1}$  is from the  $GB$  specifications. Multiplying the gain by the dominant pole ( $1/C_{II}R_{II}$ ) gives

$$GB = \frac{g_{m1}(g_{m6} + g_{m8})}{2g_{m4}C_L}$$

Assuming that  $C_L = 10 \text{ pF}$  and using the specified  $GB$  gives  $g_{m1} = 251 \mu\text{S}$ .

Since this is greater than  $72.43 \mu\text{S}$ , we choose  $g_{m1} = g_{m2} = 251 \mu\text{S}$ . Knowing  $I_5$  gives  $S_1 = S_2 = 11.45 \approx 12$ .

8.) The next step is to check that  $S_1$  and  $S_2$  are large enough to meet the  $-1\text{V}$  input CMR specification. Use the saturation formula we find that  $V_{DS5}$  is  $0.5248 \text{ V}$ . This gives  $S_5 = 6.6 \approx 7$ . The gain becomes  $A_v = 6,925\text{V/V}$  and  $GB = 10 \text{ MHz}$  for a  $10 \text{ pF}$  load. We shall assume that exceeding the specifications in this area is not detrimental to the performance of the op amp.

9.) With  $S_5 = 7$  then we can design  $S_{13}$  from the relationship

$$S_{13} = \frac{I_{13}}{I_5} S_5 = \frac{125 \mu\text{A}}{100 \mu\text{A}} 7 = 8.75$$

**Example 2 - Continued**

10.) Finally we need to design the value of  $V_{Bias}$ , which can be done with the values of  $S_5$  and  $I_5$  known. However,  $M_5$  is usually biased from a current source flowing into a MOS diode in parallel with the gate-source of  $M_5$ . The value of the current source compared with  $I_5$  would define the  $W/L$  ratio of the MOS diode.

Table 2 summarizes the values of  $W/L$  that resulted from this design procedure. The power dissipation for this design is seen to be  $2 \text{ mW}$ . The next step would be begin simulation.

**Table 2 - Summary of W/L Ratios for Example 2**

$$S_1 = S_2 = 12$$

$$S_3 = S_4 = 16$$

$$S_5 = 7$$

$$S_6 = S_7 = S_8 = S_{14} = S_{15} = 40$$

$$S_9 = S_{10} = S_{11} = S_{12} = 18.2$$

$$S_{13} = 8.75$$

### Technological Implications of the Cascode Configuration

 


Fig. 6.5-5

If a double poly CMOS process is available, internode parasitics can be minimized. As an alternative, one should keep the drain/source between the transistors to a minimum area.

 


Fig. 6.5-5A

### Input Common Mode Range for Two Types of Differential Amplifier Loads

 


Fig. 6.5-6

In order to improve the ICMR, it is desirable to use current source (sink) loads without losing half the gain.

The resulting solution is the *folded* cascode op amp.

### The Folded Cascode Op Amp

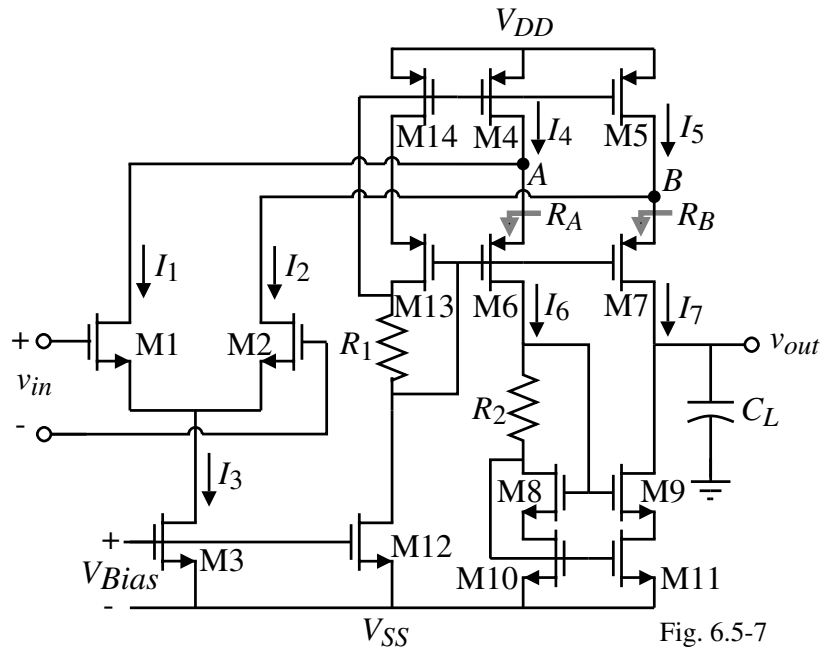


Fig. 6.5-7

We have examined the small signal performance and the frequency response in an earlier lecture.

### PSRR of the Folded Cascode Op Amp

Consider the following circuit used to model the PSRR:-

 


Fig. 6.5-9A

This model assumes that gate, source and drain of M11 and the gate and source of M9 all vary with  $V_{SS}$ .

We shall examine  $V_{out}/V_{SS}$  rather than  $PSRR^-$ . (Small  $V_{out}/V_{SS}$  will lead to large  $PSRR^-$ .)

The transfer function of  $V_{out}/V_{SS}$  can be found as

$$\frac{V_{out}}{V_{SS}} \approx \frac{sC_{gd9}R_{out}}{sC_{out}R_{out}+1} \quad \text{for } C_{gd9} < C_{out}$$

The approximate  $PSRR^-$  is sketched on the next page.



### Frequency Response of the PSRR- of the Folded Cascode Op Amp

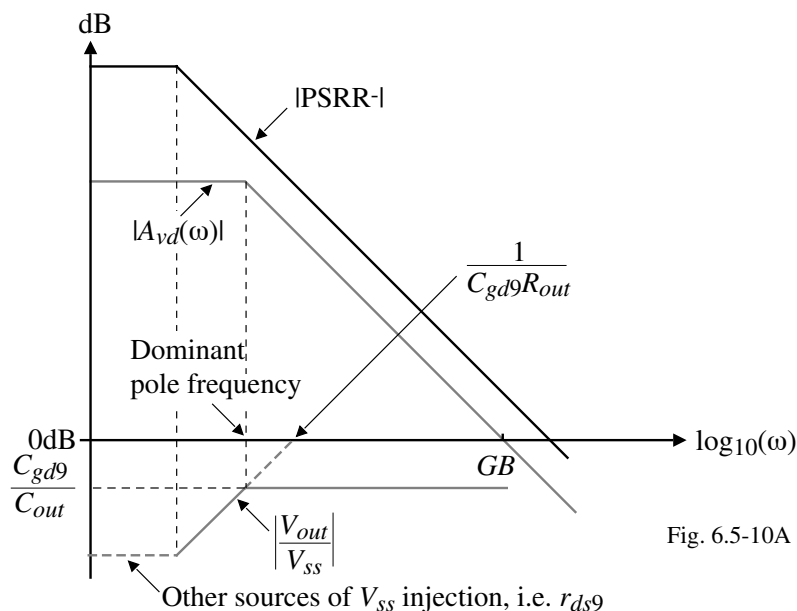


Fig. 6.5-10A

We see that the PSRR of the cascode op amp is much better than the two-stage op amp.

### Design Approach for the Folded-Cascode Op Amp

Step	Relationship/ Requirement	Design Equation/Constraint	Comments
1	Slew Rate	$I_3 = SR \cdot C_L$	
2	Bias currents in output cascodes	$I_4 = I_5 = 1.2I_3$ to $1.5I_3$	Avoid zero current in cascodes
3	Maximum output voltage, $v_{out(max)}$	$S_5 = \frac{2I_5}{K_P \cdot V_{SD5}^2}$ , $S_7 = \frac{2I_7}{K_P \cdot V_{SD7}^2}$ Let $S_4 = S_{14} = S_5$ & $S_{13} = S_6 = S_7$	$V_{SD5(sat)} = V_{SD7(sat)} = 0.5[V_{DD} - V_{out(min)}]$
4	Minimum output voltage, $v_{out(min)}$	$S_{11} = \frac{2I_{11}}{K_N \cdot V_{DS11}^2}$ , $S_9 = \frac{2I_9}{K_N \cdot V_{DS9}^2}$ Let $S_{10} = S_{11}$ & $S_8 = S_9$	$V_{DS9(sat)} = V_{DS11(sat)} = 0.5(V_{out(min)} -  V_{SS} )$
5	Self-bias cascode	$R_1 = V_{SD14(sat)}/I_{14}$ and $R_2 = V_{DS8(sat)}/I_6$	
6	$GB = \frac{g_{m1}}{C_L}$	$S_1 = S_2 = \frac{g_{m1}^2}{K_N \cdot I_3} = \frac{GB^2 \cdot C_L^2}{K_N \cdot I_3}$	
7	Minimum input CM	$S_3 = \frac{2I_3}{K_N \cdot (V_{in(min)} - V_{SS} - \sqrt{\frac{I_3}{K_N \cdot S_1}} - V_{T1})^2}$	
8	Maximum input CM	$S_4 = S_5 = \frac{2I_4}{K_P \cdot (V_{DD} - V_{in(max)} + V_{T1})^2}$	$S_4$ and $S_5$ must meet or exceed the value in step 3
9	Differential Voltage Gain	$\frac{v_{out}}{v_{in}} = \left(\frac{g_{m1}}{2} + \frac{g_{m2}}{2(1+k)}\right) R_{out} = \left(\frac{2+k}{2+2k}\right) g_{m1} R_{out}$	
10	Power dissipation	$P_{diss} = (V_{DD} - V_{SS})(I_3 + I_{12} + I_{10} + I_{11})$	

### Example 3 - Design of a Folded-Cascode Op Amp

Follow the procedure given to design the folded-cascode op amp when the slew rate is  $10\text{V}/\mu\text{s}$ , the load capacitor is  $10\text{pF}$ , the maximum and minimum output voltages are  $\pm 2\text{V}$  for  $\pm 2.5\text{V}$  power supplies, the  $GB$  is  $10\text{MHz}$ , the minimum input common mode voltage is  $-1.5\text{V}$  and the maximum input common mode voltage is  $2.5\text{V}$ . The differential voltage gain should be greater than  $5,000\text{V}/\text{V}$  and the power dissipation should be less than  $5\text{mW}$ . Use channel lengths of  $1\mu\text{m}$ .

#### Solution

Following the approach outlined above we obtain the following results.

$$I_3 = SR \cdot C_L = 10 \times 10^6 \cdot 10^{-11} = 100\mu\text{A}$$

Select  $I_4 = I_5 = 125\mu\text{A}$ .

Next, we see that the value of  $0.5(V_{DD} - V_{out}(\text{max}))$  is  $0.5\text{V}/2$  or  $0.25\text{V}$ . Thus,

$$S_4 = S_5 = S_{14} = \frac{2 \cdot 125\mu\text{A}}{50\mu\text{A}/\text{V}^2 \cdot (0.25\text{V})^2} = \frac{2 \cdot 125 \cdot 16}{50} = 80$$

and assuming worst case currents in M6 and M7 gives,

$$S_6 = S_7 = S_{13} = \frac{2 \cdot 125\mu\text{A}}{50\mu\text{A}/\text{V}^2 (0.25\text{V})^2} = \frac{2 \cdot 125 \cdot 16}{50} = 80$$

The value of  $0.5(V_{out}(\text{min}) - |V_{SS}|)$  is also  $0.25\text{V}$  which gives the value of  $S_8, S_9, S_{10}$  and  $S_{11}$

$$\text{as } S_8 = S_9 = S_{10} = S_{11} = \frac{2 \cdot I_8}{K_N' V_{DS8}^2} = \frac{2 \cdot 125}{110 \cdot (0.25)^2} = 36.36$$

### Example 3 - Continued

The value of  $R_1$  and  $R_2$  is equal to  $0.25\text{V}/125\mu\text{A}$  or  $2\text{k}\Omega$ . In step 6, the value of  $GB$  gives  $S_1$  and  $S_2$  as

$$S_1 = S_2 = \frac{GB^2 \cdot C_L^2}{K_N' I_3} = \frac{(20\pi \times 10^6)^2 (10^{-11})^2}{110 \times 10^{-6} \cdot 100 \times 10^{-6}} = 35.9$$

The minimum input common mode voltage defines  $S_3$  as

$$S_3 = \frac{2I_3}{K_N' \left( V_{in}(\text{min}) - V_{SS} - \sqrt{\frac{I_3}{K_N' S_1}} - V_{T1} \right)^2} = \frac{200 \times 10^{-6}}{110 \times 10^{-6} \left( -1.5 + 2.5 - \sqrt{\frac{100}{110 \cdot 35.9}} - 0.75 \right)^2} = 20$$

We need to check that the values of  $S_4$  and  $S_5$  are large enough to satisfy the maximum input common mode voltage. The maximum input common mode voltage of  $2.5$  requires

$$S_4 = S_5 \geq \frac{2I_4}{K_P' [V_{DD} - V_{in}(\text{max}) + V_{T1}]} = \frac{2 \cdot 125\mu\text{A}}{50 \times 10^{-6} \mu\text{A}/\text{V}^2 [0.7\text{V}]^2} = 10.2$$

which is much less than  $80$ . In fact, with  $S_4 = S_5 = 80$ , the maximum input common mode voltage is  $3\text{V}$ . Finally,  $S_{12}$ , is given as

$$S_{12} = \frac{125}{100} S_3 = 25$$

The power dissipation is found to be

$$P_{diss} = 5\text{V}(125\mu\text{A} + 125\mu\text{A} + 125\mu\text{A}) = 1.875\text{mW}$$

**Example 3 - Continued**

The small-signal voltage gain requires the following values to evaluate:

$$S_4, S_5, S_{13}, S_{14}: \quad g_m = \sqrt{2 \cdot 125 \cdot 50 \cdot 80} = 1000 \mu\text{S} \quad \text{and} \quad g_{ds} = 125 \times 10^{-6} \cdot 0.05 = 6.25 \mu\text{S}$$

$$S_6, S_7: \quad g_m = \sqrt{2 \cdot 75 \cdot 50 \cdot 80} = 774.6 \mu\text{S} \quad \text{and} \quad g_{ds} = 75 \times 10^{-6} \cdot 0.05 = 3.75 \mu\text{S}$$

$$S_8, S_9, S_{10}, S_{11}: \quad g_m = \sqrt{2 \cdot 75 \cdot 110 \cdot 36.36} = 774.6 \mu\text{S} \quad \text{and} \quad g_{ds} = 75 \times 10^{-6} \cdot 0.04 = 3 \mu\text{S}$$

$$S_1, S_2: \quad g_{mI} = \sqrt{2 \cdot 50 \cdot 110 \cdot 35.9} = 628 \mu\text{S} \quad \text{and} \quad g_{ds} = 50 \times 10^{-6} (0.04) = 2 \mu\text{S}$$

Thus,

$$R_{II} \approx g_m r_{ds9} r_{ds11} = (774.6 \mu\text{S}) \left( \frac{1}{3 \mu\text{S}} \right) \left( \frac{1}{3 \mu\text{S}} \right) = 86.07 \text{M}\Omega$$

$$R_{out} \approx 86.07 \text{M}\Omega \parallel (774.6 \mu\text{S}) \left( \frac{1}{3.75 \mu\text{S}} \right) \left( \frac{1}{2 \mu\text{S} + 6.25 \mu\text{S}} \right) = 19.40 \text{M}\Omega$$

$$k = \frac{R_{II}(g_{ds2} + g_{ds4})}{g_{mI} r_{ds7}} = \frac{86.07 \text{M}\Omega (2 \mu\text{S} + 6.25 \mu\text{S}) (3.75 \mu\text{S})}{774.6 \mu\text{S}} = 3.4375$$

The small-signal, differential-input, voltage gain is

$$A_{vd} = \left( \frac{2+k}{2+2k} \right) g_{mI} R_{out} = \left( \frac{2+3.4375}{2+6.875} \right) 0.628 \times 10^{-3} \cdot 19.40 \times 10^6 = 7,464 \text{ V/V}$$

The gain is larger than required by the specifications which should be okay.

**Comments on Folded Cascode Op Amps**

- Good PSRR
- Good ICMR
- Self compensated
- Can cascade an output stage to get extremely high gain with lower output resistance (use Miller compensation in this case)
- Need first stage gain for good noise performance
- Widely used in telecommunication circuits where large dynamic range is required

## **SUMMARY**

- Cascode op amps offer an alternate architecture to the two-stage op amp
- The cascode op amp is typically self-compensating
- The cascode op amp generally has better PSRR