

## LECTURE 210 – DC ANALYSIS OF THE 741 OP AMP (READING: GHLM – 454-462)

### Objective

The objective of this presentation is to:

- 1.) Identify the devices, circuits, and stages in the 741 operational amplifier
- 2.) Perform a dc bias analysis
- 3.) Compare hand calculations of dc analyses with PSpice simulations

### Outline

- 741 circuit topology and analysis
- PSpice analysis techniques and results
- Summary

## 741 OPERATIONAL AMPLIFIER

### Circuit

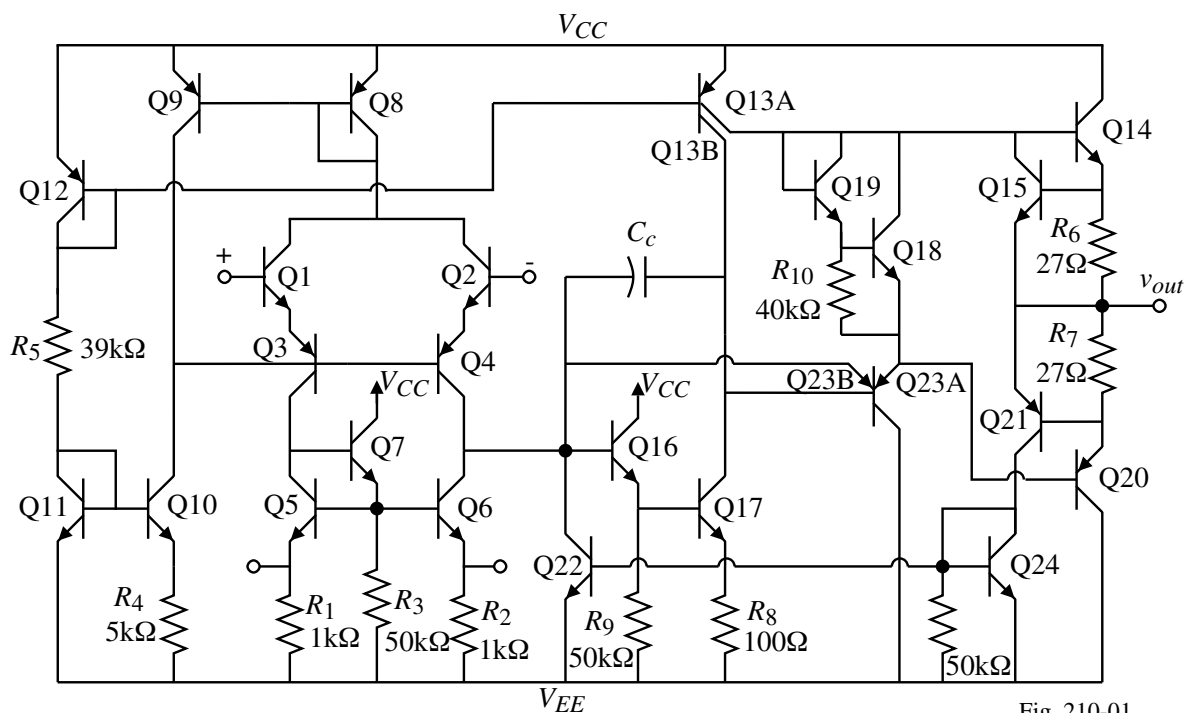


Fig. 210-01

The 741 op amp is typical of a widely used stand-alone operational amplifiers.

### Simplified, Conceptual Schematic Diagram of the 741 Op Amp


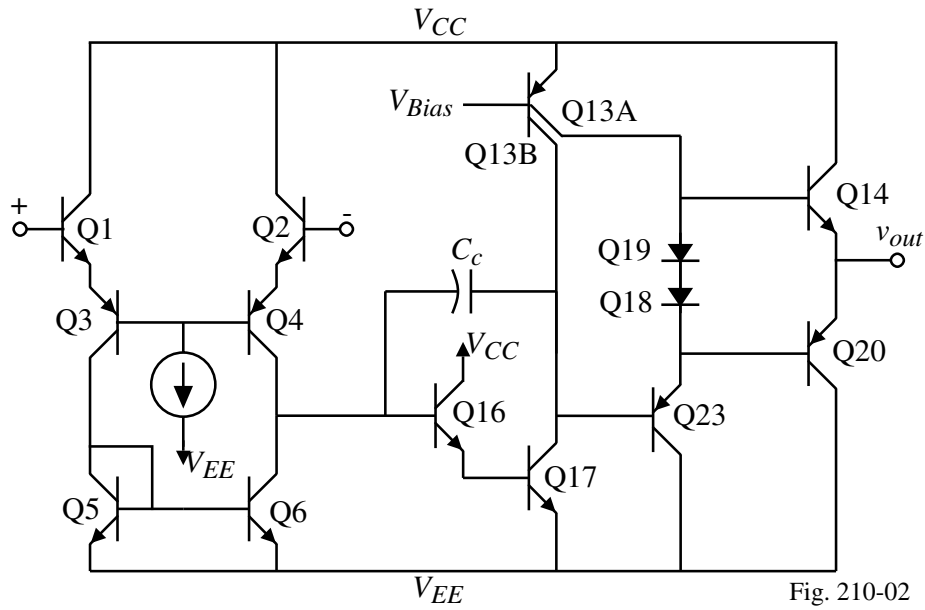


Fig. 210-02

### Multicollector Lateral PNP

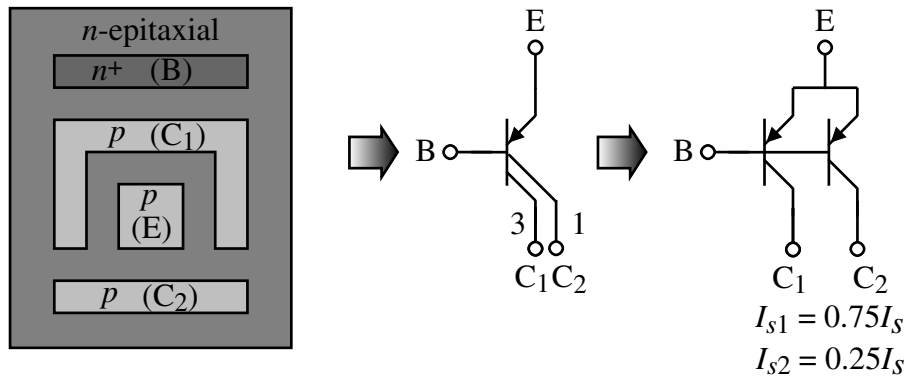


$I_S$  is the saturation current of the structure with both collectors connected together.

Fig. 210-03

### DC Analysis of the 741 Op Amp

Bias circuitry:

 

$$I_{ref} = \frac{V_{CC} - V_{EE} - 2V_{BE}}{R_5} = 733\mu A$$

$$I_2 = I_{13B} = 0.75I_{ref} = 550\mu A$$

$$I_3 = I_{13A} = 0.25I_{ref} = 180\mu A$$

$$I_1 = I_{10} = \frac{V_t}{R_4} [\ln(I_{ref}) - \ln(I_1)] = 19\mu A$$

Fig. 210-04

### Simplified Schematic of the 741 Op Amp with Idealized Biasing

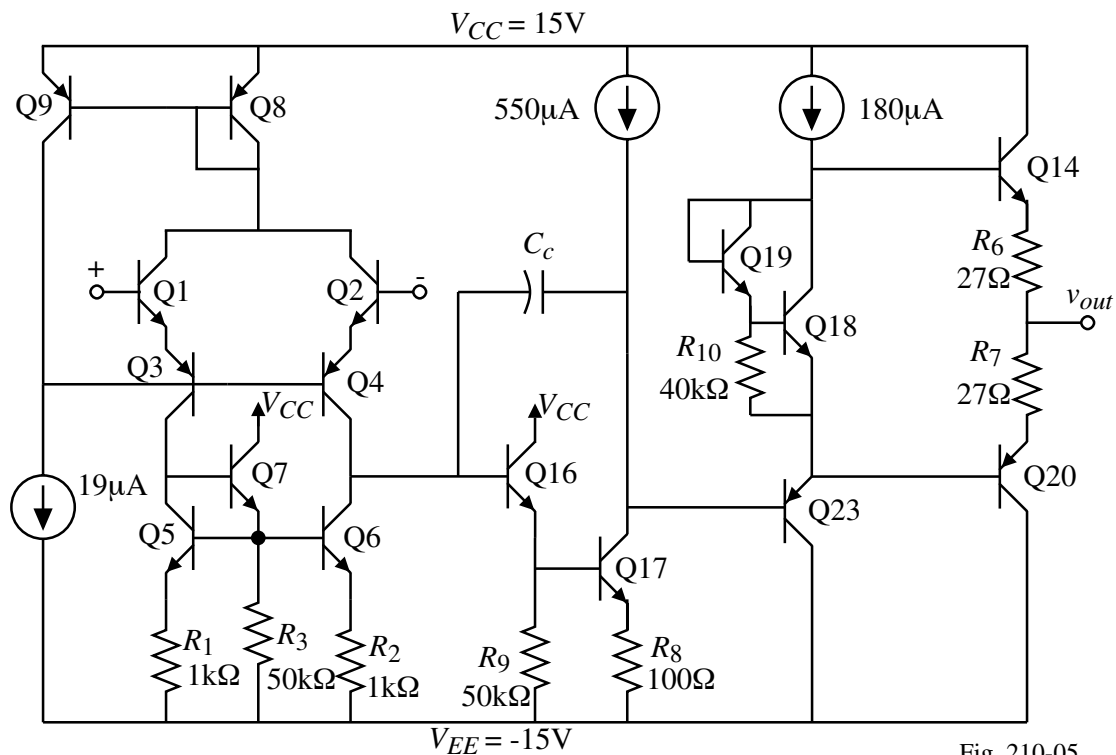


Fig. 210-05

## Input Stage Biasing of the 741 Op Amp

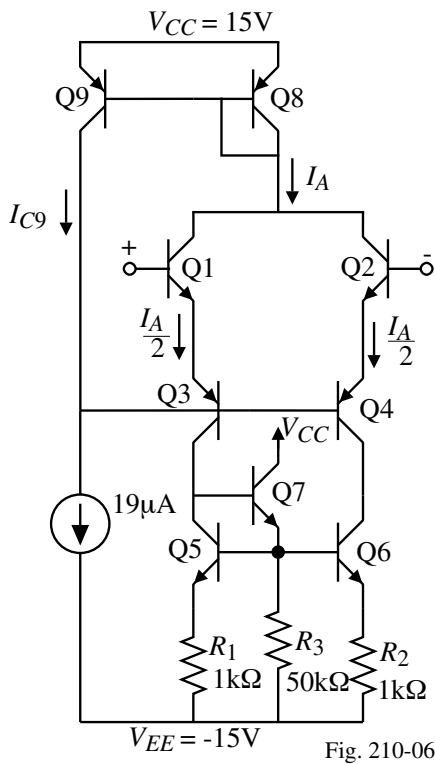


Fig. 210-06

$$I_A = I_8 = I_9 = 19\mu\text{A}$$

$$\frac{I_A}{2} = 9.5\mu\text{A}$$

$$V_{BE5} = V_t \ln\left(\frac{9.5\mu\text{A}}{I_{SNPN}}\right) = 0.553\text{V}$$

$$I_{SNPN} = 5\text{fA}$$

$$V_{BE5} = 0.555\text{V}$$

$$V_{B5} = V_{BE5} + R_1 \cdot 9.5\mu\text{A} = 0.565\text{V}$$

$$I_{R3} = I_7 = \frac{V_{B5}}{R_3} = 11.3\mu\text{A}$$

## Darlington Gain Stage Biasing

 


Fig. 210-07

$$V_{BE17} = V_t \ln\left(\frac{550\mu\text{A}}{I_{SNPN}}\right)$$

$$V_{B17} = V_{BE17} + R_8 \cdot 550\mu\text{A} = 0.716\text{V}$$

$$I_{R9} = \frac{V_{B17}}{R_9} = 14.3\mu\text{A}$$

$$I_{B17} = \frac{550\mu\text{A}}{\beta+1} = 2.2\mu\text{A}$$

$$I_{16} = I_{B17} + I_{R9} = 16.5\mu\text{A}$$

### Output Stage Biasing of the 741 Op Amp

 


Fig. 210-08

$$I_{19} = \frac{V_t}{R_{10}} \ln\left(\frac{I_{18}}{I_{SNPN}}\right)$$

$$I_{18} + I_{19} = 180\mu\text{A}$$

$$I_{18} = 164\mu\text{A}$$

$$I_{19} = 15.7\mu\text{A}$$

$$V_{BE18} + V_{BE19} \approx V_{BE14} + |V_{BE20}|$$

$$\frac{I_{18} I_{19}}{I_{SNPN18} I_{SNPN19}} = \frac{I_{14}^2}{I_{SNPN14} I_{SNPN20}}$$

$$I_{SNPN14} = 4.5 I_{SNPN}$$

$$I_{S20} = 10\text{fA}$$

$$I_{14} = 150\mu\text{A}$$

### 741 Circuit for SPICE Simulation

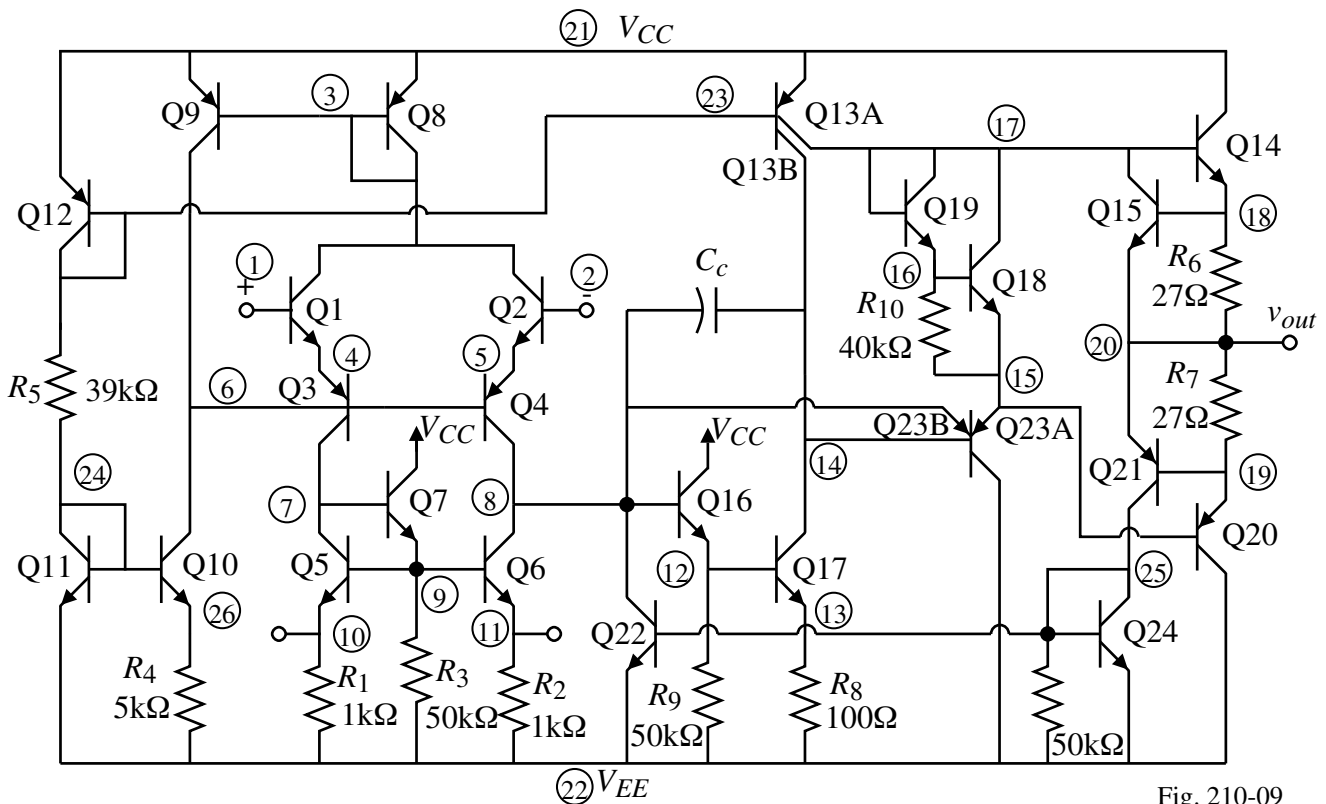


Fig. 210-09

## Spice Simulations of the 741 Op Amp

```

uA741 Operational Amp Spice File
** 741 OP AMP **
* BIAS CIRCUIT *
Q12 23 23 21 PNP
Q11 24 24 22 NPN
Q10 6 24 26 NPN
Q13A 17 23 21 PNP 1
Q13B 14 23 21 PNP 3
Q15 17 18 20 NPN
Q21 25 19 20 PNP
Q22 8 25 22 NPN
Q24 25 25 22 NPN
Q23B 22 14 8 PNP
R5 23 24 39K
R4 26 22 5K
R11 25 22 50K
CC 14 8 30PF
*
* DIFF AMP *
Q1 3 1 4 NPN
Q2 3 2 5 NPN
Q3 7 6 4 PNP
Q4 8 6 5 PNP
Q5 7 9 10 NPN
Q6 8 9 11 NPN
Q7 21 7 9 NPN
Q8 3 3 21 PNP
Q9 6 3 21 PNP
R1 10 22 1K
R2 11 22 1K
R3 9 22 50K

* DARLINGTON **
Q16 21 8 12 NPN
Q17 14 12 13 NPN
R9 12 22 50K
R8 13 22 100
* OUTPUT STAGE *
Q19 17 17 16 NPN
Q18 17 16 15 NPN
Q23A 22 14 15 PNP
Q14 21 17 18 NPN 3
Q20 22 15 19 SPNP
R10 16 15 40K
R6 18 20 27
R7 20 19 22
* POWER SUPPLY *
VCC 21 0 DC=15
VEE 22 0 DC=-15
*
** ANALYSIS **
*DC Sweep to find input offset voltage
*Connect output to inverting input for unity gain buffer
*Rshort 20 2 0.001
*VIN+ 1 0 DC 0 AC 0
*.DC VIN+ -15V +15V .1V
* Now provide input offset voltage
*VIN- 2 0 DC=851.325UV AC=0
*Open Loop Gain
*Remove Rshort
*VIN+ 1 0 AC=1
*VIN- 2 0 DC=851.325UV AC=0
*.AC DEC 20 1 10MEG

```

## SPICE File - Continued

```

*.TF V(20) VIN+
*Slew Rate - Connect output (node 20 to node 2 with +Rshort)
*VIN+ 1 0 PULSE (0 1 10us .001us .001us 10us 30us)
*.TRAN .5us 30us
*
.MODEL NPN NPN(IS=5E-15 RB=200 RC=250 BF=250 +BR=2 RE=2 VA=130 TF=.35NS CJE=1PF PE=.7V ME=.33
+CJC=.3PF PC=.55V MC=.5 CCS=3PF PS=.52 MS=.5V)
*
.MODEL PNP PNP(IS=2E-15 RB=300 RC=300 RE=10 +BF=50 BR=4 VA=50 TF=30NS CJE=.3PF PE=.55V ME=.5
+CJC=2PF PC=.55V MC=.5 CCS=3PF PS=.52V MS=.5V)
.MODEL SPNP PNP(IS=1E-14 RB=150 RC=50 RE=2 BR=4 BF=50 VA=50 TF=20NS CJE=.5PF PE=.55V ME=.5
+CJC=2PF PC=.52V MC=.5 CCS=3PF PS=.52V MS=.5V)
*
.OPTIONS LIMPTS=0
.PROBE
.END

```

## Node Voltages

\*\*\*\* SMALL SIGNAL BIAS SOLUTION      TEMPERATURE = 27.000 DEG C      \*\*\*\*

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
( 1)	0.0000	( 2)	851.3E-06	( 3)	14.4120	( 4)	-0.5442	( 5)	-0.5437
( 6)	-1.1088	( 7)	-13.8950	( 8)	-13.4680	( 9)	-14.4460	( 10)	-14.9920
(11)	-14.9920	(12)	-14.0460	(13)	-14.7480	(14)	-1.3208	(15)	-0.6239
(16)	0.0454	(17)	0.6180	(18)	0.0079	(19)	-0.0064	(20)	-5.094E-06
(21)	15.0000	(22)	-15.0000	(23)	14.3030	(24)	-14.3330	(25)	-15.0000
(26)	-14.9020								

## Bipolar Junction Transistors

NAME	Q1	Q2	Q3	Q4	Q5
MODEL	NPN	NPN	PNP	PNP	NPN
IB	3.44E-08	3.48E-08	-1.20E-07	-1.23E-07	3.74E-08
IC	<b>7.63E-06</b>	<b>7.73E-06</b>	<b>-7.55E-06</b>	<b>-7.65E-06</b>	<b>7.50E-06</b>
VBE	5.44E-01	5.45E-01	-5.65E-01	-5.65E-01	5.46E-01
VBC	-1.44E+01	-1.44E+01	1.28E+01	1.24E+01	-5.51E-01
VCE	1.50E+01	1.50E+01	-1.34E+01	-1.29E+01	1.10E+00
BETADC	2.22E+02	2.22E+02	6.28E+01	6.24E+01	2.01E+02
GM	2.95E-04	2.99E-04	2.92E-04	2.95E-04	2.90E-04
RPI	7.53E+05	7.43E+05	2.15E+05	2.11E+05	6.92E+05
RX	2.00E+02	2.00E+02	3.00E+02	3.00E+02	2.00E+02
RO	1.89E+07	1.87E+07	8.32E+06	8.16E+06	1.74E+07
CBE	1.59E-12	1.59E-12	9.40E-12	9.52E-12	1.59E-12
CBC	5.75E-14	5.75E-14	4.06E-13	4.13E-13	2.12E-13
CJS	5.60E-13	5.60E-13	5.70E-13	5.78E-13	4.31E-11
BETAAC	2.22E+02	2.22E+02	6.28E+01	6.23E+01	201.00
FT/FT2	2.85E+07	2.88E+07	4.73E+06	4.74E+06	2.5600e+07

NAME	Q6	Q7	Q8	Q9	Q16
MODEL	NPN	NPN	PNP	PNP	NPN
IC	<b>7.52E-06</b>	<b>1.11E-05</b>	<b>-1.48E-05</b>	<b>-1.93E-05</b>	<b>3.04E-05</b>

## Bipolar Junction Transistors - Continued

NAME	Q12	Q11	Q10	Q13A	Q13B
MODEL	PNP	NPN	NPN	PNP	PNP
IB	-1.34E-05	3.66E-06	8.88E-08	-1.28E-05	-3.8200e-05
IC	<b>-6.70E-04</b>	<b>7.31E-04</b>	<b>1.96E-05</b>	<b>-8.13E-04</b>	<b>-2.50E-03</b>
VBE	-6.97E-01	6.67E-01	5.69E-01	-6.97E-01	-0.69700
VBC	0.00E+00	0.00E+00	-1.32E+01	1.37E+01	1.56E+01
VCE	-6.97E-01	6.67E-01	1.38E+01	-1.44E+01	0.0000
BETADC	4.98E+01	2.00E+02	2.20E+02	6.34E+01	0.0000
GM	2.59E-02	2.82E-02	7.57E-04	3.14E-02	0.096500
RPI	1.92E+03	7.07E+03	2.91E+05	2.02E+03	677.00
RX	3.00E+02	2.00E+02	2.00E+02	3.00E+02	100.00

NAME	Q17	Q19	Q18	Q23A	Q14	Q20
MODEL	NPN	NPN	NPN	PNP	NPN	SNPN
IC	<b>2.51E-03</b>	<b>2.06E-05</b>	<b>7.91E-04</b>	<b>-8.04E-04</b>	<b>2.90E-04</b>	<b>-2.87E-04</b>
VBE	7.02E-01	5.73E-01	6.69E-01	-6.97E-01	6.10E-01	6.10E-01


### Comparison:

Transistor	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	Q9	Q10	Q11
Caculated	9.5 $\mu$ A	9.5 $\mu$ A	9.5 $\mu$ A	9.5 $\mu$ A	9.5 $\mu$ A	9.5 $\mu$ A	11.3 $\mu$ A	19 $\mu$ A	19 $\mu$ A	19 $\mu$ A	733 $\mu$ A
SPICE	7.63 $\mu$ A	7.73 $\mu$ A	7.75 $\mu$ A	7.65 $\mu$ A	7.50 $\mu$ A	7.52 $\mu$ A	11.1 $\mu$ A	14.8 $\mu$ A	19.3 $\mu$ A	19.6 $\mu$ A	731 $\mu$ A

Transistor	Q11	Q12	Q12	Q13A	Q13B	Q14	Q16	Q17	Q18	Q19	Q20
Caculated	733 $\mu$ A	733 $\mu$ A	733 $\mu$ A	813 $\mu$ A	550 $\mu$ A	150 $\mu$ A	16.5 $\mu$ A	550 $\mu$ A	164 $\mu$ A	15.7 $\mu$ A	150 $\mu$ A
SPICE	731 $\mu$ A	670 $\mu$ A	670 $\mu$ A	813 $\mu$ A	2500 $\mu$ A	290 $\mu$ A	30 $\mu$ A	2510 $\mu$ A	791 $\mu$ A	20.6 $\mu$ A	287 $\mu$ A

## 741 PSpice Simulation Results
 
### Dynamic Range and Input Offset Voltage:





### **SUMMARY**

- The 741 is a classic Op Amp that exemplifies many of our ECE 6412 circuit concepts
- DC bias in almost all transistors is set by  $R_5$
- Hand calculated and PSpice bias currents compare favorably (except for Q13B)