

## LECTURE 230 – 741 FREQUENCY RESPONSE

### (READING: GHLM – 537-544)

#### Objective

The objective of this presentation is:

- 1.) Illustrate the frequency analysis of a complex amplifier
- 2.) Examine both dominant and non-dominant poles

#### Outline

- Analysis of the high frequency response
- -3dB frequency
- Slew rate
- Summary

## HIGH FREQUENCY RESPONSE OF THE 741 OP AMP

### Simplified Schematic of the 741 Op Amp with Idealized Biasing

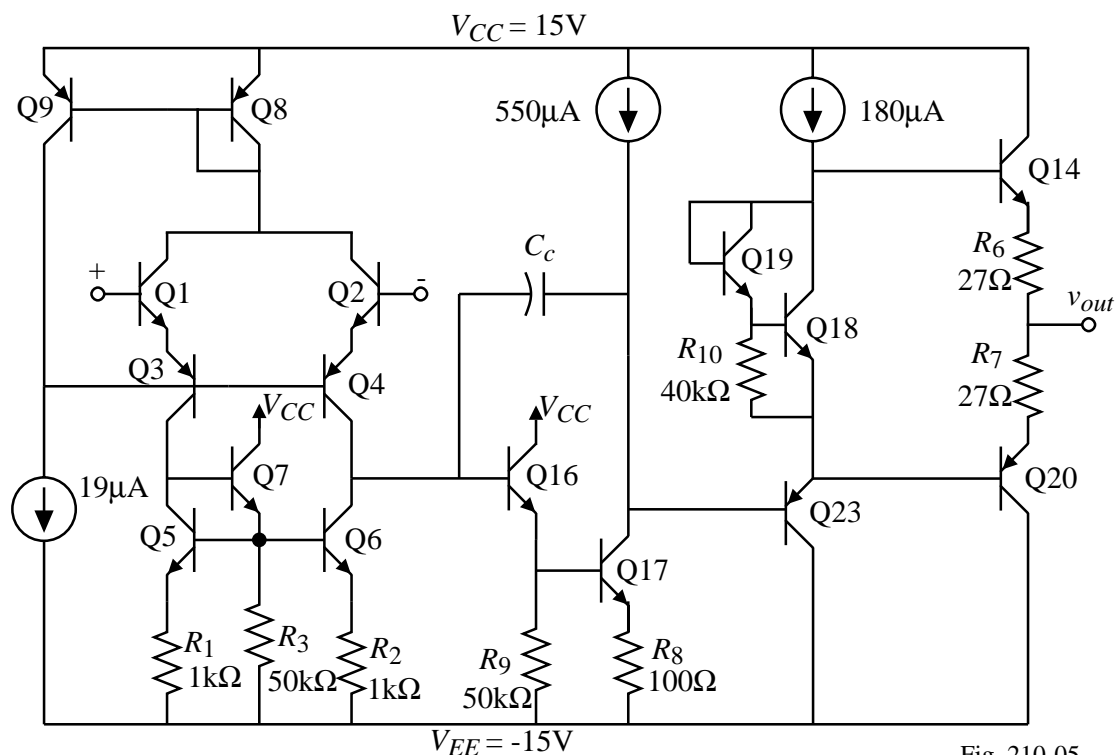


Fig. 210-05

## AC Schematic of the High-Frequency Gain Path of the 741

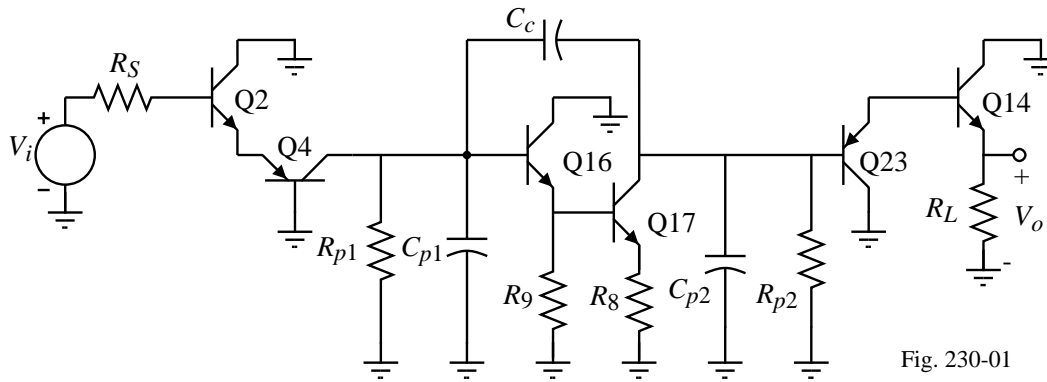


Fig. 230-01

AC Calculations:

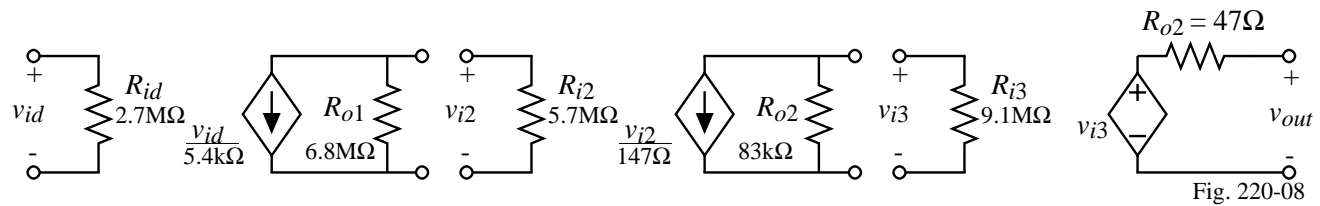


Fig. 220-08

$$R_{p1} = R_{o1} = 6.8M\Omega, \quad R_9 = 50k\Omega, \quad R_8 = 100\Omega, \quad \text{and} \quad R_{p2} = r_{o13B}$$

## Calculation of the -3dB Frequency

Use the open-circuit time constant approach on  $C_c$ .

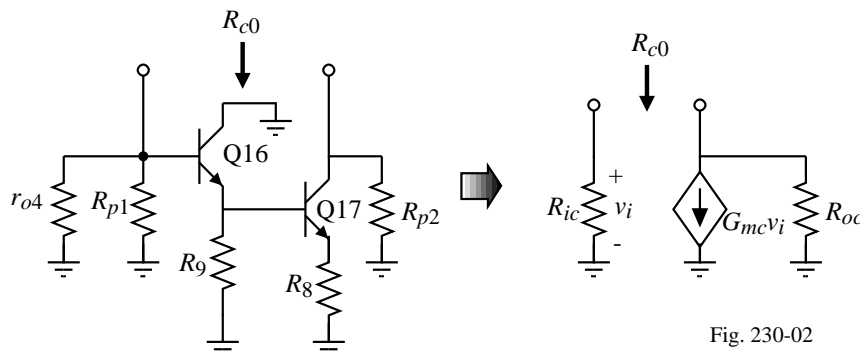


Fig. 230-02

$$R_{ic} = r_{o4} || R_{p1} || R_{i2}: \quad r_{o4} = \frac{V_{AP}}{I_{C4}} = 5.26M\Omega, \quad R_{i2} = r_{\pi 16} + (\beta_N + 1)(R_9 || R_{eq1}) = 5.72M\Omega$$

$$\therefore R_{ic} = 5.26M\Omega || 6.8M\Omega || 5.72M\Omega = 1.95M\Omega$$

$$R_{oc} = r_{o17T} || r_{o13B}:$$

$$r_{o17T} = V_{AN}/I_{C17} = 130V/550\mu A = 236.4k\Omega, \quad r_{o17T} = r_{o17}(1 + g_{m17}R_8) = 732.3k\Omega$$

$$r_{o13B} = V_{AP}/I_{C13B} = 50V/550\mu A = 90.9k\Omega$$

$$\therefore R_{oc} = 732.3k\Omega || 90.9k\Omega = 80.8k\Omega$$

$$G_{mc} = 6.39mA/V$$

### Calculation of the –3dB Frequency - Continued

Using the previous results of the open-circuit time constant gives,

$$R_{co} = R_{ic} + R_{oc} + G_{mc}R_{ic}R_{oc} = [1.95 + 0.0808 + (6.39)(80.8)(1950)]\text{M}\Omega = 1.007 \times 10^9 \Omega$$

$$\therefore C_c R_{co} = 30\text{pF} \cdot 1.007 \times 10^9 \Omega = 0.0302 \text{ seconds} \Rightarrow f_{-3\text{dB}} = \frac{1}{2\pi C_c R_{co}} = 5.27 \text{ Hz}$$

An alternate approach:

Use Miller's theorem to reflect  $C_c$  to the input of the Darlington second stage.


$$C_{eq} = (1 + A_{v2}) C_c = 545 C_c = 16.4 \text{ nF} \quad R_{Load1} = R_{ic} = 1.95 \text{ M}\Omega$$

$$f_{dom} = \frac{1}{2\pi R_{Load1} C_{eq}} = 4.97 \text{ Hz}$$

$$GB = A_{v1} A_{v2} f_{dom} = (565)(544.3)(4.97 \text{ Hz}) = 1.53 \text{ MHz}$$
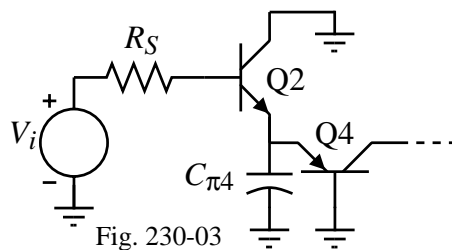
### Nondominant Poles of the 741

Many of the nondominant poles are difficult to calculate, however the following is an example one that is relatively easy. Consider the pole caused by  $C_{\pi4}$  in the circuit shown.



We will ignore the frequency of Q2 because it is npn and has a much higher  $f_T$ .

From previous work we calculated that  $g_{m2} = g_{m4} = 0.46 \text{ mA/V}$ . Assuming that  $C_{je} = 0.6 \text{ pF}$  and  $\tau_F = 25 \text{ ns}$  for the lateral pnp gives,

$$C_{b4} = \tau_F g_{m4} = 25 \times 10^{-9} \cdot 0.46 \times 10^{-3} = 10.75 \text{ pF} \Rightarrow C_{\pi4} = C_{b4} + C_{je} = 11.35 \text{ pF}$$

The open-circuit time resistance seen from  $C_{\pi4}$  is

$$R_{\pi04} = \frac{1}{2g_{m2}} = 1087 \Omega \Rightarrow \text{Nondominant pole} = \frac{1}{2\pi C_{\pi4} R_{\pi04}} = 12.9 \text{ MHz}$$

(Computer results show a pole at –15MHz)

## Nondominant Poles – Continued

Another pole exists at the output of the second stage.

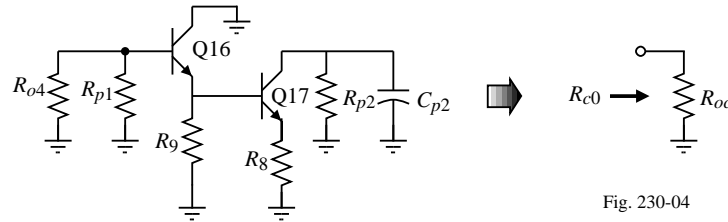


Fig. 230-04

We have calculated previously that  $R_{oc} = 80.8\text{k}\Omega$ .

The value of  $C_{p2}$  is approximately,  $C_{jc23} + C_{cs17} \approx 1\text{pF}$

$$\text{Another nondominant pole} = \frac{1}{2\pi C_{p2} R_{oc}} = 1.97\text{MHz}$$

(This is the second pole of Millers compensation)

## Slew Rate for the 741 Op Amp

The current available to charge and discharge the compensation capacitor  $C_c$  is  $2I_{C4} = 19\mu\text{A}$ . Therefore the slew rate is

$$SR = \frac{2I_{C4}}{C_c} = \frac{2(9.5\mu\text{A})}{30\text{pF}} = 0.64\text{V}/\mu\text{S}$$

### **SUMMARY**

- The  $-3\text{dB}$  frequency of a complex amplifier is reasonably easy to calculate
- Calculation of higher-order poles is more difficult
- Slew rate for the 741 op amp is slightly less than  $1\text{V}/\mu\text{s}$