

## LECTURE 240 – SIMULATION AND MEASUREMENTS OF OP AMPS (READING: AH – 310-323)

### Simulation and Measurement Considerations

Objectives:

- The objective of simulation is to verify and optimize the design.
- The objective of measurement is to experimentally confirm the specifications.

Similarity Between Simulation and Measurement:


- Same goals
- Same approach or technique

Differences Between Simulation and Measurement:

- Simulation can idealize a circuit
- Measurement must consider all nonidealities
 
### Simulating or Measuring the Open-Loop Transfer Function of the Op Amp

Circuit (Darkened op amp identifies the op amp under test):



Simulation:

This circuit will give the voltage transfer function curve. This curve should identify:

- 1.) The linear range of operation
- 2.) The gain in the linear range
- 3.) The output limits
- 4.) The systematic input offset voltage
- 5.) DC operating conditions, power dissipation
- 6.) When biased in the linear range, the small-signal frequency response can be obtained
- 7.) From the open-loop frequency response, the phase margin can be obtained ( $F = 1$ )

Measurement:

This circuit probably will not work unless the op amp gain is very low.

## A More Robust Method of Measuring the Open-Loop Frequency Response

Circuit:

 


Fig. 240-02

Resulting Closed-Loop Frequency Response:

 


Fig. 240-03

Make the  $RC$  product as large as possible.

## Simulation and Measurement of Open-Loop Frequency Response with Moderate Gain Op Amps

 


Fig. 240-04

Make  $R$  as large and measure  $v_{out}$  and  $v_i$  to get the open loop gain.

## Simulation or Measurement of the Input Offset Voltage of an Op Amp

 


Fig. 240-05

Types of offset voltages:

- 1.) Systematic offset - due to mismatches in current mirrors, exists even with ideally matched transistors.
- 2.) Mismatch offset - due to mismatches in transistors (normally not available in simulation except through Monte Carlo methods).

## Simulation of the Common-Mode Voltage Gain

 


Fig. 240-06

Make sure that the output voltage of the op amp is in the linear region.

### Measurement of CMRR and PSRR

Configuration:

Note that  $v_I \approx \frac{v_{OS}}{1000}$  or  $v_{OS} \approx 1000v_I$

How Does this Circuit Work?

CMRR:

- 1.) Set  $V_{DD}' = V_{DD} + 1V$   
 $V_{SS}' = V_{SS} + 1V$   
 $v_{OUT}' = v_{OUT} + 1V$
- 2.) Measure  $v_{OS}$  called  $v_{OS1}$
- 3.) Set  $V_{DD}' = V_{DD} - 1V$   
 $V_{SS}' = V_{SS} - 1V$   
 $v_{OUT}' = v_{OUT} - 1V$
- 4.) Measure  $v_{OS}$  called  $v_{OS2}$
- 5.)

PSRR:

- 1.) Set  $V_{DD}' = V_{DD} + 1V$   
 $V_{SS}' = V_{SS}$   
 $v_{OUT}' = 0V$
- 2.) Measure  $v_{OS}$  called  $v_{OS3}$
- 3.) Set  $V_{DD}' = V_{DD} - 1V$   
 $V_{SS}' = V_{SS}$   
 $v_{OUT}' = 0V$
- 4.) Measure  $v_{OS}$  called  $v_{OS4}$
- 5.)

$$CMRR = \frac{2000}{|v_{OS2} - v_{OS1}|}$$

$$PSRR^+ = \frac{2000}{|v_{OS4} - v_{OS3}|}$$

 


Fig. 240-07

Note:

- 1.) PSRR<sup>-</sup> can be measured similar to PSRR<sup>+</sup> by changing only  $V_{SS}$ .
- 2.) The  $\pm 1V$  perturbation can be replaced by a sinusoid to measure CMRR or PSRR as follows:

$$PSRR^+ = \frac{1000 \cdot v_{dd}}{v_{os}}, \quad PSRR^- = \frac{1000 \cdot v_{ss}}{v_{os}}$$

and  $CMRR = \frac{1000 \cdot v_{cm}}{v_{os}}$

### How Does the Previous Idea Work?

A circuit is shown which is used to measure the CMRR and PSRR of an op amp. Prove that the CMRR can be given as

$$CMRR = \frac{1000 v_{icm}}{v_{os}}$$

Solution

The definition of the common-mode rejection ratio is

$$CMRR = \left| \frac{A_{vd}}{A_{cm}} \right| = \frac{(v_{out}/v_{id})}{(v_{out}/v_{icm})}$$

However, in the above circuit the value of  $v_{out}$  is the same so that we get

$$CMRR = \frac{v_{icm}}{v_{id}}$$

But  $v_{id} = v_i$  and  $v_{os} \approx 1000v_i = 1000v_{id} \Rightarrow v_{id} = \frac{v_{os}}{1000}$

Substituting in the previous expression gives,  $CMRR = \frac{v_{icm}}{\frac{v_{os}}{1000}} = \frac{1000 v_{icm}}{v_{os}}$

 


Fig. 240-08

## Simulation of CMRR of an Op Amp

None of the above methods are really suitable for simulation of *CMRR*.

Consider the following:

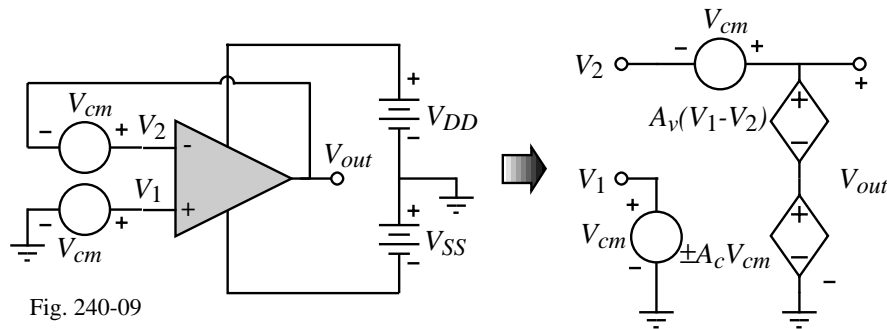


Fig. 240-09

$$V_{out} = A_v(V_1 - V_2) \pm A_{cm} \left( \frac{V_1 + V_2}{2} \right) = -A_v V_{out} \pm A_{cm} V_{cm}$$

$$V_{out} = \frac{\pm A_{cm}}{1 + A_v} V_{cm} \approx \frac{\pm A_{cm}}{A_v} V_{cm}$$

$$\therefore \boxed{|CMRR| = \frac{A_v}{A_{cm}} = \frac{V_{cm}}{V_{out}}}$$

(However,  $PSRR^+ = PSRR^-$ )

## CMRR of Ex. 6.3-1 using the Above Method of Simulation


 


Fig. 240-10

### Simulation or Measurement of *ICMR*

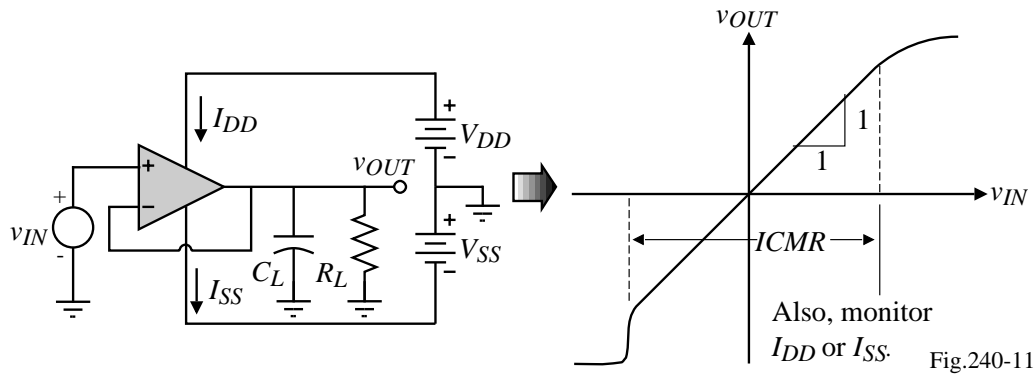


Initial jump in sweep is due to the turn-on of M5.

Should also plot the current in the input stage (or the power supply current).


### Measurement or Simulation of the Open-Loop Output Resistance

Method 1:

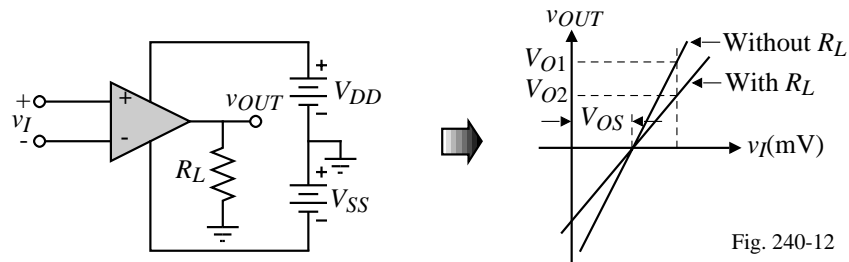

$$R_{out} = R_L \left( \frac{V_{O1}}{V_{O2}} - 1 \right) \quad \text{or vary } R_L \text{ until } V_{O2} = 0.5V_{O1} \Rightarrow R_{out} = R_L$$

Method 2:

 

$$R_{out} = \left( \frac{1}{R_o} + \frac{1}{100R} + \frac{A_v}{100R_o} \right)^{-1} \cong \frac{100R_o}{A_v}$$

## Measurement or Simulation of Slew Rate and Settling Time

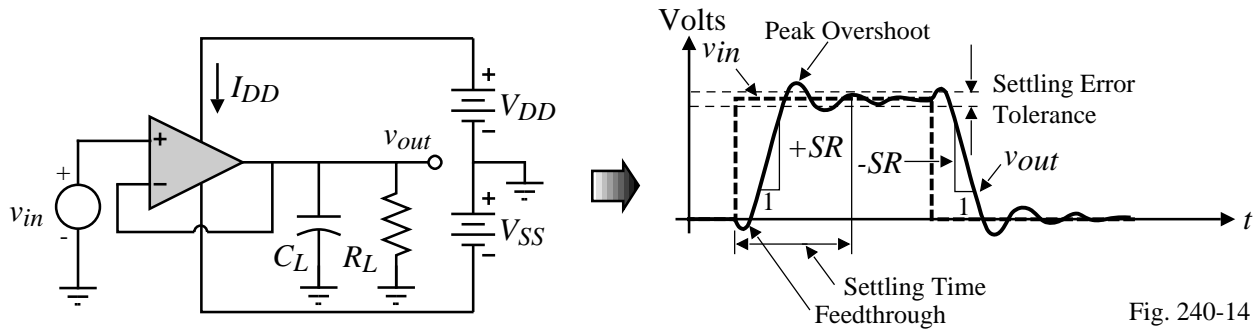


Fig. 240-14

If the slew rate influences the small signal response, then make the input step size small enough to avoid slew rate (i.e. less than 0.5V for MOS).

## Phase Margin and Peak Overshoot Relationship

It can be shown (Appendix C) that:

$$\text{Phase Margin (Degrees)} = 57.2958 \cos^{-1}[\sqrt{4\zeta^4 + 1} - 2\zeta^2]$$

$$\text{Overshoot (\%)} = 100 \exp\left(\frac{-\pi\zeta}{\sqrt{1-\zeta^2}}\right)$$

For example, a 5% overshoot corresponds to a phase margin of approximately  $64^\circ$ .

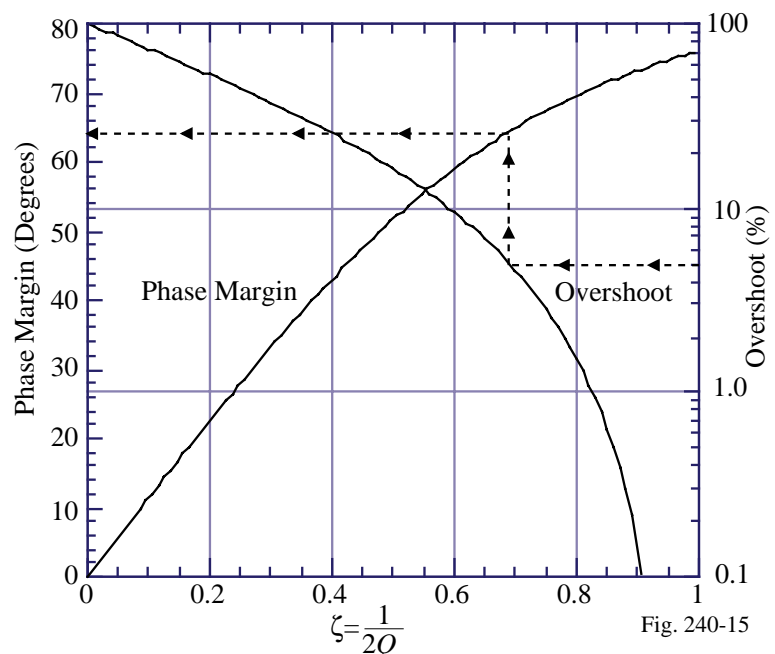


Fig. 240-15





**Example 1 - Continued**

PSPICE Input File for the Open-Loop Configuration:

EXAMPLE 1 OPEN LOOP CONFIGURATION

```
.OPTION LIMPTS=1000
```

```
VIN+ 1 0 DC 0 AC 1.0
```

```
VDD 4 0 DC 2.5
```

```
VSS 0 5 DC 2.5
```

```
VIN - 2 0 DC 0
```

```
CL 3 0 10P
```

```
X1 1 2 3 4 5 OPAMP
```

```
⋮
```

(Subcircuit of previous slide)

```
⋮
```

```
.OP
```

```
.TF V(3) VIN+
```

```
.DC VIN+ -0.005 0.005 100U
```

```
.PRINT DC V(3)
```

```
.AC DEC 10 1 10MEG
```

```
.PRINT AC VDB(3) VP(3)
```

```
.PROBE (This entry is unique to PSPICE)
```

```
.END
```

**Example 1 - Continued**

Open-loop transfer characteristic of Example 6.3-1:

 


Fig. 240-18

**Example 1 - Continued**

Open-loop transfer frequency response of Example 6.3-1:

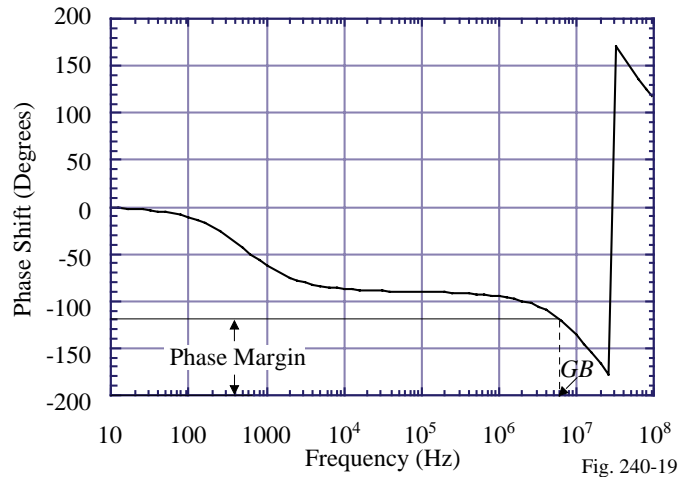
 


Fig. 240-19

**Example 1 - Continued**

Input common mode range of Example 6.3-1:

EXAMPLE 6.6-1 UNITY GAIN CONFIGURATION.

```
.OPTION LIMPTS=501
VIN+ 1 0 PWL(0 -2 10N -2 20N 2 2U 2 2.01U -2 4U -2 4.01U
+ -.1 6U -.1 6.0 1U .1 8U .1 8.01U -.1 10U -.1)
VDD 4 0 DC 2.5 AC 1.0
VSS 0 5 DC 2.5
CL 3 0 20P
X1 1 3 3 4 5 OPAMP
:
(Subcircuit of Table 6.6-1)
:
.DC VIN+ -2.5 2.5 0.1
.PRINT DC V(3)
.TRAN 0.05U 10U 0 10N
.PRINT TRAN V(3) V(1)
.AC DEC 10 1 10MEG
.PRINT AC VDB(3) VP(3)
.PROBE (This entry is unique to PSPICE)
.END
```

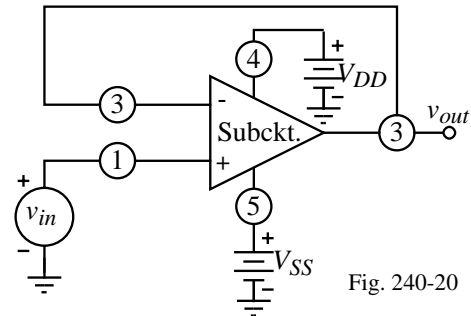


Fig. 240-20


 
 
 
 


Fig. 240-21

**Example 1 - Continued**Positive *PSRR* of Example 6.3-1:**Example 1 - Continued**Negative *PSRR* of Example 6.3-1:
 
### Example 1 – Continued

Large-signal and small-signal transient response of Example 6.3-1:



Why the negative overshoot on the slew rate?

If M7 cannot sink sufficient current then the output stage slews and only responds to changes at the output via the feedback path which involves a delay.

Note that  $-dv_{out}/dt \approx -2V/0.3\mu s = -6.67V/\mu s$ . For a 10pF capacitor this requires  $66.7\mu A$  and only  $95\mu A - 66.7\mu A = 28\mu A$  is available for  $C_C$ . For the positive slew rate, M6 can provide whatever current is required by the capacitors and can immediately respond to changes at the output.

 


Fig. 240-25

### Example 1 - Continued

Why is the negative-going overshoot larger than the positive-going overshoot on the small-signal transient response of the last slide?

Consider the following circuit and waveform:

 


Fig. 240-26

During the rise time,

(The material beneath this box is part of a homework solution)

**Example 1 - Continued**

Comparison of the Simulation Results with the Specifications of Example 6.3-1:

Specification (Power supply = $\pm 2.5\text{V}$ )	Design (Ex. 6.3-1)	Simulation (Ex. 1)
Open Loop Gain	$>5000$	10,000
GB (MHz)	5 MHz	5 MHz
Input CMR (Volts)	-1V to 2V	-1.2 V to 2.4 V,
Slew Rate (V/ $\mu\text{sec}$ )	$>10$ (V/ $\mu\text{sec}$ )	+10, -7(V/ $\mu\text{sec}$ )
P <sub>diss</sub> (mW)	$< 2\text{mW}$	0.625mW
V <sub>out</sub> range (V)	$\pm 2\text{V}$	+2.3V, -2.2V
PSRR+ (0) (dB)	-	87
PSRR- (0) (dB)	-	106
Phase margin (degrees)	$60^\circ$	$65^\circ$
Output Resistance (k $\Omega$ )	-	122.5k $\Omega$

**SUMMARY**

Simulation is a key step in electrical design - it is the step to verify and optimize

Measurement is a key step in the overall design - electrical→physical→measurement

Similarities between simulation and measurement:

- Same desired responses
- Same general method to approach the result

Dissimilarities between simulation and measurement:

- Measurement using nonideal components and simulation has ideal components
- Can access internal nodes with simulation
- Can create artificial configurations with simulation
- Parasitics are a problem with measurement