

LECTURE 270 – SERIES-SERIES FEEDBACK

(READING: GHLM – 569-579)

Objective

The objective of this presentation is:



- 1.) Illustrate the analysis of series-series feedback circuits

Outline

- Series-series feedback with nonideal source and load
- Examples
- Summary

Series-Series Feedback including Source and Load Resistances

Configuration:

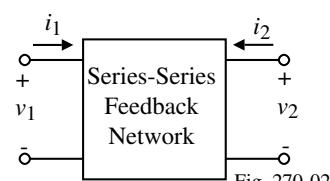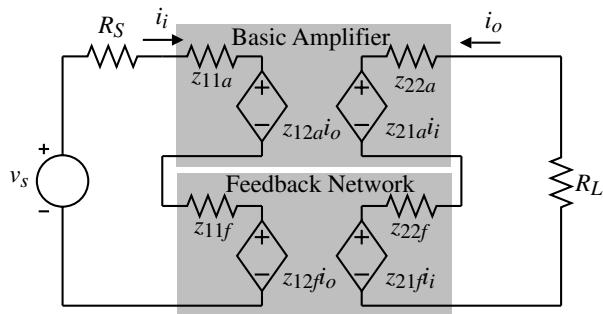

$$v_1 = z_{11}i_1 + z_{12}i_2$$

$$v_2 = z_{21}i_1 + z_{22}i_2$$

where for the new basic amplifier,

$$z_{11} = \frac{v_1}{i_1} \mid_{i_2=0} = R_S + z_{11a} + z_{11f}$$

$$z_{12} = \frac{v_1}{i_2} \mid_{i_1=0} = 0$$

$$z_{21} = \frac{v_2}{i_1} \mid_{i_2=0} = z_{21a}$$

$$z_{22} = \frac{v_2}{i_2} \mid_{i_1=0} = R_L + z_{22a} + z_{22f}$$

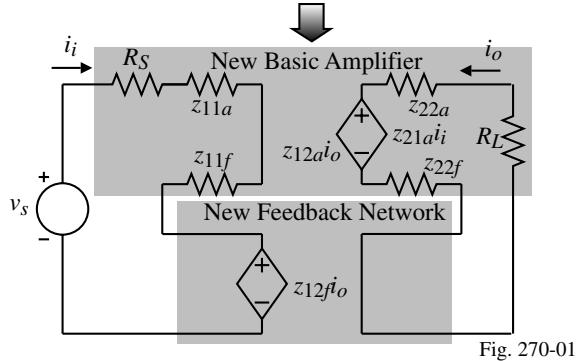


Fig. 270-01

$$\frac{i_o}{v_s} = \frac{i_2}{v_1} = A = \frac{a}{1+af} = \frac{(-z_{21a}/z_{11}z_{22})}{1+(-z_{21a}/z_{11}z_{22})z_{12f}} \Rightarrow a = \frac{-z_{21a}}{z_{11}z_{22}} \quad \text{and} \quad f = z_{12f}$$

Example 1 – Two-Transistor Feedback Amplifier

For the amplifier shown, find v_2/v_1 , v_1/i_1 , and v_2/i_2 .

Assume that $r_{\pi 1} = r_{\pi 2} = 1000\Omega$ and $\beta_{F1} = \beta_{F2} = 150$ for the BJTs.

Solution

1.) Topology identification. We see that the circuit is series-series, negative feedback. Also, note that R_S is “outside” the feedback circuit.

2.) Closed loop small-signal model is shown below.

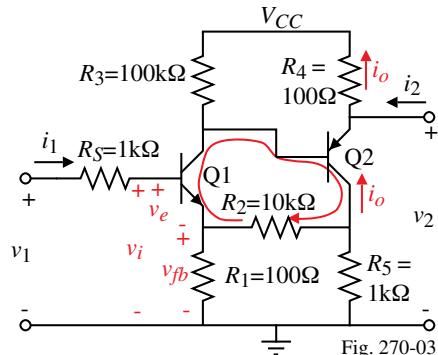


Fig. 270-03

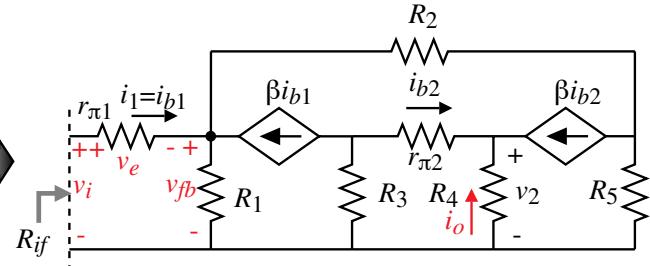
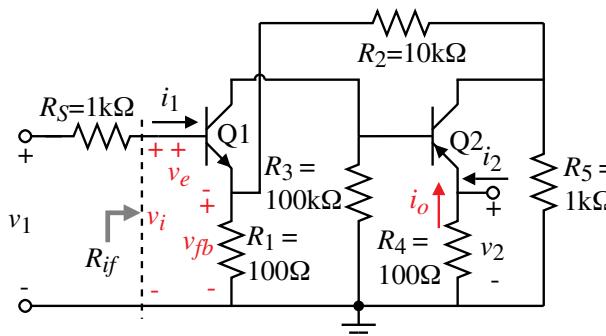


Fig. 270-04

3.) Break open the loop by finding the loading effects of the feedback network on the amplifier. This involves finding z_{11f} and z_{22f} .

Example 1 – Continued

3.) Continued

$$z_{11f} = \frac{v_{1f}}{i_{1f}} \Big|_{i_2=i_o=0}$$

(Resistance seen looking back into the feedback network from the input with $i_o = 0$.)

$$\therefore z_{11f} = R_2 + R_5$$

$$z_{22f} = \frac{v_{2f}}{i_{2f}} \Big|_{i_1=i_i=0}$$

(Resistance seen looking back into the feedback network from the input with $i_i = 0$.)

$$\therefore z_{22f} = R_1 + R_5$$

4.) Open-circuit small-signal model:

$$f = \frac{v_{fb}'}{i_{1f}'} = \left(\frac{v_{fb}'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_{o'}'} \right) = \left(\frac{-\beta R_5}{R_1 + R_2 + R_5} \times R_1 \right) \left(\frac{1}{1 + \beta} \right)$$

$$\approx \frac{-R_1 R_5}{R_1 + R_2 + R_5} = -9.009\Omega$$

$$a = \frac{i_{o'}'}{v_i'} = \left(\frac{i_{o'}'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_{b1}'} \right) \left(\frac{i_{b1}'}{v_i'} \right) =$$

$$(1 + \beta) \left(\frac{-\beta R_3}{R_3 + r_{\pi 2} + (1 + \beta) R_4} \right) \left(\frac{1}{r_{\pi 1} + (1 + \beta) [R_1 \parallel (R_2 + R_5)]} \right)$$

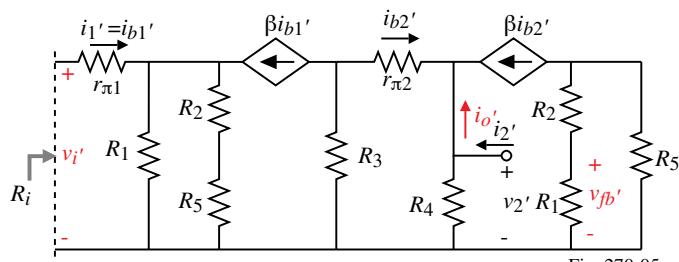


Fig. 270-05

$$= (151) \left(\frac{-150 \cdot 100 \text{k}\Omega}{116.1 \text{k}\Omega} \right) \left(\frac{1}{15.96 \text{k}\Omega} \right) = -1.222 \text{S} \quad \Rightarrow \quad T = (-1.222)(-9.009) = 11.01$$

Example 1 – Continued

5.) Input resistance, v_1/i_1 .

$$R_i = r_{\pi 1} + (1+\beta)[R_1 \parallel (R_2 + R_5)] = 15.96 \text{k}\Omega \rightarrow R_{if} = R_i(1+T) = 15.96 \text{k}\Omega \cdot 12.01 = 191.73 \text{k}\Omega$$

However, we must add R_S to this to get the requested $v_1/i_1 = 192.73 \text{k}\Omega$

6.) Voltage gain, v_2/v_1 . First find i_o/v_i .

$$\frac{i_o}{v_i} = \frac{a}{1+af} = \frac{-1.222}{1+11.01} = -0.1017 \text{S}$$

$$\frac{v_2}{v_1} = \left(\frac{i_o R_4}{v_i} \right) \left(\frac{v_i}{v_1} \right) = \left(\frac{i_o}{v_i} \right) \left(\frac{v_i}{v_1} \right) R_4 = \left(\frac{i_o}{v_i} \right) \left(\frac{R_{if}}{R_{in}} \right) R_4 = (-0.1017) \left(\frac{191.73}{192.73} \right) (100) = -10.122 \text{V/V}$$

7.) Output resistance, v_2/i_2 . First, we must realize that the resistances involved with series input or output is *in series with the loop*. Consider the equivalent model of the output.

$$R_o = R_4 + \frac{r_{\pi 2} + R_3}{1+\beta} = 100 + \frac{101 \text{k}\Omega}{151} = 769 \text{\Omega}$$

$$R_{of} = R_o(1+af) = 769(12.01) = 9234 \text{\Omega}$$

But, this is not v_2/i_2 .


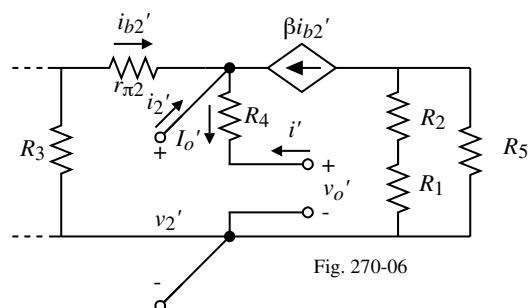
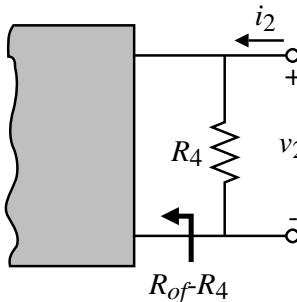


Fig. 270-06

Example 1 – Continued

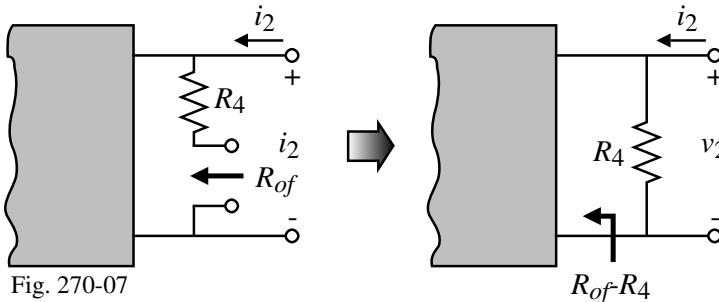- 8.) Use the model shown to calculate v_2/i_2 .



From this model, we see that



$$\frac{v_2}{i_2} = R_4 \parallel (R_{of} - R_4) = 100\Omega \parallel 9134\Omega = \underline{\underline{98.9\Omega}}$$

Example 2 – Series-Series Feedback Triple

For the amplifier shown, find v_2/v_1 , v_1/i_1 , and v_2/i_2 . Assume that all MOSFET transconductances are $1mS$.

Solution

- 1.) The feedback is negative, series-series feedback.
- 2.) Closed loop small-signal model is shown below.

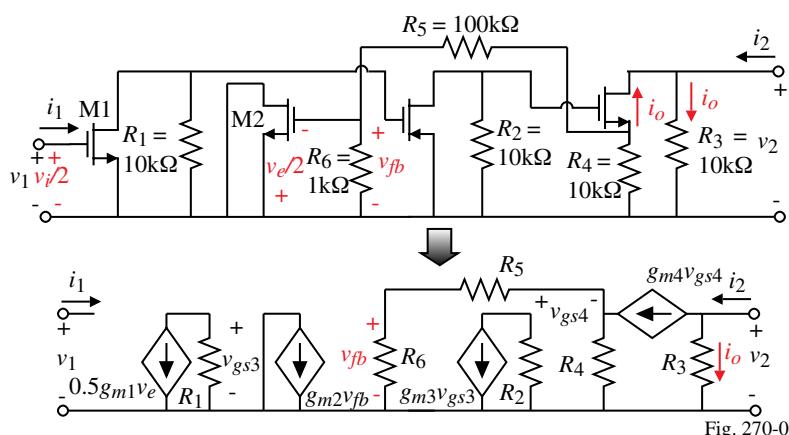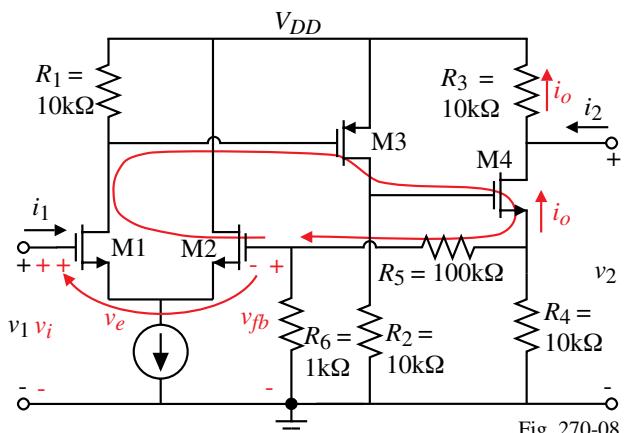

Example 2 – Continued

- 3.) Break open the loop by finding the loading effects of the feedback network on the amplifier. This involves finding z_{11f} and z_{22f} .

$$z_{11f} = \frac{v_{1f}}{i_{1f}} \Big|_{i_2=0} = R_4 + R_5$$

$$z_{22f} = \frac{v_{2f}}{i_{2f}} \Big|_{i_1=0} = R_5 + R_6$$

- 4.) The open-loop model is:

$$f = \frac{v_{fb'}}{i_o'} = \frac{-R_4 R_6}{R_4 + R_5 + R_6}$$

$$= \frac{-10 \cdot 1}{10 + 100 + 1} \text{ k}\Omega = -909 \Omega$$

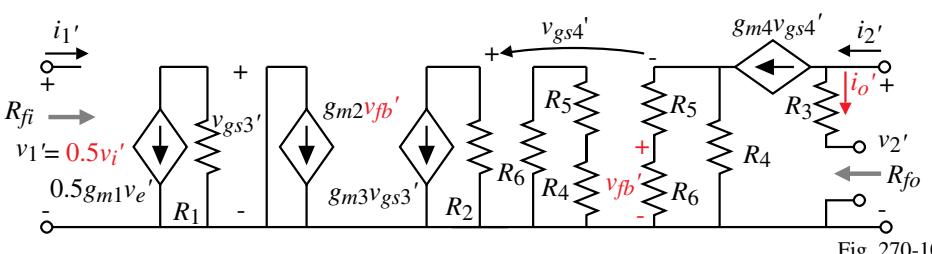


Fig. 270-10

$$a = \frac{i_o'}{v_i'} = \left(\frac{i_o'}{v_{gs4'}} \right) \left(\frac{v_{gs4'}}{v_{gs3'}} \right) \left(\frac{v_{gs3'}}{v_i'} \right) = (-g_m 4) \left(\frac{-g_m 3 R_2}{1 + g_m 4 [R_4 \parallel (R_5 + R_6)]} \right) \frac{-g_m 1 R_1}{2}$$

$$= (-1 \text{ mS})(-0.99)(-5) = -4.95 \text{ mS} \quad \Rightarrow \quad T = af = 4.5$$

- 5.) Input resistance, v_1/i_1 .

$$R_i = \infty \rightarrow R_{if} = R_i(1+T) = 5.5\infty = \underline{\underline{\infty}}$$

Example 2 – Continued

- 6.) Voltage gain, v_2/v_1 . First find i_o/v_i .

$$\frac{i_o}{v_i} = \frac{a}{1+af} = \frac{-4.95 \text{ mS}}{1+4.5} = -0.9 \text{ mS} \quad (1/f = -1.1 \text{ mS})$$

$$\frac{v_2}{v_1} = \left(\frac{i_o R_3}{v_i} \right) = (-0.9 \text{ mS})(10 \text{ k}\Omega) = \underline{\underline{-9.0 \text{ V/V}}}$$

- 7.) Output resistance, v_2/i_2 . However, since we have assumed that $r_{ds4} \approx \infty$, then

$$\frac{v_2}{i_2} = R_3 \parallel (R_{of} - R_3) = R_3 \parallel \infty = R_3 = \underline{\underline{10 \text{ k}\Omega}}$$

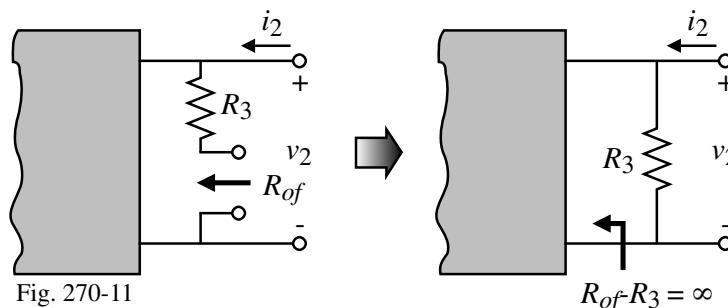


Fig. 270-11

$$R_{of} R_3 = \infty$$

(R_3 is not really inside the feedback loop and therefore is not influenced by the feedback.)

SUMMARY

- Series-series feedback increases both the input and output impedances
- If the mixing circuit is associated with the collector/drain (Example 1), then the output resistance designated as v_2/i_2 is found by finding R_{of} (which is the resistance *in series* with the output feedback loop) and using the following relationship,

$$\frac{v_2}{i_2} = R_L \parallel (R_{of} - R_L)$$

- If the mixing circuit is associated with the emitter/source (Example 2), then the output resistance designated as v_2/i_2 is simply equal to R_L .
- Several useful points to emphasize:
 - 1.) If $T \gg 1$, then $A \approx 1/f$.
 - 2.) The product of a and f must always be positive for negative feedback