

## LECTURE 300 – BUFFERED OP AMPS (READING: AH – 352-368)

### **Objective**

The objective of this presentation is:


- 1.) Illustrate the method of lowering the output resistance of simple op amps
- 2.) Show examples

### **Outline**

- Open-loop, MOSFET buffered op amps
- Closed-loop MOSFET buffered op amps
- BJT output op amps
- Summary
 
### **Goal**

To illustrate the degrees of freedom and choices of different circuit architectures that can enhance the performance of a given op amp.



### **What is a Buffered Op Amp?**

A buffered op amp is an op amp with a low value of output resistance,  $R_o$ .

Typically,  $10\Omega \leq R_o \leq 1000\Omega$

### **Requirements**

Generally the same as for the output amplifier:

- Low output resistance
- Large output signal swing
- Low distortion
- High efficiency

### **Types of Buffered Op Amps**

- Buffered op amps using MOSFETs
  - With and without negative feedback
- Buffered op amps using BJTs

### Source-Follower, Push-Pull Output Op Amp

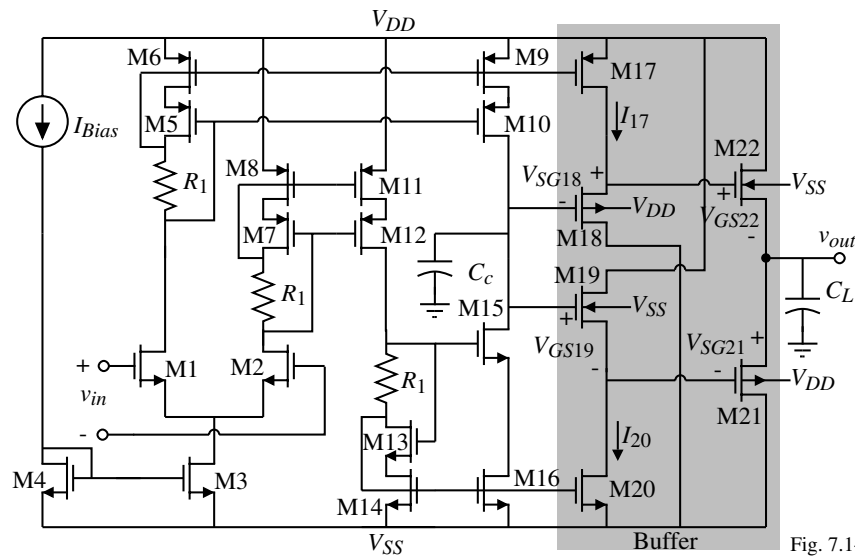


Fig. 7.1-1

$$R_{out} = \frac{1}{g_{m21} + g_{m22}} \leq 1000\Omega, A_v(0) = 65\text{dB} (I_{Bias} = 50\mu\text{A}), \text{ and } GB = 60\text{MHz for } C_L = 1\text{pF}$$

Output bias current?

$$M18\text{-}M19\text{-}M21\text{-}M22 \text{ loop} \Rightarrow V_{SG18} + V_{GS19} = V_{SG21} + V_{GS22}$$

which gives 
$$\sqrt{\frac{2I_{18}}{K_P S_{18}}} + \sqrt{\frac{2I_{19}}{K_N S_{19}}} = \sqrt{\frac{2I_{21}}{K_P S_{21}}} + \sqrt{\frac{2I_{22}}{K_N S_{22}}}$$

### Crossover-Inverter, Buffer Stage Op Amp

Principle: If the buffer has high output resistance and voltage gain (common source), this is okay if when loaded by a small  $R_L$  the gain of this stage is approximately unity.

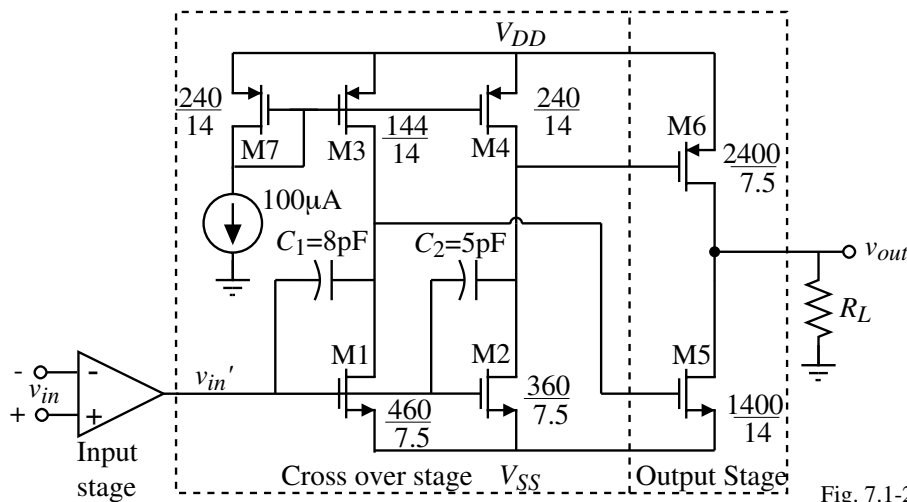


Fig. 7.1-2

This op amp is capable of delivering 160mW to a 100Ω load while only dissipating 7mW of quiescent power!

## Crossover-Inverter, Buffer Stage Op Amp - Continued

How does the output buffer work?

The two inverters, M1-M3 and M2-M4 are designed to work over different regions of the buffer input voltage,  $v_{in}'$ .

Consider the idealized voltage transfer characteristic of the crossover inverters:

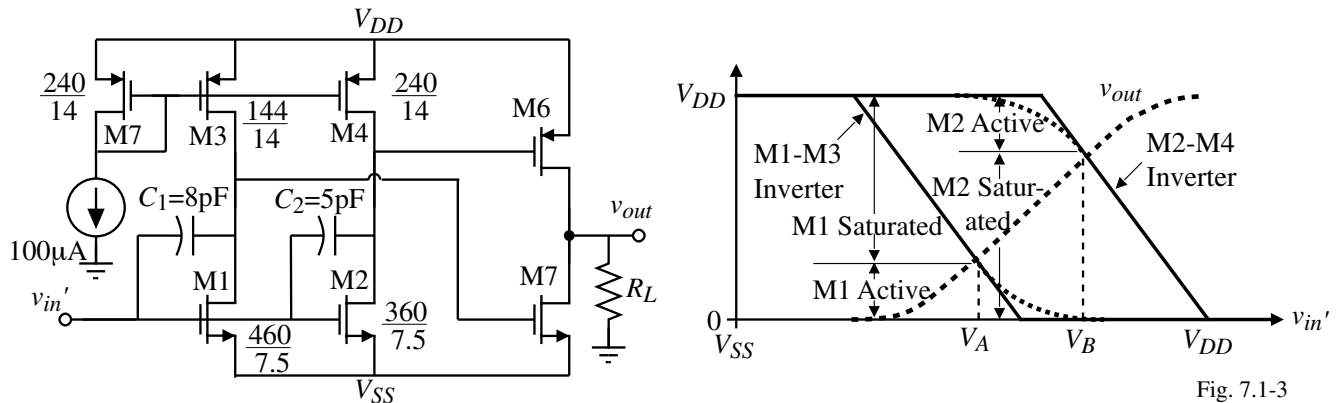


Fig. 7.1-3

Crossover voltage  $\equiv V_C = V_B - V_A \geq 0$

$V_C$  is designed to be small and positive for worst case variations in processing (Maximum value of  $V_C \approx 110$  mV)

## Crossover-Inverter, Buffer Stage Op Amp - Continued

Performance Results for the Crossover-Inverter, Buffer Stage CMOS Op Amp

Specification	Performance
Supply Voltage	$\pm 6$ V
Quiescent Power	7 mW
Output Swing (100 $\Omega$ Load)	8.1 V <sub>pp</sub>
Open-Loop Gain (100 $\Omega$ Load)	78.1 dB
Unity Gainbandwidth	260kHz
Voltage Spectral Noise Density at 1kHz	1.7 $\mu$ V/ $\sqrt{\text{Hz}}$
PSRR at 1kHz	55 dB
CMRR at 1kHz	42 dB
Input Offset Voltage (Typical)	10 mV

### Compensation of Op Amps with Output Amplifiers

Compensation of a three-stage amplifier:

This op amp introduces a third pole,  $p'_3$  (what about zeros?)

With no compensation,

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-A_{vo}}{\left(\frac{s}{p'_1} - 1\right)\left(\frac{s}{p'_2} - 1\right)\left(\frac{s}{p'_3} - 1\right)}$$


 


Fig. 7.1-4

Illustration of compensation choices:

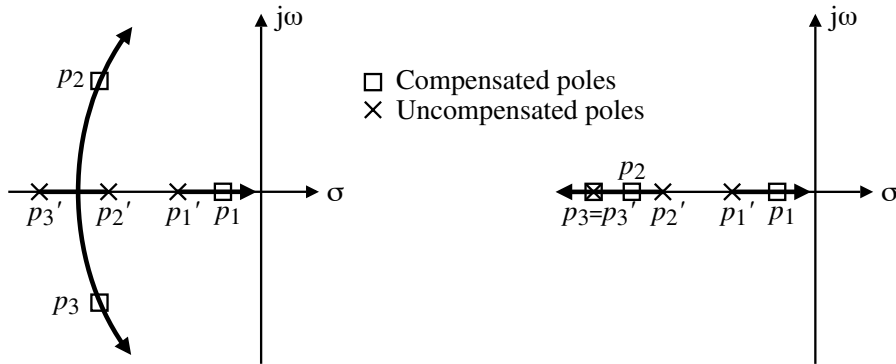

Miller compensation applied around both the second and the third stage.

Miller compensation applied around the second stage only.

Fig. 7.1-5

### Low Output Resistance Op Amp

To get low output resistance using MOSFETs, negative feedback must be used.

Ideal implementation:

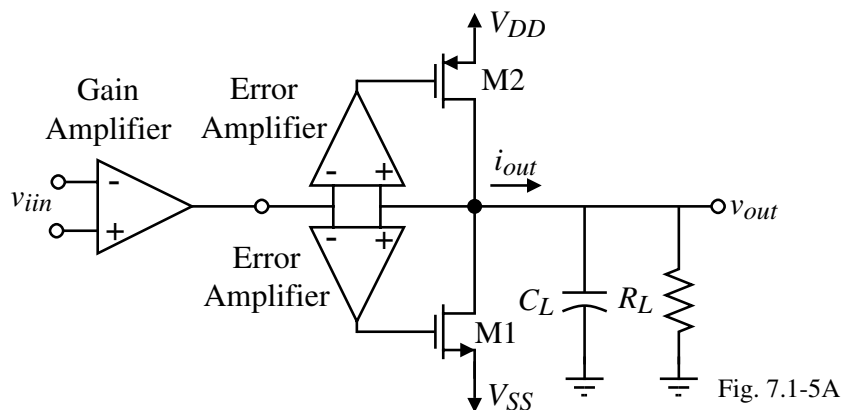



Fig. 7.1-5A

Comments:

- The output resistance will be equal to  $r_{ds1} || r_{ds2}$  divided by the loop gain
- If the error amplifiers are not perfectly matched, the bias current in M1 and M2 is not defined

## Low Output Resistance Op Amp - Continued

Offset correction circuitry:

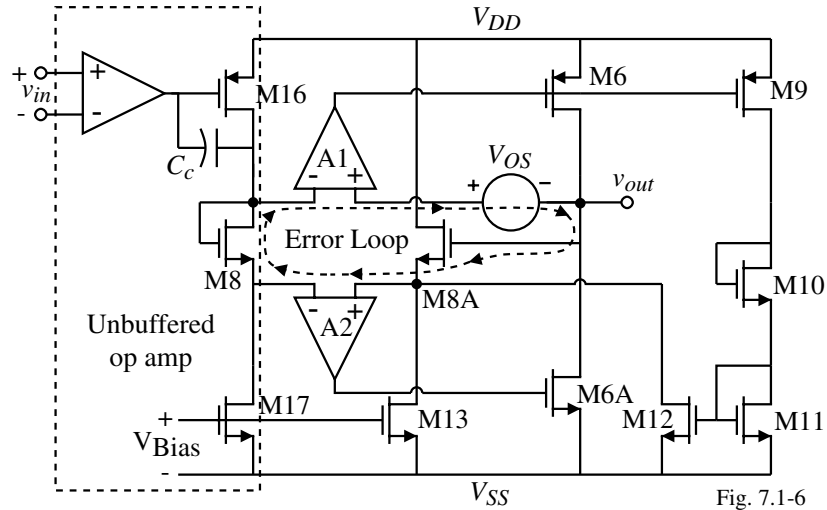


The feedback circuitry of the two error amplifiers tries to insure that the voltages in the loop sum to zero. Without the M9-M12 feedback circuit, there is no way to adjust the output for any error in the loop. The circuit works as follows:


When  $V_{OS}$  is positive, M6 tries to turn off and so does M6A.  $I_{M9}$  reduces thus reducing  $I_{M12}$ . A reduction in  $I_{M12}$  reduces  $I_{M8A}$  thus decreasing  $V_{GS8A}$ .  $V_{GS8A}$  ideally decreases by an amount equal to  $V_{OS}$ . A similar result holds for negative offsets and offsets in EA2.

## Low Output Resistance Op Amp - Continued

Error amplifiers:

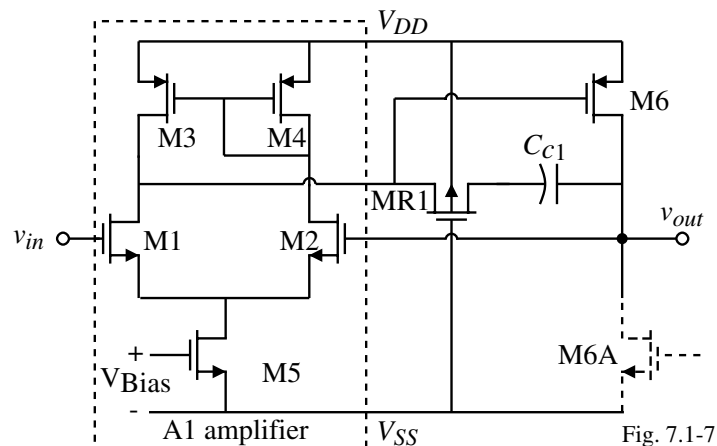
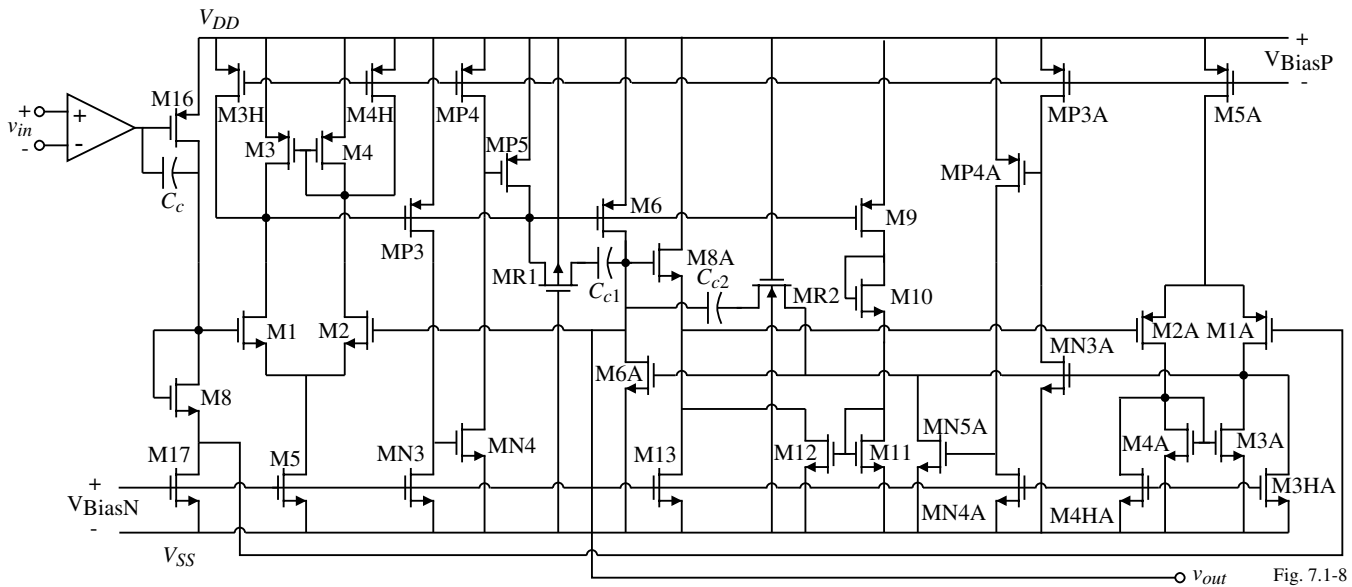
## Low Output Resistance Op Amp - Complete Schematic



### Compensation:


Uses nulling Miller compensation.

### Short circuit protection:

MP3-MN3-MN4-MP4-MP5

MN3A-MP3A-MP4A-MN4A-MN5A

(max. output  $\pm 60\text{mA}$ )

 

## Low Output Resistance Op Amp - Continued

Table 7.1-2 Performance Characteristics of the Low Output Resistance Op Amp:

Specification	Simulated Results	Measured Results
Power Dissipation	7.0 mW	5.0 mW
Open Loop Voltage Gain	82 dB	83 dB
Unity Gainbandwidth	500kHz	420 kHz
Input Offset Voltage	0.4 mV	1 mV
PSRR <sup>+</sup> (0)/PSRR <sup>-</sup> (0)	85 dB/104 dB	86 dB/106 dB
PSRR <sup>+</sup> (1kHz)/PSRR <sup>-</sup> (1kHz)	81 dB/98 dB	80 dB/98 dB
THD ( $V_{in} = 3.3\text{V}_{pp}$ )		
$R_L = 300\Omega$	0.03%	0.13%(1 kHz)
$C_L = 1000\text{pF}$	0.08%	0.32%(4 kHz)
THD ( $V_{in} = 4.0\text{V}_{pp}$ )		
$R_L = 15\text{K}\Omega$	0.05%	0.13%(1 kHz)
$C_L = 200\text{pF}$	0.16%	0.20%(4 kHz)
Settling Time (0.1%)	3 $\mu\text{s}$	<5 $\mu\text{s}$
Slew Rate	0.8 V/ $\mu\text{s}$	0.6 V/ $\mu\text{s}$
1/f Noise at 1kHz	-	130 nV/ $\sqrt{\text{Hz}}$
Broadband Noise	-	49 nV/ $\sqrt{\text{Hz}}$

$$R_{out} \approx \frac{r_{ds6} || r_{ds6A}}{\text{Loop Gain}} \approx \frac{50\text{k}\Omega}{5000} = 10\Omega$$

## Low-Output Resistance Op Amp - Continued

Component sizes for the low-resistance op amp:

Transistor/Capacitor	$\mu\text{m}/\mu\text{m}$ or pF	Transistor/Capacitor	$\mu\text{m}/\mu\text{m}$ or pF
M16	184/9	M8A	481/6
M17	66/12	M13	66/12
M8	184/6	M9	27/6
M1, M2	36/10	M10	6/22
M3, M4	194/6	M11	14/6
M3H, M4H	16/12	M12	140/6
M5	145/12	MP3	8/6
M6	2647/6	MN3	244/6
MRC	48/10	MP4	43/12
$C_C$	11.0	MN4	12/6
M1A, M2A	88/12	MP5	6/6
M3A, M4A	196/6	MN3A	6/6
M3HA, M4HA	10/12	MP3A	337/6
M5A	229/12	MN4A	24/12
M6A	2420/6	MP4A	20/12
$C_F$	10.0	MN5A	6/6

## Simpler Implementation of Negative Feedback to Achieve Low Output Resistance

 


Fig. 7.1-9

Output Resistance:

$$R_{out} = \frac{R_o}{1+LG}$$

where

$$R_o = \frac{1}{g_{ds6}+g_{ds7}}$$

and

$$|LG| = \frac{g_{m2}}{2g_{m4}} (g_{m6}+g_{m7})R_o$$

Therefore, the output resistance is

$$R_{out} = \frac{1}{(g_{ds6}+g_{ds7}) \left[ 1 + \left( \frac{g_{m2}}{2g_{m4}} \right) (g_{m6}+g_{m7})R_o \right]}$$

### Example 7.1-1 - Low Output Resistance Using the Simple Shunt Negative Feedback Buffer

Find the output resistance of above op amp using the model parameters of Table 3.1-2.

#### Solution

The current flowing in the output transistors, M6 and M7, is 1mA which gives  $R_o$  of

$$R_o = \frac{1}{(\lambda_N + \lambda_P)1\text{mA}} = \frac{1000}{0.09} = 11.11\text{k}\Omega$$

To calculate the loop gain, we find that

$$g_{m2} = \sqrt{2K_N' \cdot 10 \cdot 100\mu\text{A}} = 469\mu\text{S}$$

$$g_{m4} = \sqrt{2K_P' \cdot 1 \cdot 100\mu\text{A}} = 100\mu\text{S}$$

and

$$g_{m6} = \sqrt{2K_P' \cdot 10 \cdot 1000\mu\text{A}} = 1\text{mS}$$

Therefore, the loop gain is

$$|LG| = \frac{469}{100} \cdot 12 \cdot 11.11 = 104.2$$

Solving for the output resistance,  $R_{out}$ , gives

$$R_{out} = \frac{11.11\text{k}\Omega}{1 + 104.2} = 106\Omega \quad (\text{Assumes that } R_L \text{ is large})$$

### BJTs Available in CMOS Technology

Illustration of an NPN substrate BJT available in a p-well CMOS technology:

 


Fig. 7.1-10

Comments:

- $g_m$  of the BJT is larger than the FET so that the output resistance w/o feedback is lower
- Can use the lateral or substrate BJT but since the collector is on ac ground, the substrate BJT is preferred
- Current is required to drive the BJT



## Two-Stage Op Amp with a Class-A BJT Output Buffer Stage

Purpose of the M8-M9 source follower:

- 1.) Reduce the output resistance (includes whatever is seen from the base to ground divided by  $1+\beta_F$ )
- 2.) Reduces the output load at the drains of M6 and M7

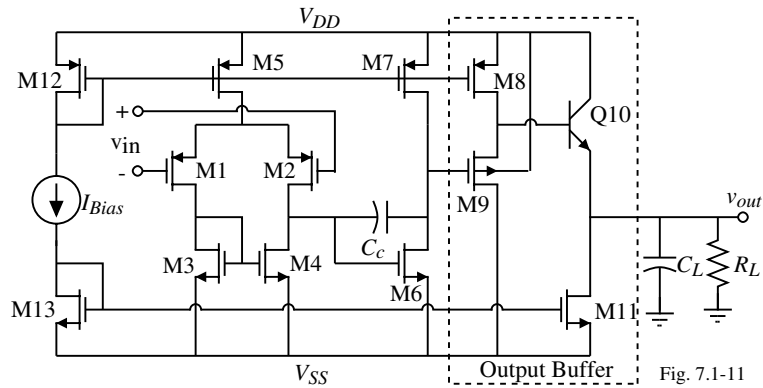


Fig. 7.1-11

Small-signal output resistance :

$$R_{out} \approx \frac{r_{\pi 10} + (1/g_{m9})}{1+\beta_F} = \frac{1}{g_{m10}} + \frac{1}{g_{m9}(1+\beta_F)}$$

$$= 51.6\Omega + 6.7\Omega = 58.3\Omega \text{ where } I_{10}=500\mu\text{A}, I_8=100\mu\text{A}, W_9/L_9=100 \text{ and } \beta_F \text{ is } 100$$

Maximum output voltage:

$$v_{OUT}(\text{max}) = V_{DD} - V_{SD8}(\text{sat}) - v_{BE10} = V_{DD} - \sqrt{\frac{2K_P'}{I_8(W_8/L_8)}} - V_t \ln\left(\frac{I_{c10}}{I_{s10}}\right)$$

Voltage gain:

$$\frac{v_{out}}{v_{in}} = \left(\frac{g_{m1}}{g_{ds2}+g_{ds4}}\right) \left(\frac{g_{m6}}{g_{ds6}+g_{ds7}}\right) \left(\frac{g_{m9}}{g_{m9}+g_{mbs9}+g_{ds8}+g_{\pi 10}}\right) \left(\frac{g_{m10}R_L}{1+g_{m10}R_L}\right)$$

Compensation will be more complex because of the additional stages.

### Example 7.1-2 - Designing the Class-A, Buffered Op Amp

Use the parameters of Table 3.1-2 along with the BJT parameters of  $I_s = 10^{-14}\text{A}$  and  $\beta_F = 100$  to design the class-A, buffered op amp to give the following specifications.

Assume the channel length is to be  $1\mu\text{m}$ .

$$V_{DD} = 2.5\text{V} \quad V_{SS} = -2.5\text{V} \quad \text{GB} = 5\text{MHz} \quad A_{vd}(0) \geq 5000\text{V/V} \quad \text{Slew rate} \geq 10\text{V}/\mu\text{s}$$

$$R_L = 500\Omega \quad R_{out} \leq 100\Omega \quad C_L = 100\text{pF} \quad \text{ICMR} = -1\text{V to } 2\text{V}$$

#### Solution

Because the specifications above are similar to the two-stage design of Ex. 6.3-1, we can use these results for the first two stages of our design. However, we must convert the results of Ex. 6.3-1 to a PMOS input stage. The results of doing this give  $W_1 = W_2 = 6\mu\text{m}$ ,  $W_3 = W_4 = 7\mu\text{m}$ ,  $W_5 = 11\mu\text{m}$ ,  $W_6 = 43\mu\text{m}$ , and  $W_7 = 34\mu\text{m}$ .

BJT follower:

$$SR = 10\text{V}/\mu\text{s} \text{ and } 100\text{pF} \text{ capacitor give } I_{11} = 1\text{mA}.$$

$$\therefore \text{ If } W_{13} = 44\mu\text{m}, \text{ then } W_{11} = 44\mu\text{m}(1000\mu\text{A}/30\mu\text{A}) = 1467\mu\text{m}.$$

$$I_{11} = 1\text{mA} \Rightarrow 1/g_{m10} = 0.0258\text{V}/1\text{mA} = 25.8\Omega$$

MOS follower:

To source 1mA, the BJT must provide 2mA which requires  $20\mu\text{A}$  from the MOS follower. Therefore, select a bias current of  $100\mu\text{A}$  for M8.

$$\text{ If } W_{12} = 44\mu\text{m}, \text{ then } W_8 = 44\mu\text{m}(100\mu\text{A}/30\mu\text{A}) = 146\mu\text{m}.$$

**Example 7.1-2 - Continued**

If  $1/g_{m10}$  is  $25.8\Omega$ , then design  $g_{m9}$  as

$$g_{m9} = \frac{1}{(R_{out} - (1/g_{m10}))(1+\beta_F)} = \frac{1}{(100-25.8)(101)} = 133.4\mu\text{S} \quad g_{m9} \text{ and } I_9 \Rightarrow W/L = 0.809$$

Let us select  $W/L = 10$  for M9 in order to make sure that the contribution of M9 to the output resistance is sufficiently small and to increase the gain closer to unity. This gives a transconductance of M9 of  $469\mu\text{S}$ .

To calculate the voltage gain of the MOS follower we need to find  $g_{mbs9}$ .

$$\therefore g_{mbs9} = \frac{g_{m9}\gamma_N}{2\sqrt{2\phi_F + V_{BS9}}} = \frac{469 \cdot 0.4}{2\sqrt{0.7+2}} = 57.1\mu\text{S}$$

where we have assumed that the value of  $V_{SB9}$  is approximately 2V.

$$\therefore A_{MOS} = \frac{469\mu\text{S}}{469\mu\text{S} + 57.1\mu\text{S} + 4\mu\text{S} + 5\mu\text{S}} = 0.8765 \text{ V/V.}$$

The voltage gain of the BJT follower is

$$A_{BJT} = \frac{500}{25.8+500} = 0.951 \text{ V/V}$$

Thus, the gain of the op amp is

$$A_{vd}(0) = (7777)(0.8765)(0.951) = 6483 \text{ V/V}$$

The power dissipation of this amplifier is,  $P_{diss.} = 5\text{V}(1255\mu\text{A}) = 6.27\text{mW}$

**Two-Stage Op Amp with a Class-AB BJT Output Buffer Stage**

This amplifier can reduce the quiescent power dissipation.

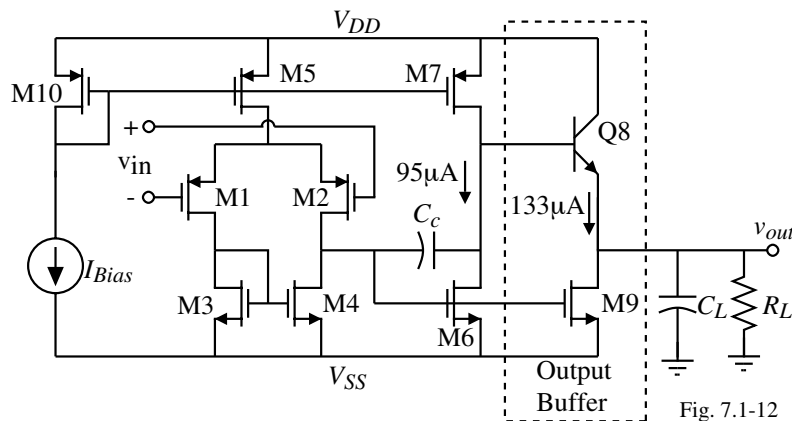


Fig. 7.1-12

Slew Rate:

$$SR^+ = \frac{I_{OUT}^+}{C_L} = \frac{(1 + \beta_F)I_7}{C_L} \quad \text{and} \quad SR^- = \frac{\beta_9(V_{DD} - 1\text{V} + |V_{SS}| - V_{T0})^2}{2C_L}$$

If  $\beta_F = 100$ ,  $C_L = 1000\text{pF}$  and  $I_7 = 95\mu\text{A}$  then  $SR^+ = 8.59\text{V}/\mu\text{s}$ .

Assuming a  $W_9/L_9 = 60$  ( $I_9 = 133\mu\text{A}$ ),  $\pm 2.5\text{V}$  power supplies and  $C_L = 1000\text{pF}$  gives  $SR^- = 35.9\text{V}/\mu\text{s}$ .

(The current is not limited by  $I_7$  as it is for the positive slew rate.)

## Two-Stage Op Amp with a Class-AB BJT Output Buffer Stage

Small-signal characteristics:

 


Fig. 7.1-13

Nodal equations:

$$g_{mI}V_{in} = (G_I + sC_c)V_1 - sC_cV_2 + 0V_{out}$$

$$0 = (g_{mII} - sC_c)V_1 + (G_{II} + g_{\pi} + sC_c + sC_{\pi})V_2 - (g_{\pi} + sC_{\pi})V_{out}$$

$$0 \approx g_{m9}V_1 - (g_{m13} + sC_{\pi})V_2 + (g_{m13} + sC_{\pi})V_{out} \quad \text{where } g_{\pi} > G_3$$

The approximate voltage transfer function is:

$$\frac{V_o(s)}{V_{in}(s)} \approx A_{v0} \frac{((s/z_1) - 1)((s/z_2) - 1)}{((s/p_1) - 1)((s/p_2) - 1)}$$

where

$$A_{v0} = \frac{-g_{mI}g_{mII}}{G_I G_{II}} \quad z_1 = \frac{1}{\frac{C_c}{g_{mII}} - \frac{C_{\pi}}{g_{m13}} \left[ 1 + \frac{g_{m9}}{g_{mII}} \right]}$$

$$z_2 = -\frac{g_{m13}}{C_{\pi}} + \frac{g_{mII}}{C_c} \left[ 1 + \frac{g_{m9}}{g_{mII}} \right]$$

$$p_1 = \frac{-G_I G_{II}}{g_{mII} C_c} \left[ 1 + \frac{g_{m9}}{\beta_F g_{mII}} + \frac{C_{\pi}}{C_c} \left( \frac{G_I G_{II}}{g_{m13} g_{mII}} \right) \right]^{-1}$$

$$p_2 \approx \frac{-g_{m13} g_{mII}}{(g_{mII} + g_{m9}) C_{\pi}}$$

## Two-Stage Op Amp with a Class-AB BJT Output Buffer Stage - Continued

Output stage current,  $I_{C8}$ :

$$I_{C8} = I_{D9} = \frac{S_9}{S_6} I_{D6} = \frac{60}{43} 95 \mu\text{A} = 133 \mu\text{A}$$

Small-signal output resistance:

$$r_{out} = \frac{r_{\pi} + R_{II}}{1 + \beta_F} = \frac{19.668 \text{ k}\Omega + 116.96 \text{ k}\Omega}{101} = 1353 \Omega$$

if  $I_6 = I_7 = 95 \mu\text{A}$ , and  $\beta_F = 100$ .

Loading effect of  $R_L$  on the voltage transfer curve (increasing  $W_9/L_9$  will improve the negative part at the cost of power dissipation):

 


Fig. 7.1-14A

### Example 7.1-3 - Performance of the Two-Stage, Class AB Output Buffer

Using the transistor currents given above for the output stages (output stage of the two-stage op amp and the buffer stage), find the small-signal output resistance and the maximum output voltage when  $R_L = 50\Omega$ . Use the W/L values of Example 7.1-2 and assume that the NPN BJT has the parameters of  $\beta_F = 100$  and  $I_S = 10\text{fA}$ .

#### Solution

It was shown on the previous slide that the small-signal output resistance is

$$r_{out} = \frac{r_{\pi} + r_{ds6} \parallel r_{ds7}}{1 + \beta_F} = \frac{19.668\text{k}\Omega + 116.96\text{k}\Omega}{101} = 1353\Omega$$

Obviously, the MOS buffer of Fig. 7.1-11 would decrease this value.

The maximum output voltage is given above is only valid if the load current is small. If this is not the case, then a better approach is to assume that all of the current in M7 becomes base current for Q8. This base current is multiplied by  $1 + \beta_F$  to give the sourcing current. If M9 is off, then all this current flows through the load resistor to give an output voltage of

$$v_{OUT(\text{max})} \approx (1 + \beta_F) I_7 R_L$$

If the value of  $v_{OUT(\text{max})}$  is close to  $V_{DD}$ , then the source-drain voltage across M7 may be too small to be in saturation causing  $I_7$  to decrease. Using the above equation, we calculate  $v_{OUT(\text{max})}$  as  $(101) \cdot 95\mu\text{A} \cdot 50\Omega$  or  $0.48\text{V}$  which is close to the simulation results shown using the parameters of Table 3.1-2.

### SUMMARY

- A buffered op amp requires an output resistance between  $10\Omega \leq R_o \leq 1000\Omega$
- Output resistance using MOSFETs only can be reduced by,
  - Source follower output ( $1/g_m$ )
  - Negative shunt feedback (frequency is a problem in this approach)
- Use of substrate (or lateral) BJT's can reduce the output resistance because  $g_m$  is larger than the  $g_m$  of a MOSFET
- Adding a buffer stage to lower the output resistance will most like complicate the compensation of the op amp