

## LECTURE 340 – LOW NOISE OP AMPS (READING: AH – 402-414, GHLM – 788-798)

### **Objective**

The objective of this presentation is:

- 1.) Review the principles of low noise design
- 2.) Show how to reduce the noise of op amps

### **Outline**

- Review of noise analysis
- Low noise op amps
- Low noise op amps using lateral BJTs
- Low noise op amps using doubly correlated sampling
- Summary

### **Introduction**

Why do we need low noise op amps?

Dynamic range:

Signal-to-noise ratio (*SNR*)

$$= \frac{\text{Maximum RMS Signal}}{\text{Noise}}$$

(*SNDR* includes both noise and distortion)


Consider a 14 bit digital-to-analog converter with a 1V reference with a bandwidth of 1MHz.

$$\text{Maximum RMS signal is } \frac{0.5V}{\sqrt{2}} = 0.3535 \text{ V}_{\text{rms}}$$

A 14 bit D/A converter requires 14x6dB dynamic range or 84 dB or 16,400.


$$\therefore \text{ The value of the least significant bit (LSB)} = \frac{0.3535}{16,400} = 21.6\mu\text{V}_{\text{rms}}$$

 If the equivalent input noise of the op amp is not less than this value, then the *LSB* cannot be resolved and the D/A converter will be in error. An op amp with an equivalent input-noise spectral density of  $10\text{nV}/\sqrt{\text{Hz}}$  will have an rms noise voltage of approximately  $(10\text{nV}/\sqrt{\text{Hz}})(1000\sqrt{\text{Hz}}) = 10\mu\text{V}_{\text{rms}}$  in a 1MHz bandwidth.



## Transistor Noise Sources (Low-Frequency)

Drain current model:

 


$$i_n^2 = \left[ \frac{8kTg_m}{3} + \frac{(KF)I_D}{fC_{ox}L^2} \right]$$

$$\text{or } i_n^2 = \left[ \frac{8kTg_m(1+\eta)}{3} + \frac{(KF)I_D}{fC_{ox}L^2} \right] \text{ if } v_{BS} \neq 0$$

$$\text{Recall that } \eta = \frac{g_m}{g_{mbs}}$$

 Gate voltage model assuming common source operation:



$$e_n^2 = \frac{\overline{i_N^2}}{g_m^2} = \left[ \frac{8kT}{3g_m} + \frac{KF}{2fC_{ox}WLK'} \right]$$

$$\text{or } e_n^2 = \left[ \frac{8kT(1+\eta)}{3g_m} + \frac{KF}{2fC_{ox}WLK'} \right] \text{ if } v_{BS} \neq 0$$

## Minimization of Noise in Op Amps

- 1.) Maximize the signal gain as close to the input as possible. (As a consequence, only the input stage will contribute to the noise of the op amp.)
- 2.) To minimize the  $1/f$  noise:
  - a.) Use PMOS input transistors with appropriately selected dc currents and  $W$  and  $L$  values.
  - b.) Use lateral BJTs to eliminate the  $1/f$  noise.
  - c.) Use chopper stabilization to reduce the low-frequency noise.

## Noise Analysis

- 1.) Insert a noise generator for each transistor that contributes to the noise. (Generally ignore the current source transistor of source-coupled pairs.)
- 2.) Find the output noise voltage across an open-circuit or output noise current into a short circuit.
- 3.) Reflect the total output noise back to the input resulting in the equivalent input noise voltage.

## A Low-Noise, Two-Stage, Miller Op Amp

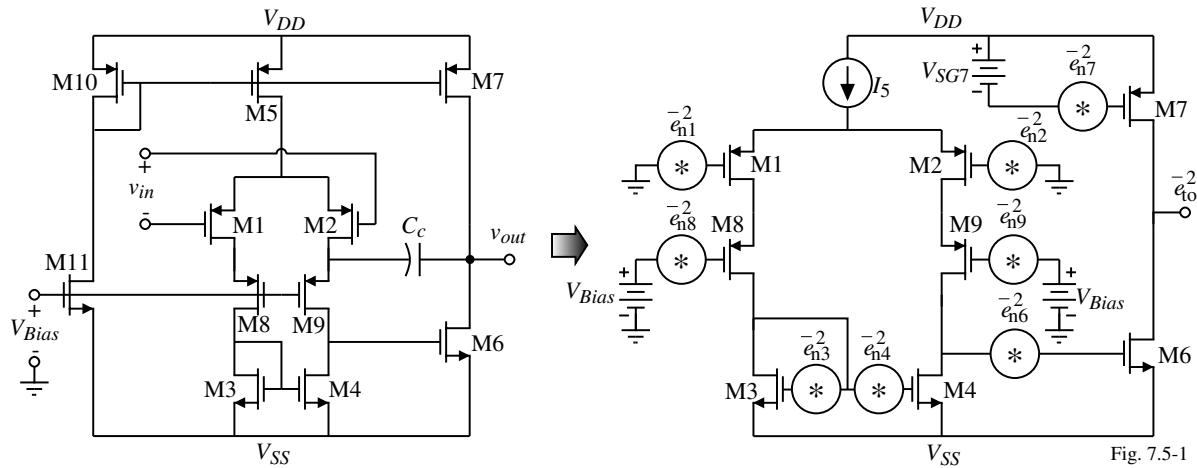


Fig. 7.5-1

The total output-noise voltage spectral density,  $e_{to}^2$ , is as follows where  $g_{m8}(\text{eff}) \approx 1/r_{ds1}$ ,

$$e_{to}^2 = g_{m6}^2 R_{II}^2 \left[ e_{n6}^2 + e_{n7}^2 + R_I^2 \left( g_{m1}^2 e_{n1}^2 + g_{m2}^2 e_{n2}^2 + g_{m3}^2 e_{n3}^2 + g_{m4}^2 e_{n4}^2 + (e_{n8}^2 / r_{ds1}^2) + (e_{n9}^2 / r_{ds2}^2) \right) \right]$$

Divide by  $(g_{m1} R_I g_{m6} R_{II})^2$  to get the eq. input-noise voltage spectral density,  $e_{eq}^2$ , as

$$e_{eq}^2 = \frac{e_{to}^2}{(g_{m1} g_{m6} R_I R_{II})^2} = \frac{2e_{n6}^2}{g_{m1}^2 R_I^2} + 2e_{n1}^2 \left[ 1 + \left( \frac{g_{m3}}{g_{m1}} \right)^2 \left( \frac{e_{n3}^2}{e_{n1}^2} \right) + \frac{e_{n8}^2}{g_{m1}^2 r_{ds1}^2 e_{n1}^2} \right] \approx 2e_{n1}^2 \left[ 1 + \left( \frac{g_{m3}}{g_{m1}} \right)^2 \left( \frac{e_{n3}^2}{e_{n1}^2} \right) \right]$$

where  $e_{n6}^2 = e_{n7}^2$ ,  $e_{n3}^2 = e_{n4}^2$ ,  $e_{n1}^2 = e_{n2}^2$  and  $e_{n8}^2 = e_{n9}^2$  and  $g_{m1} R_I$  is large.

## 1/f Noise of a Two-Stage, Miller Op Amp

Consider the 1/f noise:

Therefore the noise generators are replaced by,

$$e_{ni}^2 = \frac{B}{f W_i L_i} \quad (\text{V}^2/\text{Hz}) \quad \text{and} \quad i_{ni}^2 = \frac{2BK'I_i}{fL_i^2} \quad (\text{A}^2/\text{Hz})$$

Therefore, the approximate equivalent input-noise voltage spectral density is,

$$e_{eq}^2 = 2e_{n1}^2 \left[ 1 + \left( \frac{K_N' B_N}{K_P' B_P} \right) \left( \frac{L_1}{L_3} \right)^2 \right] \quad (\text{V}^2/\text{Hz})$$

Comments;

- Because we have selected PMOS input transistors,  $e_{n1}^2$  has been minimized if we choose  $W_1 L_1$  ( $W_2 L_2$ ) large.
- Make  $L_1 \ll L_3$  to remove the influence of the second term in the brackets.

## **Thermal Noise of a Two-Stage, Miller Op Amp**

Let us focus next on the thermal noise:

The noise generators are replaced by,

$$e_{ni}^2 \approx \frac{8kT}{3g_m} \quad (\text{V}^2/\text{Hz}) \quad \text{and} \quad i_{ni}^2 \approx \frac{8kTg_m}{3} \quad (\text{A}^2/\text{Hz})$$

where the influence of the bulk has been ignored.

The approximate equivalent input-noise voltage spectral density is,

$$e_{eq}^2 = 2e_{n1}^2 \left[ 1 + \left( \frac{g_{m3}}{g_{m1}} \right)^2 \left( \frac{e_{n3}^2}{e_{n1}^2} \right) \right] = 2e_{n1}^2 \left[ 1 + \sqrt{\frac{K_N W_3 L_1}{K_P W_1 L_3}} \right] \quad (\text{V}^2/\text{Hz})$$

Comments:

- The choices that reduce the  $1/f$  noise also reduce the thermal noise.

Noise Corner:

Equating the equivalent input-noise voltage spectral density for the  $1/f$  noise and the thermal noise gives the noise corner,  $f_c$ , as

$$f_c = \frac{3g_m B}{8kTWL}$$

## **Example 7.5-1 Design of A Two-Stage, Miller Op Amp for Low $1/f$ Noise**

Use the parameters of Table 3.1-2 along with the value of  $KF = 4 \times 10^{-28}$  F·A for NMOS and  $0.5 \times 10^{-28}$  F·A for PMOS and design the previous op amp to minimize the  $1/f$  noise. Calculate the corresponding thermal noise and solve for the noise corner frequency. From this information, estimate the rms noise in a frequency range of 1Hz to 100kHz. What is the dynamic range of this op amp if the maximum signal is a 1V peak-to-peak sinusoid?

Solution

1.) The  $1/f$  noise constants,  $B_N$  and  $B_P$  are calculated as follows.

$$B_N = \frac{KF}{2C_{ox}K_N'} = \frac{4 \times 10^{-28} \text{F} \cdot \text{A}}{2 \cdot 24.7 \times 10^{-4} \text{F/m}^2 \cdot 110 \times 10^{-6} \text{A}^2/\text{V}} = 7.36 \times 10^{-22} \quad (\text{V} \cdot \text{m})^2$$

and

$$B_P = \frac{KF}{2C_{ox}K_P'} = \frac{0.5 \times 10^{-28} \text{F} \cdot \text{A}}{2 \cdot 24.7 \times 10^{-4} \text{F/m}^2 \cdot 50 \times 10^{-6} \text{A}^2/\text{V}} = 2.02 \times 10^{-22} \quad (\text{V} \cdot \text{m})^2$$

2.) Now select the geometry of the various transistors that influence the noise performance.

To keep  $e_{n1}^2$  small, let  $W_1 = 100 \mu\text{m}$  and  $L_1 = 1 \mu\text{m}$ . Select  $W_3 = 100 \mu\text{m}$  and  $L_3 = 20 \mu\text{m}$  and let  $W_8$  and  $L_8$  be the same as  $W_1$  and  $L_1$  since they little influence on the noise.

**Example 7.5-1 - Continued**

Of course, M1 is matched with M2, M3 with M4, and M8 with M9.

$$\begin{aligned} \therefore e_{n1}^2 &= \frac{B_P}{fW_1L_1} = \frac{2.02 \times 10^{-22}}{f \cdot 100 \mu\text{m} \cdot 1 \mu\text{m}} = \frac{2.02 \times 10^{-12}}{f} \text{ (V}^2/\text{Hz)} \\ e_{eq}^2 &= 2 \times \frac{2.02 \times 10^{-12}}{f} \left[ 1 + \left( \frac{110 \cdot 7.36}{50 \cdot 2.02} \right)^2 \left( \frac{1}{20} \right)^2 \right] = \frac{4.04 \times 10^{-12}}{f} \cdot 1.1606 = \frac{4.689 \times 10^{-12}}{f} \text{ (V}^2/\text{Hz)} \end{aligned}$$

Note at 100Hz, the voltage noise in a 1Hz band is  $\approx 4.7 \times 10^{-14} \text{V}^2(\text{rms})$  or  $0.216 \mu\text{V}(\text{rms})$ .

3.) The thermal noise at room temperature is

$$e_{n1}^2 = \frac{8kT}{3g_m} = \frac{8 \cdot 1.38 \times 10^{-23} \cdot 300}{3 \cdot 707 \times 10^{-6}} = 1.562 \times 10^{-17} \text{ (V}^2/\text{Hz)}$$

which gives

$$e_{eq}^2 = 2 \cdot 1.562 \times 10^{-17} \left[ 1 + \sqrt{\frac{110 \cdot 100 \cdot 1}{50 \cdot 100 \cdot 20}} \right] = 3.124 \times 10^{-17} \cdot 1.33 = 4.164 \times 10^{-17} \text{ (V}^2/\text{Hz)}$$

4.) The noise corner frequency is found by equating the two expressions for  $e_{eq}^2$  to get

$$f_c = \frac{4.689 \times 10^{-12}}{4.164 \times 10^{-17}} = 112.6 \text{ kHz}$$

This noise corner is indicative of the fact that the thermal noise is much less than the 1/f noise.

**Example 7.5-1 - Continued**

5.) To estimate the rms noise in the bandwidth from 1Hz to 100,000Hz, we will ignore the thermal noise and consider only the 1/f noise. Performing the integration gives


$$\begin{aligned} V_{eq}(\text{rms})^2 &= \int_1^{10^5} \frac{4.689 \times 10^{-12}}{f} df = 4.689 \times 10^{-12} [\ln(100,000) - \ln(1)] \\ &= 0.540 \times 10^{-10} \text{ V}_{\text{rms}}^2 = 7.34 \mu\text{V}_{\text{rms}} \end{aligned}$$

The maximum signal in rms is 0.353V. Dividing this by 7.34 $\mu\text{V}$  gives 48,044 or 93.6dB which is equivalent to about 15 bits of resolution.


6.) Note that the design of the remainder of the op amp will have little influence on the noise and is not included in this example.
 
## Lateral BJT

Since the  $1/f$  noise is associated with current flowing at the surface of the channel, the lateral BJT offers a lower  $1/f$  noise input device because the majority of current flows beneath the surface.



Cross-section of a NPN lateral BJT.

 


Symbol. Fig. 7.5-3

Comments:


- Base of the BJT is the well
- Two collectors-one horizontal (desired) and one vertical (undesired)
- Collector efficiency is defined as  $\frac{\text{Lateral collector current}}{\text{Total collector current}}$  and is 60-70%
- Reverse biased collector-base acts like a photodetector and is often used for light-sensing purposes
 
## Field-Aided Lateral BJT

Polysilicon gates are used to ensure that the region beneath the gate does not invert forcing all current flow away from the surface and further eliminating the  $1/f$  noise.




 Cross-section of a field-aided NPN lateral BJT.



Symbol. Fig. 7.5-4
 
### Physical Layout of a Lateral PNP Transistor




Experimental Results for a x40 PNP lateral BJT:

Characteristic	Value
Transistor area	0.006mm <sup>2</sup>
Lateral $\beta$	90
Lateral efficiency	70%
Base resistance	150 $\Omega$
$e_n$ at 5 Hz	2.46nV/ $\sqrt{\text{Hz}}$
$e_n$ at midband	1.92nV/ $\sqrt{\text{Hz}}$
$f_c(e_n)$	3.2Hz
$i_n$ at 5 Hz	3.53pA/ $\sqrt{\text{Hz}}$
$i_n$ at midband	0.61pA/ $\sqrt{\text{Hz}}$
$f_c(i_n)$	162 Hz
$f_T$	85 MHz
Early voltage	16V
1.2 $\mu\text{m}$ CMOS with n-well	


Generally, the above structure is made as small as possible and then paralleled with identical geometries to achieve the desired BJT.

### Low-Noise Op Amp using Lateral BJT's at the

### Input

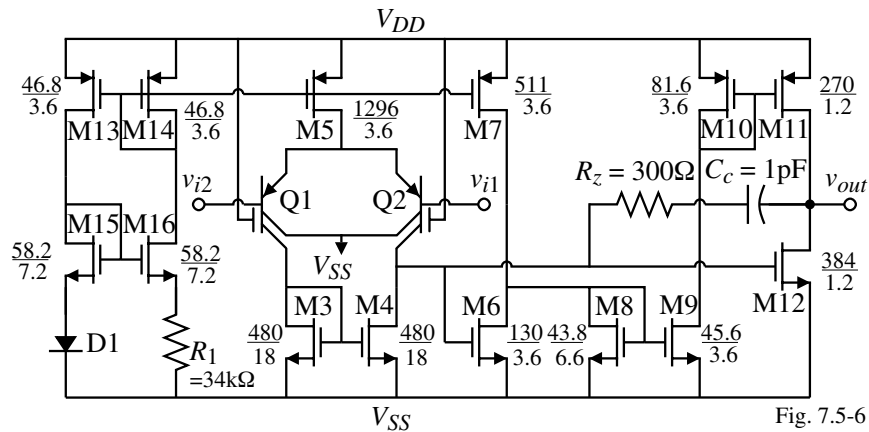

Experimental noise performance:

 

## Summary of Experimental Performance for the Low-Noise Op Amp

Experimental Performance	Value
Circuit area (1.2 $\mu\text{m}$ )	0.211 mm <sup>2</sup>
Supply Voltages	$\pm 2.5$ V
Quiescent Current	2.1 mA
-3dB frequency (at a gain of 20.8 dB)	11.1 MHz
$e_n$ at 1Hz	23.8 nV/ $\sqrt{\text{Hz}}$
$e_n$ (midband)	3.2 nV/ $\sqrt{\text{Hz}}$
$f_c(e_n)$	55 Hz
$i_n$ at 1Hz	5.2 pA/ $\sqrt{\text{Hz}}$
$i_n$ (midband)	0.73 pA/ $\sqrt{\text{Hz}}$
$f_c(i_n)$	50 Hz
Input bias current	1.68 $\mu\text{A}$
Input offset current	14.0 nA
Input offset voltage	1.0 mV
CMRR(DC)	99.6 dB
PSRR+(DC)	67.6 dB
PSRR-(DC)	73.9 dB
Positive slew rate (60 pF, 10 k $\Omega$ load)	39.0 V/ $\mu\text{S}$
Negative slew rate (60 pF, 10 k $\Omega$ load)	42.5 V/ $\mu\text{S}$

## Chopper-Stabilized Op Amps - Doubly Correlated Sampling (DCS)

Illustration of the use of chopper stabilization to remove the undesired signal,  $v_u$ , from the desired signal,  $v_{in}$ .


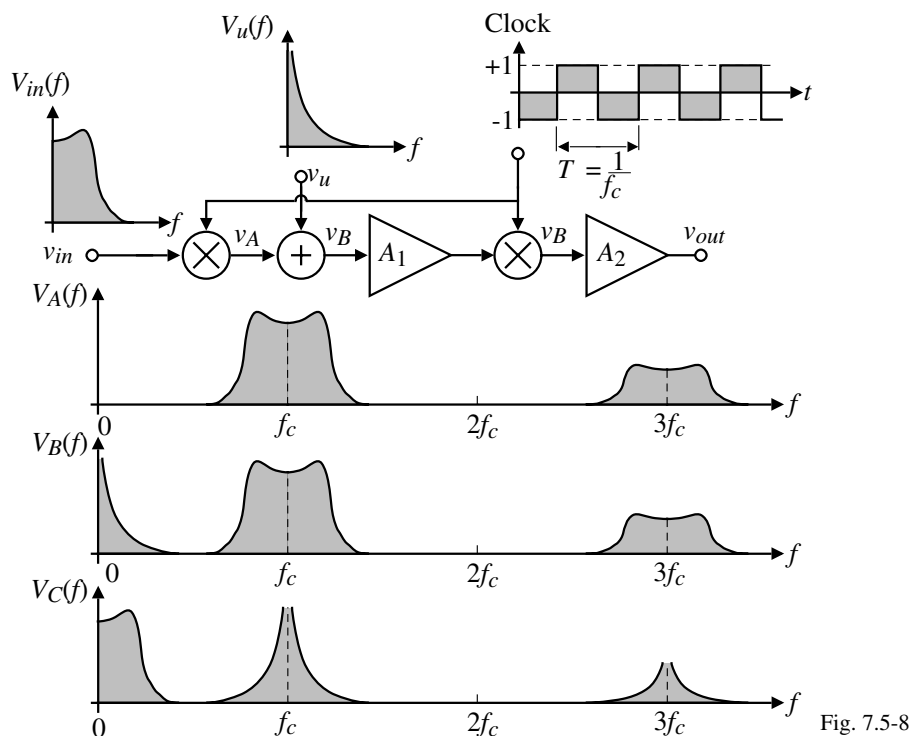


Fig. 7.5-8

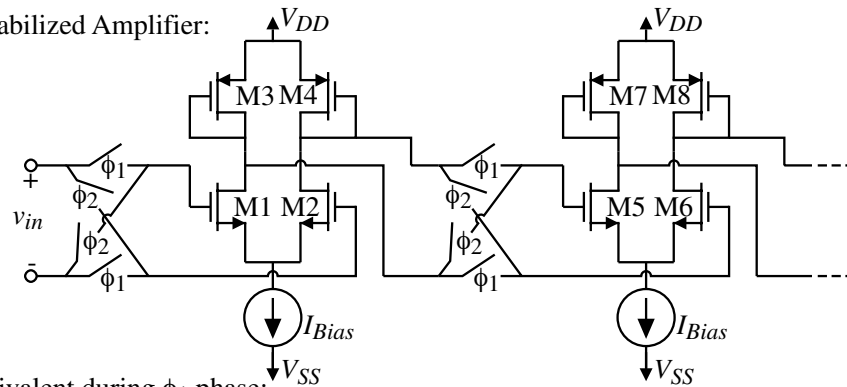

 
## Chopper-Stabilized Amplifier

Chopper-stabilized Amplifier:



Circuit equivalent during  $\phi_1$  phase:



Circuit equivalent during the  $\phi_2$  phase:

 


Fig. 7.5-10

## Experimental Noise Response of the Chopper-Stabilized Amplifier

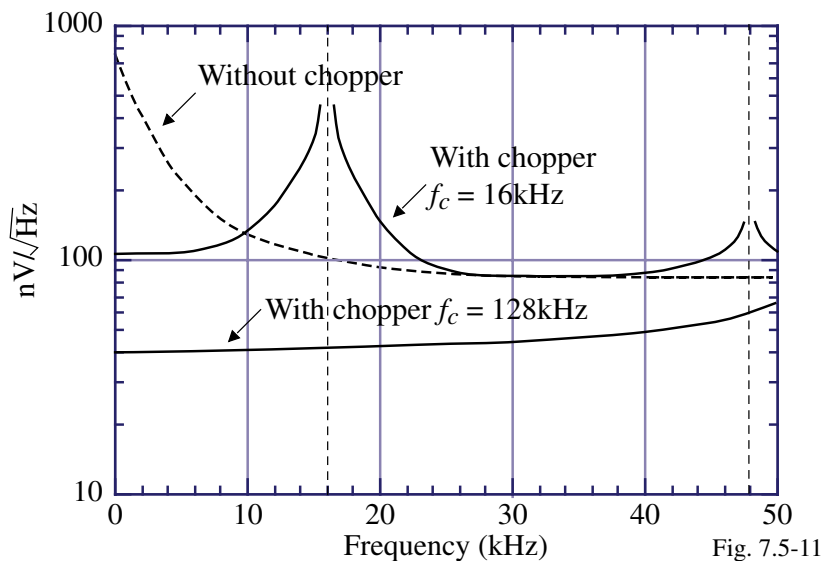


Fig. 7.5-11

Comments:

- The switches in the chopper-stabilized op amp introduce a thermal noise equal to  $kT/C$  where  $k$  is Boltzmann's constant,  $T$  is absolute temperature and  $C$  are capacitors charged by the switches (parasitics in the case of the chopper-stabilized amplifier).
- Requires two-phase, non-overlapping clocks.
- Trade-off between the lowering of  $1/f$  noise and the introduction of the  $kT/C$  noise.

## SUMMARY

- Primary sources of noise for CMOS circuits is thermal and  $1/f$
- Noise analysis:
  - 1.) Insert a noise generator for each transistor that contributes to the noise. (Generally ignore the current source transistor of source-coupled pairs.)
  - 2.) Find the output noise voltage across an open-circuit or output noise current into a short circuit.
  - 3.) Reflect the total output noise back to the input resulting in the equivalent input noise voltage.
- Noise is reduced in op amps by making the input stage gain as large as possible and reducing the noise of this stage as much as possible.
- The input stage noise can be reduced by using lateral BJTs (particularly the  $1/f$  noise)
- Doubly correlated sampling can transfer the noise at low frequencies to the clock frequency (this technique is used to achieve low input offset voltage op amps).