

## LECTURE 400 – DISCRETE-TIME COMPARATORS (LATCHES)

### (READING: AH – 475-483)

### Objective

The objective of this presentation is:

- 1.) Illustrate discrete-time comparators
- 2.) Estimate the propagation delay time

### Outline

- Switched capacitor comparators
- Regenerative comparators (latches)
- Summary

### Switched Capacitor Comparator

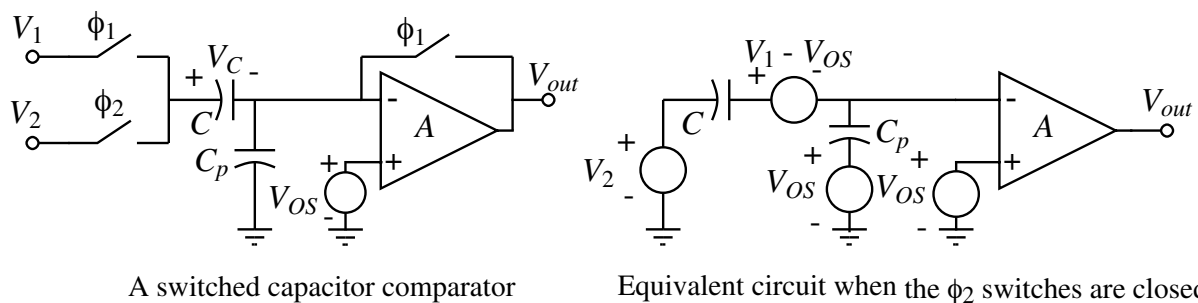


Fig. 8.5-1

$\phi_1$  Phase:

The  $V_1$  input is sampled and the dc input offset voltage is autozeroed.

$$V_C(\phi_1) = V_1 - V_{OS} \quad \text{and} \quad V_{Cp}(\phi_1) = V_{OS}$$

$\phi_2$  Phase:

$$\begin{aligned} V_{out}(\phi_2) &= -A \left[ \frac{V_2 C}{C+C_p} - \frac{(V_1 - V_{OS})C}{C+C_p} + \frac{V_{OS} C_p}{C+C_p} \right] + AV_{OS} \\ &= -A \left[ (V_2 - V_1) \frac{C}{C+C_p} + V_{OS} \left( \frac{C}{C+C_p} + \frac{C_p}{C+C_p} \right) \right] + AV_{OS} = -A(V_2 - V_1) \frac{C}{C+C_p} \approx A(V_1 - V_2) \end{aligned}$$

if  $C_p$  is smaller than  $C$ .

## Differential-In, Differential-Out Switched Capacitor Comparator

 


Fig. 8.5-2

Comments:

- Reduces the influence of charge injection
- Eliminates even harmonics

## Regenerative Comparators

Regenerative comparators use positive feedback to accomplish the comparison of two signals. Latches have a faster switching speed than the previous bistable comparators.

NMOS and PMOS latch:

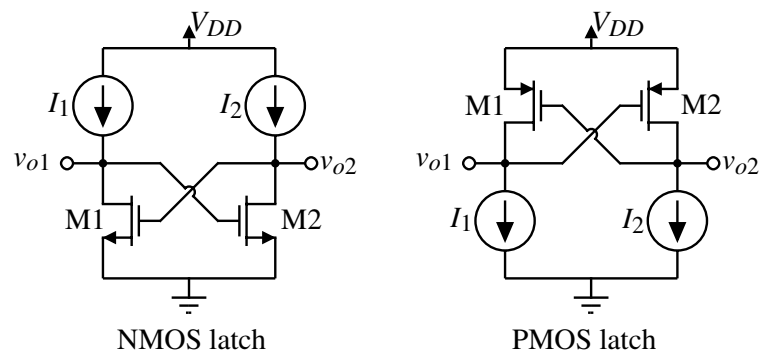


Fig. 8.5-3

How is the input applied to a latch?

The inputs are initially applied to the outputs of the latch.

$V_{o1}'$  = initial input applied to  $v_{o1}$

$V_{o2}'$  = initial input applied to  $v_{o2}$

## Step Response of a Latch

Circuit:

$R_i$  and  $C_i$  are the resistance and capacitance seen to ground from the  $i$ -th transistor.

Nodal equations:

 
 


Fig. 8.5-4

$$g_{m1} V_{o2} + G_1 V_{o1} + s C_1 \left( V_{o1} - \frac{V_{o1}'}{s} \right) = g_{m1} V_{o2} + G_1 V_{o1} + s C_1 V_{o1} - C_1 V_{o1}' = 0$$

$$g_{m2} V_{o1} + G_2 V_{o2} + s C_2 \left( V_{o2} - \frac{V_{o2}'}{s} \right) = g_{m2} V_{o1} + G_2 V_{o2} + s C_2 V_{o2} - C_2 V_{o2}' = 0$$

Solving for  $V_{o1}$  and  $V_{o2}$  gives,

$$V_{o1} = \frac{R_1 C_1}{s R_1 C_1 + 1} V_{o1}' - \frac{g_{m1} R_1}{s R_1 C_1 + 1} V_{o2} = \frac{\tau_1}{s \tau_1 + 1} V_{o1}' - \frac{g_{m1} R_1}{s \tau_1 + 1} V_{o2}$$

$$V_{o2} = \frac{R_2 C_2}{s R_2 C_2 + 1} V_{o2}' - \frac{g_{m2} R_2}{s R_2 C_2 + 1} V_{o1} = \frac{\tau_2}{s \tau_2 + 1} V_{o2}' - \frac{g_{m2} R_2}{s \tau_2 + 1} V_{o1}$$

Defining the output,  $\Delta V_o$ , and input,  $\Delta V_i$ , as

$$\Delta V_o = V_{o2} - V_{o1} \quad \text{and} \quad \Delta V_i = V_{o2}' - V_{o1}'$$

## Step Response of the Latch - Continued

Solving for  $\Delta V_o$  gives,

$$\Delta V_o = V_{o2} - V_{o1} = \frac{\tau}{s \tau + 1} \Delta V_i + \frac{g_m R}{s \tau + 1} \Delta V_o$$

or

$$\Delta V_o = \frac{\tau \Delta V_i}{s \tau + (1 - g_m R)} = \frac{\frac{\tau \Delta V_i}{1 - g_m R}}{\frac{s \tau}{1 - g_m R} + 1} = \frac{\tau' \Delta V_i}{s \tau' + 1}$$

where

$$\tau' = \frac{\tau}{1 - g_m R}$$

Taking the inverse Laplace transform gives

$$\Delta v_o(t) = \Delta V_i' e^{-t/\tau} = \Delta V_i e^{-t(1 - g_m R)/\tau} \approx e^{g_m R t/\tau} \Delta V_i, \quad \text{if } g_m R \gg 1.$$

Define the latch time constant as

$$\tau_L \approx \frac{\tau}{g_m R} = \frac{C}{g_m} = \frac{0.67 W L C_{ox}}{\sqrt{2 K' (W/L) I}} = 0.67 C_{ox} \sqrt{\frac{W L^3}{2 K' I}}$$

if  $C \approx C_{gs}$ .

$$\therefore \Delta V_{out}(t) = e^{t/\tau_L} \Delta V_i$$

## Step Response of a Latch - Continued

Normalize the output voltage by  $(V_{OH}-V_{OL})$  to get

$$\frac{\Delta V_{out}(t)}{V_{OH}-V_{OL}} = e^{t/\tau_L} \frac{\Delta V_i}{V_{OH}-V_{OL}}$$

which is plotted as,

 


Fig. 8.5-5

The propagation delay time is  $t_p = \tau_L \ln \left( \frac{V_{OH}-V_{OL}}{2\Delta V_i} \right)$

### Example 8.5-1 - Time domain characteristics of a latch.

Find the time it takes from the time the latch is enabled until the output voltage,  $\Delta V_{out}$ , equals  $V_{OH}-V_{OL}$  if the  $W/L$  of the latch NMOS transistors is  $10\mu\text{m}/1\mu\text{m}$  and the latch dc current is  $10\mu\text{A}$  when  $\Delta V_i = 0.1(V_{OH}-V_{OL})$  and  $\Delta V_i = 0.01(V_{OH}-V_{OL})$ . Find the propagation time delay ( $\Delta V_{out}=0.5(V_{OH}-V_{OL})$ ) for the latch for each of these conditions.

#### Solution

The transconductance of the latch transistors is

$$g_m = \sqrt{2 \cdot 110 \cdot 10 \cdot 10} = 148\mu\text{S}$$

The output conductance is  $0.4\mu\text{S}$  which gives  $g_m R$  of  $59.2\text{V/V}$ . Since  $g_m R$  is greater than 1, we can use the above results. Therefore the latch time constant is found as

$$\tau_L = 0.67 C_{ox} \sqrt{\frac{WL^3}{2K'I}} = 0.67(24 \times 10^{-4}) \sqrt{\frac{(10 \cdot 1) \times 10^{-18}}{2 \cdot 110 \times 10^{-6} \cdot 10 \times 10^{-6}}} = 108\text{ns}$$

If we assume that the propagation time delay is the time for the output to reach  $(V_{OH}-V_{OL})$ , then for  $\Delta V_i = 0.01(V_{OH}-V_{OL})$  that  $t_p = 4.602\tau_L = 497\text{ns}$  and for  $\Delta V_i = 0.1(V_{OH}-V_{OL})$  that  $t_p = 2.306\tau_L = 249\text{ns}$ .

If we assume that the propagation time delay is the time when the output is  $0.5(V_{OH}-V_{OL})$ , then using the above results or Fig. 8.5-5 we find for  $\Delta V_i = 0.01(V_{OH}-V_{OL})$  that  $t_p = 3.91\tau_L = 422\text{ns}$  and for  $\Delta V_i = 0.1(V_{OH}-V_{OL})$  that  $t_p = 1.61\tau_L = 174\text{ns}$ .

## Comparator using a Latch with a Built-In Threshold<sup>†</sup>

How does it operate?

- 1.) Devices in shaded region operate in the triode region.
- 2.) When the latch/reset goes high, the upper cross-coupled inverter-latch regenerates. The drain currents of M5 and M6 are steered to obtain a final state determined by the mismatch between the  $R_1$  and  $R_2$  resistances.

$$\frac{1}{R_1} = K_N \left[ \frac{W_1}{L} (v_{in}^+ - V_T) + \frac{W_2}{L} (V_{REF}^- - V_T) \right]$$

and

$$\frac{1}{R_2} = K_N \left[ \frac{W_1}{L} (v_{in}^- - V_T) + \frac{W_2}{L} (V_{REF}^+ - V_T) \right]$$

- 3.) The input voltage which causes  $R_1$  and  $R_2$  to be equal is given by

$$v_{in}(\text{threshold}) = (W_2/W_1)V_{REF}$$

$W_2/W_1 = 1/4$  generates a threshold of  $\pm 0.25V_{REF}$ .

Performance  $\rightarrow$  20Ms/s & 200 $\mu$ W

 


Fig. 8.5-6

<sup>†</sup> T.B. Cho and P.R. Gray, "A 10b, 20Msamples/s, 35mW pipeline A/D Converter," *IEEE J. Solid-State Circuits*, vol. 30, no. 3, pp. 166-172, March 1995.

## Simple, Low Power Latched Comparator<sup>†</sup>

 


Fig. 8.5-7

Dissipated 50 $\mu$ W when clocked at 2MHz.

<sup>†</sup> A. Coban, "1.5V, 1mW, 98-dB Delta-Sigma ADC", Ph.D. dissertation, School of ECE, Georgia Tech, Atlanta, GA 30332-0250.

## Dynamic Latch

Circuit:

 


Fig. 8.5-8

Input offset voltage distribution:

 


Fig. 8.5-9

Power dissipation/sampling rate =  $4.3\mu\text{W}/\text{Ms/s}$

## SUMMARY

- Discrete-time comparators must work with clocks
- Switched capacitor comparators use op amps to transfer charge and autozero
- Regenerative comparators (latches) use positive feedback
- The propagation delay of the regenerative comparator is slow at the beginning and speeds up rapidly as time increases
- The highest speed comparators will use a combination of open-loop comparators and latches