

LECTURE 050 – FOLLOWERS

(READING: GHLM – 344-362, AH – 221-226)

Objective

The objective of this presentation is:

Show how to design stages that

- 1.) Provide sufficient output power in the form of voltage or current.
- 2.) Avoid signal distortion.
- 3.) Be efficient
- 4.) Provide protection from abnormal conditions (short circuit, over temperature, etc.)


Outline

- Source follower
- Emitter follower
- Common source stage
- Common emitter stage
- Push-Pull MOS (Class B)
- Push-Pull BJT (Class B)
- Summary


SOURCE FOLLOWERS

Maximum and Minimum Output Voltage of the Source Follower

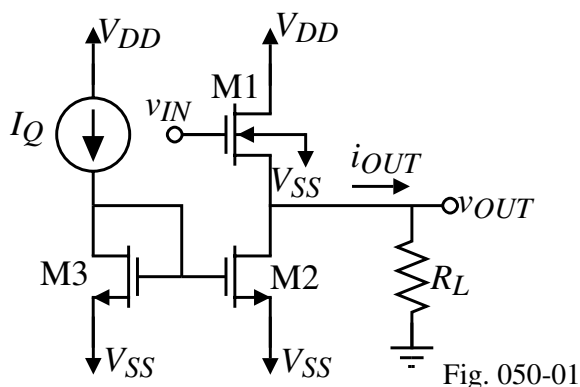N-Channel Source Follower
with current sink bias:



Voltage transfer curve:

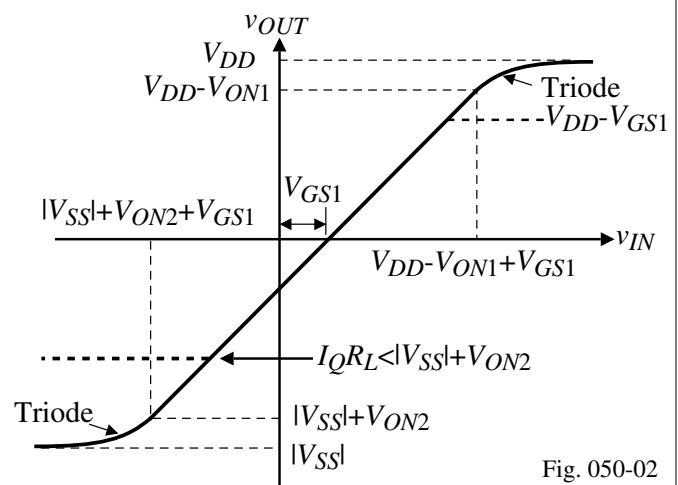

Maximum output voltage swings:

$$v_{OUT(\min)} \approx V_{SS} - V_{ON2} \text{ (if } R_L \text{ is large)}$$

$$v_{OUT(\max)} = V_{DD} - V_{ON1} \text{ (if } v_{IN} > V_{DD})$$

$$\text{or } v_{OUT(\min)} \approx -I_Q R_L \text{ (if } R_L \text{ is small)}$$

$$\text{or } v_{OUT(\max)} \approx V_{DD} - V_{GS1}$$

Output Voltage Swing of the Follower - Continued

The previous results do not include the bulk effect on V_{T1} of V_{GS1} .

Therefore,

$$V_{T1} = V_{T01} + \gamma_1 [\sqrt{2|\phi_F| - v_{BS}} - \sqrt{2|\phi_F|}] \approx V_{T01} + \gamma_1 \sqrt{v_{SB}} = V_{T01} + \gamma_1 \sqrt{v_{OUT(\max)} - V_{SS}}$$

$$\therefore v_{OUT(\max)} - V_{SS} \approx V_{DD} - V_{SS} - V_{ON1} - V_{T1} = V_{DD} - V_{SS} - V_{ON1} - V_{T01} - \gamma_1 \sqrt{v_{OUT(\max)} - V_{SS}}$$

Define $v_{OUT(\max)} - V_{SS} = v_{OUT(\max)}$

which gives the quadratic,

$$v_{OUT(\max)} + \gamma_1 \sqrt{v_{OUT(\max)}} - (V_{DD} - V_{SS} - V_{ON1} - V_{T01}) = 0$$

Solving the quadratic gives,

$$v_{OUT(\max)} \approx \frac{\gamma_1^2}{4} - \frac{\gamma_1}{2} \sqrt{\gamma_1^2 + 4(V_{DD} - V_{SS} - V_{ON1} - V_{T01})} + \frac{\gamma_1^2 + 4(V_{DD} - V_{SS} - V_{ON1} - V_{T01})}{4}$$

If $V_{DD} = 2.5\text{V}$, $\gamma_N = 0.4\text{V}^{1/2}$, $V_{TN1} = 0.7\text{V}$, and $V_{ON1} = 0.2\text{V}$, then $v_{OUT(\max)} = 3.661\text{V}$ and

$$v_{OUT(\max)} = 3.661 - 2.5 = 0.8661\text{V}$$

Maximum Sourcing and Sinking Currents for the Source Follower

Maximum Sourcing Current (into a short circuit):

We assume that the transistors are in saturation and $V_{DD} = -V_{SS} = 2.5\text{V}$, thus

$$I_{OUT(\text{sourcing})} = \frac{K'_1 W_1}{2L_1} [V_{DD} - v_{OUT} - V_{T1}]^2 - I_Q$$

where v_{IN} is assumed to be equal to V_{DD} .

If $W_1/L_1 = 10$ and if $v_{OUT} = 0\text{V}$, then

$$V_{T1} = 1.08\text{V} \Rightarrow I_{OUT} \text{ equal to } 1.11\text{ mA.}$$

However, as v_{OUT} increases above 0V , the current rapidly decreases.

Maximum Sinking Current:

For the current sink load, the sinking current is whatever the sink is biased to provide.

$$I_{OUT(\text{sinking})} = I_Q$$


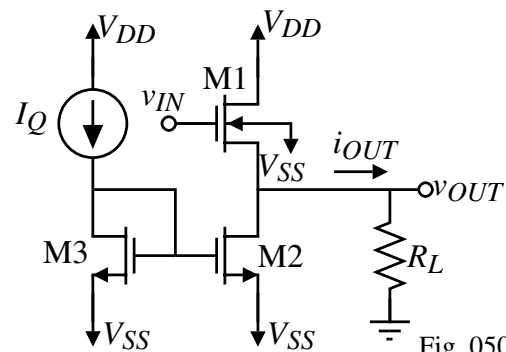


Fig. 050-01

Efficiency of the Source Follower

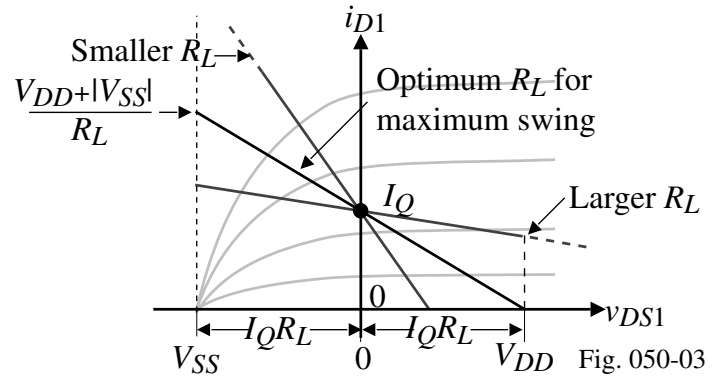Assume that the source follower can swing to power supply:



$$\text{Efficiency} = \frac{P_{RL}}{P_{Supply}} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{DD}-V_{SS})I_Q} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{DD}-V_{SS})\left(\frac{(V_{DD}-V_{SS})}{2R_L}\right)} = \left(\frac{v_{OUT(\text{peak})}}{V_{DD}-V_{SS}}\right)^2$$


Maximum efficiency occurs when $v_{OUT(\text{peak})} = V_{DD} = |V_{SS}|$ which gives 25%.

Comments:

- Maximum efficiency occurs for the optimum value of R_L which gives maximum swing.
- Other values of R_L result in less efficiency (and smaller signal swings before clipping)
- We have ignored the fact that the dynamic Q point cannot travel along the full length of the load line because of minimum and maximum voltage limits.

Small Signal Performance of the Source Follower

Small-signal model:

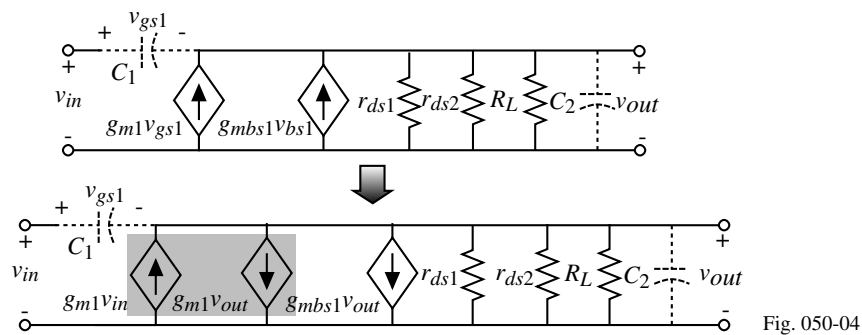

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{ds1} + g_{ds2} + g_{m1} + g_{mbs1} + G_L} \approx \frac{g_{m1}}{g_{m1} + g_{mbs1} + G_L} \approx \frac{g_{m1}R_L}{1 + g_{m1}R_L}$$

If $V_{DD} = -V_{SS} = 2.5V$, $V_{out} = 0V$, $W_1/L_1 = 10\mu m/1\mu m$, $W_2/L_2 = 1\mu m/1\mu m$, and $I_D = 500\mu A$, then

For the current sink load follower ($R_L = \infty$):

$$\frac{V_{out}}{V_{in}} = 0.869V/V, \text{ if the bulk effect were ignored, then } \frac{V_{out}}{V_{in}} = 0.963V/V$$

For a finite load, $R_L = 1000\Omega$:

$$\frac{V_{out}}{V_{in}} = 0.512V/V$$

Small Signal Performance of the Source Follower - Continued

The output resistance is:

$$R_{out} = \frac{1}{g_{m1} + g_{mbs1} + g_{ds1} + g_{ds2} + G_L}$$

For the current sink load follower:

$$R_{out} = 830\Omega$$

The frequency response of the source follower:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(g_{m1} + sC_1)}{g_{ds1} + g_{ds2} + g_{m1} + g_{mbs1} + G_L + s(C_1 + C_2)}$$

where

C_1 = capacitances connected between the input and output $\approx C_{GS1}$


$C_2 = C_{bs1} + C_{bd2} + C_{gd2}$ (or C_{gs2}) + C_L

$$z = -\frac{g_{m1}}{C_1} \quad \text{and} \quad p \approx -\frac{g_{m1} + G_L}{C_1 + C_2}$$

The presence of a LHP zero leads to the possibility that in most cases the pole and zero will provide some degree of cancellation leading to a broadband response.

EMITTER FOLLOWER

Voltage Transfer Characteristic

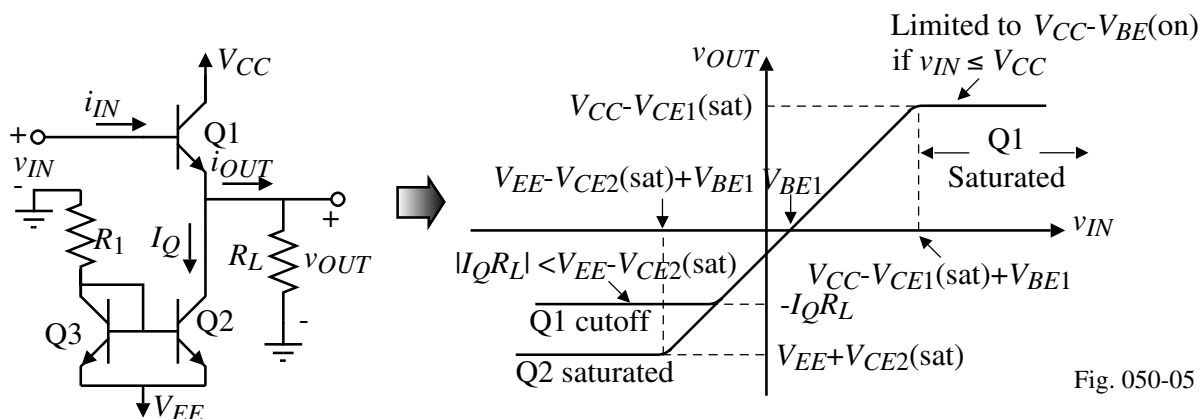

Maximum signal swings:

- $v_{OUT}(\max) = V_{CC} - V_{CE1}(\text{sat})$ or $V_{CC} - V_{BE1}$ if $v_{IN}(\max) \leq V_{CC}$

(The circuit driving the emitter follower must provide a current of $\frac{V_{CC} - V_{CE1}(\text{sat})}{\beta F R_L}$)

- $v_{OUT}(\min) = V_{EE} + V_{CE2}(\text{sat})$ or $v_{OUT}(\min) = -I_Q R_L$ (if $|I_Q R_L| < V_{EE} + V_{CE2}(\text{sat})$)
- $i_{OUT}(\text{source}) = \beta F i_{IN}$
- $i_{OUT}(\text{sink}) = I_Q$

Efficiency of the Emitter Follower

Assume that the emitter follower can swing to power supply:

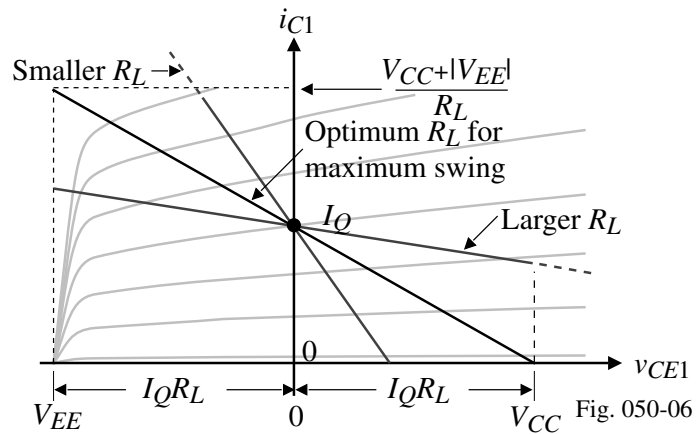


Fig. 050-06

$$\text{Efficiency} = \frac{P_{RL}}{P_{Supply}} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{CC} - V_{EE})I_Q} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{CC} - V_{EE})\left(\frac{V_{CC} - V_{EE}}{2R_L}\right)} = \left(\frac{v_{OUT(\text{peak})}}{V_{CC} - V_{EE}}\right)^2$$

Maximum efficiency occurs when $v_{OUT(\text{peak})} = V_{CC} = |V_{EE}|$ which gives 25%.

Comments:

- Maximum efficiency occurs for the optimum value of R_L which gives maximum swing.
- Other values of R_L will result in less efficiency (smaller signal swings before clipping)

Power Considerations of the Emitter Follower

Waveforms of the transistor variables for maximum efficiency ($V_{CC} = -V_{EE}$).


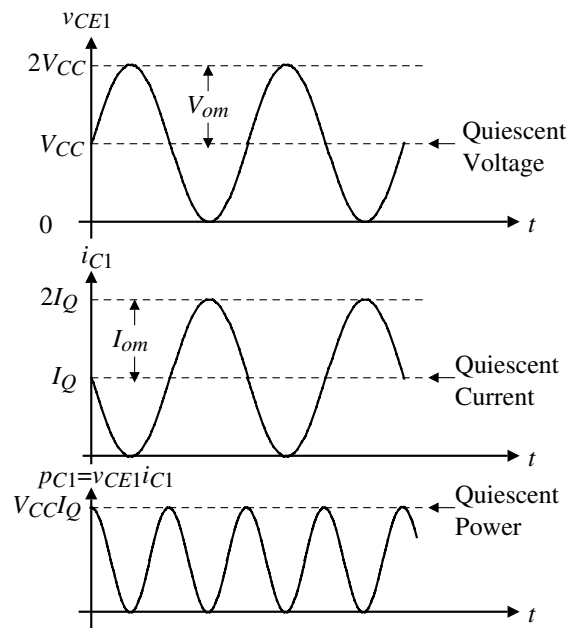


Fig. 050-07

$$p_{C1} = v_{CE1} i_{C1} = [V_{CC}(1 + \sin \omega t)][I_Q(1 - \sin \omega t)] = V_{CC} I_Q (1 - \sin^2 \omega t) = \frac{V_{CC} I_Q}{2} (1 + \cos 2\omega t)$$

Power Considerations of the Emitter Follower - Continued

Parabolas of constant power:

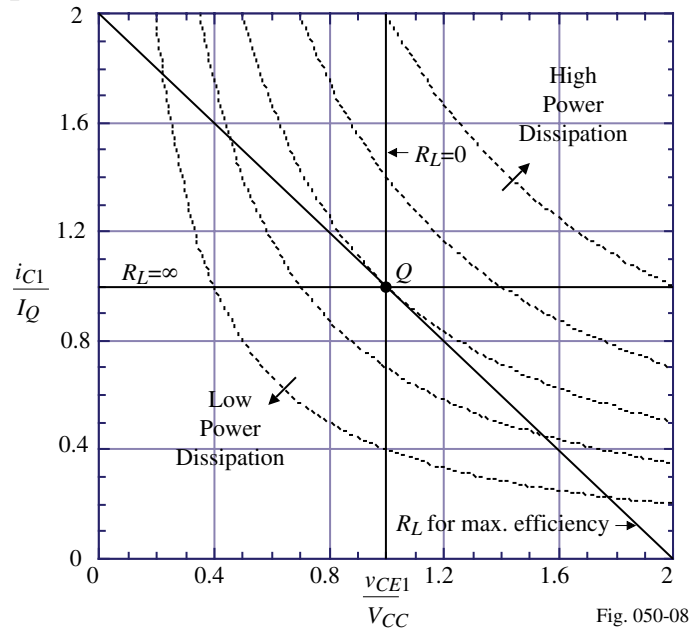

Comments:

- Maximum power dissipation occurs at the Q point for the optimum R_L corresponding to maximum efficiency.
- For smaller values of R_L the power dissipation can become very large.

Example - Design of an Emitter Follower for Maximum Efficiency

The emitter follower shown has $V_{CC} = -V_{EE} = 5V$, $R_1 = 2.15k\Omega$, and $V_{CE}(\text{sat}) = 0.2V$. Find the optimum value of R_L for maximum efficiency and find the value of this efficiency.

Solution

The optimum R_L for maximum efficiency is found as,

$$R_L = \frac{V_{CC} - V_{CE}(\text{sat})}{I_Q}$$

$$I_Q = \frac{-V_{EE} - V_{BE}}{R_1} = \frac{5 - 0.7}{2.15k\Omega} = 2\text{mA}$$


$$\therefore R_L = \frac{5 - 0.2}{2\text{mA}} = 2.4k\Omega$$

The efficiency can be found by calculating the power to the load and from the sources.

$$P_{L(\text{max})} = \left(\frac{V_{CC} - V_{CE}(\text{sat})}{\sqrt{2}} \right) \left(\frac{I_Q}{\sqrt{2}} \right) = 0.5(4.8V)(2\text{mA}) = 4.8\text{mW}$$

$$P_{\text{supply}} = 2V_{CC}I_Q = 2(5)(2\text{mA}) = 20\text{mW}$$
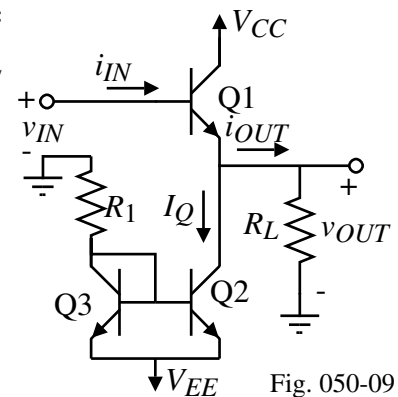
$$\therefore \eta = \frac{P_{L(\text{max})}}{P_{\text{supply}}} = \frac{4.8}{20} = 0.24 \text{ or } 24\% \text{ which is close to the theoretical maximum.}$$



Emitter Follower - Small Signal Performance

The small signal model of the emitter follower is:

$$R_{in} = R_S + r_{\pi} + (1 + \beta_F)R_L$$

$$R_{out} \approx 1/g_m \text{ (excluding } R_L)$$

$$v_{out} = (g_m + g_{\pi})v_1 R_L = (g_m + g_{\pi})(i_{in} r_{\pi})R_L$$

$$= (g_m + g_{\pi}) r_{\pi} R_L \left(\frac{v_{in}}{R_{in}} \right)$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{(g_m + g_{\pi}) r_{\pi} R_L}{R_S + r_{\pi} + (1 + \beta_F)R_L} \approx \frac{R_L}{R_L + \frac{1}{g_m} + \frac{R_S}{\beta_F}}$$

If $\beta_F = 100$, $g_m = 20\text{mA/V}$, $R_L = R_S = 1\text{k}\Omega$, $C_{\pi} = 5\text{pF}$ and $C_L = 10\text{pF}$, we get

$$R_{in} = 1\text{k}\Omega + 5\text{k}\Omega + 101\text{k}\Omega = 107\text{k}\Omega, \quad R_{out} = 50\Omega, \quad \frac{v_{out}}{v_{in}} = \frac{1\text{k}\Omega}{1\text{k}\Omega + 50\Omega + 9.9\Omega} = 0.943\text{V/V}$$

The transfer function assuming $R_S = 0$, is given as,

$$\frac{V_{out}}{V_{in}} = \frac{g_m + g_{\pi} + sC_{\pi}}{g_m + g_{\pi} + G_L + sC_{\pi} + sC_L} \Rightarrow \text{Zero} \approx -\frac{g_m}{C_{\pi}} \quad \text{and} \quad \text{Pole} \approx -\frac{g_m + G_L}{C_{\pi} + C_L}$$

$$\text{Zero} = -4 \times 10^9 \text{ rads./sec.} \quad \text{and} \quad \text{Pole} = -1.4 \times 10^9 \text{ rads./sec.}$$

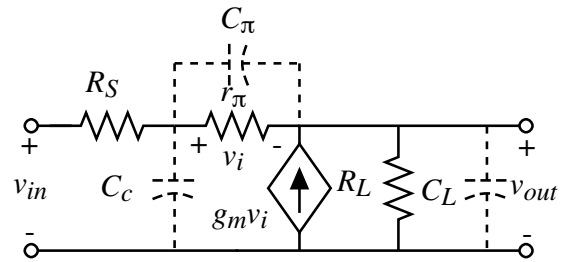


Fig. 050-10

SUMMARY

Requirements of Output Stages

- The objectives are to provide output power in form of voltage and/or current.
- In addition, the output amplifier should be linear and be efficient.
- Low output resistance is required to provide power efficiently to a small load resistance.
- High source/sink currents are required to provide sufficient output voltage rate due to large load capacitances.
- Types of output stages considered:
 - Source and emitter follower (Class A)
- Did not consider the distortion analysis of GHLM, Sec. 5.3.2