

LECTURE 080 – SINGLE-STAGE FREQUENCY RESPONSE - II (READING: GHLM – 504-516)

Objective

The objective of this presentation is:

- 1.) Illustrate the frequency analysis of single stage amplifiers
- 2.) Introduce the Miller technique and the approximate method of solving for two poles

Outline

- Differential and Common Frequency Response of the Differential Amplifier
- Emitter/Source Follower Frequency Response
- Common Base/Gate Frequency Response
- Summary

Emitter Follower Input Impedance

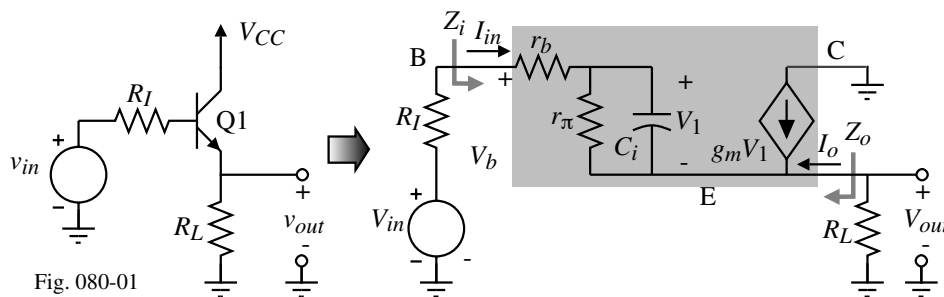


Fig. 080-01

If we let $z_{\pi} = \frac{r_{\pi}}{1+sC_i r_{\pi}}$, then

$$V_i = V_b = I_{in}(r_b + z_{\pi}) + (I_{in} + g_m z_{\pi} I_{in})R_L \rightarrow Z_i = \frac{V_i}{I_{in}} = r_b + z_{\pi} + (1 + g_m z_{\pi})R_L$$

$$\therefore Z_i = r_b + \frac{r_{\pi}}{1+sC_i r_{\pi}} + \left(1 + \frac{g_m r_{\pi}}{1+sC_i r_{\pi}}\right) R_L = r_b + \left(\frac{(1+g_m R_L)r_{\pi}}{1+sC_i r_{\pi}}\right) + R_L$$

$$Z_i = r_b + \frac{(1+g_m R_L)r_{\pi}}{sC_i} + R_L = r_b + \frac{R}{1+sCR} + R_L$$

where $R = (1+g_m R_L)r_{\pi}$ and $C = C_i/(1+g_m R_L)$

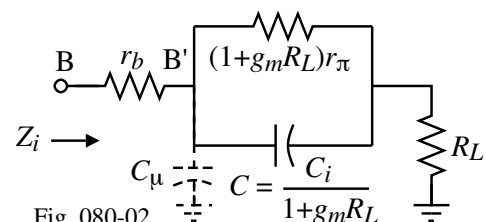


Fig. 080-02

Emitter Follower Output Impedance

From the previous model (or from the impedance transformation aspect of a BJT) we can write,

$$Z_o = \frac{V_{out}}{I_o} = \frac{z_\pi + R_I + r_b}{1 + g_m z_\pi} = \frac{z_\pi + R_I'}{1 + g_m z_\pi} = \frac{\frac{r_\pi}{1 + sC_i r_\pi} + R_I'}{1 + \frac{g_m r_\pi}{1 + sC_i r_\pi}} = \frac{r_\pi + R_I' + sC_i r_\pi R_I'}{\beta_0 + 1 + sC_i r_\pi}$$

Multiplying top and bottom by R_I'/β_0 , gives

$$Z_o \approx \frac{\left(\frac{1}{g_m} + \frac{R_I'}{\beta_0} + sC_i r_\pi \frac{R_I'}{\beta_0}\right) R_I'}{R_I' + sC_i r_\pi \frac{R_I'}{\beta_0}} = \frac{(R_1 + sL)R_2}{R_2 + sL} \quad \text{assuming } \beta_0 \gg 1.$$

Equivalent output circuit:

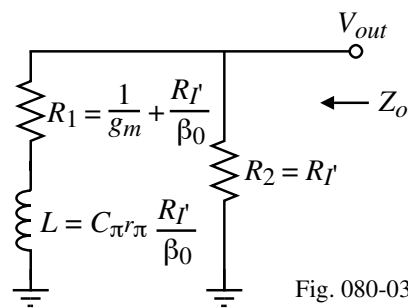


Fig. 080-03

Source Follower Frequency Response

From the previous lecture for the MOSFET $r_\pi = \infty$, $r_b = 0$, and $R'_L = \frac{1}{g_{mbs}} \parallel R_L = \frac{R_L}{1 + g_{mbs} R_L}$

$$\frac{v_{out}}{v_{in}} = \frac{g_m R'_L + \frac{R'_L}{r_\pi}}{1 + g_m R'_L + \frac{R'_L + R'_L}{r_\pi}} \left[\frac{1 - \frac{s}{z_1}}{1 - \frac{s}{p_1}} \right] \rightarrow \frac{v_{out}}{v_{in}} = \frac{g_m R'_L}{1 + g_m R'_L} \left[\frac{1 - \frac{s}{z_1}}{1 - \frac{s}{p_1}} \right]$$

where $z_1 = -\frac{g_m}{C_{gs}}$, $p_1 = -\frac{1}{R_1 C_{gs}}$ and $R_1 = \frac{R_I + R'_L}{1 + g_m R'_L} \approx \frac{1}{g_m}$

Example

Calculate the transfer function for a source follower with $C_{gs} = 7.33 \text{ pF}$, $K'W/L = 100 \text{ mA/V}^2$, $R_L = 2 \text{ k}\Omega$, $R_I = 190 \Omega$, and $I_D = 4 \text{ mA}$. Let $g_{mbs} \approx 0$, $C_{gd} = 0$, $C_{gb} = 0$, and $C_{bs} = 0$.

Solution

$$g_m = \sqrt{2(100)4} \text{ mA/V} = 28.2 \text{ mA/V}.$$

$$\frac{v_{out}}{v_{in}} = \frac{28.2 \cdot 2}{1 + 28.2 \cdot 2} = 0.983 \text{ V/V}$$

$$|z_1| = \omega_T = \frac{g_m}{C_{gs}} = 3.85 \times 10^9 \text{ rads/s},$$

$$R_1 = \frac{R_I + R'_L}{1 + g_m R'_L} = \frac{190 + 2000}{1 + 28.2 \cdot 2} = 38.2 \Omega,$$

$$p_1 = -\frac{10^{12}}{38.2 \cdot 7.33} = -3.57 \times 10^9 \text{ rads/s}$$

(C_{gd} , C_{gb} , and C_{bs} cause two poles, 1 zero)

Source Follower Output Impedance

The output impedance of the source follower can be found from the previous general analysis or from the following model:

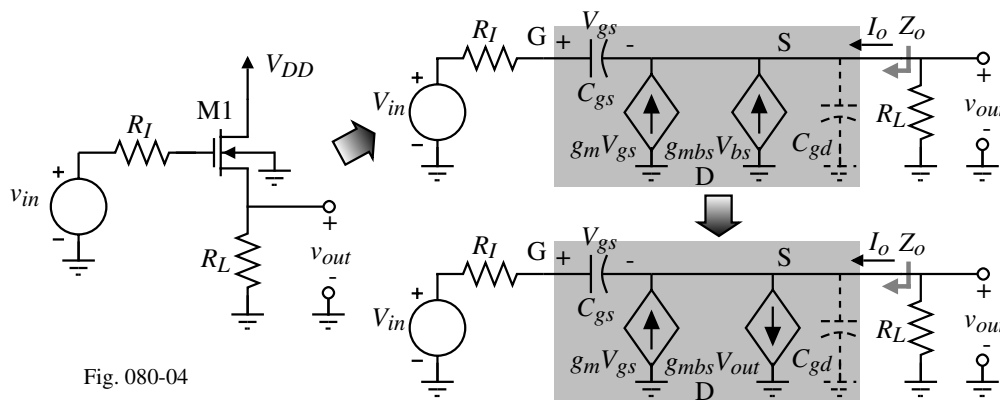


Fig. 080-04

Summing currents at the output,

$$I_o + g_m V_{gs} + s C_{gs} V_{gs} = g_{mbs} V_{out} \quad \text{and} \quad V_{gs} = -\frac{V_{out}}{s C_{gs} R_I + 1}$$

$$\therefore I_o = g_{mbs} V_{out} - (g_m + s C_{gs}) \left(\frac{-V_{out}}{s C_{gs} R_I + 1} \right) \quad \rightarrow \quad \frac{I_o}{V_{out}} = g_{mbs} + \frac{g_m + s C_{gs}}{1 + s C_{gs} R_I}$$

$$Z_o = \frac{V_{out}}{I_o} = \frac{1 + s C_{gs} R_I}{(g_m + g_{mbs}) + s C_{gs} (R_I g_{mbs} + 1)} = \frac{1}{g_m + g_{mbs}} \left[\frac{1 + s C_{gs} R_I}{1 + s C_{gs} \left(\frac{R_I g_{mbs} + 1}{g_m + g_{mbs}} \right)} \right]$$

Identification of the Output Impedance

Find the value of R_1 , R_2 , and L in the equivalent output impedance model shown for the source follower.

Note that,

$$Z_o = \frac{R_2(R_1 + sL)}{R_1 + R_2 + sL} \approx \frac{R_2(R_1 + sL)}{R_2 + sL} \quad \text{if} \quad R_1 \ll R_2$$

The best way to solve this problem is to use the limits of Z_o .

$$\lim Z_o (s \rightarrow 0) = \frac{R_1 R_2}{R_1 + R_2} \approx R_1 = \frac{1}{g_m + g_{mbs}} \quad \text{where} \quad R_1 \ll R_2$$

$$\lim Z_o (s \rightarrow \infty) = R_2 = \frac{R_I}{R_I g_{mbs} + 1}$$

$$\therefore L = \frac{C_{gs}(1 + R_I g_{mbs})}{g_m + g_{mbs}} = \frac{C_{gs} R_I R_1}{R_2}$$

If one includes C_{gd} in parallel with the equivalent circuit, the potential for resonance of the

output impedance will occur roughly at $\sqrt{\frac{1}{LC_{gd}}}$ if R_1 is small. Using the values of the previous example with $g_{mbs} = 0.1 g_m$ and $C_{gd} = 0.5$ pf gives $R_1 = 32.2 \Omega$, $R_2 = 123.7 \Omega$ and $L = (7.33 \text{ pF} \cdot 190 \Omega \cdot 32.2 \Omega / 123.7 \Omega) = 0.362 \text{ nH} \Rightarrow f_{osc} = 11.8 \text{ GHz}$

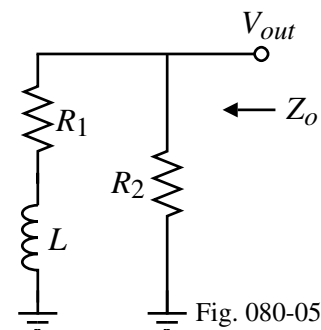


Fig. 080-05

Frequency Response of Current Buffers

Current buffers include the common base and common gate configurations.

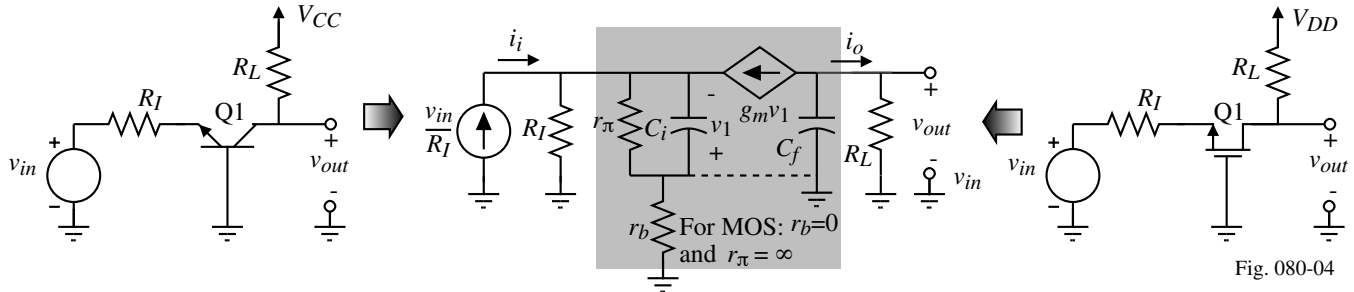


Fig. 080-04

Summing the currents at the input node (neglecting R_I),

$$i_i + \frac{v_1}{z_\pi} + g_m v_1 \approx 0 \quad \text{where} \quad z_\pi = \frac{r_\pi}{1 + sC_i r_\pi} \rightarrow i_i = -v_1 \left(g_m + \frac{1}{r_\pi} + sC_i \right)$$

The short-circuit output current gain can be found as,

$$i_o = -g_m v_1 = \frac{g_m}{g_m + \frac{1}{r_\pi} + sC_i} i_i = \frac{g_m r_\pi}{1 + g_m r_\pi + sC_i r_\pi} i_i \rightarrow \frac{i_o}{i_i} = \frac{g_m r_\pi}{1 + g_m r_\pi} \frac{1}{1 + s \frac{r_\pi}{1 + g_m r_\pi} C_i}$$

Common-Base Amplifier Frequency Response

Replace C_i with C_π gives,

$$\frac{i_o}{i_i} = \frac{g_m r_\pi}{1 + g_m r_\pi} \frac{1}{1 + s \frac{r_\pi}{1 + g_m r_\pi} C_\pi} \approx \frac{\beta_0}{1 + \beta_0} \frac{1}{1 + s \frac{C_\pi}{g_m}} \quad \text{if } \beta_0 \gg 1 \text{ where } \beta_0 = g_m r_\pi$$

\therefore The low frequency gain, $\frac{i_o}{i_i} = \alpha_0$ and a pole is at $p_1 = -\frac{g_m}{C_\pi} \approx -\omega_T$

If the output current flows through R_L , then the current gain has another pole due to C_μ :

$$\frac{i_o}{i_i} = \frac{g_m r_\pi}{1 + g_m r_\pi} \frac{1}{1 + s \frac{r_\pi}{1 + g_m r_\pi} C_\pi} \frac{1}{1 + s R_L C_\mu} \approx \frac{\beta_0}{1 + \beta_0} \left(\frac{1}{1 + s \frac{C_\pi}{g_m}} \right) \left(\frac{1}{1 + s R_L C_\mu} \right) = A_i \left(\frac{1}{1 + \frac{s}{p_1}} \right) \left(\frac{1}{1 + \frac{s}{p_2}} \right)$$

Example:

If $I_C = 1\text{mA}$, $\beta_0 = 100$, $C_\pi = 10\text{pF}$, $C_\mu = 0.5\text{pF}$, $C_{cs} = 1\text{pf}$, and $R_L = 2\text{k}\Omega$, evaluate the CB amplifier.

$$g_m = 1/26 \text{ mS}$$

$$A_i = 0.99, p_1 = -2.6 \times 10^{12} \text{ rad/s}, \text{ and } p_2 = -\frac{1}{R_L(C_\mu + C_{cs})} = -0.333 \times 10^9 \text{ rad/s}$$

Common Gate Amplifier Frequency Response

Short-circuit current gain:

$$\frac{i_o}{i_i} = \frac{g_m r_\pi}{1 + g_m r_\pi} \frac{1}{1 + s \frac{r_\pi}{1 + g_m r_\pi} C_i} \quad (r_\pi = \infty \text{ and } g_m \leftarrow g_m + g_{mbs}) \quad \rightarrow \quad \frac{i_o}{i_i} = \frac{1}{1 + s \frac{C_{gs} + C_{bs}}{g_m + g_{mbs}}}$$

Current gain ($R_L \neq 0$):

$$\frac{i_o}{i_i} = \frac{1}{1 + s \frac{C_{gs} + C_{bs}}{g_m + g_{mbs}}} \left(\frac{1}{1 + s R_L C_{gd}} \right) = A_i \left(\frac{1}{1 + \frac{s}{p_1}} \right) \left(\frac{1}{1 + \frac{s}{p_2}} \right)$$

where

$$A_i = 1, \quad p_1 = -\frac{g_m + g_{mbs}}{C_{gs} + C_{bs}} \quad \text{and} \quad p_2 = -\frac{1}{R_L C_{gd}}$$

Example

Calculate the transfer function for a common-gate amplifier with $C_{gs} = 7.33 \text{ pF}$, $K'W/L = 100 \text{ mA/V}^2$, $R_L = 2 \text{ k}\Omega$, and $I_D = 4 \text{ mA}$. Let $g_{mbs} \approx 0$, $C_{gd} = 1 \text{ pF}$, and $C_{bs} = 2 \text{ pF}$.

$$g_m = \sqrt{2 \cdot 4 \cdot 100} \text{ mS} = 28.2 \text{ mS} \quad \therefore \quad p_1 = -\frac{28.2 \times 10^{-3}}{9.33 \times 10^{-12}} = -3.03 \times 10^9 \text{ rad/s}$$

$$\text{and} \quad p_2 = -\frac{1}{2000 \cdot 10^{-12}} = 0.5 \times 10^9 \text{ rad/s}$$

SUMMARY

- The emitter follower and source follower have very high frequency responses
- The -3dB frequency will most likely be caused by the pole at the output of the follower
- The equivalent output of the emitter follower is inductive
- The common base and common gate amplifiers have a current gain of 1
- The CB and CG amplifiers have a high frequency response because of the low input resistance at the input
- If $R_L \neq 0$, the pole at the output of the CB and CG amplifiers causes the -3dB frequency
- The common base amplifier has an input impedance that is inductive
- More detailed analysis of these amplifiers leads to complex poles which will influence the high frequency behavior