

LECTURE 120 – COMPENSATION OF OP AMPS - I

(READING: GHLM – 624-638, AH – 249-260)

INTRODUCTION

The objective of this presentation is to present the principles of compensating two-stage op amps.

Outline

- Compensation of Op Amps
 - General principles
 - Miller, Nulling Miller
 - Self-compensation
 - Feedforward
- Summary

GENERAL PRINCIPLES OF OP AMP COMPENSATION

Objective

Objective of compensation is to achieve stable operation when negative feedback is applied around the op amp.

Types of Compensation

1. Miller - Use of a capacitor feeding back around a high-gain, inverting stage.
 - Miller capacitor only
 - Miller capacitor with an unity-gain buffer to block the forward path through the compensation capacitor. Can eliminate the RHP zero.
 - Miller with a nulling resistor. Similar to Miller but with an added series resistance to gain control over the RHP zero.
2. Feedforward - Bypassing a positive gain amplifier resulting in phase lead. Gain can be less than unity.
3. Self compensating - Load capacitor compensates the op amp.

Single-Loop, Negative Feedback Systems

Block diagram:

$A(s)$ = differential-mode voltage gain of the op amp

$F(s)$ = feedback transfer function from the output of op amp back to the input.

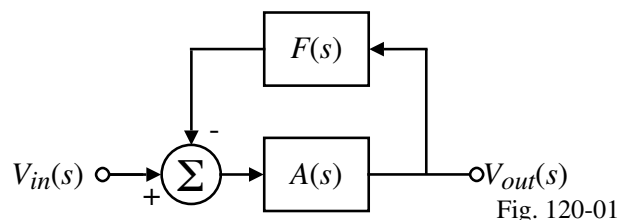


Fig. 120-01

Definitions:

- Open-loop gain = $L(s) = -A(s)F(s)$
- Closed-loop gain = $\frac{V_{out}(s)}{V_{in}(s)} = \frac{A(s)}{1+A(s)F(s)}$

Stability Requirements:

The requirements for stability for a single-loop, negative feedback system is,

$$|A(j\omega_0^\circ)F(j\omega_0^\circ)| = |L(j\omega_0^\circ)| < 1$$

where ω_0° is defined as

$$\text{Arg}[-A(j\omega_0^\circ)F(j\omega_0^\circ)] = \text{Arg}[L(j\omega_0^\circ)] = 0^\circ$$

Another convenient way to express this requirement is

$$\text{Arg}[-A(j\omega_{0\text{dB}})F(j\omega_{0\text{dB}})] = \text{Arg}[L(j\omega_{0\text{dB}})] > 0^\circ$$

where $\omega_{0\text{dB}}$ is defined as

$$|A(j\omega_{0\text{dB}})F(j\omega_{0\text{dB}})| = |L(j\omega_{0\text{dB}})| = 1$$

Illustration of the Stability Requirement using Bode Plots

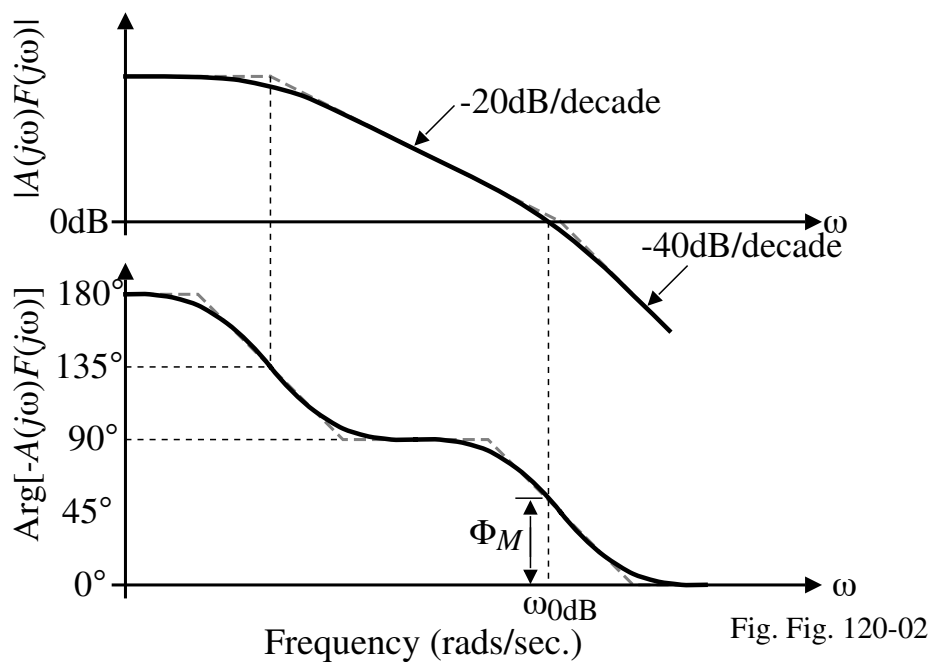



Fig. Fig. 120-02

A measure of stability is given by the phase when $|A(j\omega)F(j\omega)| = 1$. This phase is called *phase margin*.

$$\text{Phase margin} = \Phi_M = \text{Arg}[-A(j\omega_{0\text{dB}})F(j\omega_{0\text{dB}})] = \text{Arg}[L(j\omega_{0\text{dB}})]$$

Why Do We Want Good Stability?

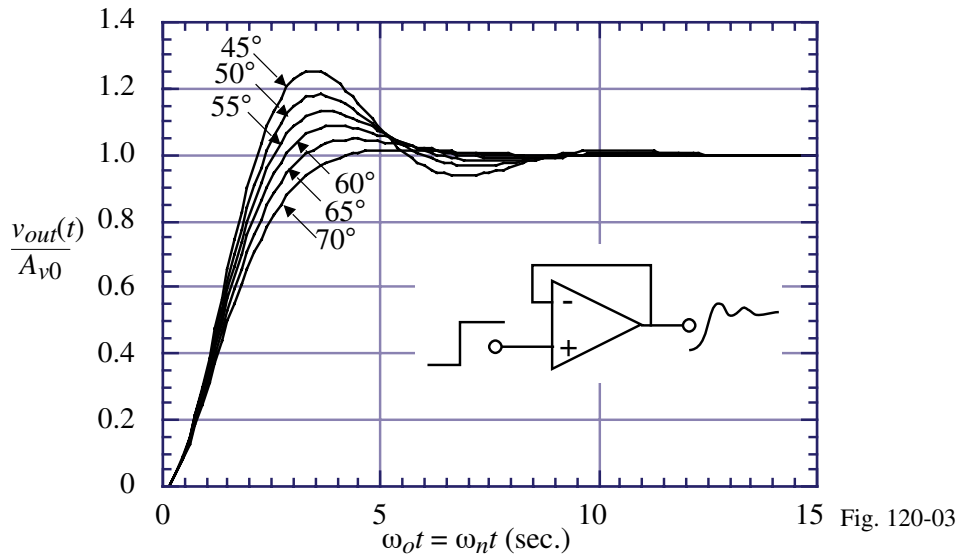
Consider the step response of second-order system which closely models the closed-loop gain of the op amp.



A “good” step response is one that quickly reaches its final value. Therefore, we see that phase margin should be at least 45° and preferably 60° or larger. (A rule of thumb for satisfactory stability is that there should be less than three rings.)

Uncompensated Frequency Response of Two-Stage Op Amps

Two-Stage Op Amps:

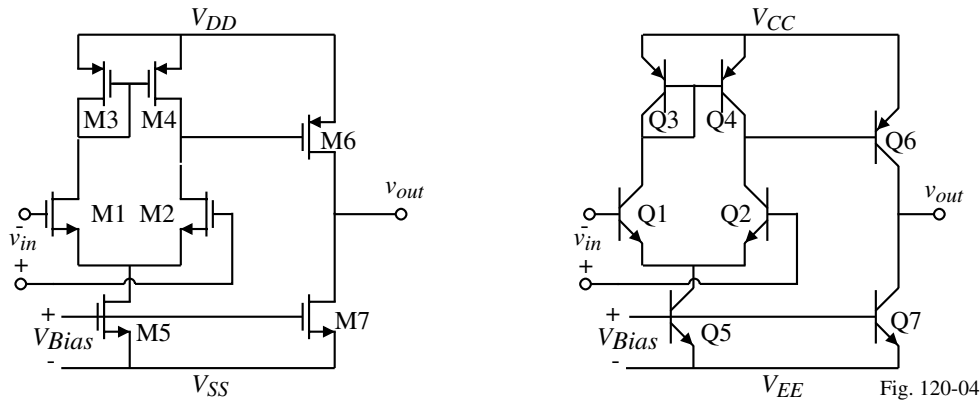

Small-Signal Model:

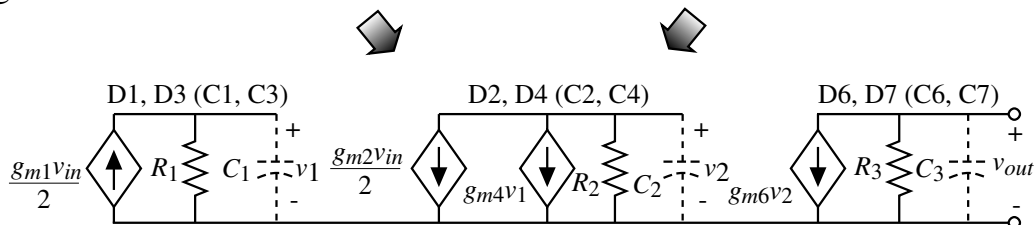


Fig. 120-05

Note that this model neglects the base-collector and gate-drain capacitances for purposes of simplification.

Uncompensated Frequency Response of Two-Stage Op Amps - Continued

For the MOS two-stage op amp:

$$R_1 \approx \frac{1}{g_{m3}} \parallel r_{ds3} \parallel r_{ds1} \approx \frac{1}{g_{m3}} \quad R_2 = r_{ds2} \parallel r_{ds4} \quad \text{and} \quad R_3 = r_{ds6} \parallel r_{ds7}$$

$$C_1 = C_{gs3} + C_{gs4} + C_{bd1} + C_{bd3} \quad C_2 = C_{gs6} + C_{bd2} + C_{bd4} \quad \text{and} \quad C_3 = C_L + C_{bd6} + C_{bd7}$$

For the BJT two-stage op amp:

$$R_1 = \frac{1}{g_{m3}} \parallel r_{\pi3} \parallel r_{\pi4} \parallel r_{o1} \parallel r_{o3} \approx \frac{1}{g_{m3}} \quad R_2 = r_{\pi6} \parallel r_{o2} \parallel r_{o4} \approx r_{\pi6} \quad \text{and} \quad R_3 = r_{o6} \parallel r_{o7}$$

$$C_1 = C_{\pi3} + C_{\pi4} + C_{cs1} + C_{cs3} \quad C_2 = C_{\pi6} + C_{cs2} + C_{cs4} \quad \text{and} \quad C_3 = C_L + C_{cs6} + C_{cs7}$$

Assuming the pole due to C_1 is much greater than the poles due to C_2 and C_3 gives,

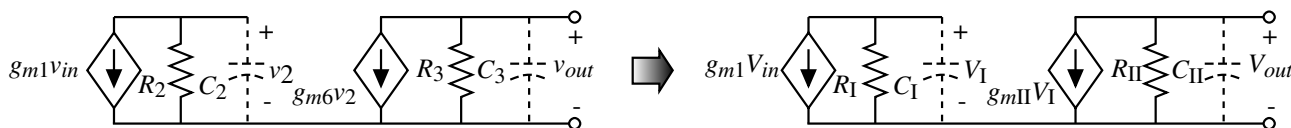


Fig. 120-06

The locations for the two poles are given by the following equations

$$p'_1 = \frac{-1}{R_I C_I} \quad \text{and} \quad p'_2 = \frac{-1}{R_{II} C_{II}}$$

where R_I (R_{II}) is the resistance to ground seen from the output of the first (second) stage and C_I (C_{II}) is the capacitance to ground seen from the output of the first (second) stage.

Uncompensated Frequency Response of an Op Amp

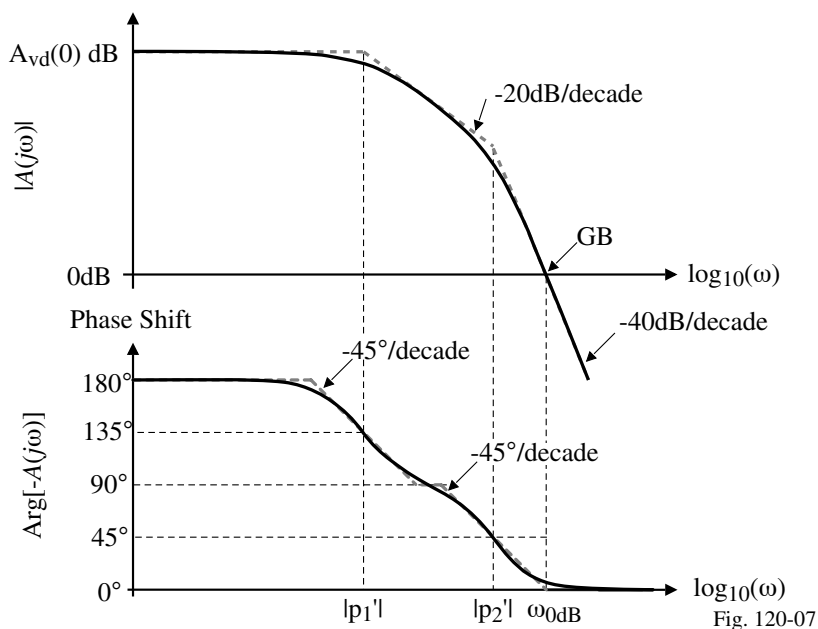


Fig. 120-07

If we assume that $F(s) = 1$ (this is the worst case for stability considerations), then the above plot is the same as the loop gain.

Note that the phase margin is much less than 45° .

Therefore, the op amp must be compensated before using it in a closed-loop configuration.

MILLER COMPENSATION

Two-Stage Op Amp

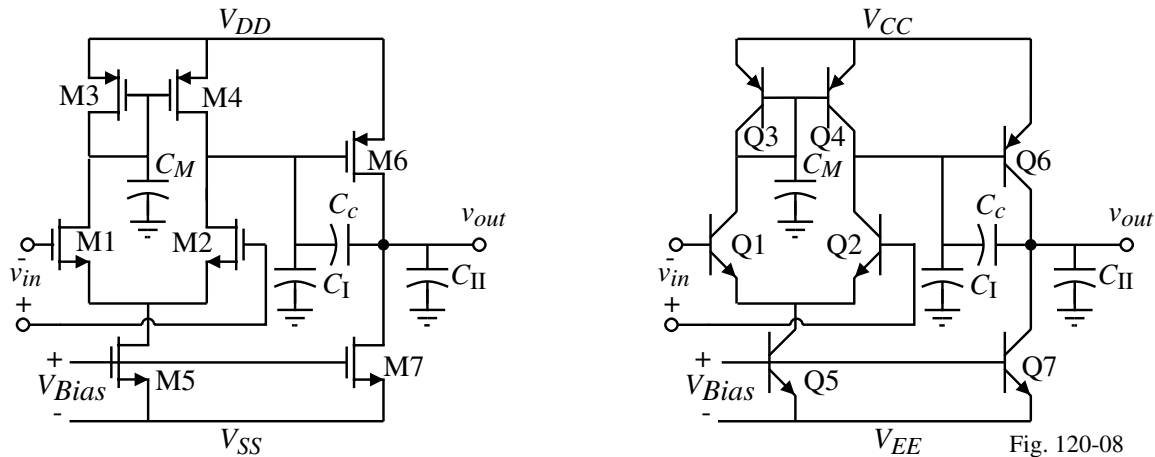


Fig. 120-08

The various capacitors are:

C_c = accomplishes the Miller compensation

C_M = capacitance associated with the first-stage mirror (mirror pole)

C_I = output capacitance to ground of the first-stage

C_{II} = output capacitance to ground of the second-stage

Compensated Two-Stage, Small-Signal Frequency Response Model Simplified

Use the CMOS op amp to illustrate the above concept:

Assume:

$$g_{m3} \gg g_{ds1} + g_{ds3} \quad \text{and} \quad \frac{g_{m3}}{C_M} \gg GB$$

Therefore,

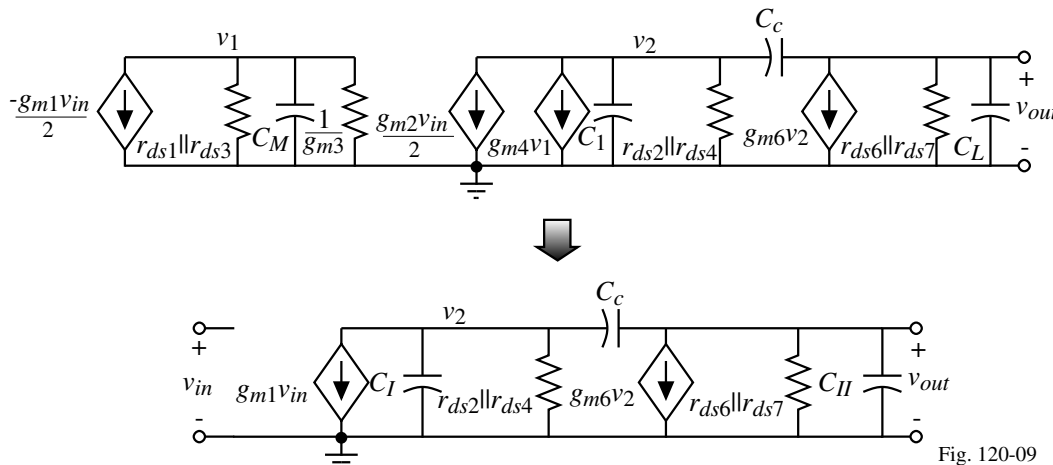


Fig. 120-09

Same circuit holds for the BJT op amp with different component relationships.

Generalized Two-Stage Frequency Response Analysis

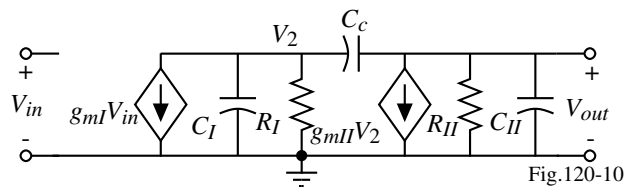


Fig.120-10

where

$$g_{mI} = g_{m1} = g_{m2}, R_I = r_{ds2} || r_{ds4}, C_I = C_1$$

and

$$g_{mII} = g_{m6}, R_{II} = r_{ds6} || r_{ds7}, C_{II} = C_2 = C_L$$

Nodal Equations:

$$-g_{mI}V_{in} = [G_I + s(C_I + C_c)]V_2 - [sC_c]V_{out} \quad \text{and} \quad 0 = [g_{mII} - sC_c]V_2 + [G_{II} + sC_{II} + sC_c]V_{out}$$

Solving using Cramer's rule gives,

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{g_{mI}(g_{mII} - sC_c)}{G_I G_{II} + s[G_{II}(C_I + C_{II}) + G_I(C_{II} + C_c) + g_{mII}C_c] + s^2[C_I C_{II} + C_c C_I + C_c C_{II}]}$$

$$= \frac{A_o [1 - s(C_c / g_{mII})]}{1 + s[R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c] + s^2[R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II})]}$$

where, $A_o = g_{mI}g_{mII}R_I R_{II}$

In general, $D(s) = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) = 1 - s\left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2} \rightarrow D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$, if $|p_2| \gg |p_1|$

$$\therefore \boxed{p_1 = \frac{-1}{R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c} \approx \frac{-1}{g_{mII}R_I R_{II}C_c}, \quad \boxed{z = \frac{g_{mII}}{C_c}}$$

$$\boxed{p_2 = \frac{-[R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c]}{R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II})} \approx \frac{-g_{mII}C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \approx \frac{-g_{mII}}{C_{II}}, \quad C_{II} > C_c > C_I}$$

Summary of Results for Miller Compensation of the Two-Stage Op Amp

There are three roots of importance:

1.) Right-half plane zero:

$$z_1 = \frac{g_{mII}}{C_c} = \frac{g_{m6}}{C_c}$$

This root is very undesirable- it boosts the magnitude while decreasing the phase.

2.) Dominant left-half plane pole (the Miller pole):

$$p_1 \approx \frac{-1}{g_{mII}R_I R_{II}C_c} = \frac{-(g_{ds2} + g_{ds4})(g_{ds6} + g_{ds7})}{g_{m6}C_c}$$

This root accomplishes the desired compensation.

3.) Left-half plane output pole:

$$p_2 \approx \frac{-g_{mII}}{C_{II}} \approx \frac{-g_{m6}}{C_L}$$

This pole must be \geq unity-gainbandwidth or the phase margin will not be satisfied.

Root locus plot of the Miller compensation:

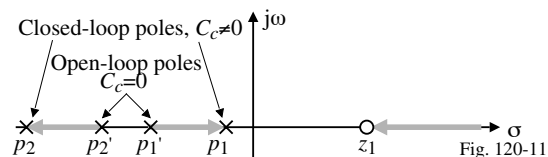


Fig. 120-11

Compensated Open-Loop Frequency Response of the Two-Stage Op Amp

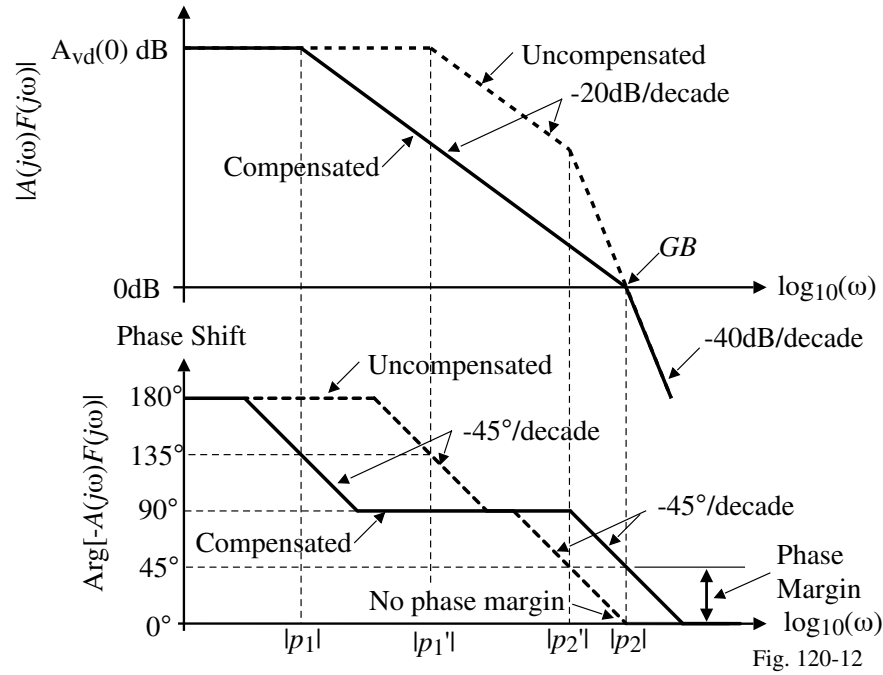


Fig. 120-12

Note that the unity-gainbandwidth, GB , is

$$GB = A_{vd}(0) \cdot |p_1| = (g_{mI}g_{mII}R_I R_{II}) \frac{1}{g_{mII}R_I R_{II} C_c} = \frac{g_{mI}}{C_c} = \frac{g_{m1}}{C_c} = \frac{g_{m2}}{C_c}$$

Conceptual Perspective of These Roots

1.) The Miller pole:

$$|p_1| \approx \frac{1}{R_I (g_{m6} R_{II} C_c)}$$

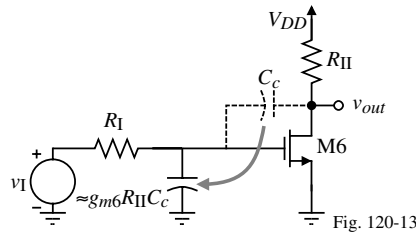


Fig. 120-13

2.) The left-half plane output pole:

$$|p_2| \approx \frac{g_{m6}}{C_{II}}$$

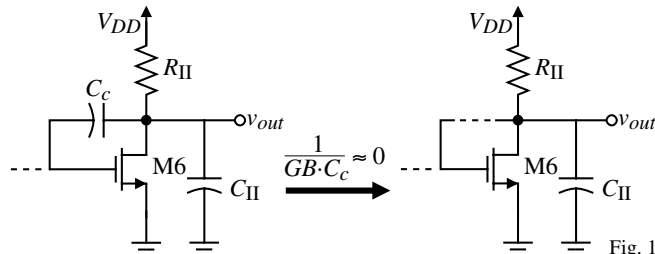


Fig. 120-14

3.) Right-half plane zero (Zeros always arise from multiple paths from the input to output):

$$v_{out} = \left(\frac{-g_{m6} R_{II} (1/sC_c)}{R_{II} + 1/sC_c} \right) v' + \left(\frac{R_{II}}{R_{II} + 1/sC_c} \right) v'' = \frac{-R_{II} \left(\frac{g_{m6}}{sC_c} - 1 \right)}{R_{II} + 1/sC_c} v$$

where $v = v' = v''$.

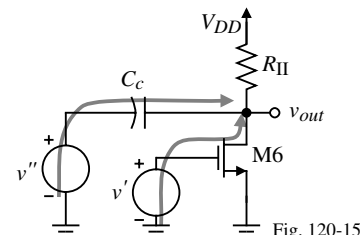


Fig. 120-15

Influence of the Mirror Pole

Up to this point, we have neglected the influence of the pole, p_3 , associated with the current mirror of the input stage. A small-signal model for the input stage that includes C_3 is shown below:

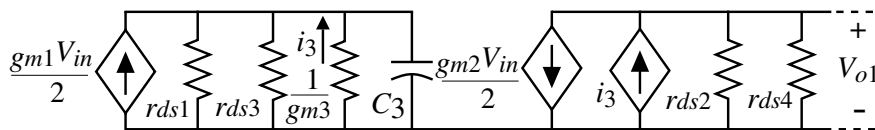


Fig. 120-16

The transfer function from the input to the output voltage of the first stage, $V_{o1}(s)$, can be written as

$$\frac{V_{o1}(s)}{V_{in}(s)} = \frac{-g_{m1}}{2(g_{ds2}+g_{ds4})} \left[\frac{g_{m3}+g_{ds1}+g_{ds3}}{g_{m3}+g_{ds1}+g_{ds3}+sC_3} + 1 \right] \approx \frac{-g_{m1}}{2(g_{ds2}+g_{ds4})} \left[\frac{sC_3 + 2g_{m3}}{sC_3 + g_{m3}} \right]$$

We see that there is a pole and a zero given as

$$p_3 = -\frac{g_{m3}}{C_3} \quad \text{and} \quad z_3 = -\frac{2g_{m3}}{C_3}$$

Because the pole and zero are an octave away from each other and because these roots are much larger, the influence of the mirror pole (zero) can be neglected.

Influence of the Mirror Pole – Continued

Fortunately, the presence of the zero tends to negate the effect of the pole. Generally, the pole and zero due to C_3 is greater than GB and will have very little influence on the stability of the two-stage op amp.

The plot shown illustrates the case where these roots are less than GB and even then they have little effect on stability.

In fact, they actually increase the phase margin slightly because GB is decreased.

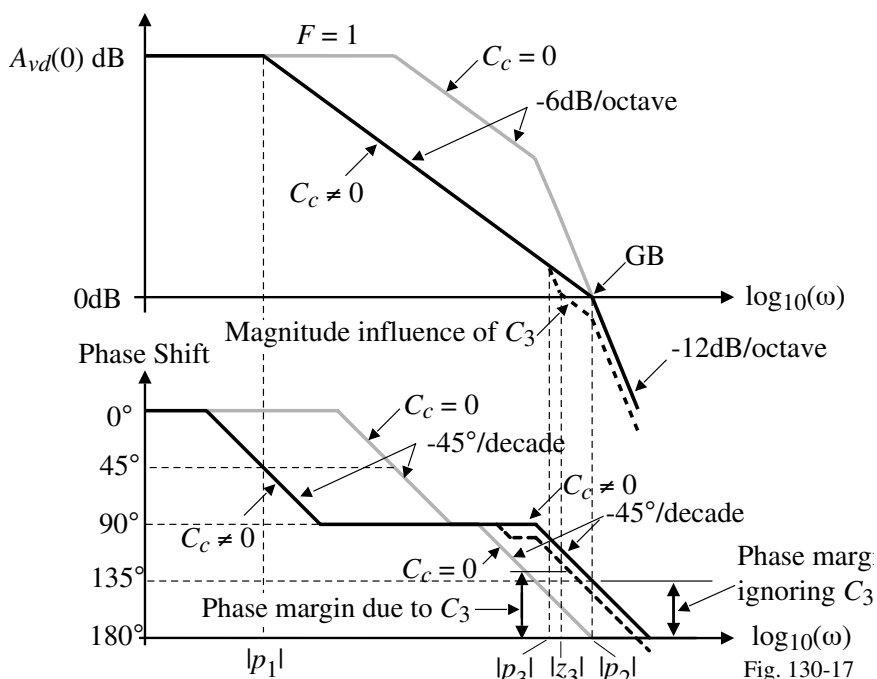


Fig. 130-17

SUMMARY

Compensation

- Designed so that the op amp with unity gain feedback (buffer) is stable
- Types
 - Miller
 - Miller with nulling resistors
 - Self Compensating
 - Feedforward