

## LECTURE 130 – COMPENSATION OF OP AMPS-II

### (READING: GHLM – 638-652, AH – 260-269)

### INTRODUCTION

The objective of this presentation is to continue the ideas of the last lecture on compensation of op amps.

#### Outline

- Compensation of Op Amps
  - General principles
  - Miller, Nulling Miller
  - Self-compensation
  - Feedforward
- Summary

### Conditions for Stability of the Two-Stage Op Amp (Assuming $p_3 \geq GB$ )

- Unity-gainbandwidth is given as:

$$GB = A_v(0) \cdot |p_1| = \left( \frac{gm_I gm_{II} R_I R_{II}}{gm_{II} R_I R_{II} C_c} \right) = \frac{gm_I}{C_c} = \left( \frac{gm_1 gm_2 R_1 R_2}{gm_2 R_1 R_2 C_c} \right) = \frac{gm_1}{C_c}$$

- The requirement for 45° phase margin is:

$$\pm 180^\circ - \text{Arg}[AF] = \pm 180^\circ - \tan^{-1}\left(\frac{\omega}{|p_1|}\right) - \tan^{-1}\left(\frac{\omega}{|p_2|}\right) - \tan^{-1}\left(\frac{\omega}{z}\right) = 45^\circ$$

Let  $\omega = GB$  and assume that  $z \geq 10GB$ , therefore we get,

$$\pm 180^\circ - \tan^{-1}\left(\frac{GB}{|p_1|}\right) - \tan^{-1}\left(\frac{GB}{|p_2|}\right) - \tan^{-1}\left(\frac{GB}{z}\right) = 45^\circ$$

$$135^\circ \approx \tan^{-1}(A_v(0)) + \tan^{-1}\left(\frac{GB}{|p_2|}\right) + \tan^{-1}(0.1) = 90^\circ + \tan^{-1}\left(\frac{GB}{|p_2|}\right) + 5.7^\circ$$

$$39.3^\circ \approx \tan^{-1}\left(\frac{GB}{|p_2|}\right) \Rightarrow \frac{GB}{|p_2|} = 0.818 \Rightarrow \boxed{|p_2| \geq 1.22GB}$$

- The requirement for 60° phase margin:

$$\boxed{|p_2| \geq 2.2GB \text{ if } z \geq 10GB}$$


- If 60° phase margin is required, then the following relationships apply:

$$\frac{gm_6}{C_c} > \frac{10gm_1}{C_c} \Rightarrow \boxed{gm_6 > 10gm_1} \quad \text{and} \quad \frac{gm_6}{C_2} > \frac{2.2gm_1}{C_c} \Rightarrow \boxed{C_c > 0.22C_2}$$
 
## Controlling the Right-Half Plane Zero

Why is the RHP zero a problem?

Because it boosts the magnitude but lags the phase - the worst possible combination for stability.




Solution of the problem:

If zeros are caused by two paths to the output, then eliminate one of the paths.
 
## Use of Buffer to Eliminate the Feedforward Path through the Miller Capacitor

Model:

The transfer function is given by the following equation,



$$\frac{V_o(s)}{V_{in}(s)} = \frac{(g_{mI})(g_{mII})(R_I)(R_{II})}{1 + s[R_I C_I + R_{II} C_{II} + R_I C_c + g_{mII} R_I R_{II} C_c] + s^2[R_I R_{II} C_{II} (C_I + C_c)]}$$

Using the technique as before to approximate  $p_1$  and  $p_2$  results in the following

$$p_1 \cong \frac{-1}{R_I C_I + R_{II} C_{II} + R_I C_c + g_{mII} R_I R_{II} C_c} \cong \frac{-1}{g_{mII} R_I R_{II} C_c}$$

and

$$p_2 \cong \frac{-g_{mII} C_c}{C_{II} (C_I + C_c)}$$

Comments:

Poles are approximately what they were before with the zero removed.

For 45° phase margin,  $|p_2|$  must be greater than  $GB$

For 60° phase margin,  $|p_2|$  must be greater than  $1.73GB$

## Use of Buffer with Finite Output Resistance to Eliminate the RHP Zero

Assume that the unity-gain buffer has an output resistance of  $R_o$ .

Model:

 


Fig. 430-03

It can be shown that if the output resistance of the buffer amplifier,  $R_o$ , is not neglected that another pole occurs at,

$$p_4 \approx \frac{-1}{R_o [C_I C_c / (C_I + C_c)]}$$

and a LHP zero at

$$z_2 \approx \frac{-1}{R_o C_c}$$

Closer examination shows that if a resistor, called a *nulling resistor*, is placed in series with  $C_c$  that the RHP zero can be eliminated or moved to the LHP.

## Use of Nulling Resistor to Eliminate the RHP Zero (or turn it into a LHP zero)<sup>†</sup>

 


Fig. 430-04

Nodal equations:

$$g_{mI} V_{in} + \frac{V_I}{R_I} + s C_I V_I + \left( \frac{s C_c}{1 + s C_c R_z} \right) (V_I - V_{out}) = 0$$

$$g_{mII} V_I + \frac{V_o}{R_{II}} + s C_{II} V_{out} + \left( \frac{s C_c}{1 + s C_c R_z} \right) (V_{out} - V_I) = 0$$

Solution:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{a \{ 1 - s[(C_c/g_{mII}) - R_z C_c] \}}{1 + bs + cs^2 + ds^3}$$

where

$$a = g_{mI} g_{mII} R_I R_{II}$$

$$b = (C_{II} + C_c) R_{II} + (C_I + C_c) R_I + g_{mII} R_I R_{II} C_c + R_z C_c$$

$$c = [R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II}) + R_z C_c (R_I C_I + R_{II} C_{II})]$$

$$d = R_I R_{II} R_z C_I C_{II} C_c$$

<sup>†</sup> W.J. Parrish, "An Ion Implanted CMOS Amplifier for High Performance Active Filters", Ph.D. Dissertation, 1976, Univ. of CA., Santa Barbara.

### Use of Nulling Resistor to Eliminate the RHP - Continued

If  $R_z$  is assumed to be less than  $R_I$  or  $R_{II}$  and the poles widely spaced, then the roots of the above transfer function can be approximated as

$$p_1 \cong \frac{-1}{(1 + g_{mII}R_{II})R_I C_c} \cong \frac{-1}{g_{mII}R_{II}R_I C_c}$$

$$p_2 \cong \frac{-g_{mII}C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \cong \frac{-g_{mII}}{C_{II}}$$

$$p_4 = \frac{-1}{R_z C_I} \quad (p_3 \text{ has been used previously for the mirror pole so we choose } p_4 \text{ for the nulling resistor pole)}$$

and

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

Note that the zero can be placed anywhere on the real axis.

### Conceptual Illustration of the Nulling Resistor Approach

 


Fig. Fig. 430-05

The output voltage,  $V_{out}$ , can be written as

$$V_{out} = \frac{-g_{m6}R_{II}\left(R_z + \frac{1}{sC_c}\right)}{R_{II} + R_z + \frac{1}{sC_c}} V' + \frac{R_{II}}{R_{II} + R_z + \frac{1}{sC_c}} V'' = \frac{-R_{II}\left[g_{m6}R_z + \frac{g_{m6}}{sC_c} - 1\right]}{R_{II} + R_z + \frac{1}{sC_c}} V$$

when  $V = V' = V''$ .

Setting the numerator equal to zero and assuming  $g_{m6} = g_{mII}$  gives,

$$z_1 = \frac{1}{C_c(1/g_{mII} - R_z)}$$

## A Design Procedure that Allows the RHP Zero to Cancel the Output Pole, $p_2$

We desire that  $z_1 = p_2$  in terms of the previous notation.

Therefore,

$$\frac{1}{C_c(1/g_{mII} - R_z)} = \frac{-g_{mII}}{C_{II}}$$

The value of  $R_z$  can be found as

$$R_z = \left( \frac{C_c + C_{II}}{C_c} \right) (1/g_{mII})$$

With  $p_2$  canceled, the remaining roots are  $p_1$  and  $p_4$  (the pole due to  $R_z$ ). For unity-gain stability, all that is required is that

$$|p_4| > A_v(0)|p_1| = \frac{A_v(0)}{g_{mII}R_{II}R_I C_c} = \frac{g_{mI}}{C_c}$$

and


$$(1/R_z C_I) > (g_{mI}/C_c) = GB$$

Substituting  $R_z$  into the above inequality and assuming  $C_{II} \gg C_c$  results in

$$C_c > \sqrt{\frac{g_{mI}}{g_{mII}}} C_I C_{II}$$


This procedure gives excellent stability for a fixed value of  $C_{II}$  ( $\approx C_L$ ).

 Unfortunately, as  $C_L$  changes,  $p_2$  changes and the zero must be readjusted to cancel  $p_2$ .


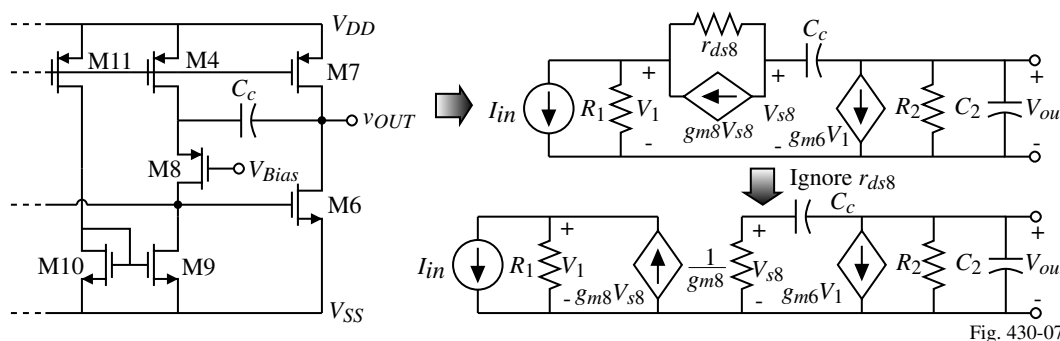
## Increasing the Magnitude of the Output Pole<sup>†</sup>

The magnitude of the output pole,  $p_2$ , can be increased by introducing gain in the Miller capacitor feedback path. For example,



The resistors  $R_1$  and  $R_2$  are defined as

$$R_1 = \frac{1}{g_{ds2} + g_{ds4} + g_{ds9}} \quad \text{and} \quad R_2 = \frac{1}{g_{ds6} + g_{ds7}}$$

where transistors M2 and M4 are the output transistors of the first stage.

Nodal equations:

$$I_{in} = G_1 V_1 - g_{m8} V_{s8} = G_1 V_1 - \left( \frac{g_{m8} s C_c}{g_{m8} + s C_c} \right) V_{out} \quad \text{and} \quad 0 = g_{m6} V_1 + \left[ G_2 + s C_2 + \frac{g_{m8} s C_c}{g_{m8} + s C_c} \right] V_{out}$$

<sup>†</sup> B.K. Ahuja, "An Improved Frequency Compensation Technique for CMOS Operational Amplifiers," *IEEE J. of Solid-State Circuits*, Vol. SC-18, No. 6 (Dec. 1983) pp. 629-633.

## Increasing the Magnitude of the Output Pole - Continued

Solving for the transfer function  $V_{out}/I_{in}$  gives,

$$\frac{V_{out}}{I_{in}} = \left( \frac{-g_{m6}}{G_1 G_2} \right) \left[ \frac{\left( 1 + \frac{sC_c}{g_{m8}} \right)}{1 + s \left[ \frac{C_c}{g_{m8}} + \frac{C_2}{G_2} + \frac{C_c}{G_2} + \frac{g_{m6}C_c}{G_1 G_2} \right] + s^2 \left( \frac{C_c C_2}{g_{m8} G_2} \right)} \right]$$

Using the approximate method of solving for the roots of the denominator gives

$$p_1 = \frac{-1}{\frac{C_c}{g_{m8}} + \frac{C_c}{G_2} + \frac{C_2}{G_2} + \frac{g_{m6}C_c}{G_1 G_2}} \approx \frac{-6}{g_{m6}r_{ds}^2 C_c}$$

and

$$p_2 \approx \frac{\frac{-\frac{g_{m6}r_{ds}^2 C_c}{6}}{C_c C_2}}{\frac{g_{m8} G_2}{g_{m8} G_2}} = \frac{g_{m8} r_{ds}^2 G_2}{6} \left( \frac{g_{m6}}{C_2} \right) = \left( \frac{g_{m8} r_{ds}}{3} \right) |p_2'|$$

where all the various channel resistance have been assumed to equal  $r_{ds}$  and  $p_2'$  is the output pole for normal Miller compensation.

Result:

Dominant pole is approximately the same and the output pole is increased by  $\approx g_m r_{ds}$ .

## Concept Behind the Increasing of the Magnitude of the Output Pole

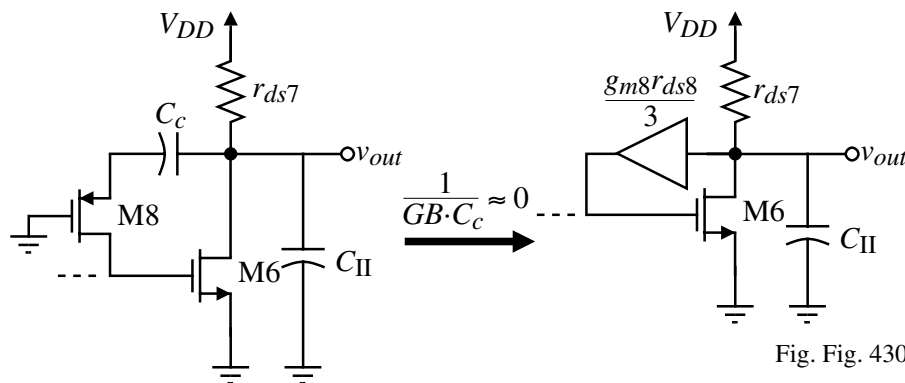


Fig. Fig. 430-08

$$R_{out} = r_{ds7} \parallel \left( \frac{3}{g_{m6} g_{m8} r_{ds8}} \right) \approx \frac{3}{g_{m6} g_{m8} r_{ds8}}$$

Therefore, the output pole is approximately,

$$|p_2| \approx \frac{g_{m6} g_{m8} r_{ds8}}{3 C_{II}}$$

Besides, the common gate amplifier stops the feedforward path preventing the RHP zero.

### FEEDFORWARD COMPENSATION

Use two parallel paths to achieve a LHP zero for lead compensation purposes.

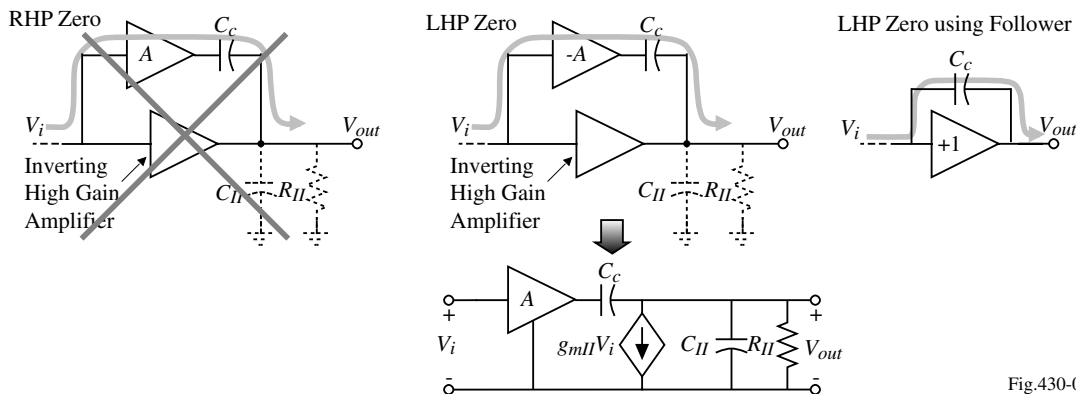


Fig.430-09

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{AC_c}{C_c + C_{II}} \left( \frac{s + g_{mII}/AC_c}{s + 1/[R_{II}(C_c + C_{II})]} \right)$$

To use the LHP zero for compensation, a compromise must be observed.

- Placing the zero below  $GB$  will lead to boosting of the loop gain that could deteriorate the phase margin.
- Placing the zero above  $GB$  will have less influence on the leading phase caused by the zero.

Note that a source follower is a good candidate for the use of feedforward compensation.

### SELF-COMPENSATED OP AMPS

*Self compensation* occurs when the load capacitor is the compensation capacitor (can never be unstable for resistive feedback)

 


Fig. 430-10

Voltage gain:

$$\frac{v_{out}}{v_{in}} = A_v(0) = G_m R_{out}$$

Dominant pole:

$$p_1 = \frac{-1}{R_{out} C_L}$$

Unity-gainbandwidth:

$$GB = A_v(0) \cdot |p_1| = \frac{G_m}{C_L}$$

Stability:

Large load capacitors simply reduce  $GB$  but the phase is still  $90^\circ$  at  $GB$ .

## **SUMMARY**

### **Compensation**

- Designed so that the op amp with unity gain feedback (buffer) is stable
- Types
  - Miller
  - Miller with nulling resistors
  - Self Compensating
  - Feedforward