

## LECTURE 180 – POWER SUPPLY REJECTION RATIO (READING: GHLM – 434-439, AH – 286-293)

### Objective

The objective of this presentation is:

- 1.) Illustrate the calculation of PSRR
- 2.) Examine the PSRR of the two-stage, Miller compensated op amp

### Outline

- Definition of PSRR
- Calculation of PSRR for the two-stage op amp
- Conceptual reason for PSRR
- Summary

### What is PSRR?

$$PSRR = \frac{A_v(V_{dd}=0)}{A_{dd}(V_{in}=0)}$$

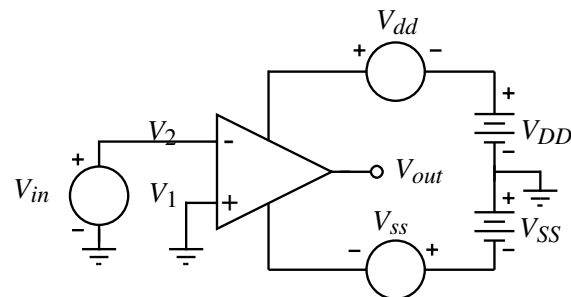


Fig.180-01

### How do you calculate PSRR?

You could calculate  $A_v$  and  $A_{dd}$  and divide, however

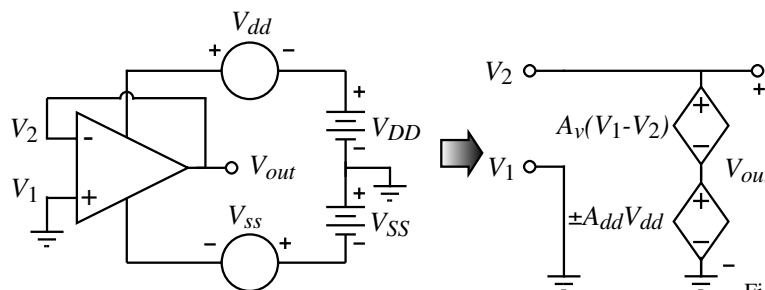


Fig. 180-02

$$V_{out} = A_{dd}V_{dd} + A_v(V_1 - V_2) = A_{dd}V_{dd} - A_vV_{out} \rightarrow V_{out}(1 + A_v) = A_{dd}V_{dd}$$

$$\therefore \frac{V_{out}}{V_{dd}} = \frac{A_{dd}}{1 + A_v} \approx \frac{A_{dd}}{A_v} = \frac{1}{PSRR+} \quad (\text{Good for frequencies up to } GB)$$

## Positive *PSRR* of the Two-Stage Op Amp

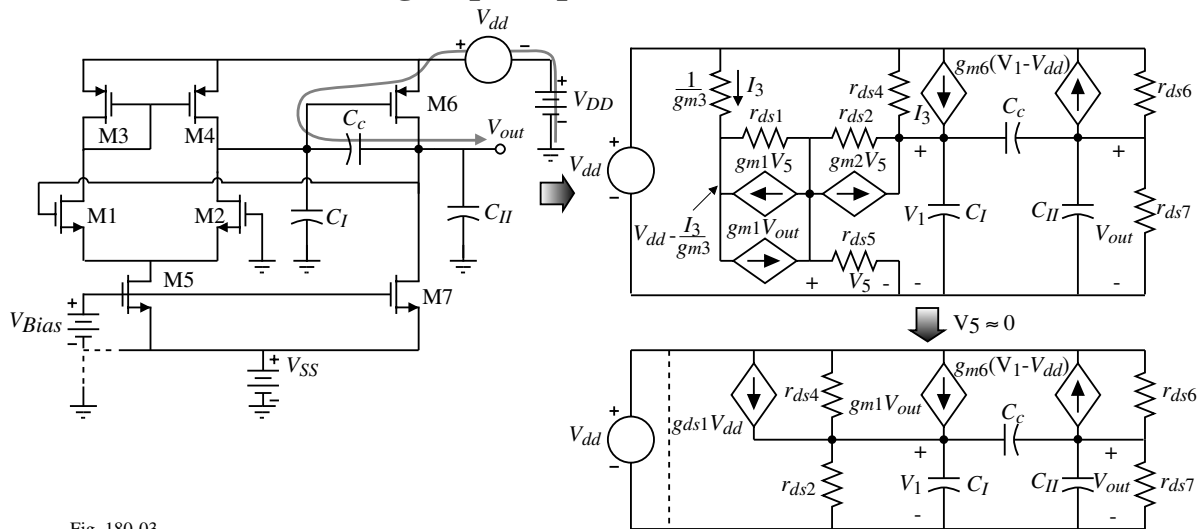


Fig. 180-03

The nodal equations are:

$$(g_{ds1} + g_{ds4})V_{dd} = (g_{ds2} + g_{ds4} + sC_c + sC_I)V_1 - (g_{m1} + sC_c)V_{out}$$

$$(g_{m6} + g_{ds6})V_{dd} = (g_{m6} - sC_c)V_1 + (g_{ds6} + g_{ds7} + sC_c + sC_{II})V_{out}$$

Using the generic notation the nodal equations are:

$$G_I V_{dd} = (G_I + sC_c + sC_I)V_1 - (g_{mI} + sC_c)V_{out}$$

$$(g_{mII} + g_{ds6})V_{dd} = (g_{mII} - sC_c)V_1 + (G_{II} + sC_c + sC_{II})V_{out}$$

where  $G_I = g_{ds1} + g_{ds4} = g_{ds2} + g_{ds4}$ ,  $G_{II} = g_{ds6} + g_{ds7}$ ,  $g_{mI} = g_{m1} = g_{m2}$  and  $g_{mII} = g_{m6}$

## Positive *PSRR* of the Two-Stage Op Amp - Continued

Using Cramer's rule to solve for the transfer function,  $V_{out}/V_{dd}$ , and inverting the transfer function gives the following result.

$$\frac{V_{dd}}{V_{out}} = \frac{s^2[C_c C_I + C_I C_{II} + C_{II} C_c] + s[G_I(C_c + C_{II}) + G_{II}(C_c + C_I) + C_c(g_{mII} - g_{mI})] + G_I G_{II} + g_{mI} g_{mII}}{s[C_c(g_{mII} + G_I + g_{ds6}) + C_I(g_{mII} + g_{ds6})] + G_I g_{ds6}}$$


We may solve for the approximate roots of numerator as

$$PSRR^+ = \frac{V_{dd}}{V_{out}} \approx \left( \frac{g_{mI} g_{mII}}{G_I g_{ds6}} \right) \left[ \frac{\left( \frac{sC_c}{g_{mI}} + 1 \right) \left( \frac{s(C_c C_I + C_I C_{II} + C_c C_{II})}{g_{mII} C_c} + 1 \right)}{\left( \frac{s g_{mII} C_c}{G_I g_{ds6}} + 1 \right)} \right]$$

where  $g_{mII} > g_{mI}$  and that all transconductances are larger than the channel conductances.

$$\therefore PSRR^+ = \frac{V_{dd}}{V_{out}} = \left( \frac{g_{mI} g_{mII}}{G_I g_{ds6}} \right) \left[ \frac{\left( \frac{sC_c}{g_{mI}} + 1 \right) \left( \frac{sC_{II}}{g_{mII}} + 1 \right)}{\frac{s g_{mII} C_c}{G_I g_{ds6}} + 1} \right] = \left( \frac{G_{II} A_{vo}}{g_{ds6}} \right) \frac{\left( \frac{s}{GB} + 1 \right) \left( \frac{s}{|p_2|} + 1 \right)}{\left( \frac{s G_{II} A_{vo}}{g_{ds6} GB} + 1 \right)}$$
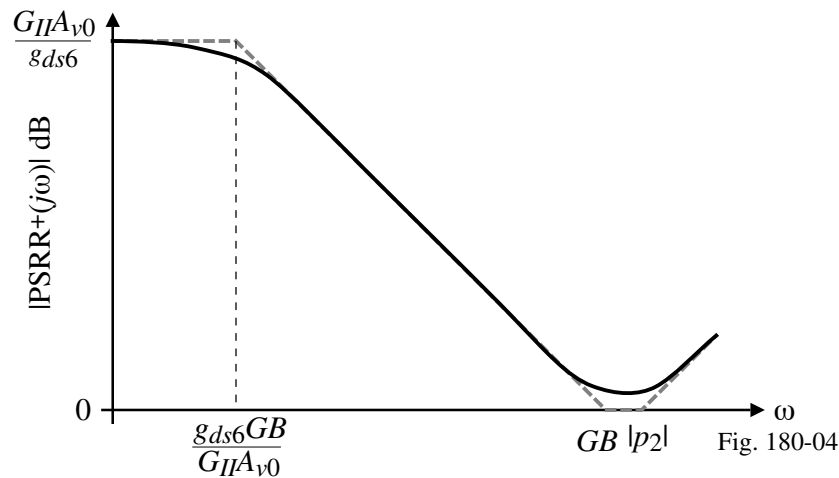
## Positive $PSRR$ of the Two-Stage Op Amp - Continued




At approximately the dominant pole, the  $PSRR^+$  falls off with a  $-20\text{dB/decade}$  slope and degrades the higher frequency  $PSRR^+$  of the two-stage op amp.

Using the values of Example 6.3-1 we get:

$$PSRR^+(0) = 68.8\text{dB}, \quad z_1 = -5\text{MHz}, \quad z_2 = -15\text{MHz} \quad \text{and} \quad p_1 = -906\text{Hz}$$
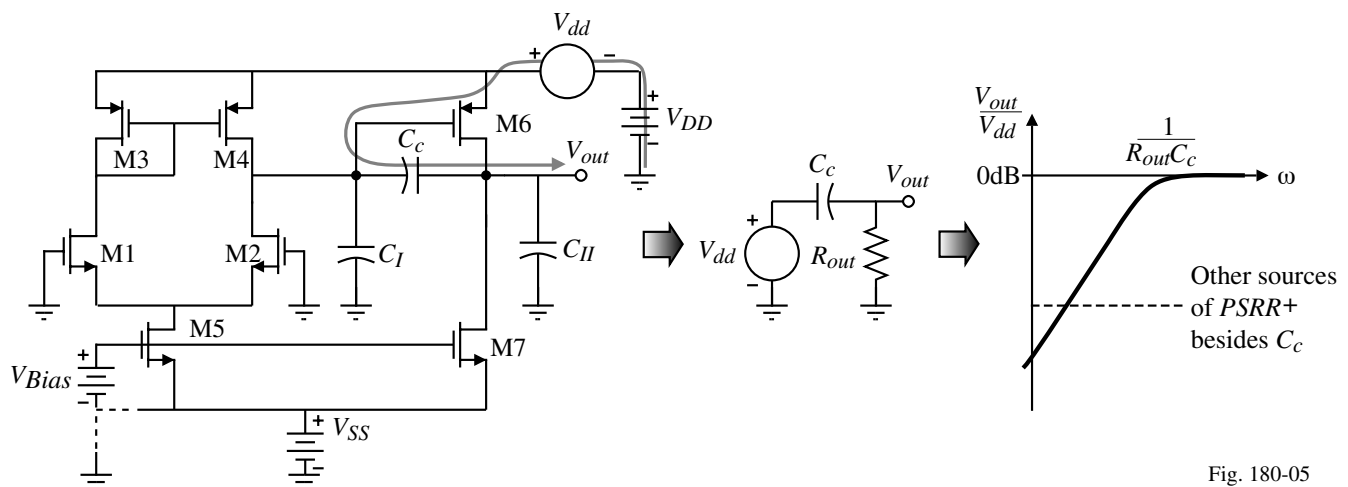
## Concept of the $PSRR^+$ for the Two-Stage Op Amp



- 1.) The M7 current sink causes  $V_{SG6}$  to act like a battery.
- 2.) Therefore,  $V_{dd}$  couples from the source to gate of M6.
- 3.) The path to the output is through any capacitance from gate to drain of M6.

Conclusion:

The Miller capacitor  $C_c$  couples the positive power supply ripple directly to the output.

Must reduce or eliminate  $C_c$ .

## Negative $PSRR$ of the Two-Stage Op Amp with $V_{Bias}$ Grounded

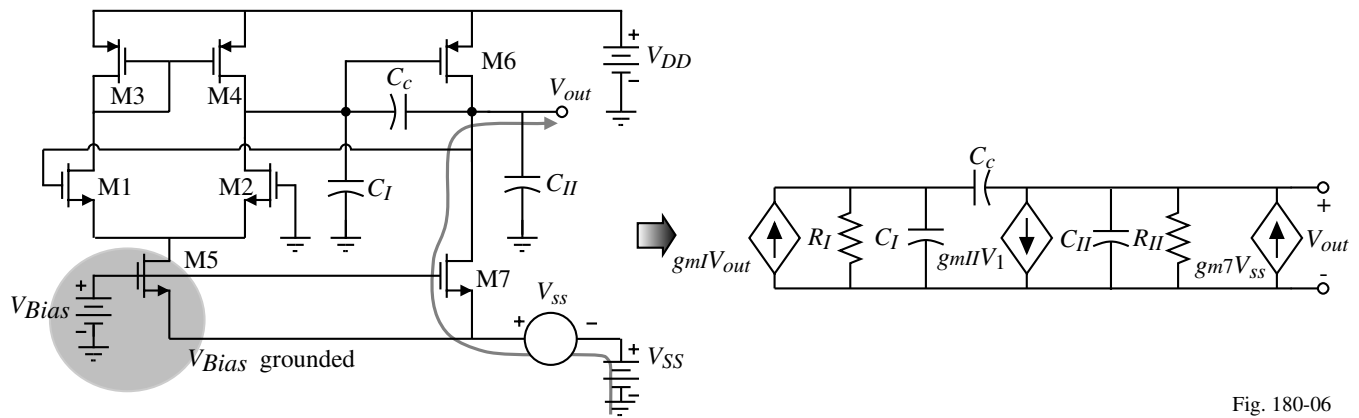


Fig. 180-06

Nodal equations for  $V_{Bias}$  grounded:

$$0 = (G_I + sC_c + sC_I)V_1 - (g_{mI} + sC_c)V_o$$

$$g_{m7}V_{ss} = (g_{mII} - sC_c)V_1 + (G_{II} + sC_c + sC_{II})V_o$$

Solving for  $V_{out}/V_{ss}$  and inverting gives

$$\frac{V_{ss}}{V_{out}} = \frac{s^2[C_c C_I + C_I C_{II} + C_{II} C_c] + s[G_I(C_c + C_{II}) + G_{II}(C_c + C_I) + C_c(g_{mII} - g_{mI})] + G_I G_{II} + g_{mI} g_{mII}}{[s(C_c + C_I) + G_I] g_{m7}}$$

## Negative $PSRR$ of the Two-Stage Op Amp with $V_{Bias}$ Grounded - Continued

Again using techniques described previously, we may solve for the approximate roots as

$$PSRR^- = \frac{V_{ss}}{V_{out}} \approx \left( \frac{g_{mI} g_{mII}}{G_I g_{m7}} \right) \left[ \frac{\left( \frac{sC_c}{g_{mI}} + 1 \right) \left( \frac{s(C_c C_I + C_I C_{II} + C_c C_{II})}{g_{mII} C_c} + 1 \right)}{\left( \frac{s(C_c + C_I)}{G_I} + 1 \right)} \right]$$

This equation can be rewritten approximately as

$$PSRR^- = \frac{V_{ss}}{V_{out}} \approx \left( \frac{g_{mI} g_{mII}}{G_I g_{m7}} \right) \left[ \frac{\left( \frac{sC_c}{g_{mI}} + 1 \right) \left( \frac{sC_{II}}{g_{mII}} + 1 \right)}{\left( \frac{sC_c}{G_I} + 1 \right)} \right] = \left( \frac{G_{II} A_{v0}}{g_{m7}} \right) \left[ \frac{\left( \frac{s}{GB} + 1 \right) \left( \frac{s}{|p_2|} + 1 \right)}{\left( \frac{s}{GB} \frac{g_{mI}}{G_I} + 1 \right)} \right]$$

Comments:

$PSRR^-$  zeros =  $PSRR^+$  zeros

DC gain  $\approx$  Second-stage gain,

$PSRR^-$  pole  $\approx$  (Second-stage gain) x ( $PSRR^+$  pole)

Assuming the values of Ex. 6.3-1 gives a gain of 23.7 dB and a pole -147 kHz. The dc value of  $PSRR^-$  is very poor for this case, however, this case can be avoided by correctly implementing  $V_{Bias}$  which we consider next.

## Negative $PSRR$ of the Two-Stage Op Amp with $V_{Bias}$ Connected to $V_{SS}$

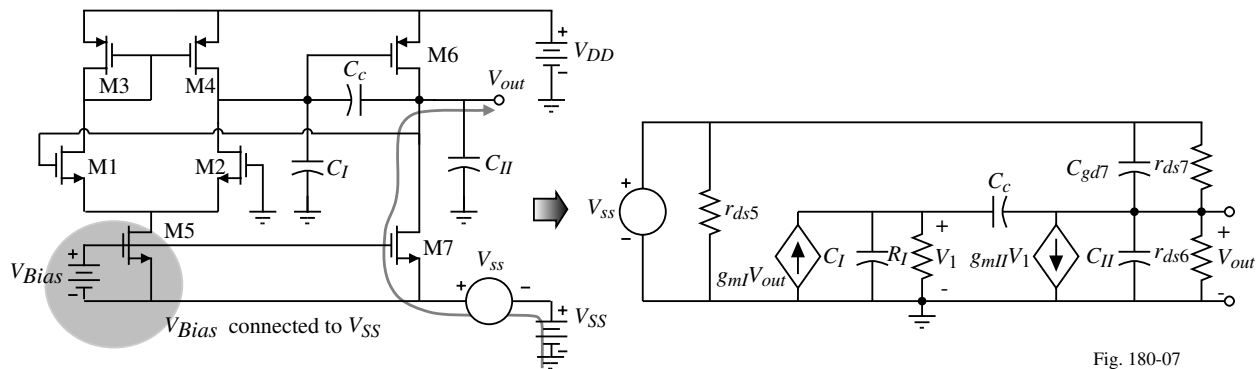


Fig. 180-07

If the value of  $V_{Bias}$  is independent of  $V_{SS}$ , then the model shown results. The nodal equations for this model are

$$0 = (G_I + sC_c + sC_I)V_1 - (g_{mI} + sC_c)V_{out}$$

and

$$(g_{ds7} + sC_{gd7})V_{ss} = (g_{mII} - sC_c)V_1 + (G_{II} + sC_c + sC_{II} + sC_{gd7})V_{out}$$

Again, solving for  $V_{out}/V_{ss}$  and inverting gives

$$\frac{V_{ss}}{V_{out}} = \frac{s^2[C_c C_I + C_I C_{II} + C_{II} C_c + C_I C_{gd7} + C_c C_{gd7}] + s[G_I(C_c + C_{II} + C_{gd7}) + G_{II}(C_c + C_I) + C_c(g_{mII} - g_{mI})] + G_I G_{II} + g_{mI} g_{mII}}{(sC_{gd7} + g_{ds7})(s(C_I + C_c) + G_I)}$$

## Negative $PSRR$ of the Two-Stage Op Amp with $V_{Bias}$ Connected to $V_{SS}$ - Continued

Assuming that  $g_{mII} > g_{mI}$  and solving for the approximate roots of both the numerator and denominator gives

$$PSRR^- = \frac{V_{ss}}{V_{out}} \approx \left( \frac{g_{mI} g_{mII}}{G_I g_{ds7}} \right) \left[ \frac{\left( \frac{sC_c}{g_{mI}} + 1 \right) \left( \frac{s(C_c C_I + C_I C_{II} + C_c C_{II})}{g_{mII} C_c} + 1 \right)}{\left( \frac{sC_{gd7}}{g_{ds7}} + 1 \right) \left( \frac{s(C_I + C_c)}{G_I} + 1 \right)} \right]$$

This equation can be rewritten as

$$PSRR^- = \frac{V_{ss}}{V_{out}} \approx \left( \frac{G_{II} A_{v0}}{g_{ds7}} \right) \left[ \frac{\left( \frac{s}{GB} + 1 \right) \left( \frac{s}{|p_2|} + 1 \right)}{\left( \frac{sC_{gd7}}{g_{ds7}} + 1 \right) \left( \frac{sC_c}{G_I} + 1 \right)} \right]$$


Comments:

- DC gain has been increased by the ratio of  $G_{II}$  to  $g_{ds7}$
- Two poles instead of one, however the pole at  $-g_{ds7}/C_{gd7}$  is large and can be ignored.


Using the values of Ex. 6.3-1 and assume that  $C_{ds7} = 10\text{fF}$ , gives,

$$PSRR^-(0) = 76.7\text{dB} \quad \text{and} \quad \text{Poles at } -71.2\text{kHz and } -149\text{MHz}$$
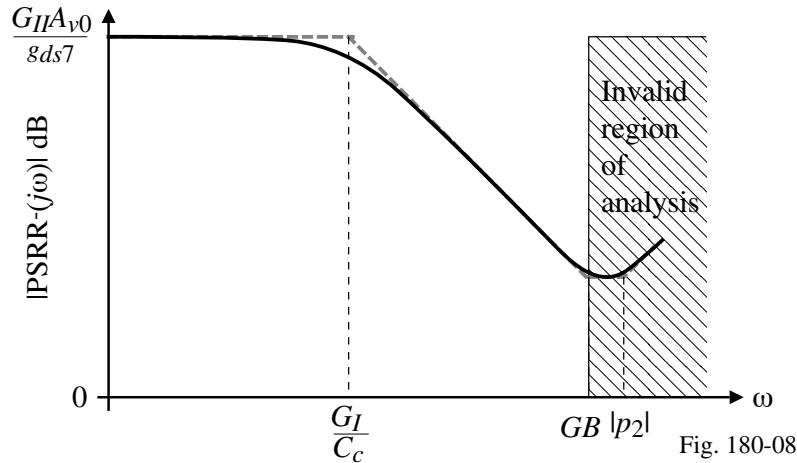
### Frequency Response of the Negative PSRR of the Two-Stage Op Amp with $V_{Bias}$ Connected to $V_{SS}$


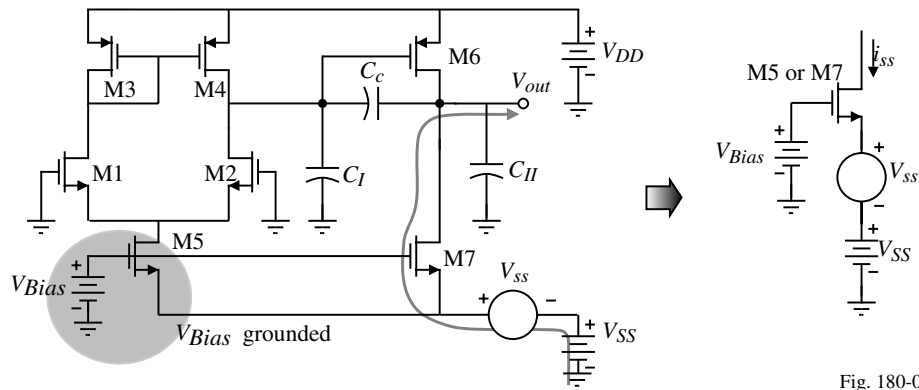
### Approximate Model for Negative PSRR with $V_{Bias}$ Connected to Ground




Path through the input stage is not important as long as the  $CMRR$  is high.


Path through the output stage:

$$v_{out} \approx i_{ss}Z_{out} = g_{m7}Z_{out}V_{ss}$$
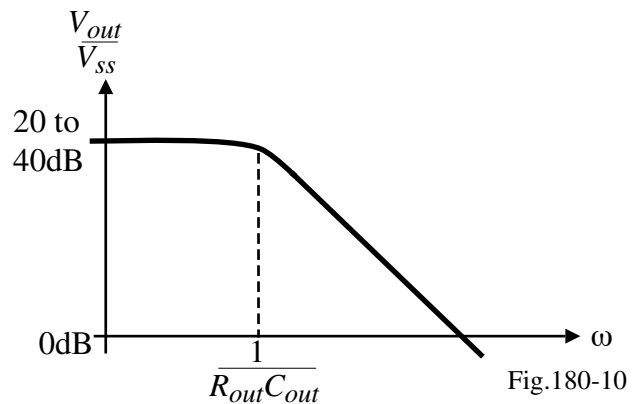
$$\therefore \frac{V_{out}}{V_{ss}} = g_{m7}Z_{out} = g_{m7}R_{out} \left( \frac{1}{sR_{out}C_{out}+1} \right)$$



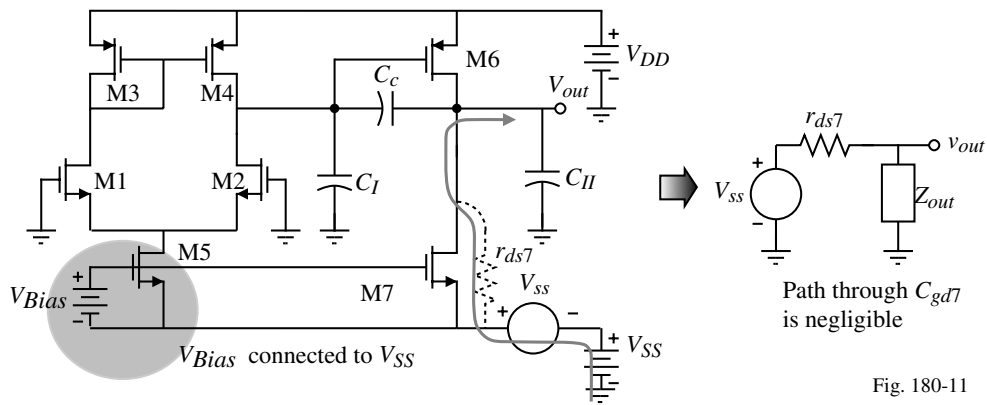**Approximate Model for Negative PSRR with  $V_{Bias}$  Connected to  $V_{SS}$**



What is  $Z_{out}$ ?

$$Z_{out} = \frac{V_t}{I_t} \Rightarrow$$

$$I_t = g_{mII}V_1 = g_{mII} \left( \frac{g_{mI}V_t}{G_I + sC_I + sC_C} \right)$$

$$\text{Thus, } Z_{out} = \frac{G_I + s(C_I + C_C)}{g_{mI}g_{mII}}$$

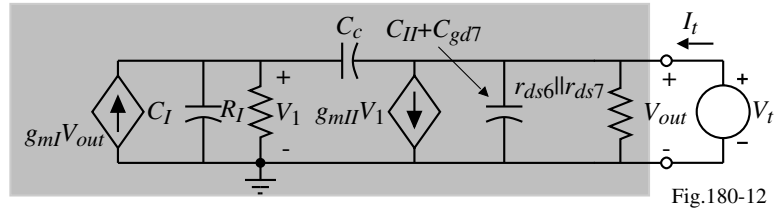


Fig.180-12

$$\therefore \frac{V_{SS}}{V_{out}} = \frac{1 + \frac{r_{ds7}}{Z_{out}}}{1} = \frac{s(C_C + C_I) + G_I + g_{mI}g_{mII}r_{ds7}}{s(C_C + C_I) + G_I} \Rightarrow \text{ Pole at } \frac{-G_I}{C_C + C_I}$$

The two-stage op amp will never have good PSRR because of the Miller compensation.

**SUMMARY**

- PSRR is a measure of the influence of power supply ripple on the op amp output voltage
- PSRR can be calculated by putting the op amp in the unity-gain configuration with the input shorted.
- The Miller compensation capacitor allows the power supply ripple at the output to be large
- The two-stage op amp will never have good PSRR unless some modifications are made.