

LECTURE 310 – HIGH SPEED/FREQUENCY OP AMPS (READING: AH – 368-384)

Objective

The objective of this presentation is:

- 1.) Explore op amps having high frequency response and/or high slew rate
- 2.) Give examples


Outline

- Extending the GB of conventional op amps
- Switched op amps
- Current feedback op amps
- Programmable gain amplifiers
- Parallel path op amps
- Summary

What is the Influence of GB on the Frequency Response?

The op amp is primarily designed to be used with negative feedback. When the product of the op amp gain and feedback gain (loss) is not greater than unity, negative feedback does not work satisfactorily.

 Example of a gain of -10 voltage amplifier:



What causes the GB ?

We know that


$$GB = \frac{g_m}{C}$$

where g_m is the transconductance that converts the input voltage to current and C is the capacitor that causes the dominant pole.

This relationship assumes that all higher-order poles are greater than GB .

What is the Limit of GB?

 The following illustrates what happens when the next higher pole is not greater than GB:



For a two-stage op amp, the poles and zeros are:

- 1.) Dominant pole $p_1 = \frac{-g_{m1}}{A_v(0)C_c}$
- 2.) Output pole $p_2 = \frac{-g_{m6}}{C_L}$
- 3.) Mirror pole $p_3 = \frac{-g_{m3}}{C_{gs3} + C_{gs4}}$
- 4.) Nulling pole $p_4 = \frac{-1}{R_z C_I}$
- 5.) Nulling zero $z_1 = \frac{-1}{R_z C_c - (C_c / g_{m6})}$

A Procedure to Increase the GB of a Two-Stage Op Amp

- 1.) Use the nulling zero to cancel the closest pole beyond the dominant pole.
- 2.) The maximum GB would be equal to the magnitude of the second closest pole beyond the dominant pole.
- 3.) Adjust the dominant pole so that $GB \approx 2.2 \times$ (second closest pole beyond the dominant pole)

Illustration which assumes that p_2 is the next closest pole beyond the dominant pole:

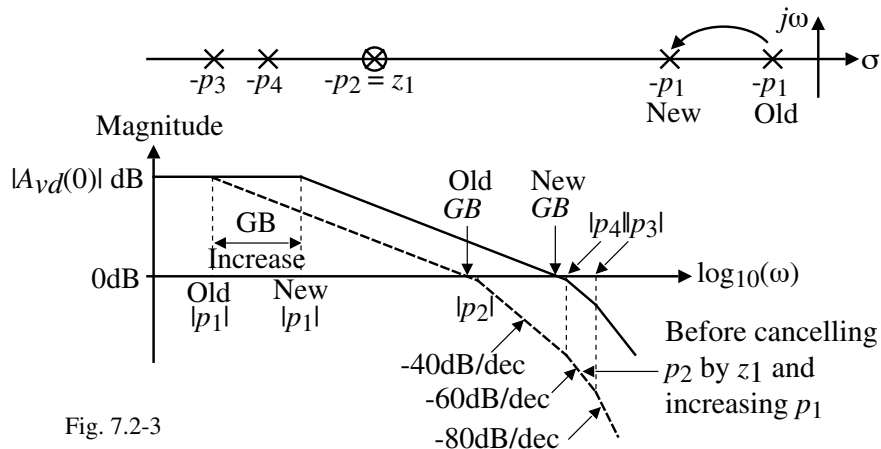


Fig. 7.2-3

Example 7.2-1 - Increasing the GB of the Op Amp Designed in Ex. 6.3-1

Use the two-stage op amp designed in Example 6.3-1 and apply the above approach to increase the gainbandwidth as much as possible.

Solution

1.) First find the values of p_2 , p_3 , and p_4 .

(a.) From Ex. 6.3-2, we see that

$$p_2 = -94.25 \times 10^6 \text{ rads/sec.}$$

(b.) p_3 was found in Ex. 6.3-1 as

$$p_3 = -2.81 \times 10^9 \text{ rads/sec.}$$

(c.) To find p_4 , we must find C_I which is the output capacitance of the first stage of the op amp. C_I consists of the following capacitors,

$$C_I = C_{bd2} + C_{bd4} + C_{gs6} + C_{gd2} + C_{gd4}$$

For C_{bd2} the width is $3\mu\text{m} \Rightarrow L_1+L_2+L_3 = 3\mu\text{m} \Rightarrow AS/AD=9\mu\text{m}^2$ and $PS/PD = 12\mu\text{m}$.

For C_{bd4} the width is $15\mu\text{m} \Rightarrow L_1+L_2+L_3 = 3\mu\text{m} \Rightarrow AS/AD=45\mu\text{m}^2$ and $PS/PD = 36\mu\text{m}$.

From Table 3.2-1:

$$C_{bd2} = (9\mu\text{m}^2)(770 \times 10^{-6} \text{F/m}^2) + (12\mu\text{m})(380 \times 10^{-12} \text{F/m}) = 6.93 \text{fF} + 4.56 \text{fF} = 11.5 \text{fF}$$

$$C_{bd4} = (45\mu\text{m}^2)(560 \times 10^{-6} \text{F/m}^2) + (36\mu\text{m})(350 \times 10^{-12} \text{F/m}) = 25.2 \text{fF} + 12.6 \text{fF} \approx 37.8 \text{fF}$$

 


Fig. 7.2-3A

Example 7.2-1 - Continued

C_{gs6} is given by Eq. (10b) of Sec. 3.2 and is

$$\begin{aligned} C_{gs6} &= CGDO \cdot W_6 + 0.67(C_{ox} W_6 L_6) = (220 \times 10^{-12})(94 \times 10^{-6}) + (0.67)(24.7 \times 10^{-4})(94 \times 10^{-12}) \\ &= 20.7 \text{fF} + 154.8 \text{fF} = 175.5 \text{fF} \end{aligned}$$

$$C_{gd2} = 220 \times 10^{-12} \times 3\mu\text{m} = 0.66 \text{fF} \quad \text{and} \quad C_{gd4} = 220 \times 10^{-12} \times 15\mu\text{m} = 3.3 \text{fF}$$

Therefore, $C_I = 11.5 \text{fF} + 37.8 \text{fF} + 175.5 \text{fF} + 0.66 \text{fF} + 3.3 \text{fF} = 228.8 \text{fF}$. Although C_{bd2} and C_{bd4} will be reduced with a reverse bias, let us use these values to provide a margin. In fact, we probably ought to double the whole capacitance to make sure that other layout parasitics are included. Thus let C_I be 300fF .

In Ex. 6.3-2, R_z was $4.591 \text{k}\Omega$ which gives $p_4 = -0.726 \times 10^9 \text{ rads/sec}$.

2.) Using the nulling zero, z_1 , to cancel p_2 , gives p_4 as the next smallest pole.

For 60° phase margin $GB = |p_4|/2.2$ if the next smallest pole is more than $10GB$.

$$\therefore GB = 0.726 \times 10^9 / 2.2 = 0.330 \times 10^9 \text{ rads/sec. or } 52.5 \text{MHz.}$$

This value of GB is designed from the relationship that $GB = g_{m1}/C_c$. Assuming g_{m1} is constant, then $C_c = g_{m1}/GB = (94.25 \times 10^{-6}) / (0.330 \times 10^9) = 286 \text{fF}$. It might be useful to increase g_{m1} in order to keep C_c above the surrounding parasitic capacitors ($C_{gd6} = 20.7 \text{fF}$). The success of this method assumes that there are no other roots with a magnitude smaller than $10GB$.

Example 7.2-2 - Increasing the GB of the Folded Cascode Op Amp of Ex. 6.5-3

Use the folded-cascode op amp designed in Example 6.5-3 and apply the above approach to increase the gainbandwidth as much as possible. Assume that the drain/source areas are equal to $2\mu\text{m}$ times the width of the transistor and that all voltage dependent capacitors are at zero voltage.

Solution

The poles of the folded cascode op amp are:

$$p_A \approx \frac{-1}{R_A C_A} \quad (\text{the pole at the source of M6})$$

$$p_B \approx \frac{-1}{R_B C_B} \quad (\text{the pole at the source of M7})$$

$$p_6 \approx \frac{-1}{(R_2 + 1/g_{m10})C_6} \quad (\text{the pole at the drain of M6})$$

$$p_8 \approx \frac{-g_{m8}}{C_8} \quad (\text{the pole at the source of M8}) \quad p_9 \approx \frac{-g_{m9}}{C_9} \quad (\text{the pole at the source of M9})$$

$$\text{and } p_{10} \approx \frac{-g_{m10}}{C_{10}} \quad (\text{the pole at the gates of M10 and M11})$$

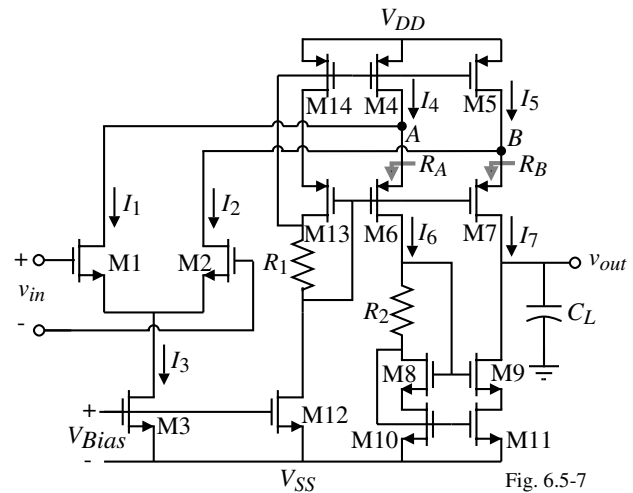


Fig. 6.5-7

Example 7.2-2 - Continued

Let us evaluate each of these poles.

1.) For p_A , the resistance R_A is approximately equal to g_{m6} and C_A is given as

$$C_A = C_{gs6} + C_{bd1} + C_{gd1} + C_{bd4} + C_{bs6} + C_{gd4}$$

From Ex. 6.5-3, $g_{m6} = 744.6\mu\text{S}$ and capacitors giving C_A are found using the parameters of Table 3.2-1 as,

$$C_{gs6} = (220 \times 10^{-12} \cdot 80 \times 10^{-6}) + (0.67)(80 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 149\text{fF}$$

$$C_{bd1} = (770 \times 10^{-6})(35.9 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2.37.9 \times 10^{-6}) = 84\text{fF}$$

$$C_{gd1} = (220 \times 10^{-12} \cdot 35.9 \times 10^{-6}) = 8\text{fF}$$

$$C_{bd4} = C_{bs6} = (560 \times 10^{-6})(80 \times 10^{-6} \cdot 2 \times 10^{-6}) + (350 \times 10^{-12})(2.82 \times 10^{-6}) = 147\text{fF}$$

and

$$C_{gd4} = (220 \times 10^{-12})(80 \times 10^{-6}) = 17.6\text{fF}$$

Therefore,

$$C_A = 149\text{fF} + 84\text{fF} + 8\text{fF} + 147\text{fF} + 17.6\text{fF} + 147\text{fF} = 0.553\text{pF}$$

Thus,

$$p_A = \frac{-744.6 \times 10^{-6}}{0.553 \times 10^{-12}} = -1.346 \times 10^9 \text{ rads/sec.}$$

2.) For the pole, p_B , the capacitance connected to this node is

$$C_B = C_{gd2} + C_{bd2} + C_{gs7} + C_{gd5} + C_{bd5} + C_{bs7}$$

Example 7.2-2 - Continued

The various capacitors above are found as

$$C_{gd2} = (220 \times 10^{-12} \cdot 35.9 \times 10^{-6}) = 8 \text{ fF}$$

$$C_{bd2} = (770 \times 10^{-6})(35.9 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2 \cdot 37.9 \times 10^{-6}) = 84 \text{ fF}$$

$$C_{gs7} = (220 \times 10^{-12} \cdot 80 \times 10^{-6}) + (0.67)(80 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 149 \text{ fF}$$

$$C_{gd5} = (220 \times 10^{-12})(80 \times 10^{-6}) = 17.6 \text{ fF}$$

and

$$C_{bd5} = C_{bs7} = (560 \times 10^{-6})(80 \times 10^{-6} \cdot 2 \times 10^{-6}) + (350 \times 10^{-12})(2 \cdot 82 \times 10^{-6}) = 147 \text{ fF}$$

The value of C_B is the same as C_A and g_{m6} is assumed to be the same as g_{m7} giving $p_B = p_A = -1.346 \times 10^9$ rads/sec.

3.) For the pole, p_6 , the capacitance connected to this node is

$$C_6 = C_{bd6} + C_{gd6} + C_{gs8} + C_{gs9}$$

The various capacitors above are found as

$$C_{bd6} = (560 \times 10^{-6})(80 \times 10^{-6} \cdot 2 \times 10^{-6}) + (350 \times 10^{-12})(2 \cdot 82 \times 10^{-6}) = 147 \text{ fF}$$

$$C_{gs8} = (220 \times 10^{-12} \cdot 36.4 \times 10^{-6}) + (0.67)(36.4 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 67.9 \text{ fF}$$

and

$$C_{gs9} = C_{gs8} = 67.9 \text{ fF} \quad C_{gd6} = C_{gd5} = 17.6 \text{ fF}$$

Therefore,

$$C_6 = 147 \text{ fF} + 17.6 \text{ fF} + 67.9 \text{ fF} + 67.9 \text{ fF} = 0.300 \text{ pF}$$

Example 7.2-2 - Continued

From Ex. 6.5-3, $R_2 = 2 \text{ k}\Omega$ and $g_{m6} = 744.6 \times 10^{-6}$. Therefore, p_6 , can be expressed as

$$-p_6 = \frac{1}{(2 \times 10^3 + (10^6/744.6)) \cdot 0.300 \times 10^{-12}} = 0.966 \times 10^9 \text{ rads/sec.}$$

4.) Next, we consider the pole, p_8 . The capacitance connected to this node is

$$C_8 = C_{bd10} + C_{gd10} + C_{gs8} + C_{bs8}$$

These capacitors are given as,

$$C_{bs8} = C_{bd10} = (770 \times 10^{-6})(36.4 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2 \cdot 38.4 \times 10^{-6}) = 85.2 \text{ fF}$$

$$C_{gs8} = (220 \times 10^{-12} \cdot 36.4 \times 10^{-6}) + (0.67)(36.4 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 67.9 \text{ fF}$$

and

$$C_{gd10} = (220 \times 10^{-12})(36.4 \times 10^{-6}) = 8 \text{ fF}$$

The capacitance C_8 is equal to

$$C_8 = 67.9 \text{ fF} + 8 \text{ fF} + 85.2 \text{ fF} + 85.2 \text{ fF} = 0.246 \text{ pF}$$

Using the g_{m8} of Ex. 6.5-3 of $774.6 \mu\text{S}$, the pole p_8 is found as, $-p_8 = 3.149 \times 10^9$ rads/sec.

5.) The capacitance for the pole at p_9 is identical with C_8 . Therefore, since g_{m9} is also $774.6 \mu\text{S}$, the pole p_9 is equal to p_8 and found to be $-p_9 = 3.149 \times 10^9$ rads/sec.

6.) Finally, the capacitance associated with p_{10} is given as

$$C_{10} = C_{gs10} + C_{gs11} + C_{bd8}$$

These capacitors are given as

Example 7.2-2 - Continued

$$C_{gs10} = C_{gs11} = (220 \times 10^{-12} \cdot 36.4 \times 10^{-6}) + (0.67)(36.4 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 67.9 \text{ fF}$$

and

$$C_{bd8} = (770 \times 10^{-6})(36.4 \times 10^{-6} \cdot 2 \times 10^{-6}) + (380 \times 10^{-12})(2 \cdot 38.4 \times 10^{-6}) = 85.2 \text{ fF}$$

Therefore,

$$C_{10} = 67.9 \text{ fF} + 67.9 \text{ fF} + 85.2 \text{ fF} = 0.221 \text{ pF}$$

which gives the pole p_{10} as $-744.6 \times 10^{-6} / 0.246 \times 10^{-12} = -3.505 \times 10^9$ rads/sec.

The poles are summarized below:

$$p_A = -1.346 \times 10^9 \text{ rads/sec} \quad p_B = -1.346 \times 10^9 \text{ rads/sec} \quad p_6 = -0.966 \times 10^9 \text{ rads/sec}$$

$$p_8 = -3.149 \times 10^9 \text{ rads/sec} \quad p_9 = -3.149 \times 10^9 \text{ rads/sec} \quad p_{10} = -3.505 \times 10^9 \text{ rads/sec}$$

The smallest of these poles is p_6 . Since p_A and p_B are not much larger than p_6 , we will find the new GB by dividing p_6 by 5 (rather than 2.2) to get 200×10^6 rads/sec. Thus the new GB will be $200/2\pi$ or 32MHz. The magnitude of the dominant pole is given as

$$p_{\text{dominant}} = \frac{GB}{A_{vd}(0)} = \frac{200 \times 10^6}{7,464} = 26,795 \text{ rads/sec.}$$

The value of load capacitor that will give this pole is

$$C_L = \frac{1}{p_{\text{dominant}} \cdot R_{\text{out}}} = \frac{1}{26.795 \times 10^3 \cdot 19.4 \text{ M}\Omega} \approx 1.9 \text{ pF}$$

Therefore, the new $GB = 32\text{MHz}$ compared with the old $GB = 10\text{MHz}$.**Conclusion for Increasing the GB of Op Amps**

Maximum GB depends on the input transconductance and the capacitance that causes the dominant pole.

Quantity	MOSFET Op Amp	BJT Op Amp
g_m dependence	$\sqrt{2K' \left(\frac{W}{L}\right) I_D}$	$\frac{I_C}{kT/q} = \frac{I_C}{V_t}$
Maximum g_m	$\approx 1 \text{ mA/V}$	$\approx 20 \text{ mA/V}$
GB for 10pF	15 MHz	300 MHz
GB for 1pF	150 MHz	3 GHz

Note that the power dissipation will be large for large GB because current is needed for large g_m .

Assumption:

All higher-order roots are above GB .

The larger GB , the more difficult this becomes.

Conclusion:


- The best CMOS op amps have a GB of 10-50MHz
- The best BJT op amps have a GB of 100-200MHz

Switched Amplifiers


Switched amplifiers are time varying circuits that yield circuits with smaller parasitic capacitors and therefore higher frequency response. Such circuits are called *dynamically biased*.

- Switched amplifiers require a nonoverlapping clock
- Switched amplifiers only work during a portion of a clock period
- Bias conditions are setup on one clock phase and then maintained by capacitance on the active phase
- Switched amplifiers use switches and capacitors resulting in feedthrough problems
- Simplified circuits on the active phase minimize the parasitics

Typical clock:

 

Dynamically Biased Inverting Amplifier

 

During phase 1 the offset and bias of the inverter is sampled and applied to C_{OS} and C_B .

During phase 2 C_{OS} is connected in series with the input and provides offset canceling plus bias for M1. C_B provides the bias for M2.

(This circuit illustrates the concept of switched amplifiers but is too simple to illustrate the reduction of bias parasitics.)

Dynamically Biased, Push-Pull, Cascode Op Amp

 


Fig.7.2-5


Push-pull, cascode amplifier: M1-M2 and M3-M4

Bias circuitry: M5-M6-C2 and M7-M8-C1

Parasitics can be further reduced by using a double-poly process to eliminate bulk-drain and bulk-source capacitances at the drain of M1-source of M2 and drain of M4-source of M3 (see Fig. 6.5-5).

Dynamically Biased, Push-Pull, Cascode Op Amp - Continued

Operation:

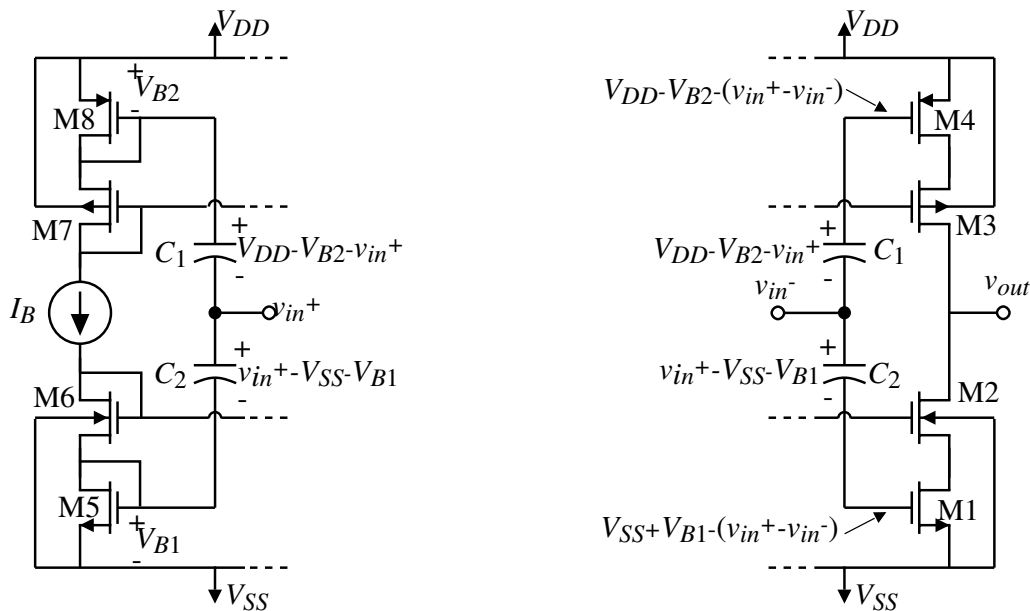

Equivalent circuit during the ϕ_1 clock period

Equivalent circuit during the ϕ_2 clock period.

Fig. 7.2-6

Dynamically Biased, Push-Pull, Cascode Op Amp - Continued

This circuit will operate on both clock phases[†].

 


Fig. 7.2-7

Performance (1.5μm CMOS):

- 1.6mW dissipation
- $GB \approx 130\text{MHz}$ ($C_L=2.2\text{pF}$)
- Settling time of 10ns ($C_L=10\text{pF}$)

This amplifier was used with a 28.6MHz clock to realize a 5th-order switched capacitor filter having a cutoff frequency of 3.5MHz.

[†] S. Masuda, et. al., "CMOS Sampled Differential Push-Pull Cascode Op Amp," *Proc. of 1984 International Symposium on Circuits and Systems*, Montreal, Canada, May 1984, pp. 1211-12-14.

Current Feedback Op Amps

Why current feedback:

- Higher GB
- Less voltage swing \Rightarrow more dynamic range

What is a current amplifier?

 


Fig. 7.2-8A

Requirements:

$$i_o = A_i(i_1 - i_2)$$

$$R_{i1} = R_{i2} = 0\Omega$$

$$R_o = \infty$$

Ideal source and load requirements:

$$R_{source} = \infty$$

$$R_{Load} = 0\Omega$$

Bandwidth Advantage of a Current Feedback Amplifier

Consider the inverting voltage amplifier shown using a current amplifier with negative current feedback:

The output current, i_o , of the current amplifier can be written as

$$i_o = A_i(s)(i_1 - i_2) = -A_i(s)(i_{in} + i_o)$$

The closed-loop current gain, i_o/i_{in} , can be found as

$$\frac{i_o}{i_{in}} = \frac{-A_i(s)}{1 + A_i(s)}$$

However, $v_{out} = i_o R_2$ and $v_{in} = i_{in} R_1$. Solving for the voltage gain, v_{out}/v_{in} gives

$$\frac{v_{out}}{v_{in}} = \frac{i_o R_2}{i_{in} R_1} = \left(\frac{-R_2}{R_1} \right) \left(\frac{A_i(s)}{1 + A_i(s)} \right)$$

If $A_i(s) = \frac{A_o}{\frac{s}{\omega_A} + 1}$, then

$$\frac{v_{out}}{v_{in}} = \left(\frac{-R_2}{R_1} \right) \left(\frac{A_o}{1 + A_o} \right) \left(\frac{\omega_A(1 + A_o)}{s + \omega_A(1 + A_o)} \right) \Rightarrow A_v(0) = \frac{-R_2 A_o}{R_1(1 + A_o)} \quad \text{and} \quad \boxed{\omega_{-3dB} = \omega_A(1 + A_o)}$$

 


Fig. 7.2-9

Bandwidth Advantage of a Current Feedback Amplifier - Continued

The unity-gainbandwidth is,

$$GB = |A_v(0)| \omega_{-3dB} = \frac{R_2 A_o}{R_1(1 + A_o)} \cdot \omega_A(1 + A_o) = \frac{R_2}{R_1} A_o \cdot \omega_A = \frac{R_2}{R_1} GB_i$$

where GB_i is the unity-gainbandwidth of the current amplifier.

Note that if GB_i is constant, then increasing R_2/R_1 (the voltage gain) increases GB .

Illustration:

 


Fig. 7.2-10

Note that $GB_2 > GB_1 > GB_i$

The above illustration assumes that the GB of the voltage amplifier realizing the voltage buffer is greater than the GB achieved from the above method.

A Simple Current Mirror Implementation of a High Frequency Amplifier

Since the gain of the current amplifier does not need to be large, consider a unity-gain current mirror implementation:

 


Fig. 7.2-11

An inverting amplifier with a gain of 10 is achieved if $R_2 = 20R_1$ assuming the gain of the current mirror is unity.

What is the GB of this amplifier?

$$GB = |A_v(0)|_{\omega=3\text{dB}} = \frac{R_2 A_o}{R_1(1+A_o)} \cdot \frac{1}{R_2 C_o} = \frac{A_o}{(1+A_o)R_1 C_o} = \frac{1}{2R_1 C_o}$$

where C_o is the capacitance seen at the output of the current mirror.

If $R_1 = 10\text{k}\Omega$ and $C_o = 250\text{fF}$, then $GB = 31.83\text{MHz}$.

Limitations:

$$R_1 > R_{in} = 1/g_{m1} \quad \text{and} \quad R_2 < r_{ds2} \parallel r_{ds6} \quad \Rightarrow \quad \frac{R_2}{R_1} \ll g_{m1}(r_{ds2} \parallel r_{ds6})$$

A Wide-Swing, Cascode Current Mirror Implementation of a High Frequency Amplifier

The current mirror shown below increases the value of R_2 by increasing the output resistance of the current mirror.

 


Fig. 7.2-12

New limitations:

$$R_1 > \frac{1}{g_{m1}} \quad \text{and} \quad R_2 < g_{m4}r_{ds4}r_{ds2} \parallel g_{m6}r_{ds6}r_{ds8} \quad \Rightarrow \quad \frac{R_2}{R_1} \ll g_{m1}(g_{m4}r_{ds4}r_{ds2} \parallel g_{m6}r_{ds6}r_{ds8})$$

Example 7.2-3 - Design of a High GB Voltage Amplifier using Current Feedback

Design the wide-swing, cascode voltage amplifier to achieve a gain of -10V/V and a GB of 500MHz which corresponds to a -3dB frequency of 50MHz.

Solution

Since we know what the gain is to be, let us begin by assuming that C_o will be 100fF. Thus to get a GB of 500MHz, R_1 must be 3.2k Ω and $R_2 = 32$ k Ω . Therefore, $1/g_{m1}$ must be less than 3200 Ω (say 300 Ω). Therefore we can write

$$g_{m1} = \sqrt{2KI'(W/L)} = \frac{1}{300\Omega} \rightarrow 5.56 \times 10^{-6} = K' \cdot I \cdot \frac{W}{L} \rightarrow 0.0505 = I \cdot \frac{W}{L}$$

At this point we have a problem because if W/L is small to minimize C_o , the current will be too high. If we select $W/L = 200\mu\text{m}/1\mu\text{m}$ we will get a current of 0.25mA. However, using this W/L for M4 and M6 will give a value of C_o that is greater than 100fF. Therefore, select $W/L = 200$ for M1, M3, M5 and M7 and $W/L = 20\mu\text{m}/1\mu\text{m}$ for M2, M4, M6, and M8 which gives a current in these transistors of 25 μA .

Since R_2/R_1 is multiplied by 1/11 let R_2 be 110 times R_1 or 352k Ω .

Now select a W/L for M12 of $20\mu\text{m}/1\mu\text{m}$ which will now permit us to calculate C_o . We will assume zero-bias on all voltage dependent capacitors. Furthermore, we will assume the diffusion area as $2\mu\text{m}$ times the W . C_o can be written as

$$C_o = C_{gd4} + C_{bd4} + C_{gd6} + C_{bd6} + C_{gs12}$$

Example 7.2-3 - Design of a High GB Voltage Amplifier using Current Feedback - Cont'd

The information required to calculate these capacitors is found from Table 3.2-1. The various capacitors are,

$$C_{gd4} = C_{gd6} = CGDO \times 10\mu\text{m} = (220 \times 10^{-12})(20 \times 10^{-6}) = 4.4\text{fF}$$

$$C_{bd4} = CJ \times AD_4 + CJSW \times PD_4 = (770 \times 10^{-6})(20 \times 10^{-12}) + (380 \times 10^{-12})(44 \times 10^{-6}) = 15.4\text{fF} + 16.7\text{fF} = 32.1\text{fF}$$

$$C_{bd6} = (560 \times 10^{-6})(20 \times 10^{-12}) + (350 \times 10^{-12})(44 \times 10^{-6}) = 26.6\text{fF}$$


$$C_{gs12} = (220 \times 10^{-12})(20 \times 10^{-6}) + (0.67)(20 \times 10^{-6} \cdot 10^{-6} \cdot 24.7 \times 10^{-4}) = 37.3\text{fF}$$

Therefore,

$$C_o = 4.4\text{fF} + 32.1\text{fF} + 4.4\text{fF} + 26.6\text{fF} + 37.3\text{fF} = 105\text{fF}$$

Note that if we had not reduced the W/L of M2, M4, M6, and M8 that C_o would have easily exceeded 100fF. Since 105fF is close to our original guess of 100fF, let us keep the values of R_1 and R_2 . If this value was significantly different, then we would adjust the values of R_1 and R_2 so that the GB is 500MHz. One must also check to make sure that the input pole is greater than 500MHz.

The design is completed by assuming that $I_{Bias} = 100\mu\text{A}$ and that the current in M9 through M12 be $100\mu\text{A}$. Thus $W_{13}/L_{13} = W_{14}/L_{14} = 20\mu\text{m}/1\mu\text{m}$ and W_9/L_9 through W_{12}/L_{12} are $20\mu\text{m}/1\mu\text{m}$.

 Example 7.2-3 - Continued**Simulation Results:**

$f_{-3dB} \approx 38\text{MHz}$ $GB \approx 300\text{MHz}$ Closed-loop gain = 18dB (Loss of -2dB is attributed to source follower and R_1)

Note second pole at about 1GHz. To get these results, it was necessary to bias the input at -1.7VDC using $\pm 3\text{V}$ power supplies.

If R_1 is decreased to $1\text{k}\Omega$ results in:

Gain of 26.4dB, $f_{-3dB} = 32\text{MHz}$, and $GB = 630\text{MHz}$

A 71 MHz Programmable Gain Amplifier using a Current Amplifier

The following circuit has been submitted for fabrication in $0.25\mu\text{m}$ CMOS:

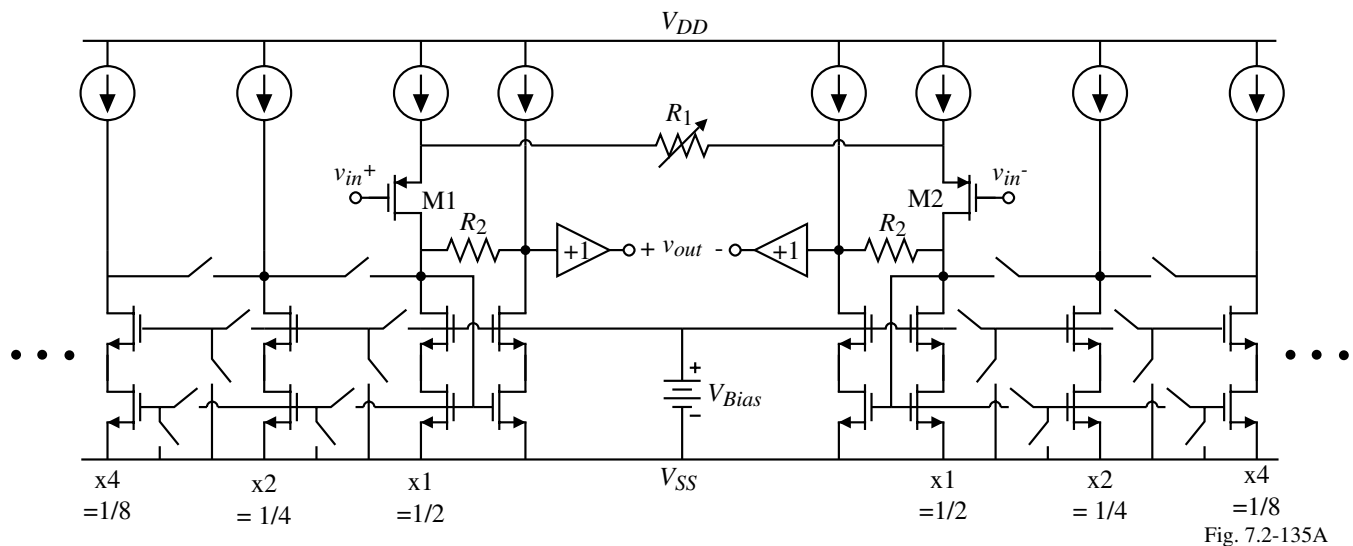



Fig. 7.2-135A

R_1 and the current mirrors are used for gain variation. R_2 is fixed.

Can cascade this amplifier for higher gains

$$BW = BW_i \sqrt{2^{1/n} - 1} \quad \text{for } n = 2, BW = 0.64 BW_i$$

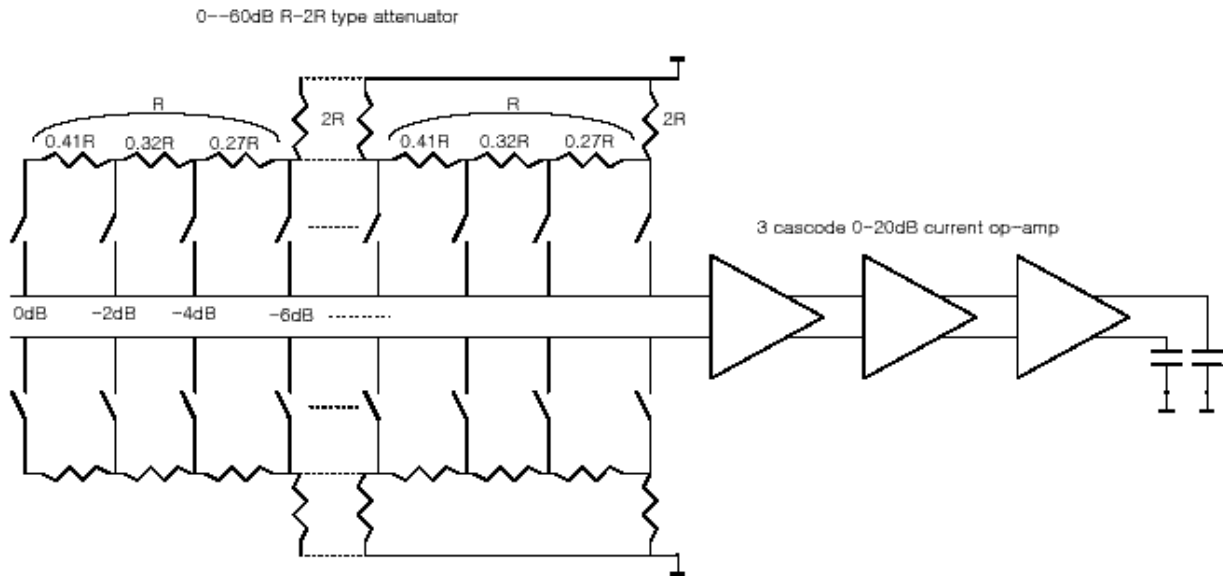Implementation of a 60dB Gain, 500MHz -3dB Frequency PGA




Simulation Results

Output voltage swing is 1.26V for a 2.5V power supply.

Voltage gain is 0 to 60dB in 2dB steps (gain error = $\pm 0.17\text{dB}$)

Maximum GB is 1.5GHz

Total current: 3.6mA

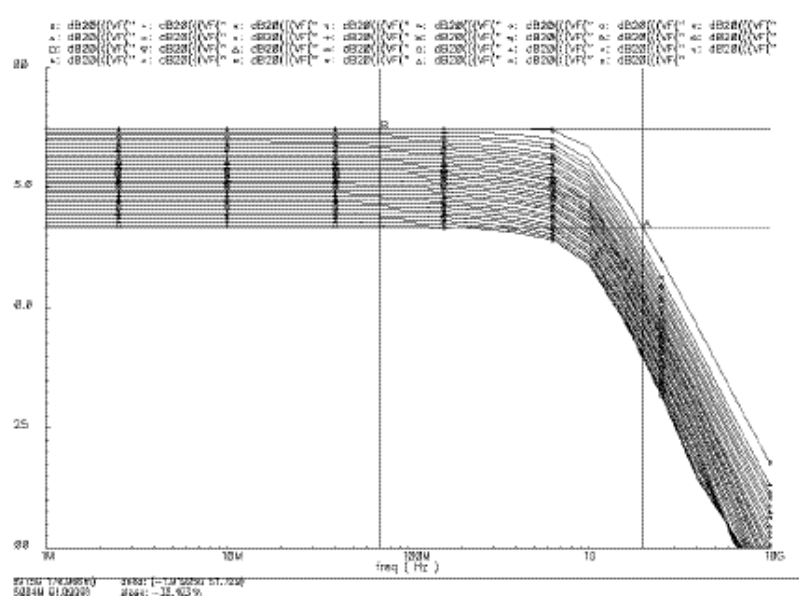

A 71 MHz CMOS Programmable Gain Amplifier†

Uses 3 ac-coupled stages.

First stage (0-20dB, common source for matching and NF):

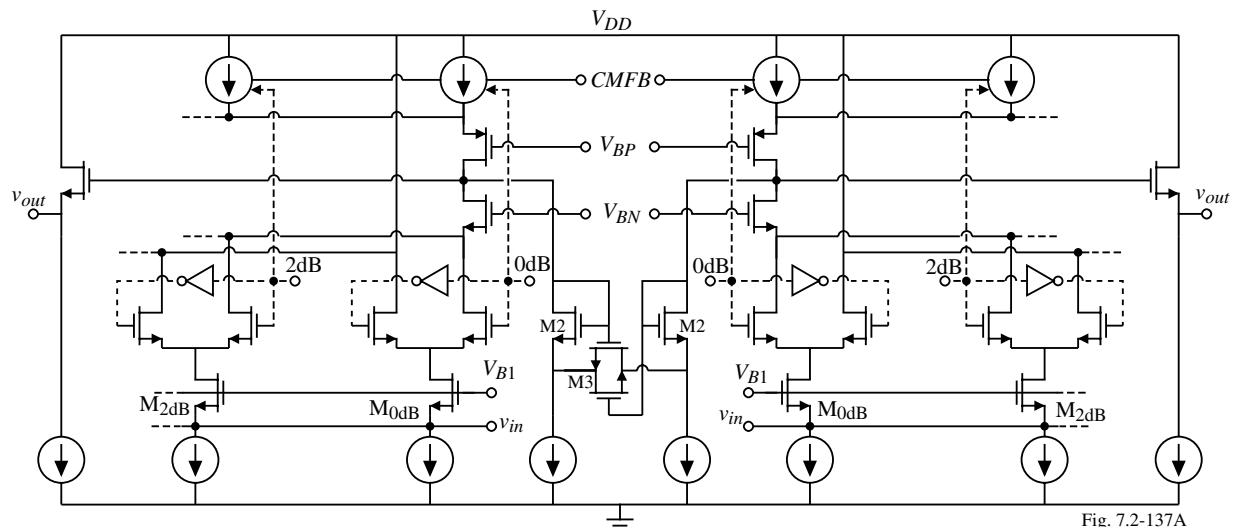


Fig. 7.2-137A

$R_{in} = 330\Omega$ to match source driving requirement

All current sinks are identical for the differential switches.

Dominant pole at 150MHz.

† P. Orsatti, F. Piazza, and Q. Huang, "A 71 MHz CMOS IF-Bandpass Strip for GSM, *IEEE J. Solid-State Circuits*, vol. 35, No. 1, Jan. 2000, pp. 104-108.

A 71 MHz PGA – Continued

Second stage (-10dB to 20dB):

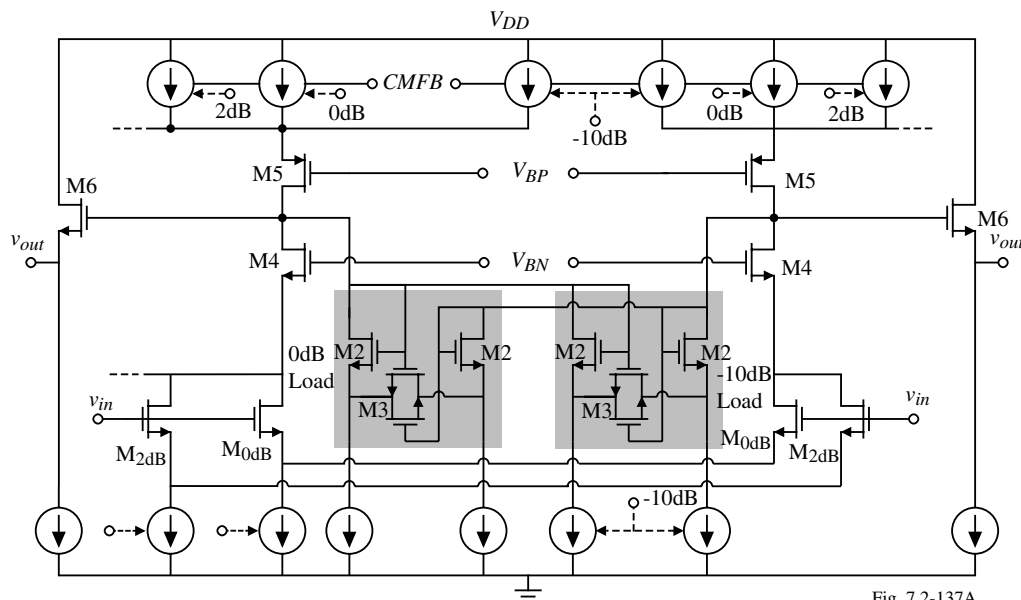


Fig. 7.2-137A

Dominant pole is also at 150MHz

For $V_{DD} = 2.5V$, at 60dB gain, the total current is 2.6mA

$IIP_3 \approx +1dBm$

Parallel Path Op Amps

This type of op amp combines a high-gain, low-frequency path with a low-gain, high-frequency path.

 


Fig. 7.2-14

Comments:

- Op amp will be conditionally stable
- Compensation will be challenging

Multipath Nested Miller Compensation[†]

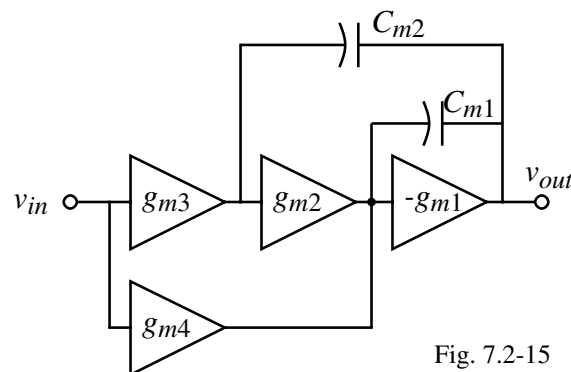


Fig. 7.2-15

Comments:

- All Miller capacitances must be around inverting stages
- Ensure that the RHP zeros generated by the Miller compensation are canceled
- Avoid pole-zero doublets which can introduce a slow time constant

[†] R.G.H. Eschauzier and J.H.Huijsing, *Frequency Compensation Techniques for Low-Power Operational Amplifiers*, Kluwer Academic publishers, 1995, Chapter 6.

Illustration of Hybrid Nested Miller Compensation[†]

(Note that this example is not multipath.)

Compensating Results:

- 1) C_{m1} pushes p_4 to higher frequencies and p_3 down to lower frequencies
- 2) C_{m2} pushes p_2 to higher frequencies and p_1 down to lower frequencies
- 3) C_{m3} pushes p_3 to higher frequencies (feedback path) & pulls p_1 further to lower frequencies

Equations:

$$GB \approx g_{m1}/C_{m3} \quad p_2 \approx g_{m2}/C_{m3} \quad p_3 \approx g_{m3}C_{m3} / (C_{m1}C_{m2}) \quad p_4 \approx g_{m4}/C_L$$

Design:

$$GB < p_2, p_3, p_4$$

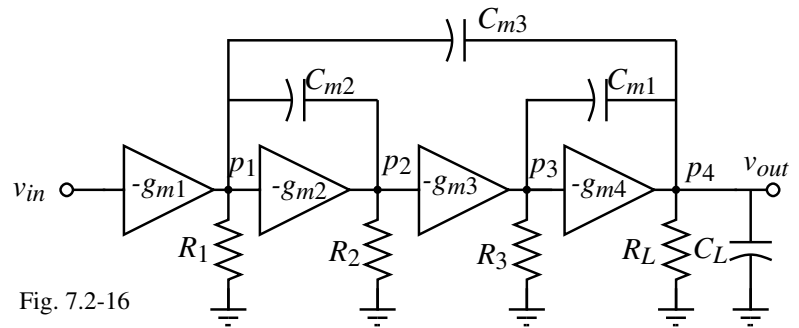


Fig. 7.2-16

[†]R.G. H. Eschauzier *et. al.*, "A Programmable 1.5V CMOS Class-AB Operational Amplifier with Hybrid Nested Miller Compensation for 120dB Gain and 6MHz UGT," *IEEE J. of Solid State Circuits*, vol. 29, No. 12, pp. 1497-1504, Dec. 1994.

Illustration of the Hybrid Nested Miller Compensation Technique

 


Fig. 7.2-17

SUMMARY

- Normal op amps limited by g_m/C
- Typical limit for CMOS op amp is $GB \approx 50\text{MHz}$
- Other approaches to high frequency CMOS op amps:
 - Current amplifiers (Transimpedance amplifiers)
 - Switched amplifier (simplifies the circuit \Rightarrow reduce capacitances)
 - Parallel path op amps (compensation becomes more complex)
- What does the future hold?
 - Reduction of channel lengths mean:
 - * Reduced capacitances \Rightarrow Higher GB 's
 - * Higher transconductances (larger values of K') \Rightarrow Higher GB 's
 - * Increased channel conductance \Rightarrow Lower gains (more stages required)
 - * Reduction of power supply \Rightarrow Increased capacitances

In other words, there should be some improvement in op amp GB 's but it won't be inversely proportional to the decrease in channel length. I.e. maybe GB 's $\approx 100\text{MHz}$ for $0.2\mu\text{m}$ CMOS.