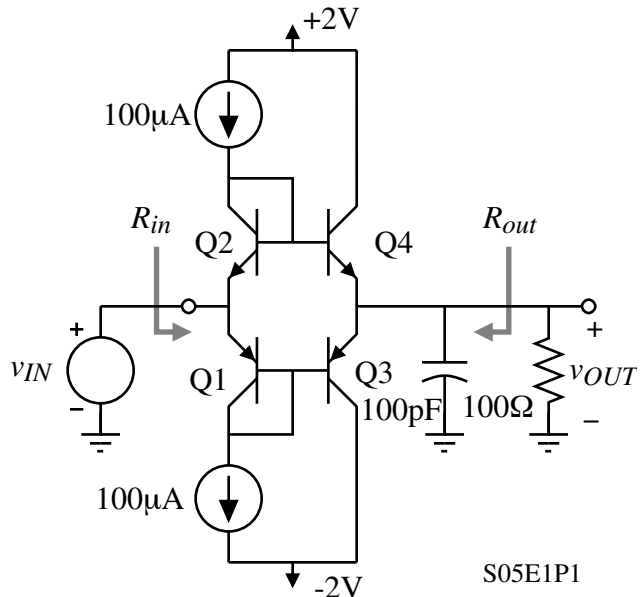


EXAMINATION NO. 1
(Average score = 56.2/100)

Problem 1 - (25 points)

An emitter follower, push-pull output stage is shown. Assume that $\beta_N = \beta_P = 100$, $V_t = 25\text{mV}$, and $I_s = 10\text{fA}$.

- a.) If the emitter areas of Q1 and Q2 are $10\mu\text{m}^2$, find the emitter area of Q3 and Q4 so that the collector current in Q3 and Q4 is 1mA when $v_{IN} = v_{OUT} = 0$.
- b.) What is the \pm peak output voltage of this amplifier? Assume the $100\mu\text{A}$ sources can have a minimum voltage across them of 0.2V.
- c.) What is the \pm slew rate of this amplifier in $\text{V}/\mu\text{s}$?
- d.) What is the small-signal input and output resistance of this amplifier when $v_{IN} = v_{OUT} = 0$? (Do not include the load resistance in the output resistance.)



Solution

$$a.) V_{EB1} + V_{BE2} = V_{BE4} + V_{EB3} \rightarrow \frac{I_{C1}^2}{I_{s1}I_{s2}} = \frac{I_{C3}^2}{I_{s3}I_{s4}} \rightarrow I_{s3} = I_{s4} = \frac{I_{C3}I_{s1}}{I_{C1}} = 10I_{s1}$$

$$\therefore A_{E3} = A_{E4} = 10A_{E1} = \underline{\underline{100\mu\text{m}^2}}$$

$$b.) V_{peak} = \pm(100\mu\text{A})(1+\beta_o)R_L = \pm 100\mu\text{A} \cdot 101 \cdot 100\Omega = \pm 1.01\text{V}$$

Check to make sure this answer is okay. $V_{BE4} = V_t \ln\left(\frac{10.1\text{mA}}{10\text{fA}}\right) = 0.691\text{V}$

$$\therefore \text{Maximum swing is } 2 - 0.691 - 0.2 = 1.109\text{V so } V_{peak} = \underline{\underline{\pm 1.01\text{V}}}$$

$$c.) \pm SR = \left(\frac{10.1\text{mA}}{100\text{pF}}\right) = \underline{\underline{101\text{V}/\mu\text{s}}}$$


d.) Small signal model:

$$V_t = \frac{I_t}{2} \left(\frac{1}{g_{m2}} + r_{\pi 4} \right) + R_L I_t (1 + \beta_o)$$

$$g_{m2} = \frac{100\mu\text{A}}{25\text{mV}} = \frac{1}{250\Omega}$$


$$g_{m4} = \frac{1\text{mA}}{25\text{mV}} = \frac{1}{25\Omega} \quad R_{in} = 0.5[250 + 25(101)] + 101(100) = \underline{\underline{11.487\text{k}\Omega}}$$

$$R_{out} = 0.5 \left[\frac{1}{g_{m4}} + \frac{1}{1 + \beta_o} \right] = 0.5[25 + (250/101)] = \underline{\underline{13.37\Omega}}$$

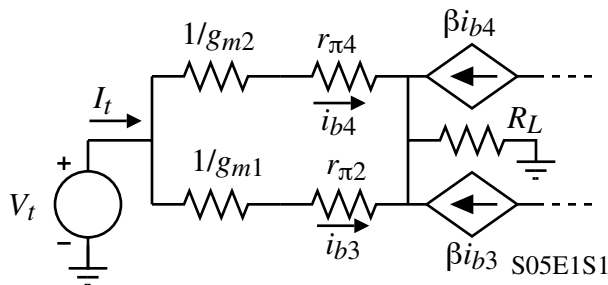

Problem 2 - (25 points)


Find the value for the small-signal output resistance R_{out} ignoring R_L and the value of the small-signal input resistance for the amplifier shown. Let the dc currents through M1 and M2 be $500\mu\text{A}$, $W_1/L_1 = 100\mu\text{m}/1\mu\text{m}$ and $W_2/L_2 = 200\mu\text{m}/1\mu\text{m}$. Assume the parameters of the NMOS transistors are $K_N' = 110\text{V}/\mu\text{A}^2$, $V_{TN} = 0.7\text{V}$, and for the PMOS transistors are $K_P' = 50\text{V}/\mu\text{A}^2$, $V_{TP} = -0.7\text{V}$. Ignore r_{ds1} and r_{ds2} .

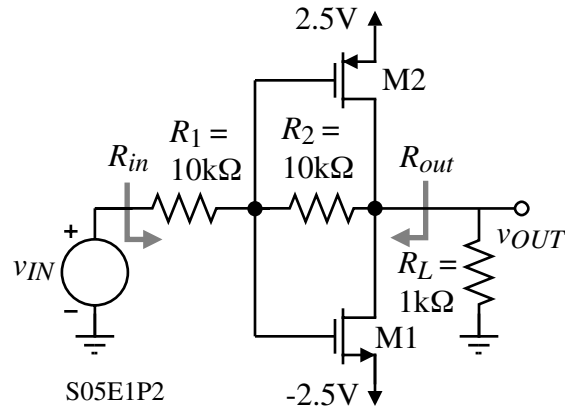Solution

Calculating the small-signal parameters gives,

$$g_{m1} = \sqrt{2 \cdot 110 \cdot 500 \cdot 100} = 3.316\text{mS}, \quad g_{m2} = \sqrt{2 \cdot 50 \cdot 500 \cdot 200} = 3.162\text{mS}$$

The small-signal model is given as,

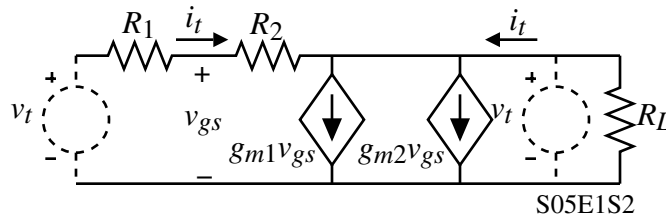

For R_{out} , sum the currents at the output (with the LH $v_t = 0$) to get,

$$i_t = v_t \left[\frac{1}{R_1 + R_2} + \frac{g_{m1} + g_{m2}}{2} \right] \rightarrow R_{out} = \frac{v_t}{i_t} = \left[\frac{1}{R_1 + R_2} + \frac{g_{m1} + g_{m2}}{2} \right]^{-1} = \underline{\underline{308\Omega}}$$

For R_{in} , remove the RH v_t and write a loop equation at the input to get,

$$v_t = i_t(R_1 + R_2) + (i_t - g_{m1}v_{gs} - g_{m2}v_{gs})R_L = i_t(R_1 + R_2 + R_L) - (g_{m1} + g_{m2})v_{gs}$$


But $v_{gs} = v_t - i_t R_1$ which gives,

$$R_{in} = \frac{v_t}{i_t} = \frac{R_1 + R_2 + R_L + (g_{m1} + g_{m2})R_L R_1}{1 + (g_{m1} + g_{m2})R_L} = \frac{201\text{k}\Omega + (3.316 + 3.162)(1)(100\text{k}\Omega)}{1 + (3.316 + 3.162)(1)}$$

$$R_{in} = \underline{\underline{113.5\text{k}\Omega}}$$

Problem 3 - (25 points)

Find the midband voltage gain and the -3dB frequency in Hertz for the circuit shown.

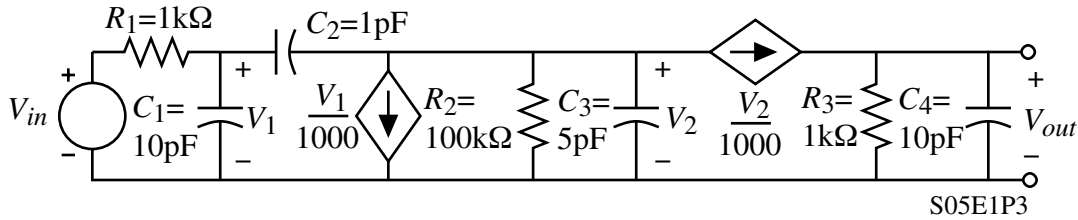Solution

The midband voltage gain can be expressed as,

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_2} \frac{V_2}{V_1} \frac{V_1}{V_{in}} = (1) \left(\frac{-R_2}{R_2 + 1000} \right) (1) = \underline{\underline{-0.99V/V}}$$

Finding the open-circuit, time constants:

$$R_{C1O}: \quad R_{C1O} = R_1 = 1\text{k}\Omega$$

$$\rightarrow R_{C1O}C_1 = 10\text{ns}$$

$$R_{C2O}:$$

$$v_t = R_1 i_t + R_2 \left[i_t + \frac{V_1}{1000} + \frac{V_2}{1000} \right]$$

$$\text{But } v_t = V_1 - V_2 \text{ and } V_1 = R_1 i_t,$$

$$\therefore v_t = R_1 i_t + R_2 i_t + \frac{2R_1 R_2 i_t}{1000} - \frac{R_2 v_t}{1000}$$

$$R_{C2O} = \frac{v_t}{i_t} = \frac{R_1 + R_2 + 0.002R_1 R_2}{1 + 0.001R_2}$$

$$= \frac{1\text{k}\Omega + 100\text{k}\Omega + 200\text{k}\Omega}{1 + 100} = 2.98\text{k}\Omega$$

$$\rightarrow R_{C2O}C_2 = 2.98\text{ns}$$

$$R_{C3O}: \quad R_{C3O} = R_2 \parallel 1\text{k}\Omega = 0.99\text{k}\Omega$$


$$\rightarrow R_{C3O}C_3 = 4.95\text{ns}$$

$$R_{C4O}: \quad R_{C4O} = R_3 = 1\text{k}\Omega$$

$$\rightarrow R_{C4O}C_4 = 10\text{ns}$$


$$\Sigma T_{oc} = (10 + 2.98 + 4.95 + 10)\text{ns} = 27.93\text{ns}$$

$$\omega_{-3\text{dB}} \approx \frac{1}{\Sigma T_{oc}} = 35.8 \times 10^6 \quad \rightarrow \quad f_{-3\text{dB}} = \underline{\underline{5.698 \text{ MHz}}}$$

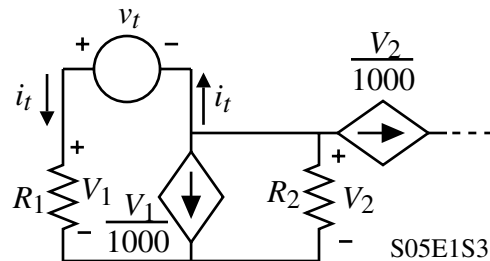

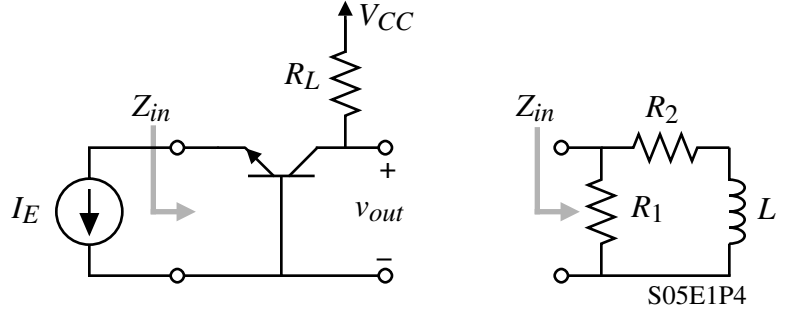Problem 4 - (25 points)

On page 514 of the text, the statement is made that “the common base input impedance is low at low frequencies and becomes inductive at high frequencies”... Find the small-signal input impedance to the common base amplifier and express the values of the equivalent circuit, R_1 , R_2 , and



L in terms of the parameters of the BJT small signal model (r_b , r_π , C_π , and β_o). Ignore r_o and assume that $R_1 > R_2$.

Solution


Use the following small signal model for this problem.

$$I_t + \frac{V_\pi}{Z_\pi} + g_m V_\pi = 0 \rightarrow I_t = -V_\pi \left(g_m + \frac{1}{Z_\pi} \right)$$

and

$$V_t = -V_\pi - \frac{V_\pi}{Z_\pi} r_b \rightarrow V_t = -V_\pi \left(1 + \frac{r_b}{Z_\pi} \right)$$
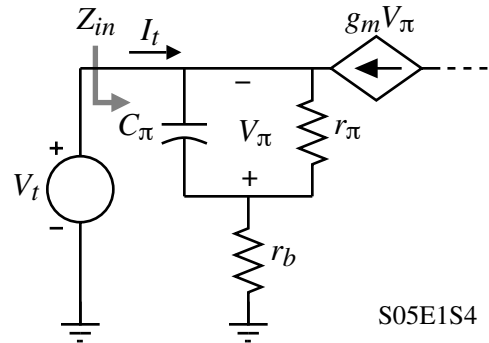
$$\therefore Z_{in} = \frac{V_t}{I_t} = \left(\frac{Z_\pi + r_b}{1 + g_m Z_\pi} \right) \text{ where } Z_\pi = \frac{r_\pi}{sC_\pi r_\pi + 1}$$



Now,

$$\begin{aligned} Z_{in} &= \frac{r_b + \frac{r_\pi}{sC_\pi r_\pi + 1}}{1 + \frac{g_m r_\pi}{sC_\pi r_\pi + 1}} = \frac{r_b(1 + sC_\pi r_\pi) + r_\pi}{1 + g_m r_\pi + sC_\pi r_\pi} = \frac{(r_b + r_\pi) + sC_\pi r_\pi r_b}{1 + \beta_o + sC_\pi r_\pi} \\ &= \frac{\frac{(r_b + r_\pi)}{\beta_o} + \frac{sC_\pi r_\pi r_b}{\beta_o}}{1 + \frac{1}{\beta_o} + \frac{sC_\pi r_\pi}{\beta_o}} = \frac{\left(\frac{(r_b + r_\pi)}{\beta_o} + \frac{sC_\pi r_\pi r_b}{\beta_o} \right) r_b}{r_b + \frac{r_b}{\beta_o} + \frac{sC_\pi r_\pi r_b}{\beta_o}} \approx \frac{\left(\frac{(r_b + r_\pi)}{\beta_o} + \frac{sC_\pi r_\pi r_b}{\beta_o} \right) r_b}{r_b + \frac{sC_\pi r_\pi r_b}{\beta_o}} \\ Z_{in} &= \frac{R_1(R_2 + sL)}{R_1 + R_2 + sL} \approx \frac{R_1(R_2 + sL)}{R_1 + sL} \text{ if } R_1 > R_2 \end{aligned}$$

Equating the two expressions for Z_{in} gives,

$$\boxed{R_1 = r_b, R_2 = \frac{(r_b + r_\pi)}{\beta_o}, \text{ and } L = \frac{C_\pi r_\pi r_b}{\beta_o}}$$

Design the circuit for $V_{OL} = 0.1V$, $L = 0.1\mu m$ in $0.1\mu m$ technology.


* Resistive Load inverter:

$E_{CL} = 0.6V$
 $V_{OH} = 1.2V$
 $V_{OL} = 0.1V$
 $C_{ox} = 1.6 \mu F/cm^2$
 $\mu_n = 270 \frac{cm^2}{V \cdot s}$
 $V_{th} = 8 \times 10^6$

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{W_N}{L_N} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{OL}}{E_C L}\right)} \left[\frac{2(V_{OH} - V_T)V_{OL} - V_{OL}^2}{(V_{OH} - V_T)V_{OL} - \frac{V_{OL}^2}{2}} \right]$$

$$\frac{1.2 - 0.1}{10k} = \frac{W_N}{0.1} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.1}{0.6}\right)} \left[\frac{2(1.2 - 0.4)0.1 - 0.1^2}{2} \right]$$

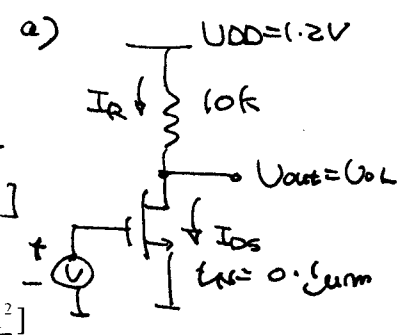$\therefore W_N = 0.2 \mu m$ $W = 0.39 \mu m$ ✓




* Saturated Enhancement Load inverter (ignoring body-effect):

$I_D (lin) = I_D (sat)$

$$\frac{W_I}{L_I} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{out}}{E_{CN} L_I}\right)} \left[(V_{in} - V_{TI})V_{out} - \frac{V_{out}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{out} - V_{TL})^2}{(V_{DD} - V_{out} - V_{TL}) + E_{CN} L_L}$$

$$\frac{W_I}{0.1} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.1}{0.6}\right)} \left[\frac{2(1.2 - 0.4)0.1 - 0.1^2}{2} \right] = \frac{0.1(10^{-4})(8)(1.6)(1.2 - 0.1 - 0.4)^2}{(1.2 - 0.1 - 0.4) + 0.6}$$

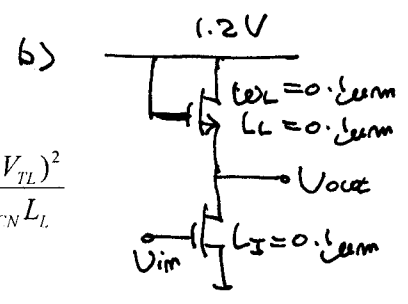$\therefore W_N = 0.1 \mu m$ $W = 0.174 \mu m$ ✓




* Linear Enhancement Load inverter (ignoring body-effect): Load is saturated

$$\frac{W_I}{L_I} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{out}}{E_{CN} L_I}\right)} \left[(V_{in} - V_{TI})V_{out} - \frac{V_{out}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{out} - V_{TL})^2}{(V_{DD} - V_{out} - V_{TL}) + E_{CN} L_L}$$

$$\frac{W_I}{0.1} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.1}{0.6}\right)} \left[\frac{2(1.2 - 0.4)0.1 - 0.1^2}{2} \right] = \frac{0.1(10^{-4})(8)(1.6)(1.6 - 0.1 - 0.4)^2}{(1.6 - 0.1 - 0.4) + 0.6}$$

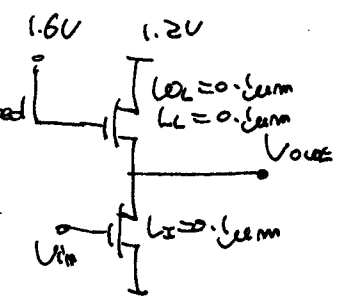$\therefore W_N = 0.6 \mu m$ $W = 0.328 \mu m$ ✓



The linear enhancement load inverter requires the largest pull-down device since it has the strongest pull up device. The resistive load inverter is next and the saturated enhancement load requires the smallest pull-down device.

Problem 3 - P4.10

We will illustrate the process and estimate the solutions for this problem.

We already know that $V_{OH} = 1.2V$ and $V_{OL} = 0V$. For V_S use: