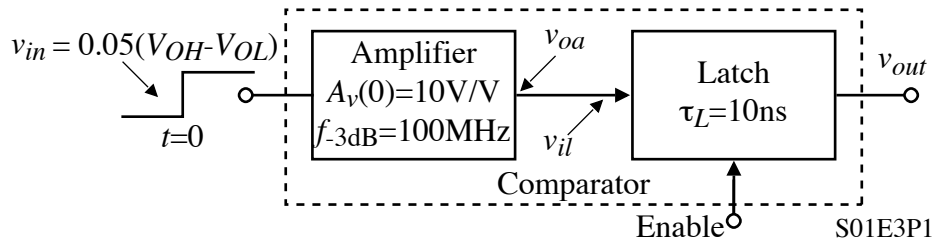


**FINAL EXAMINATION - SOLUTIONS**

(Average score = 89/100)

**Problem 1 - (20 points - This problem is required)**

A comparator consists of an amplifier cascaded with a latch as shown below. The amplifier has a voltage gain of 10V/V and  $f_{-3dB} = 100\text{MHz}$  and the latch has a time constant of 10ns. The maximum and minimum voltage swings of the amplifier and latch are  $V_{OH}$  and  $V_{OL}$ . When should the latch be enabled after the application of a step input to the amplifier of  $0.05(V_{OH}-V_{OL})$  to get minimum overall propagation time delay? What is the value of the minimum propagation time delay? It may be useful to recall that the propagation time delay of the latch is given as  $t_p = \tau_L \ln\left(\frac{V_{OH}-V_{OL}}{2v_{il}}\right)$  where  $v_{il}$  is the latch input ( $\Delta V_i$  of the text).



Solution

The solution is based on the figure shown.

We note that,

$$v_{oa}(t) = 10[1 - e^{-\omega_{-3dB}t}]0.05(V_{OH}-V_{OL}).$$

If we define the input voltage to the latch as,

$$v_{il} = x \cdot (V_{OH}-V_{OL})$$

then we can solve for  $t_1$  and  $t_2$  as follows:

$$x \cdot (V_{OH}-V_{OL}) = 10[1 - e^{-\omega_{-3dB}t_1}]0.05(V_{OH}-V_{OL}) \rightarrow x = 0.5[1 - e^{-\omega_{-3dB}t_1}]$$

This gives,

$$t_1 = \frac{1}{\omega_{-3dB}} \ln\left(\frac{1}{1-2x}\right)$$


From the propagation time delay of the latch we get,

$$t_2 = \tau_L \ln\left(\frac{V_{OH}-V_{OL}}{2v_{il}}\right) = \tau_L \ln\left(\frac{1}{2x}\right)$$

$$\therefore t_p = t_1 + t_2 = \frac{1}{\omega_{-3dB}} \ln\left(\frac{1}{1-2x}\right) + \tau_L \ln\left(\frac{1}{2x}\right) \rightarrow \frac{dt_p}{dx} = 0 \text{ gives } x = \frac{\pi}{1+2\pi} = 0.4313$$


$$t_1 = \frac{10\text{ns}}{2\pi} \ln(1+2\pi) = 1.592\text{ns} \cdot 1.9856 = \underline{3.16\text{ns}} \text{ and } t_2 = 10\text{ns} \ln\left(\frac{1+2\pi}{2\pi}\right) = 1.477\text{ns}$$

$$\therefore t_p = t_1 + t_2 = 3.16\text{ns} + 1.477\text{ns} = \underline{4.637\text{ns}}$$

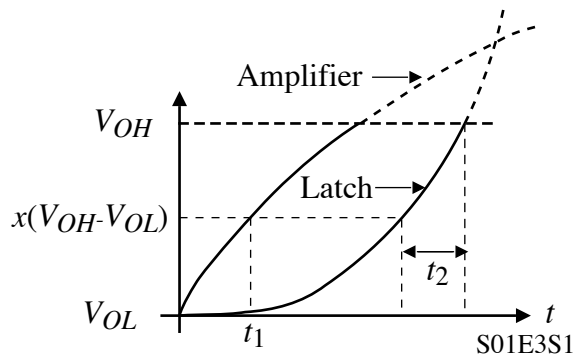

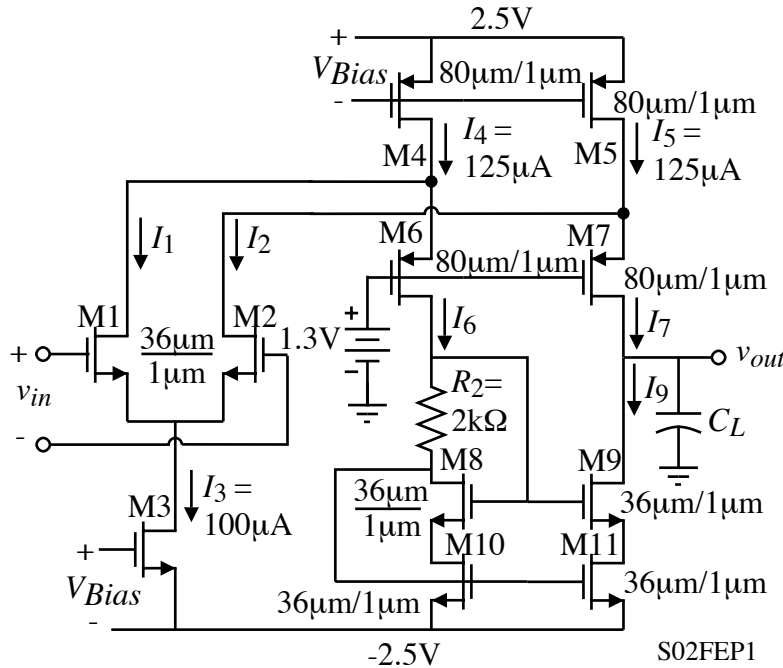**Problem 2 - (20 points - This problem is required)**

If the folded-cascode op amp shown having a small-signal voltage gain of 7464V/V is used as a comparator, find the dominant pole if  $C_L = 5\text{pF}$ . If the input step is 10mV, determine whether the response is linear or slewing and find the propagation delay time. Assume the parameters of the NMOS transistors are  $K_N' = 110\text{V}/\mu\text{A}^2$ ,  $V_{TN} = 0.7\text{V}$ ,  $\lambda_N = 0.04\text{V}^{-1}$  and for the PMOS transistors are  $K_P' = 50\text{V}/\mu\text{A}^2$ ,  $V_{TP} = -0.7\text{V}$ ,  $\lambda_P = 0.05\text{V}^{-1}$ .



Solution

$V_{OH}$  and  $V_{OL}$  can be found from many approaches. The easiest is simply to assume that  $V_{OH}$  and  $V_{OL}$  are 2.5V and -2.5V, respectively. However, no matter what the input, the values of  $V_{OH}$  and  $V_{OL}$  will be in the following range,

$$(V_{DD} - 2V_{ON}) < V_{OH} < V_{DD} \quad \text{and} \quad V_{DD} < V_{OH} < (V_{SS} + 2V_{ON})$$

The reasoning is as follows, suppose  $V_{in} > 0$ . This gives  $I_1 > I_2$  which gives  $I_6 < I_7$  which gives  $I_9 < I_7$ .  $V_{out}$  will increase until  $I_7$  equals  $I_9$ . The only way this can happen is for M5 and M7 to leave saturation. The same reasoning holds for  $V_{in} < 0$ .

Therefore assuming that  $V_{OH}$  and  $V_{OL}$  are 2.5V and -2.5V, respectively, we get

$$V_{in}(\text{min}) = \frac{5\text{V}}{7464} = 0.67\text{mV} \quad \rightarrow \quad k = \frac{10\text{mV}}{0.67\text{mV}} = 14.93$$

**Problem 2 – Continued**

The folded-cascode op amp as a comparator can be modeled by a single dominant pole. This pole is found as,

$$p_1 = \frac{1}{R_{out}C_L} \text{ where } R_{out} \approx g_{m9}r_{ds9}r_{ds11} \parallel [g_{m7}r_{ds7}(r_{ds2} \parallel r_{ds5})]$$

$$g_{m9} = \sqrt{2 \cdot 75 \cdot 110 \cdot 36} = 771 \mu\text{S}, \quad g_{ds9} = g_{ds11} = 75 \times 10^{-6} \cdot 0.04 = 3 \mu\text{S}, \quad g_{ds2} = 50 \times 10^{-6} (0.04) = 2 \mu\text{S}$$

$$g_{m7} = \sqrt{2 \cdot 75 \cdot 50 \cdot 80} = 775 \mu\text{S}, \quad g_{ds5} = 125 \times 10^{-6} \cdot 0.05 = 6.25 \mu\text{S}, \quad g_{ds7} = 50 \times 10^{-6} (0.05) = 3.75 \mu\text{S}$$

$$g_{m9}r_{ds9}r_{ds11} = (771 \mu\text{S}) \left( \frac{1}{3 \mu\text{S}} \right) \left( \frac{1}{3 \mu\text{S}} \right) = 85.67 \text{M}\Omega$$

$$g_{m7}r_{ds7}(r_{ds2} \parallel r_{ds5}) \approx (775 \mu\text{S}) \left( \frac{1}{3.75 \mu\text{S}} \right) \left( \frac{1}{2 \mu\text{S}} \parallel \frac{1}{6.25 \mu\text{S}} \right) = 25.05 \text{M}\Omega,$$

$$R_{out} \approx 85.67 \text{M}\Omega \parallel 25.05 \text{M}\Omega = 19.4 \text{M}\Omega$$

The dominant pole is found as,  $p_1 = \frac{1}{R_{out}C_L} = \frac{1}{19.4 \times 10^6 \text{pF}} = 10,318 \text{ rps}$

The time constant is  $\tau_1 = 96.9 \mu\text{s}$ .

For a dominant pole system, the step response is,  $v_{out}(t) = A_{vd}(1 - e^{-t/\tau_1})V_{in}$

The slope is the largest at  $t = 0$ . Evaluating this slope gives,

$$\frac{dv_{out}}{dt} = \frac{A_{vd}}{\tau_1} e^{-t/\tau_1} V_{in} \text{ For } t = 0, \text{ the slope is } \frac{A_{vd}}{\tau_1} V_{in} = \frac{7464}{96.9 \mu\text{s}} (10 \text{mV}) = 0.77 \text{V}/\mu\text{s}$$

The slew rate of this op amp/comparator is  $SR = \frac{I_3}{C_L} = \frac{100 \mu\text{A}}{5 \text{pF}} = 20 \text{V}/\mu\text{s}$

Therefore, the comparator does not slew and its propagation delay time is found from the linear response as,

$$t_P = \tau_1 \ln \left( \frac{2k}{2k-1} \right) = 96.9 \mu\text{s} \cdot \ln \left( \frac{2 \cdot 14.93}{2 \cdot 14.93 - 1} \right) = (96.9 \mu\text{s})(0.0341) = \underline{\underline{3.3 \mu\text{s}}}$$

**Problem 3 – (20 points – This problem is optional)**


An source follower, push-pull output stage is shown. Assume the parameters of the NMOS transistors are  $K_N' = 110 \text{V}/\mu\text{A}^2$ ,  $V_{TN} = 0.7 \text{V}$ ,  $\lambda_N = 0.04 \text{V}^{-1}$  and for the PMOS transistors are  $K_P' = 50 \text{V}/\mu\text{A}^2$ ,  $V_{TP} = -0.7 \text{V}$ ,  $\lambda_P = 0.05 \text{V}^{-1}$ .

a.) If  $W_1/L_1 = W_2/L_2 = 10$ , find the  $W_3/L_3$  and  $W_4/L_4$  so that the drain current in M3 and M4 is 1mA when  $v_{IN} = v_{OUT} = 0$ .

b.) What is the  $\pm$ peak output voltage of this amplifier? Assume the  $100\mu\text{A}$  sources can have a minimum voltage across them of 0.2V.

c.) What is the  $\pm$ slew rate of this amplifier in  $\text{V}/\mu\text{s}$ ?

d.) What is the small-signal input and output resistance of this amplifier when  $v_{IN} = v_{OUT} = 0$ ? (Do not include the load resistance in the output resistance.)

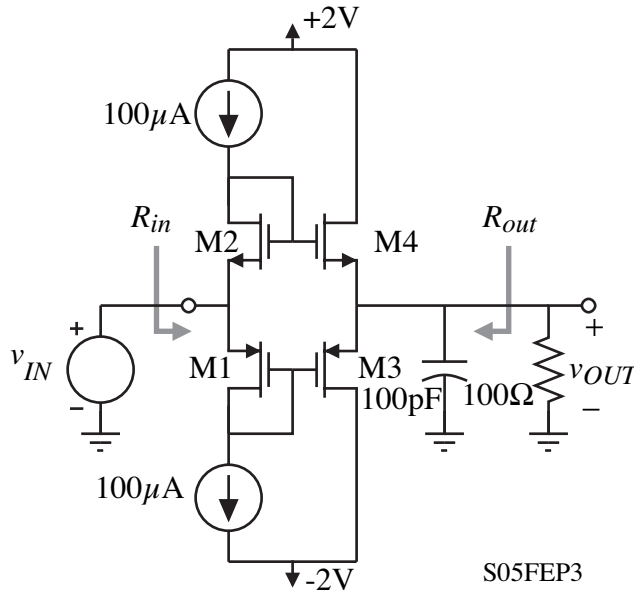**Solution**

a.) With  $v_{IN} = v_{OUT} = 0$ , the  $W/L$  ratios of M3 and M4 are given by the current ratios. Thus,  $W_3/L_3 = W_4/L_4 = \underline{100}$ .

b.) The current limit due to 1mA is  $\pm 1 \text{V}$ . Check to see if voltage limit is less.

$$V_{GS4}(1\text{mA}) = \sqrt{\frac{2 \cdot 1\text{mA}}{110 \cdot 100}} + 0.7 = 0.426 + 0.7 = 1.126 \text{V}$$

$$V_{out}(\text{max}) = 2 - 0.2 - 1.126 = \underline{0.674 \text{V}}$$

$$V_{GS3}(1\text{mA}) = \sqrt{\frac{2 \cdot 1\text{mA}}{50 \cdot 100}} + 0.7 = 0.632 + 0.7 = 1.332 \text{V}$$

$$V_{out}(\text{min}) = 2 - 0.2 - 1.332 = \underline{0.467 \text{V}}$$

c.) The slew rate is

$$\pm SR = \frac{1\text{mA}}{100\text{pF}} = \underline{10 \text{V}/\mu\text{s}}$$

$$\text{d.) } R_{in} = \infty. \quad R_{out} = \frac{1}{g_{m3} + g_{m4}} \quad g_{m4} = \sqrt{2 \cdot 110 \cdot 1000 \cdot 100} \mu\text{S} = 4.69 \text{mS}$$

$$g_{m3} = \sqrt{2 \cdot 50 \cdot 1000 \cdot 100} \mu\text{S} = 3.162 \text{mS} \quad R_{out} = \frac{1000}{3.162 + 4.69} = \underline{127 \Omega}$$



**Problem 4 - (20 points - This problem is optional)**

The simplified schematic of a feedback amplifier is shown. Use the method of feedback analysis to find  $v_2/v_1$ ,  $R_{in} = v_1/i_1$ , and  $R_{out} = v_2/i_2$ . Assume that all transistors are matched and that  $\beta = 100$ ,  $r_\pi = 5k\Omega$  and  $r_o = \infty$ .

Solution

Open-loop, quasi-ac model:

Small-signal, open-loop model:

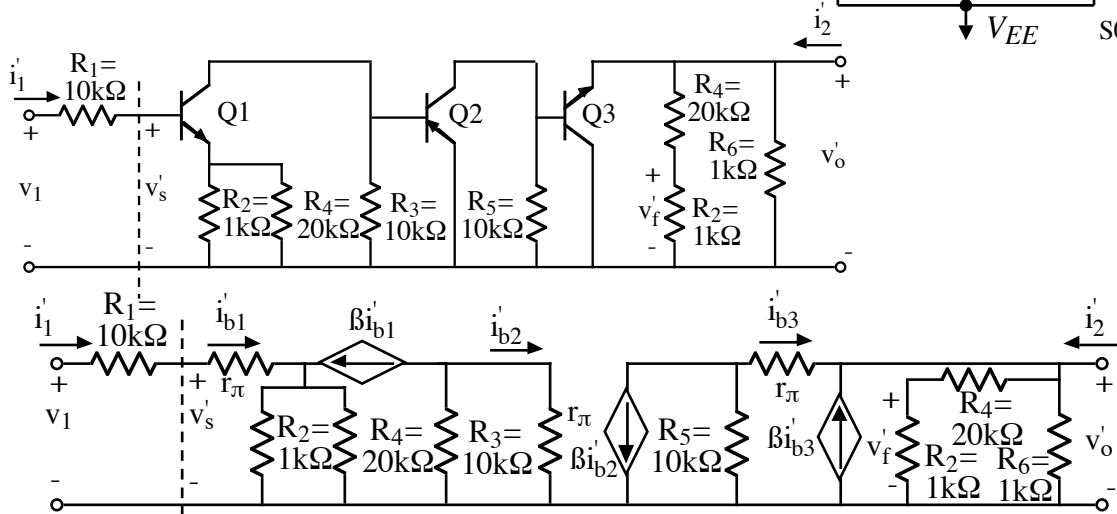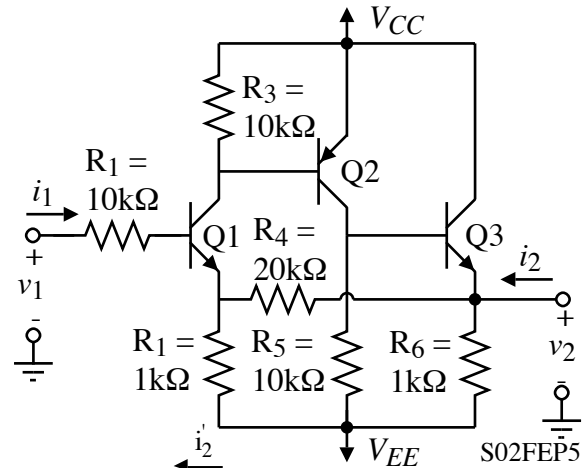

$$R_i = \frac{v_s'}{i_{b1}'} = r_\pi + (1+\beta)(R_2 \parallel R_4) = 5k\Omega + (101)(1k\Omega \parallel 20k\Omega) = 101.19k\Omega$$

$$a = \frac{v_o'}{v_s'} = \left(\frac{v_o'}{i_{b3}'}\right) \left(\frac{i_{b3}'}{i_{b2}'}\right) \left(\frac{i_{b2}'}{i_{b1}'}\right) \left(\frac{i_{b1}'}{v_s'}\right)$$

$$= (1+\beta)[R_6 \parallel (R_2+R_4)] \left(\frac{-\beta R_5}{R_5+r_\pi+(1+\beta)[R_6 \parallel (R_2+R_4)]}\right) \left(\frac{-\beta R_3}{R_3+r_\pi}\right) \left(\frac{1}{R_i}\right)$$

$$= [(101)(954.55)](-8.976)(-66.67)(1/101.19k\Omega) = 570.16 \text{ V/V}$$

$$f = \frac{R_2}{R_2+R_4} = \frac{1}{21} = 0.0476 \quad \text{and} \quad R_o = \frac{v_o'}{i_2'} = R_6 \parallel (R_2+R_4) \parallel \left(\frac{r_\pi+R_5}{1+\beta}\right) = 128.5\Omega$$

Closed-loop quantities are:

$$A_{vf} = \frac{v_o}{v_s} = \frac{a}{1+af} = \frac{570.16}{1+27.15} = 20.25, \quad R_{if} = (1+af)R_i = 2.848M\Omega$$

$$\therefore \boxed{R_{out} = R_{of} = \frac{R_o}{1+A_v\beta_f} = \frac{128.5\Omega}{28.15} = 4.565\Omega}$$


$$\boxed{R_{in} = R_1+R_{if} = 2.858M\Omega}$$

and

$$\boxed{\frac{v_2}{v_1} = A_{vf} \frac{R_{if}}{R_1+R_{if}} = 20.18 \text{ V/V}}$$

**Problem 5 - (20 points - This problem is optional)**

A two-stage, BiCMOS op amp is shown. For the PMOS transistors, the model parameters are  $K_P' = 50 \mu\text{A}/\text{V}^2$ ,  $V_{TP} = -0.7\text{V}$  and  $\lambda_P = 0.05\text{V}^{-1}$ . For the NPN BJTs, the model parameters are  $\beta_F = 100$ ,  $V_{CE}(\text{sat}) = 0.2\text{V}$ ,  $V_A = 25\text{V}$ ,  $V_t = 26\text{mV}$ ,  $I_s = 10\text{fA}$  and  $n=1$ . (a.) Identify which input is positive and which input is negative. (b.) Find the numerical values of differential voltage gain,  $A_v(0)$ ,  $GB$  (in Hertz), the slew rate,  $SR$ , and the location of the RHP zero. (c.) Find the numerical value of the maximum and minimum input common mode voltages.

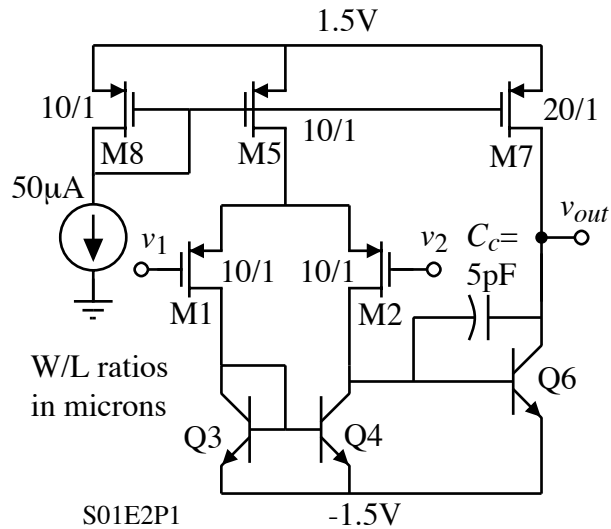**Solution**

(a.) The plus and minus signs on the schematic show which input is positive and negative.

(b.) The differential voltage gain,  $A_v(0)$ , is given as

$$A_v(0) = \frac{g_{m1}}{g_{ds2} + g_{o4} + g_{\pi6}} \cdot \frac{g_{m6}}{g_{ds7} + g_{o6}} \quad g_{m1} = g_{m2} = \sqrt{2 \cdot 50 \cdot 25 \cdot 10} = 158.1 \mu\text{S}$$

$$r_{ds2} = \frac{1}{\lambda_P I_D} = \frac{20}{25 \mu\text{A}} = 0.8 \text{M}\Omega, \quad r_{o4} = \frac{V_A}{I_C} = \frac{25\text{V}}{25 \mu\text{A}} = 1 \text{M}\Omega, \quad g_{m6} = \frac{I_C}{V_t} = \frac{100 \mu\text{A}}{26 \text{mV}} = 3846 \mu\text{S}$$

$$r_{\pi6} = \frac{\beta_F}{g_{m6}} = 26 \text{k}\Omega, \quad r_{ds7} = \frac{1}{\lambda_P I_D} = \frac{20}{100 \mu\text{A}} = 0.2 \text{M}\Omega \quad \text{and} \quad r_{o6} = \frac{V_A}{I_C} = \frac{25\text{V}}{100 \mu\text{A}} = 0.25 \text{M}\Omega$$

$$\therefore |A_v(0)| = [158.1(0.8 || 1 || 0.026)][3846(0.2 || 0.25)] = 3.888 \cdot 427.36 = \underline{\underline{1,659.6\text{V/V}}}$$

$$GB = \frac{g_{m1}}{C_c} = \frac{158.1 \mu\text{S}}{5 \text{pF}} = 31.62 \times 10^6 \text{ rads/sec} \rightarrow \underline{\underline{GB = 5.0325 \text{MHz}}}$$

$$SR = \frac{50 \mu\text{A}}{5 \text{pF}} = \underline{\underline{10 \text{V}/\mu\text{s}}}$$

$$\text{RHP zero} = \frac{g_{m6}}{C_c} = \frac{3.846 \text{mS}}{5 \text{pF}} = \underline{\underline{769.24 \times 10^6 \text{ rads/sec. (122MHz)}}}$$

(c.) The maximum input common mode voltage is given as


$$v_{icm}^+ = V_{CC} - V_{DS5}(\text{sat}) - V_{SG1} = 1.5 - \sqrt{\frac{2 \cdot 50}{50 \cdot 10}} - 0.7 - \sqrt{\frac{2 \cdot 25}{50 \cdot 10}} = 0.8 - 0.447 - 0.316 =$$

$$\therefore v_{icm}^+ = \underline{\underline{0.0367\text{V}}}$$

$$v_{icm}^- = -1.5 + V_{BE3} - V_{T1} = -1.5 + V_t \ln\left(\frac{25 \mu\text{A}}{10 \text{fA}}\right) - 0.7 = -2.2 + 0.5626 = \underline{\underline{-1.6374\text{V}}}$$

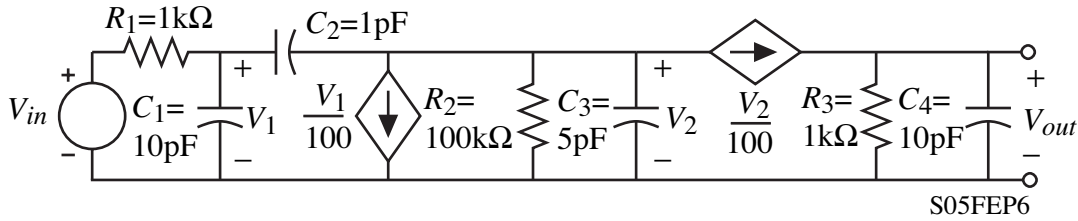**Problem 6 - (20 points - This problem is optional)**

Find the midband voltage gain and the  $-3\text{dB}$  frequency in Hertz for the circuit shown.



Solution

The midband voltage gain can be expressed as,

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_2} \frac{V_2}{V_1} \frac{V_1}{V_{in}} = (10) \left( \frac{-R_2}{R_2 + 1000} \right) (1) = \underline{\underline{-9.9\text{V/V}}}$$

Finding the open-circuit, time constants:

$R_{C1O}$ :  $R_{C1O} = R_1 = 1\text{k}\Omega$

$\rightarrow R_{C1O}C_1 = 10\text{ns}$

$R_{C2O}$ :

$$v_t = R_1 i_t + R_2 \left[ i_t + \frac{V_1}{100} + \frac{V_2}{100} \right]$$

But  $v_t = V_1 - V_2$  and  $V_1 = R_1 i_t$ ,

$$\therefore v_t = R_1 i_t + R_2 i_t + \frac{2R_1 R_2 i_t}{100} - \frac{R_2 v_t}{100}$$

$$R_{C2O} = \frac{v_t}{i_t} = \frac{R_1 + R_2 + 0.02R_1 R_2}{1 + 0.01R_2}$$

$$= \frac{1\text{k}\Omega + 100\text{k}\Omega + 2000\text{k}\Omega}{1 + 1000} = 2.099\text{k}\Omega \rightarrow R_{C2O}C_2 = 2.1\text{ns}$$

$R_{C3O}$ :  $R_{C3O} = R_2 \parallel 100\Omega = 99.9\Omega$

$\rightarrow R_{C3O}C_3 = 0.5\text{ns}$

$R_{C4O}$ :  $R_{C4O} = R_3 = 1\text{k}\Omega$

$\rightarrow R_{C4O}C_4 = 10\text{ns}$

$$\Sigma T_{oc} = (10 + 2.1 + 0.5 + 10)\text{ns} = 22.6\text{ns}$$

$$\omega_{-3\text{dB}} \approx \frac{1}{\Sigma T_{oc}} = 44.25 \times 10^6 \rightarrow f_{-3\text{dB}} = \underline{\underline{7.04\text{ MHz}}}$$

