 


## Homework Assignment No. 6 - Solutions

### Problem 1 - (10 points)

For the CMOS op amp shown, find the following quantities.

- 1.) Slew rate (V/sec.)
- 2.) Positive and negative output voltage limits (all transistors remain in saturation)
- 3.) Positive and negative input common voltage limits (all transistors remain in saturation and use nominal parameter values)
- 4.) Small signal voltage gain
- 5.) Unity-gainbandwidth (MHz) and 6.) Power dissipation (mW).



### Solution

$$1.) \quad SR = \frac{I_5}{C_c} = \frac{50\mu A}{5pF} = 10^7 \text{ V/second} \quad \Rightarrow \quad \boxed{SR = 10^7 \text{ V/sec}}$$

$$2.) \quad V_{SD7} = \sqrt{\frac{2I_7}{K_P(W/L)}} = \sqrt{\frac{500\mu A}{50 \cdot 50}} = 0.447 \text{ V} \quad \text{and} \quad V_{DS6} = \sqrt{\frac{500\mu A}{110 \cdot 50}} = 0.3015 \text{ V}$$

$$\therefore \quad \boxed{V_{out}(\max) = 2.5 - 0.447 = 2.053 \text{ V}} \quad \&$$

$$\boxed{V_{out}(\min) = -2.5 \text{ V} + 0.3015 \text{ V} = -2.198 \text{ V}}$$

$$3.) \quad ICM(\min) = -2.5 \text{ V} + V_{GS3} - |V_{TP}| = -2.5 \text{ V} + \sqrt{\frac{2 \cdot 25}{110 \cdot 10}} + 0.7 \text{ V} - 0.7 \text{ V}$$

$$\therefore \quad ICM(\min) = -2.5 + 0.213 = -2.287 \text{ V} \quad \Rightarrow \quad \boxed{ICM(\min) = -2.287 \text{ V}}$$

$$ICM(\max) = ? \quad V_{SD5}(\text{sat}) = \sqrt{\frac{2 \cdot 50}{50 \cdot 10}} = 0.4472 \text{ V} \quad \text{and} \quad V_{SG1} = \sqrt{\frac{2 \cdot 25}{50 \cdot 10}} + 0.7 = 1.016 \text{ V}$$

$$\therefore \quad ICM(\max) = 2.5 - V_{SD5}(\text{sat}) - V_{SG1} = 2.5 - 0.4472 - 1.016 = 1.0366 \text{ V}$$

$$\boxed{ICM(\max) = 1.0366 \text{ V}}$$

$$4.) \quad A_v = \frac{g_{m1}g_{m6}}{(g_{sd2} + g_{ds4})(g_{ds6} + g_{sd7})} \quad g_{m1} = \sqrt{\frac{2K_P W_1 I_1}{L_1}} = \sqrt{2 \cdot 50 \cdot 10 \cdot 25} = 158 \mu S$$

$$g_{m6} = \sqrt{\frac{2K_P W_6 I_6}{L_6}} = \sqrt{2 \cdot 110 \cdot 50 \cdot 250} = 1658 \mu S \quad G_I = 0.09 \cdot 250 \mu A = 22.5 \mu S$$

$$\text{and} \quad G_{II} = 0.09 \cdot 250 \mu A = 22.5 \mu S$$

$$\therefore \quad A_v = \frac{158 \cdot 1658}{22.5 \cdot 22.5} = 3,489 \text{ V/V} \quad \Rightarrow \quad \boxed{A_v = 5,176 \text{ V/V}}$$

$$5.) \quad GB = \frac{g_{m1}}{C_c} = \frac{158 \mu S}{5pF} = 31.6 \text{ Mrads/sec} \quad \Rightarrow \quad \boxed{GB = 5.03 \text{ MHz}}$$

$$6.) \quad P_{diss} = 5 \times 350 \mu A = 1.75 \text{ mW} \quad \Rightarrow \quad \boxed{P_{diss} = 1.75 \text{ mW}}$$

Problem 2 - (10 points)

Bias current calculation:

$$V_{T8} + V_{ON8} + I_8 \cdot R_S = V_{dd} - V_{ss} \text{ or, } V_{T8} + \sqrt{\frac{2 \cdot I_8}{3 \cdot K'_p}} = 5 - I_8 \cdot R_S \text{ .} \quad (1)$$

Solving for  $I_8$  quadratically would give,  $I_8$   $36\mu\text{A}$ ,  $I_5$   $36\mu\text{A}$ , and  $I_7$   $60\mu\text{A}$ Using the formula,  $g_m = \sqrt{2 \cdot K' \frac{W}{L} I}$  and  $g_{ds} = \lambda I$  we get,

$$g_{m2} = 60\mu\text{S} \text{ , } g_{ds2} = 0.9\mu\text{S} \text{ , } g_{ds4} = 0.72\mu\text{S} \quad (2)$$

$$g_{m6} = 363\mu\text{S} \text{ , } g_{ds6} = 3\mu\text{S} \text{ , } g_{ds7} = 2.4\mu\text{S} \quad (3)$$

Small-signal open-loop gain:

The small-signal voltage gain can be expressed as,

$$A_{v1} = \frac{-g_{m2}}{(g_{ds2} + g_{ds4})} = -37 \text{ and } A_{v2} = \frac{-g_{m6}}{(g_{ds6} + g_{ds7})} = -67$$

Thus, total open-loop gain is,

$$A_v = A_{v1} \cdot A_{v2} = \underline{\underline{2489\text{V/V}}} \quad (3)$$

Output resistance:

$$R_{out} = \frac{1}{(g_{ds6} + g_{ds7})} = 185\text{K}\Omega \quad (5)$$

Power dissipation:

$$P_{diss} = 5(36 + 36 + 60)\mu\text{W} = 660\mu\text{W} \quad (6)$$

ICMR:

$$V_{in,max} = 2.5 - V_{T1} - V_{ON1} - V_{ON5} = 0.51\text{V} \quad (7)$$

$$V_{in,min} = -2.5 - V_{T1} + V_{T3} + V_{ON3} = -2.21\text{V} \quad (8)$$

Output voltage swing:

$$V_{0,max} = 2.5 - V_{ON7} = 1.81\text{V} \quad (9)$$

Slew Rate:

Slew rate under no load condition can be given as,

$$SR = \frac{I_5}{C_c} = 6\text{V} / \mu\text{s}$$

In presence of a load capacitor of 20 pF, slew rate would be,

$$SR = \min\left[\frac{I_5}{C_c}, \frac{I_7}{C_L}\right]$$

Problem 6.3-7 - Continued

CMRR:

Under perfectly balanced condition where  $I_1 = I_2$ , if a small signal common-mode variation occurs at the two input terminals, the small signal currents  $i_1 = i_2 = i_3 = i_4$  and the differential output current at node (7) is zero. So, ideally, common-mode gain would be zero and the value for CMRR would be infinity.

GBW:

Let us design M9 and M10 first. Both these transistors would operate in triode region and will carry zero dc current. Thus,  $V_{ds9} = V_{ds10} \cong 0$ . The equation of drain current in triode region is given as,

$$I_D \cong K' \frac{W}{L} (V_{GS} - V_T) V_{DS}.$$

The on resistance of the MOS transistor in triode region of operation would be,

$$R_{ON} = K' \frac{W}{L} (V_{GS} - V_T).$$

It is intended to make the effective resistance of M9 and M10 equal to  $\frac{1}{g_{m6}}$ .

$$\text{So, } K'_9 \left( \frac{W_9}{L_9} \right) (V_{GS9} - V_{T9}) + K'_{10} \left( \frac{W_{10}}{L_{10}} \right) (V_{GS10} - V_{T10}) = g_{m6} \quad (11)$$

$$V_{D4} = V_{D3} = -2.5 + V_{T3} + V_{ON3} = -1.51V$$

Thus,

$$V_{GS9} \cong 4V \quad \text{and} \quad V_{GS10} \cong -1V.$$

Putting the appropriate values in (11), we can solve for the aspect ratios of M9 and M10. One of the solutions could be,

$$K'_9 \left( \frac{W_9}{L_9} \right) = \frac{1}{1} \quad \text{and} \quad K'_{10} \left( \frac{W_{10}}{L_{10}} \right) = \text{very small} \quad (12)$$

The dominant pole could be calculated as,

$$p_1 = \frac{-(g_{ds4} + g_{ds2})}{2\pi \cdot A_{V1} \cdot C_C} = -1.16 \text{ KHz.}$$

And the load pole would be,

$$p_2 = \frac{-g_{m6}}{2\pi \cdot C_L} = -2.8 \text{ MHz.} \quad \text{for a 20 pF load.}$$

It can be noted that in this problem, the product of the open-loop gain and the dominant pole is approximately equal to the load pole. Thus, the gain bandwidth is approximately equal to 2.8 MHz and the phase margin would be close to 45 degrees.

Problem 6.3-7 - Continued

PSRR:

If a small ripple  $v_s$  is applied at the  $V_{dd}$  terminal, then the gain of this ripple from this terminal to the output can be expressed as,

$$\frac{v_o}{v_s} = \frac{\left(1 - \frac{R_S}{R_S + (1/g_{m8})}\right) g_{m7}}{g_{ds6} + g_{ds7}} = 2.8V/V$$

Thus, PSRR due to variations in  $V_{dd}$  would be,  $A_V \mu.8 = 2489 / 2.8 = 889$  .

SPICE file:

```
.model nmos nmos vto=0.7 lambda=0.04 kp=110u
.model pmos pmos vto=-0.8 lambda=0.05 kp=50u

vdd 1 0 dc 2.5 ac 0
vss 10 0 dc -2.5 ac 0
vinp 5 0 dc 0 ac 1
*vinn 4 0 dc 0 ac 0

m8 2 2 1 1 pmos w=3u l=1u
rs 2 10 100k
m5 3 2 1 1 pmos w=3u l=1u
m1 6 8 3 3 pmos w=2u l=1u
m2 7 5 3 3 pmos w=2u l=1u
m3 6 6 10 10 nmos w=4u l=1u
m4 7 6 10 10 nmos w=4u l=1u
m7 8 2 1 1 pmos w=5u l=1u
m6 8 7 10 10 nmos w=10u l=1u
cc 7 9 6p
cl 8 0 20p
m9 8 1 9 9 nmos w=1u l=1u
m10 8 10 9 9 pmos w=1u l=100u

.op
.ac dec 10 1 100meg
.option post
.end

Operating points:

**** mosfets

subckt
element 0:m8      0:m5      0:m1      0:m2      0:m3      0:m4
model      0:pmos      0:pmos      0:pmos      0:pmos      0:nmos      0:nmos
region      Cutoff      Cutoff      Cutoff      Cutoff      Saturati      Saturati
id          -35.3708u    -34.8506u    -17.4107u    -17.4399u    17.4107u    17.4399u
ibs         0.          0.          0.          0.          0.          0.
ibd         14.6292f     11.4726f     28.7676f     28.3314f     -9.7598f     -10.1959f
```

Problem 6.3-7 - Continued

```

vgs      -1.4629   -1.4629   -1.3517   -1.3527   975.9818m  975.9818m
vds      -1.4629   -1.1473   -2.8768   -2.8331   975.9818m  1.0196
vbs      0.         0.         0.         0.         0.         0.
vth      -800.0000m -800.0000m -800.0000m -800.0000m 700.0000m
700.0000m
vdsat    -662.9217m -662.9217m -551.7476m -552.7377m 275.9818m
275.9818m
beta     160.9719u  158.6045u  114.3838u  114.1657u  457.1773u  457.9449u
gam eff  527.6252m  527.6252m  527.6252m  527.6252m  527.6252m  527.6252m
gm       106.7118u  105.1423u  63.1110u   63.1037u   126.1726u  126.3844u
gds      1.6480u     1.6480u     761.0636n  763.7975n  670.2604n  670.2604n
gmb      36.9704u     36.4266u     21.8648u   21.8623u   43.7126u   43.7860u
cdtot    2.021e-18    1.585e-18    2.649e-18  2.609e-18  1.797e-18  1.878e-18
cgtot    7.005e-16    7.000e-16    4.693e-16  4.692e-16  9.467e-16  9.467e-16
cstot    6.906e-16    6.906e-16    4.604e-16  4.604e-16  9.208e-16  9.208e-16
cbtot    7.806e-18    7.806e-18    6.216e-18  6.205e-18  2.402e-17  2.402e-17
cgs      6.906e-16    6.906e-16    4.604e-16  4.604e-16  9.208e-16  9.208e-16
cgd      2.021e-18    1.585e-18    2.649e-18  2.609e-18  1.797e-18  1.878e-18

```

```



subckt
element 0:m7      0:m6      0:m9      0:m10
model   0:pmos    0:nmos    0:nmos    0:pmos
region  Cutoff    Saturati  Linear    Cutoff
id      -61.7971u  61.7971u  0.         0.
ibs     0.         0.         0.         0.
ibd     24.9901f  -25.0099f  0.         0.
vgs     -1.4629    1.0196    2.4990    -2.5010
vds     -2.4990    2.5010    0.         0.
vbs     0.         0.         0.         0.
vth     -800.0000m 700.0000m 700.0000m -800.0000m
vdsat   -662.9217m 319.5939m 0.         0.
beta    281.2376u  1.2100m  110.0000u  500.0000n
gam eff  527.6252m  527.6252m  527.6252m  527.6252m
gm       186.4385u  386.7225u  0.         0.
gds      2.7467u     2.2471u   197.8911u  850.4951n
gmb      64.5917u   133.9802u  0.         0.
cdtot    5.753e-18    1.152e-17  1.727e-16  17.2658f
cgtot    1.1698f     2.3660f   3.463e-16  34.6349f
cstot    1.1511f     2.3021f   1.727e-16  17.2658f
cbtot    1.301e-17    5.233e-17  9.769e-19  1.033e-16
cgs      1.1511f     2.3021f   1.727e-16  17.2658f
cgd      5.753e-18    1.152e-17  1.727e-16  17.2658f

```


Results from SPICE simulation:

- i. Unloaded output (load capacitor = 0)
  - GBW = 1.5 MHz., Phase Margin = 90 deg, 1% settling time = 0.39 us.
- ii. Loaded output (load capacitor = 20 pF)
  - GBW = 1.5 MHz., Phase Margin = 65 deg, 1% settling time = 0.48 us.

Problem 6.3-7 - Continued

  

Problem 6.3-7 - Continued

 

**Problem 3 - (10 points)**

Small signal differential voltage gain:


By intuitive analysis methods,

$$\frac{v_{o1}}{v_{in}} = \frac{-0.5g_{m1}}{g_{ds1} + g_{ds3}}$$

and

$$\frac{v_{out}}{v_{o1}} = \frac{-g_{m4}}{g_{ds4} + g_{ds5}}$$
 
$$\therefore \frac{v_{out}}{v_{in}} = \frac{0.5g_{m1}g_{m4}}{(g_{ds1}+g_{ds3})(g_{ds4}+g_{ds5})}$$



$$g_{m1} = \sqrt{\frac{2K_N W_1 I_{D1}}{L_1}} = \sqrt{24 \cdot 2.4 \cdot 10} \times 10^{-6} = 43.82 \mu\text{S}$$

$$g_{ds1} = \lambda_N I_{D1} = 0.01 \cdot 10 \mu\text{A} = 0.1 \mu\text{S}, \quad g_{ds3} = \lambda_P I_{D3} = 0.02 \cdot 10 \mu\text{A} = 0.2 \mu\text{S}$$

$$g_{m4} = \sqrt{\frac{2K_P W_4 I_{D4}}{L_4}} = \sqrt{2 \cdot 8 \cdot 10 \cdot 100} \times 10^{-6} = 126.5 \mu\text{S}$$

$$g_{ds4} = \lambda_P I_{D4} = 0.02 \cdot 100 \mu\text{A} = 2 \mu\text{S}, \quad g_{ds5} = \lambda_N I_{D5} = 0.01 \cdot 100 \mu\text{A} = 1 \mu\text{S}$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{0.5 \cdot 43.82 \cdot 126.5}{(0.1 + 0.2)(1 + 2)} = 3,079 \text{ V/V}$$

Output resistance:

$$R_{out} = \frac{1}{g_{ds4} + g_{ds5}} = \frac{10^6}{1 + 2} = 333 \text{ k}\Omega$$

Dominant pole,  $p_1$ :

$$|p_1| = \frac{1}{R_1 C_1} \quad \text{where } R_1 = \frac{1}{g_{ds1} + g_{ds3}} = \frac{10^6}{0.1 + 0.2} = 3.33 \text{ M}\Omega$$

and

$$C_1 = C_c (1 + |A_{v2}|) = 5 \text{ pF} \left( 1 + \frac{g_{m4}}{g_{ds4} + g_{ds5}} \right) = 5 \left( 1 + \frac{126.5}{3} \right) = 215.8 \text{ pF}$$

$$\therefore |p_1| = \frac{10^6}{3.33 \cdot 215.8} = 1,391 \text{ rads/sec} \rightarrow |p_1| = 1,391 \text{ rads/sec} = 221 \text{ Hz}$$

$$\text{GB} = \frac{0.5 \cdot g_{m1}}{C_c} = \frac{0.5 \cdot 43.82 \times 10^{-6}}{5 \times 10^{-12}} = 4.382 \text{ Mrads/sec}$$

$$\text{GB} = 4.382 \text{ Mrads/sec} = 0.697 \text{ MHz}$$

$$\text{SR} = \frac{I_{D6}}{C_c} = \frac{10 \mu\text{A}}{5 \text{ pF}} = 2 \text{ V}/\mu\text{s}$$

$$P_{diss} = 10 \text{ V} (140 \mu\text{A}) = 1.4 \text{ mW}$$

Problem 4 - Design Problem 2 (50 points)