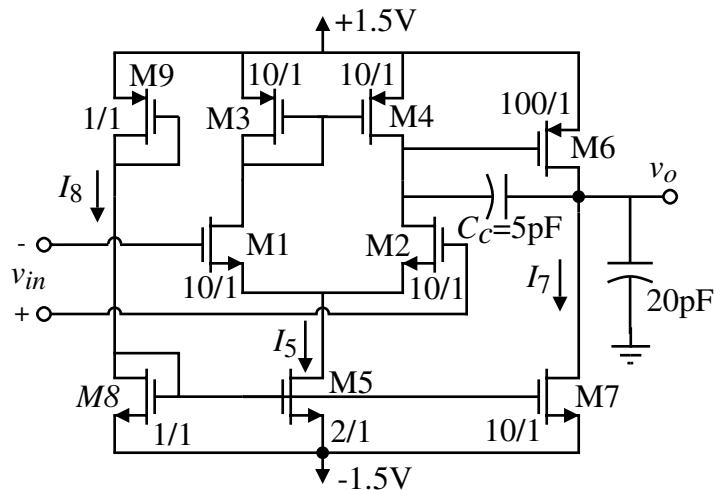


Homework Assignment No. 7 -Solutions

Problem 1 - (10 points)

Find the low frequency PSRR and all roots of the positive and negative power supply rejection ratio performance for the two-stage op amp of Fig. P6.3-9.



Solution

Referring to the figure

$$V_{DD} - V_{SS} = V_{T8} + V_{T9} + \sqrt{\frac{2I_8}{K_N(W/L)_8}} + \sqrt{\frac{2I_8}{K_P(W/L)_9}}$$

or, $I_8 = 60 \mu A$

Now,

$$g_{m1} = 363.3 \mu S, g_{ds2} = 2.4 \mu S, g_{ds4} = 3 \mu S, g_{m6} = 774.6 \mu S, g_{ds6} = 30 \mu S$$

and $g_{ds7} = 24 \mu S$

$$\therefore A_{v1} = 67.3 \text{ and } A_{v2} = 14.3$$

For the positive PSRR, the low frequency PSRR is

$$PSRR^+ = \frac{A_v(0)G_{II}}{g_{ds6}} = 1737$$

and poles and zeros are

$$p_1 = \frac{(GB)g_{ds6}}{A_v(0)G_{II}} = 6.66 \text{ KHz}, z_1 = GB = 11.6 \text{ MHz. and } z_2 = p_2 = 6.2 \text{ MHz.}$$

For the negative PSRR, the low frequency PSRR is given by

$$PSRR^- = \frac{A_v(0)G_{II}}{g_{ds7}} = 2171$$

and the poles and zeros are

$$p_1 = \frac{(GB)G_I}{g_{m1}} = 172.4 \text{ KHz, } z_1 = GB = 11.6 \text{ MHz and } z_2 = p_2 = 6.2 \text{ MHz.}$$

Figure P6.3-10

Problem 2 – (10 points)

A CMOS op amp that uses a 5V power supply is shown. All transistor lengths are 1 μm and operate in the saturation region. Design all of the W values of every transistor of this op amp to meet the following specifications: Slew rate = $\pm 10\text{V}/\mu\text{s}$, $V_{\text{out(max)}} = 4\text{V}$, $V_{\text{out(min)}} = 1\text{V}$, $V_{\text{ic(min)}} = 1.5\text{V}$, $V_{\text{ic(max)}} = 4\text{V}$ and GB = 10MHz.

Your design should meet or exceed these specifications. Ignore bulk effects and summarize your W values to the nearest micron, the bias current, $I_5(\mu\text{A})$, the power dissipation, the differential voltage gain, A_{vd} , and V_{BP} and V_{BN} in the table shown.

Solution

$$1.) I_5 = C_L \cdot SR = 250\mu\text{A}$$

$$2.) g_{m1} = GB \cdot C_L = 20\pi \times 106.25\text{pF} = 1,570.8\mu\text{S} \Rightarrow \frac{W_1}{L_1} = \frac{(1.570 \times 10^{-3})^2}{2 \cdot 110 \cdot 125 \times 10^{-6}} = 90$$

$$3.) W_3=W_4=W_6=W_7=W_8 = \frac{2I_D}{K'(V_{DS}(\text{sat}))^2} = \frac{2 \cdot 250}{50 \cdot 0.25} = 40 \quad (\text{assumed } I_D \text{ of } 250\mu\text{A worst case})$$

$$4.) W_9=W_{10}=W_{11} = \frac{2I_D}{K'(V_{DS}(\text{sat}))^2} = \frac{2 \cdot 250}{110 \cdot 0.25} = 18 \quad (\text{assumed } I_D \text{ of } 250\mu\text{A worst case})$$

$$5.) V_{icm(\text{min})} = V_{DS5(\text{sat})} + V_{GS1} \rightarrow V_{DS5(\text{sat})} = 1.5 - (0.159 + 0.7) = 0.6411\text{V}$$

$$\therefore W_5 = \frac{2I_D}{K'(V_{DS}(\text{sat}))^2} = \frac{2 \cdot 250}{110 \cdot 0.6411^2} = 11$$

$$6.) A_{vd} = g_{m1} R_{out} \quad g_{mN} = 704\mu\text{S}, \quad r_{dsN} = 0.2\text{M}\Omega, \quad g_{mP} = 707\mu\text{S}, \quad r_{dsN} = 0.16\text{M}\Omega$$

$$R_{out} \approx g_{mN} \cdot r_{dsN}^2 \parallel g_{mP} \cdot r_{dsP}^2 = 28.14\text{M}\Omega \parallel 18.1\text{M}\Omega = 11\text{M}\Omega$$

$$\therefore A_{vd} = 1.57\text{mS} \cdot 11\text{M}\Omega = 17,329\text{V/V}$$

$$7.) V_{BP} = 5 - V_{DSP(\text{sat})} + V_{GSP(\text{sat})} = 5 - 0.5 + 0.5 + 0.7 = 3.3\text{V}$$

$$V_{BN} = V_{DSP(\text{sat})} + V_{GSP(\text{sat})} = 0.5 + 0.5 + 0.7 = 1.7\text{V}$$

$$8.) P_{diss} = 5(250\mu\text{A} + 250\mu\text{A}) = 2.5\text{mW}$$

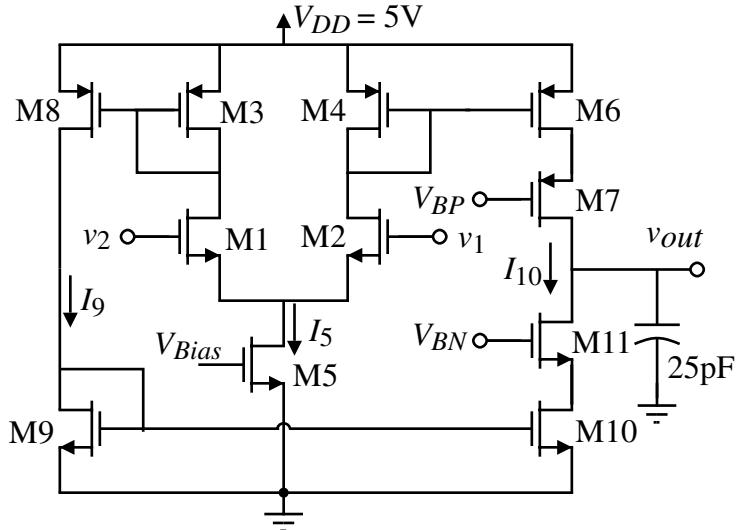


Figure P6.5-13

V_{BP} and V_{BN} in the table shown.

W1=W2	W3=W4=W6 =W7=W8	W9=W10 =W11	W5	$I_5(\mu\text{A})$	A_{vd}	V_{BP}	V_{BN}	P_{diss}
90 μm	40 μm	18 μm	11 μm	250 μA	17,329 V/V	3.3V	1.7V	2.5mW

Problem 3 – (10 points)

6.15

$$200 \text{ mA} = |I_{D_4}| = |I_{D_5}| = |I_{D_6}| = I_{D_4}$$

$$100 \text{ mA} = I_{D_1} = I_{D_2} = I_{D_3} = I_{D_4}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 (8.85 \times 10^{-14} \text{ F/cm})}{80 \text{ \AA}} = 431 \text{ nF/cm}^2$$

$$4nC_{ox} = 450 \frac{\text{cm}^2}{\text{V.s}} \cdot 431 \frac{\text{nF}}{\text{cm}^2} = 194 \text{ mA/V}$$

$$k'_n = 194 \text{ mA/V}$$

$$k'_p = 64.7 \text{ mA/V}$$

$$\frac{V_o}{V_i} = -g_{m_2} (r_{o2} || r_{o4}) g_{m_6} (r_{o6} || r_{o7})$$

$$\frac{1}{r_{o2}} = \frac{I_{D_2}}{L_{eff}} \frac{dX_d}{dV_{BS}} = \frac{100 \text{ mA}}{0.724 \text{ m}} (0.04 \mu) = 5.56 \mu$$

$$r_{o2} = 180 \text{ k}\Omega = r_{o4}$$

$$r_{o6} = 90 \text{ k}\Omega = r_{o7}$$

$$L_{eff} = L - X_d - 2L_d \\ = 1 - 0.1 - 2(0.09) \\ = 0.724 \text{ m}$$

$$g_{m_2} = \sqrt{2 k'_p \frac{W}{L_{eff}} I_{D_2}} \\ = \sqrt{2 (64.7 \mu) \left(\frac{150}{0.72}\right) (100 \mu)} \\ = 1640 \text{ mA/V}$$

$$g_{m_6} = \sqrt{2 (194 \mu) \left(\frac{100}{0.72}\right) (200 \mu)} \\ = 3280 \text{ mA/V}$$

$$\frac{V_o}{V_i} = -(1.64 \text{ m}) (90 \text{ k}) (3.28 \text{ m}) (45 \text{ k}) \\ = -2.18 \times 10^4$$

common mode range:

From (6.75),

$$V_{IC} > V_{t_1} + V_{t_3} + V_{OV_3} - V_{SS}$$

$$V_{OV_3} = \sqrt{\frac{2(100)}{194 (50/0.72)}} = 0.12 \text{ V}$$

$$V_{IC} > -0.8 + 0.6 + 0.12 - 1.5$$

$$V_{IC} > -1.58 \text{ V}$$

From (6.77),

$$V_{IC} < V_{t_1} + V_{OV_1} + V_{OV_5} + V_{DD}$$

$$V_{OV_5} = -\sqrt{\frac{2(200)}{64.7 (150/0.72)}} = -0.17 \text{ V}$$

$$V_{OV_1} = -\sqrt{\frac{2(100)}{64.7 (150/0.72)}} = -0.12 \text{ V}$$

$$V_{IC} < -0.8 - 0.12 - 0.17 + 1.5$$

$$V_{IC} < 0.41 \text{ V}$$

From (6.86),

$$\frac{V_o}{V_{dd}} \equiv 0$$

From (6.87),

$$\frac{V_o}{V_{SS}} = \frac{r_{o7}}{r_{o6} + r_{o7}} = 0.5$$

Problem 3 – Continued

```

TWO-STAGE CMOS AMPLIFIER
*****
VDD 120 0 1.5
VSS 120 0 -1.5
M1 7 6 4 4 PDSB M=1000 L=10
M2 8 6 4 4 PDSB M=1000 L=10
M3 7 1 120 120 NMOS M=500 L=10
M4 8 7 120 120 NMOS M=500 L=10
M5 4 3 120 120 PMOS M=1000 L=10
M6 9 8 120 120 NMOS M=1000 L=10
M7 7 9 120 120 NMOS M=1000 L=10
M8 5 3 120 120 NMOS M=1000 L=10
M9 2 1 120 120 NMOS M=1000 L=10
M10 3 2 120 120 NMOS M=1000 L=10
NMOS 3 200 1200
+ VDD DC CURRENT IS ADJUSTED BY TRIAL AND ERROR
+ DO NOT SET THE CURRENT TO ZERO.
VDD 5 2 4.00
VDD 6 3 0
VDD 7 1 0
VDD 8 1 0
*LEFT = LAMBDA = 0.01 - 0.1 * (VDS-0.6) + 0.1 + 0.75 DM
*COMMON-EMITTER/COMMON-Emitter = 0.000176733 = 0.0002
.MODEL NMOS MEDEV LEVEL=1 KP=1.00E-07 VTO=-0.6 LAMBDA=0.0002
.MODEL PMOS MEDEV LEVEL=1 KP=0.170777 VTO=-0.8 LAMBDA=0.0002
.OPTIONS NORMALL NORMD
.AC 1000 0.001
.OPTIONS VTFOL=1.0 KFOL=1.0 KELTOL=1.0
.AC
.VP V120 V112
.JRD

**** OPERATING POINT INFORMATION THDM= 27.000 THDP= 27.000
      MODE 1 VOLTAGE MODE 2 VOLTAGE MODE 3 VOLTAGE MODE 4 VOLTAGE
V112  = 0.   0.00  < 0.0002-01 0.00  = 0.3578-01
V113  = 0.4000-05 0.00  < 0.   0.00  -0.3578-01
V118  =-1.0000-01 0.00  < 0.0002-04 0.000  = 1.0000-00
V120  =-1.0000-00

.EFFECT
ELEMENT 0.000 0.000 0.000 0.000
MODEL 0.0000 0.0000 0.0000 0.0000
ID -0.7732E-01 -0.7732E-01 0.7732E-01 0.7732E-01
VDD 0.   0.   0.   0.
VSS 0.4000E-04 0.4000E-04 -0.3578E-01 -0.3578E-01
V112 -0.3578E-01 -0.3578E-01 0.3578E-01 0.3578E-01
V113 -0.3578E-01 -0.3578E-01 0.3578E-01 0.3578E-01
V118 0.   0.   0.   0.
V120 -0.3578E-01 -0.3578E-01 0.3578E-01 0.3578E-01
VDDAT 0.3578E-01 0.3578E-01 0.3578E-01 0.3578E-01
VSSAT 0.3578E-01 0.3578E-01 0.3578E-01 0.3578E-01
CM 0.000 0.000 0.000 0.000
CM 0.4000E-03 0.4000E-03 0.4000E-03 0.4000E-03
CD 0.0000E-04 0.0000E-04 0.0000E-04 0.0000E-04
CR 0.   0.   0.   0.

.EFFECT
ELEMENT 0.000 0.000 0.000 0.000
MODEL 0.0000 0.0000 0.0000 0.0000
ID -1.0048E-04 0.0002E-04 -0.0002E-04 -0.0002E-04
VDD 0.   0.   0.   0.
VSS 0.6432E-15 -0.6432E-14 0.6432E-14 0.6432E-15
V112 -0.0000E-01 0.0000E-01 -0.0000E-01 0.0000E-01
V113 0.6432E-01 0.6432E-01 -0.6432E-01 0.6432E-01
V118 0.   0.   0.   0.
V120 -0.0000E-01 0.0000E-01 -0.0000E-01 0.0000E-01
VDDAT 0.1000E-01 0.1000E-01 0.1000E-01 0.1000E-01
VSSAT 0.1000E-01 0.1000E-01 0.1000E-01 0.1000E-01
CM 0.000 0.000 0.000 0.000
CM 0.1000E-03 0.1000E-03 0.1000E-03 0.1000E-03
CD 0.0000E-04 0.0000E-04 0.0000E-04 0.0000E-04
CR 0.   0.   0.   0.

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V112(V112)  = -0.0002E-01
IMPEDANCE AT V112  = 1.0000E-03
OUTPUT IMPEDANCE AT V112  = 4.7500E-05
V112(V112)  = -0.0002E-01
IMPEDANCE AT V112  = 1.0000E-03
OUTPUT IMPEDANCE AT V112  = 4.7500E-05

TWO-STAGE CMOS AMPLIFIER (MAXIMUM COMMON-MODE INPUT VOLTAGE)
*****
VDD 120 0 1.5
VSS 120 0 -1.5
M1 7 6 4 4 PDSB M=1000 L=10
M2 8 6 4 4 PDSB M=1000 L=10
M3 7 1 120 120 NMOS M=500 L=10
M4 8 7 120 120 NMOS M=500 L=10
M5 4 3 120 120 PMOS M=1000 L=10
M6 9 8 120 120 NMOS M=1000 L=10
M7 7 9 120 120 NMOS M=1000 L=10
M8 5 3 120 120 NMOS M=1000 L=10
M9 2 1 120 120 NMOS M=1000 L=10
M10 3 2 120 120 NMOS M=1000 L=10
NMOS 3 200 1200
+ VDD DC CURRENT IS ADJUSTED BY TRIAL AND ERROR
+ DO NOT SET THE CURRENT TO ZERO.
V112 5 2 10.70
V112 6 3 0
* MAXIMUM VALUE OF VDD IS ADJUSTED BY TRIAL AND ERROR
* UNTIL NO SATURATION IN THE ACTIVE REGION
* WHERE |VDD| > |VOLAT| FOR NMOS
VDD 5 2 10.70
*LEFT = LAMBDA = 0.01 - 0.1 * (VDS-0.6) + 0.1 + 0.75 DM
*COMMON-EMITTER/COMMON-Emitter = 0.000176733 = 0.0002
.MODEL NMOS MEDEV LEVEL=1 KP=1.00E-07 VTO=-0.6 LAMBDA=0.0002
.MODEL PMOS MEDEV LEVEL=1 KP=0.170777 VTO=-0.8 LAMBDA=0.0002
.OPTIONS NORMALL NORMD
.AC 1000 0.001
.OPTIONS VTFOL=1.0 KFOL=1.0 KELTOL=1.0
.AC
.VP V120 V112
.JRD

**** OPERATING POINT INFORMATION THDM= 27.000 THDP= 27.000
      MODE 1 VOLTAGE MODE 2 VOLTAGE MODE 3 VOLTAGE MODE 4 VOLTAGE
V112  = 0.   0.00  < 0.0002-01 0.00  = 0.3578-01
V113  = 0.4000-05 0.00  < 0.   0.00  -0.3578-01
V118  =-1.0000-01 0.00  < 0.0002-04 0.000  = 1.0000-00
V120  =-1.0000-00

.EFFECT
ELEMENT 0.000 0.000 0.000 0.000
MODEL 0.0000 0.0000 0.0000 0.0000
ID -0.0002-01 -0.0002-01 0.0002-01 0.0002-01
VDD 0.   0.   0.   0.
VSS 0.3578-01 0.3578-01 0.3578-01 0.3578-01
V112 -0.3578-01 -0.3578-01 0.3578-01 0.3578-01
V113 -0.3578-01 -0.3578-01 0.3578-01 0.3578-01
V118 0.   0.   0.   0.
V120 -0.3578-01 -0.3578-01 0.3578-01 0.3578-01
VDDAT 0.3578-01 0.3578-01 0.3578-01 0.3578-01
VSSAT 0.3578-01 0.3578-01 0.3578-01 0.3578-01
CM 0.000 0.000 0.000 0.000
CM 0.3578E-01 0.3578E-01 0.3578E-01 0.3578E-01
CD 0.0000E-04 0.0000E-04 0.0000E-04 0.0000E-04
CR 0.   0.   0.   0.

.EFFECT
ELEMENT 0.000 0.000 0.000 0.000
MODEL 0.0000 0.0000 0.0000 0.0000
ID 0.0000 0.0000 0.0000 0.0000
VDD 0.   0.   0.   0.
VSS 0.6432E-15 -0.6432E-14 0.6432E-14 0.6432E-15
V112 -0.0000E-01 0.0000E-01 -0.0000E-01 0.0000E-01
V113 0.6432E-01 0.6432E-01 -0.6432E-01 0.6432E-01
V118 0.   0.   0.   0.
V120 -0.0000E-01 0.0000E-01 -0.0000E-01 0.0000E-01
VDDAT 0.1000E-01 0.1000E-01 0.1000E-01 0.1000E-01
VSSAT 0.1000E-01 0.1000E-01 0.1000E-01 0.1000E-01
CM 0.000 0.000 0.000 0.000
CM 0.1000E-03 0.1000E-03 0.1000E-03 0.1000E-03
CD 0.0000E-04 0.0000E-04 0.0000E-04 0.0000E-04
CR 0.   0.   0.   0.

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V112(V112)  = -0.0002E-01
IMPEDANCE AT V112  = 1.0000E-03
OUTPUT IMPEDANCE AT V112  = 4.7500E-05
V112(V112)  = -0.0002E-01
IMPEDANCE AT V112  = 1.0000E-03
OUTPUT IMPEDANCE AT V112  = 4.7500E-05

```

Problem 3 – Continued

```


TWO-STAGE CIRCUIT AMPLIFIER (SECOND COMMON-MODE INPUT VOLTAGE)
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PDSB N=1000 L=10
M2 6 4 4 4 PDSB N=1000 L=10
M3 1 7 200 200 NDSB N=1000 L=10
M4 8 7 200 200 NDSB N=1000 L=10
M5 4 3 200 100 PDSB N=1000 L=10
M6 9 8 200 200 NDSB N=1000 L=10
M7 5 3 100 100 PDSB N=1000 L=10
M8 2 3 100 100 PDSB N=1000 L=10
D1 1 200 200
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR.
* DO NOT SET THE OUTPUT TO ZERO.
VIL 5 2 -0.75
VTC 4 3 0
* THE MINIMUM VALUE OF VTC IS ADJUSTED BY TRIAL AND ERROR.
* MODEL M1, M2, M3 OPERATES IN THE ACTIVE REGION
* VDSR2 = |VDS| + |VDSAT| FOR M2
VDS 2 0 -1.00
*VDSAT = LOA2 = 2.0 - 0.1 = 1.900.001 = 0.1 + 0.12 .00
*LOA2 = (2.0/VDSR2)/LOP = 0.0400/1.900 = 0.0000
.MODEL MOSFET M2 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M3 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M1 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M4 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M5 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M6 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M7 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M8 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
*OPTIMIZATION MODELS
.MOPT OFF=0
.OPTION VOUT=1000 M2LEVEL=1P M3LEVEL=1P
.OPT
.OFF
.VT1 VIL VIL
.REF
**** OPERATING POINT INFORMATION  VDSB= 27.000 VSSB= 27.000
      BIAS  >VOLTRMS  BIAS  >VOLTRMS  BIAS  >VOLTRMS
      VIL  =-1.0000E-01 0.0  = 0.0000E-01 0.0  = 0.0000E-01 0.0
      VIL  =-1.0000E-01 0.0  =-1.0000E-01 0.0  =-1.0000E-01 0.0
      VIL  =-7.0000E-01 0.0  = 0.0000E-01 0.0  = 0.0000E-01 0.0
      VIL  =-1.0000E-00 0.0
**** MODESTY
ELEMENT 1:100 0:100 0:100 0:100
MODEL 0:10000 0:10000 0:10000 0:10000
ID  -1.0000E-01 -1.0000E-01 1.0000E-01 1.0000E-01
M1  0. 0. 0. 0.
M2  1.0000E-10 1.0000E-10 -1.0000E-10 -1.0000E-10
M3  -9.0000E-01 -9.0000E-01 7.0000E-01 7.0000E-01
M4  -9.0000E-01 -9.0000E-01 7.0000E-01 7.0000E-01
M5  0. 0. 0. 0.
M6  -8.0000E-01 -8.0000E-01 6.0000E-01 6.0000E-01
VDSAT  -0.4710E-01 -0.4710E-01 1.0000E-01 1.0000E-01
VTHA  0.7070E-02 0.7070E-02 0.7070E-02 0.7070E-02
GND OFF 0. 0. 0.
M1  1.0000E-01 1.0000E-01 1.0000E-01 1.0000E-01
M2  0.0000E-01 0.0000E-01 0.0000E-01 0.0000E-01
M3  0. 0. 0. 0.
**** MODESTY
ELEMENT 0:100 0:100 0:100 0:100
MODEL 0:10000 0:10000 0:10000 0:10000
ID  -1.0000E-01 0.0000E-01 -1.0000E-01 -1.0000E-01
M1  0. 0. 0. 0.
M2  1.0000E-10 1.0000E-10 1.0000E-10 1.0000E-10
M3  -9.0000E-01 -9.0000E-01 7.0000E-01 7.0000E-01
M4  -9.0000E-01 -9.0000E-01 7.0000E-01 7.0000E-01
M5  0. 0. 0. 0.
M6  -8.0000E-01 -8.0000E-01 -8.0000E-01 -8.0000E-01
VDSAT  -0.3700E-01 0.3700E-01 -0.3700E-01 -0.3700E-01
VTHA  0.7070E-02 0.7070E-02 0.7070E-02 0.7070E-02
M7  1.0000E-02 1.0000E-02 1.0000E-02 1.0000E-02
M8  0. 0. 0. 0.
GND OFF 0. 0. 0.
M1  0.0000E-01 0.0000E-01 0.0000E-01 0.0000E-01
M2  1.0000E-01 1.0000E-01 1.0000E-01 1.0000E-01
M3  0.0000E-01 0.0000E-01 0.0000E-01 0.0000E-01
M4  0. 0. 0. 0.
**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V101/V201  = -1.7000E-04
ZINVT RESISTANCE AT VIL  = 1.0000E+00
ZOUTVT RESISTANCE AT VIL  = 4.7000E+00

```

```

TWO-STAGE CIRCUIT AMPLIFIER (VALUES FROM VTC)
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PDSB N=1000 L=10
M2 6 4 4 4 PDSB N=1000 L=10
M3 1 7 200 200 NDSB N=1000 L=10
M4 8 7 200 200 NDSB N=1000 L=10
M5 4 3 200 100 PDSB N=1000 L=10
M6 9 8 200 200 NDSB N=1000 L=10
M7 5 3 100 100 PDSB N=1000 L=10
M8 2 3 100 100 PDSB N=1000 L=10
D1 1 200 200
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR.
* DO NOT SET THE OUTPUT TO ZERO.
VIL 5 2 0.75
VTC 4 3 0
* THE MINIMUM VALUE OF VTC IS ADJUSTED BY TRIAL AND ERROR.
* MODEL M1, M2, M3 OPERATES IN THE ACTIVE REGION
* VDSR2 = |VDS| + |VDSAT| FOR M2
VDS 2 0 1.00
*VDSAT = LOA2 = 2.0 - 0.1 = 1.900.001 = 0.1 + 0.12 .00
*LOA2 = (2.0/VDSR2)/LOP = 0.0400/1.900 = 0.0000
.MODEL MOSFET M2 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M3 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M1 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M4 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M5 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M6 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M7 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
.MODEL MOSFET M8 LEVEL=1 KP=1000 VTO=-0.4 LAMBDA=0.0005
*OPTIONS OPTIMIZATION MODELS
.MOPT OFF=0
.OPTION VOUT=1000 M2LEVEL=1P M3LEVEL=1P
.OPT
.OFF
.VT1 VIL VIL
.REF
**** OPERATING POINT INFORMATION  VDSB= 27.000 VSSB= 27.000
      BIAS  >VOLTRMS  BIAS  >VOLTRMS  BIAS  >VOLTRMS
      VIL  =-1.0000E-01 0.0  = 0.0000E-01 0.0  = 0.0000E-01 0.0
      VIL  =-1.0000E-01 0.0  =-1.0000E-01 0.0  =-1.0000E-01 0.0
      VIL  =-7.0000E-01 0.0  = 0.0000E-01 0.0  = 0.0000E-01 0.0
      VIL  =-1.0000E-00 0.0
**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V101/V201  = -1.7000E-04
ZINVT RESISTANCE AT VIL  = 1.0000E+00
ZOUTVT RESISTANCE AT VIL  = 4.7000E+00

```

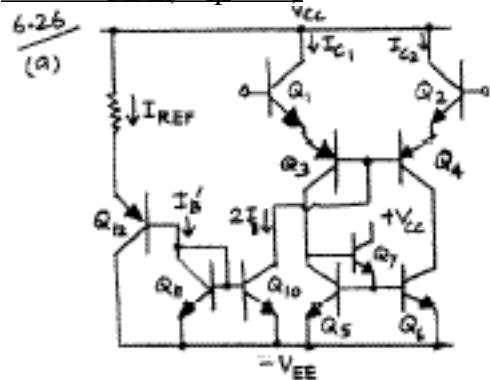Problem 4 – (10 points)

$$I_{c_1} = I_{c_2} = 10 \text{ mA} \quad \beta_{pnp} = 50$$

$$I_B = \frac{I_{c_1}}{\beta_{pnp}} \quad \therefore 2I_B = 0.39 \text{ mA} \approx I'_B$$

$$1 + \beta_{pnp}$$

$$\therefore I_{REF} = (1 + \beta_{pnp}) I'_B = 20 \text{ mA}$$

TTL INPUT DATA SCHEME (A)

VDD	100	2	10
VBE	200	0	-15
IREF	100	1	200
Q1	100	0	10
Q2	100	0	15
Q3	100	0	10
Q4	100	0	10
Q5	100	0	10
Q6	100	0	10
Q7	100	0	10
Q8	100	0	10
Q9	100	0	10
Q10	100	0	10
Q11	100	0	10
Q12	100	0	10
Q13	100	0	10
Q14	100	0	10

* WITH VDC = -12.6 V,
 * VCEO = VDC - VBE1 - |VBE2| = (-12.6)
 * = -12.6 - 0.6 - 0.6 + 15 = 1.2 V
 * THIS IS NEEDED TO OPERATE Q11 IN THE FORWARD-ACTIVE REGION.

VDC = 0

VII = 0

VII = -12.6

VII = -12.6 AC 1

.MODEL PNP NPN BF=250 IS=2E-15

.MODEL PNP NPN BF=250 IS=2E-15

.OPTION NOISE NOISE0

.WIDTH 0.07=10

.OP

* VOUT IS USED TO MEASURE THE DC SHORT CIRCUIT OUTPUT

* CURRENTS TO FIND IR

* THE DC VALUE OF VOUT WAS GIVEN IN THE PROBLEM STATEMENT.

VOUT = 10 100 1.6

.AC DBO 1 1 10


.PRINT AC DC(VOUT) DC(VOUT)

* THE TRANSCONDUCTANCE CAN ALSO BE MEASURED BY MEASURING
 * THE VOLTAGE SWING CONNECTED AT THE OUTPUT AND THE
 * DC ANALYSIS ABOVE, FINDING THE VOLTAGE GAIN AND OUTPUT
 * VOLTAGE SWING & IT IS SIMPLY AN OPERATING POINT
 * AND CHARACTERISTICS = (VOLTAGE GAIN/OUTPUT RESISTANCE)
 * THE RESULT IS VDC = 1.73624/0.23737 = 1188.5 mV
 * DC VDC = VDC

*** OPERATING POINT INFORMATION TMIN= -27.000 TMAX= 27.000
 * node *voltage node *voltage node *voltage
 * 0.0 = -2.1820E-01 0.1 = -1.4530E-01 0.2 = -1.3700E-01
 * 0.1 = -2.1820E-01 0.2 = -1.4530E-01 0.3 = -1.3500E-01
 * 0.2 = -2.1820E-01 0.3 = -1.4530E-01 0.1 = -1.4440E-01
 * 0.3 = -2.1820E-01 0.1 = -1.4530E-01 0.2 = -1.3600E-01

***** BIPOLAR JUNCTION TRANSISTORS

BIPOLAR
 ELEMENT Q1-Q2 0.125 0.024 0.025
 MODEL 0.025V 0.000V 0.000 0.000
 IB 3.9458E-04 3.9458E-04 -3.9458E-04 -3.9458E-04
 IC 3.9458E-04 -3.9458E-04 -3.9458E-04 3.9458E-04
 VBE 3.5338E-01 3.5338E-01 -3.5338E-01 3.5338E-01
 VCE 3.8138E-01 3.8138E-01 -3.8138E-01 3.8138E-01
 VBC -3.7938E-01 -3.7938E-01 3.7938E-01 -3.7938E-01
 VE -3.5938E-01 -3.5938E-01 3.5938E-01 3.5938E-01
 POWER 3.7773E-04 3.7773E-04 3.7773E-04 3.7773E-04
 ISIDEA 3.5828E-01 3.5828E-01 4.9128E-01 3.5828E-01
 ID 3.6133E-04 3.6133E-04 3.7938E-04 3.7938E-04
 IR 4.5555E-05 4.5555E-05 1.3328E-05 1.3328E-05
 IA 0.0 0.0 0.0 0.0
 IO 3.5238E-13 3.5238E-13 3.8423E-14 3.8423E-13
 ISIDEAC 3.5098E-01 3.5098E-01 4.9128E-01 3.5098E-01

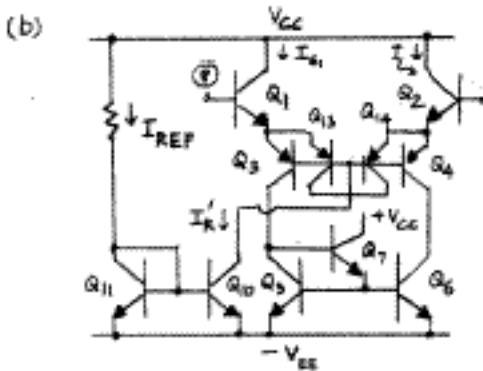

$$I_{c_1} = I_{c_2} = 10 \text{ mA}$$

$$I_{E_3} = I_{E_{13}} = I_{E_{14}} = I_{E_4} \approx \frac{I_{c_1}}{2} = 5 \text{ mA}$$

$$I_R' = 2 |I_{c_3}| + 4 |I_{B_{13}}|$$

$$= 2 \left(\frac{5 \text{ mA}}{1+50} \right) \cdot 50 + 4 \cdot \left(\frac{5 \text{ mA}}{1+50} \right)$$

$$= 10.2 \text{ mA} = I_{REF}$$

Problem 4 – Continued


```

***** REPORTS 0:04 0:07 0:013 0:013 0:013
ELEMENTS 0:009 0:009 0:009 0:009 0:009
MODEL 0:009 0:009 0:009 0:009 0:009
IB 3.8603e-05 3.8548e-05 3.8548e-05 3.8539e-05 3.8539e-05
IC 9.1999e-05 7.7102e-05 7.7102e-05 7.6908e-05 7.6908e-05
VC 5.9320e-01 4.2820e-01 4.2820e-01 4.5590e-01 4.5590e-01
VBE 1.2400e-05 3.8448e-01 3.8448e-01 6.6590e-01 6.6590e-01
VBC 4.3448e-05 4.3448e-01 4.3448e-01 6. 6.6590e-01
VB 1.3448e-01 4.3448e-01 4.3448e-01 1.4510e-01 1.4510e-01
POWER 1.8660e-05 3.3240e-05 3.3240e-05 3.4770e-05 3.4770e-05
BTFAC 3.5599e-03 3.5599e-03 3.5599e-03 3.5599e-03 3.5599e-03
IB 7.7102e-05 3.8548e-05 3.8548e-05 1.5548e-05 1.5548e-05
IC 9.1999e-05 7.7102e-05 7.7102e-05 7.6908e-05 7.6908e-05
VC 5.9320e-03 4.2820e-03 4.2820e-03 4.5590e-03 4.5590e-03
VBE 1.2400e-05 3.8448e-01 3.8448e-01 6.6590e-01 6.6590e-01
VBC 4.3448e-05 4.3448e-01 4.3448e-01 6. 6.6590e-01
VB 1.3448e-01 4.3448e-01 4.3448e-01 1.4510e-01 1.4510e-01
POWER 1.8660e-05 3.3240e-05 3.3240e-05 3.4770e-05 3.4770e-05
BTFAC 3.5599e-03 3.5599e-03 3.5599e-03 3.5599e-03 3.5599e-03
***** AC ANALYSIS ***** TRIM= 27.000 TEMP= 27.000
      1 VOUT 1 VIN 2 VOUT
      VOUT VOUT
  1.0000e+00 1.0000e-04 4.1740e-11
  1.0000e+01 1.0000e-09 4.1740e-11

***** DC INPUT LOADS ***** (1)
*****+
VCC 100 0 10
VBE 100 0 -10
IBUF 100 4 10.00
Q1 100 0 10 0.00
Q2 100 9 11 0.00
Q3 11 8 10 0.00
Q4 10 8 11 0.00
Q5 11 10 10 0.00
Q6 10 11 10 0.00
Q7 100 10 11 0.00
Q8 4 0 10 0.00
Q9 0 4 10 0.00
+ REMOVE Q12 FROM THE CIRCUIT.
+ IT WAS ONLY NEEDED FOR PART (A).
Q10 100 100 100 PNP
Q11 4 4 10 PNP
Q12 4 4 11 PNP
+ NOTE VBC = -22.4 V.
+ VCB10 = VBC - VBE10 = (10000) = -2.4 V.
+ -12.4 + -2.4 = -14.8 + 10 = -1.2 V
+ THIS IS EQUATED TO VBE10 IN THE FORWARD-BIASING REGION.
+ THIS IS EQUATED TO VBE10 IN THE FORWARD-BIASING REGION.
V11 0 0 -12.4
V12 0 0 -12.4 AC 1
.AC NWE 100 100 10e-12
.AC NPF 100 100 10e-12
/OPTIONS REPORT=NODC
/PRINT OUT=0
.OI
+ VOUT IS USED TO DETERMINE THE AC SHORT CURRENT OUTPUT
+ CURRENT TO FIND IC.
+ THE DC VALUE OF VOUT WAS GIVEN IN THE PROBLEM STATEMENT.
VOUT 10 100 1.0
+ AC ONE = 1.10
+ PRINT AC (VBE10) IF (VBE10)

***** REPORTS 0:04 0:07 0:013 0:013 0:013
ELEMENTS 0:009 0:009 0:009 0:009 0:009
MODEL 0:009 0:009 0:009 0:009 0:009
IB 3.8603e-05 3.8548e-05 3.8548e-05 3.8539e-05 3.8539e-05
IC 9.1999e-05 7.7102e-05 7.7102e-05 7.6908e-05 7.6908e-05
VC 5.9320e-01 4.2820e-01 4.2820e-01 4.5590e-01 4.5590e-01
VBE 1.2400e-05 3.8448e-01 3.8448e-01 6.6590e-01 6.6590e-01
VBC 4.3448e-05 4.3448e-01 4.3448e-01 6. 6.6590e-01
VB 1.3448e-01 4.3448e-01 4.3448e-01 1.4510e-01 1.4510e-01
POWER 1.8660e-05 3.3240e-05 3.3240e-05 3.4770e-05 3.4770e-05
BTFAC 3.5599e-03 3.5599e-03 3.5599e-03 3.5599e-03 3.5599e-03
***** AC ANALYSIS ***** TRIM= 27.000 TEMP= 27.000
      1 VOUT 1 VIN 2 VOUT
      VOUT VOUT
  1.0000e+00 1.0000e-05 8.4100e-11
  1.0000e+01 1.0000e-05 8.4100e-11

```

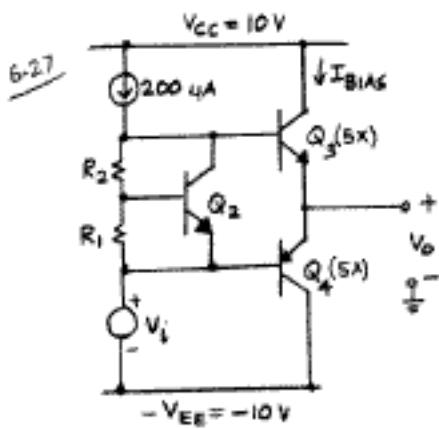Problem 5 – (10 points)

Neglect current flow through R_1 and R_2 from 200 μ A source.

$$\therefore I_{C2} = 200 \text{ } \mu\text{A}, V_{BE2} = V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$\begin{aligned} V_{BE4} + V_{BE3} &= V_{BE2} + \frac{V_{BE2} \times R_2}{R_1} \\ &= \frac{V_T}{R_1} (R_1 + R_2) \ln \frac{I_{C2}}{I_{S2}} \\ &= V_T \ln \left(\frac{I_{C3} |I_{C4}|}{I_{S3} I_{S4}} \right) \end{aligned}$$

Areas of Q_3, Q_4 are 5 times of Q_1 and Q_2 . Therefore,

$$I_{S1} = I_{S2} = 10^{-15} \text{ A} = I_S$$

$$I_{S3} = I_{S4} = 5 \times 10^{-15} \text{ A} = 5 I_S$$

$$V_T \ln \left(\frac{I_{BIAS}}{25 I_S^2} \right) = V_T \left(1 + \frac{R_2}{R_1} \right) \ln \left(\frac{I_{C2}}{I_S} \right)$$

$$\begin{aligned} \therefore I_{BIAS} &= 5 I_S \left(\frac{I_{C2}}{I_S} \right)^{\frac{1}{2} \left(1 + \frac{R_2}{R_1} \right)} \\ &= 5 \left(I_{C2} \right)^{\frac{1}{2} \left(1 + \frac{R_2}{R_1} \right)} \left(I_S \right)^{\frac{1}{2} \left(1 - \frac{R_2}{R_1} \right)} \end{aligned} \rightarrow ①$$

$$\frac{R_2}{R_1} = \frac{2 \ln \left(\frac{I_{BIAS}}{5 I_S} \right)}{\ln \left(\frac{I_{C2}}{I_S} \right)} - 1$$

$$I_{BIAS} = 50 \text{ mA}, I_S = 10^{-15} \text{ A}, I_{C2} = 200 \text{ mA}$$

$$\therefore \frac{R_2}{R_1} = 0.77$$

From ①, If we choose $\frac{R_2}{R_1} = 1$

$$\text{then } I_{BIAS} = 5 (I_{C2})^{\frac{1}{2} (1 + \frac{R_2}{R_1})}$$

$$= 1000 \text{ mA} = 1 \text{ mA}$$

and I_{BIAS} is independent of temperature. In general, if $\frac{R_2}{R_1} \neq 1$ then I_{BIAS} is dependent on temperature because I_S depends on temperature.

Problem 5 – Continued

```

TAC OUTPUT-STAGE BIAS SCHEME
* BALANCE TO CHECK BAND CROSSOVERS
*****  

VDS 180 0 10  

VBS 200 0 -10  

DCEP 100 3 2000  

Q1 3 4 1 200  

Q2 100 3 6 200 5  

Q4 200 8 6 200 5  

RL 4 5 100K  

R2 3 4 77K  

V1 3 200 0.004  

.MODEL NPN PNP KP=10000 IB=0.0001  

.MODEL PNP NPN KP=10000 IB=0.0001  

.OPTIONS NOVAR BIAS  

.WINDE OUT=0  

.OV  

.IND  

**** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -15.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 7.7488-01 0:14 + 1.4718-01 0:15 = -5.3408-01
+014 = 9.1128-01 0:100 + 1.8008-01 0:100 = -1.3008-01
***** BIPOLAR JUNCTION TRANSISTORS
SUBCIR
ELEMENT 0:03 0:04 0:04
MODEL 0:0000 0:0000 0:0000
IB 7.6508-07 3.3148-03 -1.9358-06
IC 1.8138-04 7.7408-05 -1.4978-03
VBS 7.4578-03 -1.8708-02 -1.3108-01
VCE 1.3748-00 9.3088+00 -1.0008+01
BETAD 2.5008+02 2.5008+02 5.0008+01
***** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -15.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 7.1808-01 0:14 + 1.1558-01 0:15 = -5.3408-01
+014 = 8.1258-02 0:100 + 1.3008+01 0:100 = -1.3008+01
***** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -5.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 7.1808-01 0:14 + 1.1558-01 0:15 = -5.3408-01
+014 = 8.1258-02 0:100 + 1.3008+01 0:100 = -1.3008+01
***** BIPOLAR JUNCTION TRANSISTORS
SUBCIR
ELEMENT 0:02 0:03 0:04
MODEL 0:0000 0:0000 0:0000
IB 1.9518-04 3.0508-09 -5.0008-09
IC 1.8138-04 1.0008-05 -5.0008-05
VBS 6.7218-05 3.0508-03 -5.0008-01
VCE 1.3118-08 1.0008-01 -5.0008+00
BETAD 1.5008+02 2.5008+02 5.0008+00
***** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -5.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 6.5858-01 0:14 + 1.3008-02 0:15 = -5.3408-01
+014 = 8.3278-02 0:100 + 1.0008+01 0:100 = -1.3008+01
TAC OUTPUT-STAGE BIAS SCHEME
* SET OF 10 BIAS VALUES AND 100 TEMPERATURE SWING
*****  

VDS 180 0 10  

VBS 200 0 -10  

DCEP 100 3 2000  

Q1 3 4 1 200  

Q2 100 3 6 200 5  

Q4 200 8 6 200 5  

RL 4 5 100K  

R2 3 4 77K  

V1 3 200 0.004  

.MODEL NPN PNP KP=1000 IB=0.0001  

.MODEL PNP NPN KP=1000 IB=0.0001  

.OPTIONS NOVAR BIAS  

.WINDE OUT=0  

.OV  

.IND  

**** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -5.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 8.9708-01 0:14 + 2.1208-01 0:15 = -5.3408-01
+014 = 1.4978-01 0:100 + 1.0008+01 0:100 = -1.0008+01
***** BIPOLAR JUNCTION TRANSISTORS
SUBCIR
ELEMENT 0:02 0:03 0:04
MODEL 0:0000 0:0000 0:0000
IB 7.6408-07 1.3318-05 -6.4408-07
IC 1.9108-04 3.3518-03 -3.3328-05
VBS 8.3808-05 3.4608-03 -1.4878-01
VCE 1.4318-08 8.4808-02 -1.0158-01
BETAD 2.5008+02 2.5008+02 5.0008+01
***** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -55.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 8.9708-01 0:14 + 2.1208-01 0:15 = -5.3408-01
+014 = 1.4978-01 0:100 + 1.0008+01 0:100 = -1.0008+01
***** BIPOLAR JUNCTION TRANSISTORS
SUBCIR
ELEMENT 0:02 0:03 0:04
MODEL 0:0000 0:0000 0:0000
IB 7.6408-07 1.3318-05 -6.4408-07
IC 1.9108-04 3.3518-03 -3.3328-05
VBS 8.3808-05 3.4608-03 -1.4878-01
VCE 1.4318-08 8.4808-02 -1.0158-01
BETAD 2.5008+02 2.5008+02 5.0008+01
***** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -25.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 8.3758-01 0:14 + 1.8908-01 0:15 = -5.3408-01
+014 = 1.2508-01 0:100 + 1.0008+01 0:100 = -1.0008+01
***** BIPOLAR JUNCTION TRANSISTORS
SUBCIR
ELEMENT 0:02 0:03 0:04
MODEL 0:0000 0:0000 0:0000
IB 7.6508-07 2.3808-07 -1.8208-06
IC 1.9138-04 5.2158-05 -5.3348-09
VBS 7.3508-05 7.5408-04 -7.1608-01
VCE 1.4338-08 9.8708-02 -1.0008+01
BETAD 2.5008+02 2.5008+02 5.0008+01
***** OPERATING POINT INFORMATION THRM= 27.000 TEMP= -45.000
NODE 1-VOLTAGE NODE 2-VOLTAGE NODE 3-VOLTAGE NODE 4-VOLTAGE
+013 = 7.6508-07 2.7808-07 -4.8108-06
IC 1.9138-04 2.4408-04 -2.4978-06
VBS 6.6618-05 8.6628-01 -8.3308-01
VCE 1.3328-08 1.0008+01 -9.8008+00
BETAD 2.5008+02 2.5008+02 5.0008+01


```

Problem 5 – Continued

```
**** OPERATING POINT INFORMATION  TEMP= 27.000 TEMP= 25.000
      MODE: +VOLTMAGE      MODE: -VOLTMAGE      MODE: +VOLTAGE
+0:0 = 1.7358E-01 0:14 = -2.4882E-01 0:15 = -0.1408E-01
+0:0 = -6.1278E-02 0:150 = 1.0000E+01 0:150 = -0.3000E+01
**** BIPOLAR JUNCTION TRANSISTORS
ELEMENTS:
ELEMENT 0:0:0 0:0:1 0:0:2
MODEL 0:0:0:0 0:0:0:1 0:0:0:2
IB 1.6338E-07 1.1438E-04 -0.2138E-05
IC 1.1928E-04 3.0148E-04 -0.3448E-04
VBE 0.7108E-01 0.1000E-01 -0.2478E-01
VCE 1.0638E+00 1.0638E+01 -0.5138E+02
BETAS 2.5000E+02 2.5000E+02 0.3000E+02

**** OPERATING POINT INFORMATION  TEMP= 27.000 TEMP= 125.000
      MODE: +VOLTMAGE      MODE: -VOLTMAGE      MODE: +VOLTAGE
+0:0 = 1.5138E-01 0:14 = -0.9778E-03 0:15 = -0.1408E-01
+0:0 = -0.2398E-02 0:150 = 1.0000E+01 0:150 = -1.0000E+01
**** BIPOLAR JUNCTION TRANSISTORS
ELEMENTS:
ELEMENT 0:0:0 0:0:1 0:0:2
MODEL 0:0:0:0 0:0:0:1 0:0:0:2
IB 1.6338E-07 1.4538E-05 -0.1368E-05
IC 1.4338E-04 3.4338E-04 -0.3738E-04
VBE 0.7108E-01 0.1000E-01 -0.2748E-01
VCE 1.0638E+00 1.0638E+01 -0.3678E+02
BETAS 2.5000E+02 2.5000E+02 0.3000E+02

**** OPERATING POINT INFORMATION  TEMP= 27.000 TEMP= 125.000
      MODE: +VOLTMAGE      MODE: -VOLTMAGE      MODE: +VOLTAGE
+0:0 = 0.6338E-01 0:14 = -0.6348E-03 0:15 = -0.7608E-01
+0:0 = -1.3438E-01 0:150 = 1.0000E+00 0:150 = -1.0000E+01
**** BIPOLAR JUNCTION TRANSISTORS
ELEMENTS:
ELEMENT 0:0:0 0:0:1 0:0:2
MODEL 0:0:0:0 0:0:0:1 0:0:0:2
IB 1.6338E-07 1.7138E-04 -0.4858E-05
IC 1.4338E-04 3.3938E-04 -0.3448E-04
VBE 0.7108E-01 0.1000E-01 -0.7138E-01
VCE 1.0638E+00 1.0638E+01 -0.9738E+02
BETAS 2.5000E+02 2.5000E+02 0.3000E+02
```

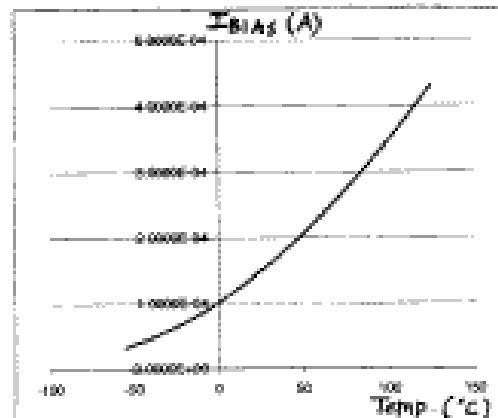

TEMP (DEG C)	I(B) = IBIAS (A)	TEMP	I(B) = IBIAS (A)
-50	0.3518E-05	45	1.0358E-01
-10	0.1028E-05	65	2.6408E-01
-10	0.1028E-05	85	3.0148E-01
5	0.1138E-04	105	3.6388E-01
15	0.1438E-04	125	4.3988E-01