


EXAMINATION NO. 2 - SOLUTIONS
(Average Score = 80/100)

Problem 1 - (25 points)

A frequency synthesizer is shown below and has the following parameters:

$$F(s) = \frac{1 + 0.01s}{s} \quad K_o = 2 \times 10^6 \text{ (rads/V)} \quad K_d = 0.8 \text{ (V/rad.)}$$
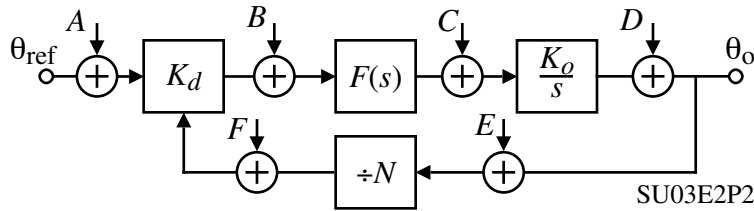
$$\beta = 2\pi \quad N = 150 \quad f_{ref} = 120 \text{ kHz}$$



- (a.) Where would you introduce the modulating voltage, v_p , if you wish to phase modulate the output of the synthesizer (A, B, C, D, E, or F)?
- (b.) What is the peak amplitude of a 1kHz ac signal needed to produce an output peak phase deviation of 0.5 radians?

Solution

- (a.) The modulating voltage should be introduced at B.
- (b.) The transfer function between the input modulating voltage and the output phase is given as,

$$\theta_o(s) = \frac{K_o}{s} F(s) \left[V_p(s) - K_d \frac{\theta_o}{N} \right] \rightarrow \theta_o(s) \left[1 + \frac{K_o K_d F(s)}{sN} \right] = \frac{K_o F(s)}{s} V_p(s)$$

$$\frac{\theta_o(s)}{V_p(s)} = \frac{K_o F(s)}{s + \frac{K_v F(s)}{N}} = \frac{K_o(1 + 0.01s)}{s^2 + \frac{0.01K_v}{N}s + \frac{K_v}{N}}$$

$$\therefore \omega_n = \sqrt{\frac{K_v}{N}} = \sqrt{\frac{1.6 \times 10^6}{150}} = 103 \text{ rads/sec. (16.4 Hz)} \quad \text{and} \quad \zeta = \frac{K_v}{100N} \sqrt{\frac{N}{K_v}} \approx 1$$

Since, $f_n \ll 1\text{kHz}$, the transfer function can be approximated as,

$$\left| \frac{\theta_o(j\omega)}{V_p(j\omega)} \right| \approx \frac{0.01K_o}{\omega} = \frac{20,000}{2000\pi} = 3.183$$

\therefore A phase deviation of 0.5 radians requires a modulating voltage of 0.5/3.183 or 0.157V


Peak deviation of the modulating voltage = 0.157V

Problem 2 - (25 points)

(a.) Find the transfer function of the filter shown assuming an ideal op amp.

(b.) Sketch a Bode plot for the magnitude of this filter if $R_1 = R_2 = 10\text{k}\Omega$ and $C_2 = 0.159\mu\text{F}$.

(c.) For the values in part (b.), find the single sideband spur at a reference frequency of 25 kHz if the op amp has an input offset current of $I_{os} = 50\text{nA}$ and an input offset voltage of $V_{io} = 100\mu\text{V}$. Assume that the spurious deviation due to the offset voltage at 25 kHz can be expressed as $\theta_d = 100V_{pm}$, where V_{pm} is the phase modulation caused by the offset voltage of the filter.

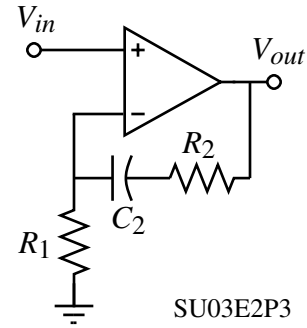

Solution


(a.) The transfer function assuming an ideal op amp can be found as,

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{Z_1 + Z_2}{Z_1} = \frac{R_1 + R_2 + (1/sC_2)}{R_1} = \frac{s(R_1 + R_2)C_2 + 1}{sC_2R_1}$$

(b.) If $R_1 = R_2 = 10\text{k}\Omega$ and $C_2 = 0.159\mu\text{F}$, then the filter transfer function becomes,

$$F(s) = \frac{s(R_1 + R_2)C_2 + 1}{sC_2R_1} = \frac{s0.00318 + 1}{0.00159s} = \frac{\frac{s}{314.5} + 1}{\frac{s}{628.9}}$$

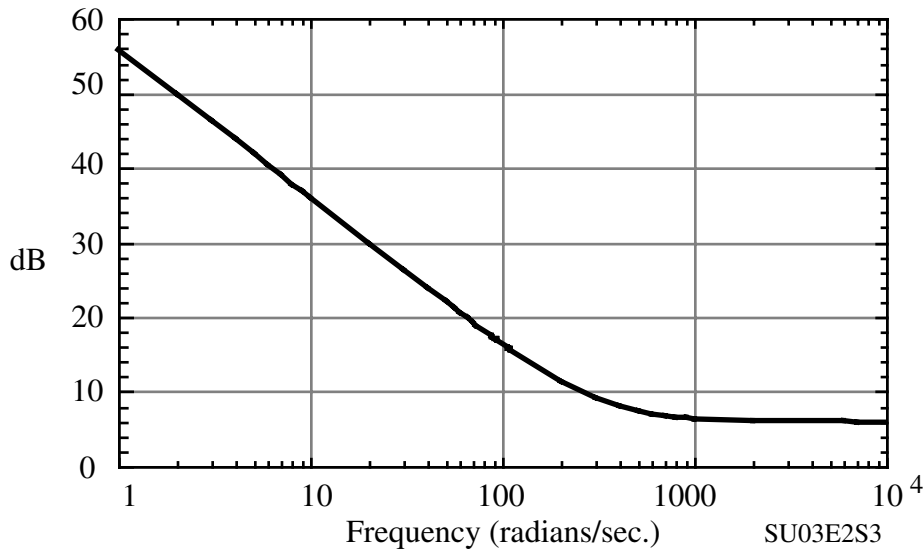The sketch for the magnitude of this transfer function is below.




(c.) First, find the offset voltage at the input of the filter, V_{OS} , from the figure shown.

$$V_{OS} = V_{io} + I_{os}R_1 = 100\mu\text{V} + 50\text{nA} \cdot 10\text{k}\Omega$$

$$V_{OS} = 0.1\text{mV} + 0.5\text{mV} = 0.6\text{mV} = 600\mu\text{V}$$

$$\therefore \theta_d = 100V_{pm} = 100(2 \cdot V_{OS}) = 0.12$$

$$SSB = 20 \log_{10}(\theta_d/2) = \underline{\underline{-24.44 \text{ dBc}}}$$

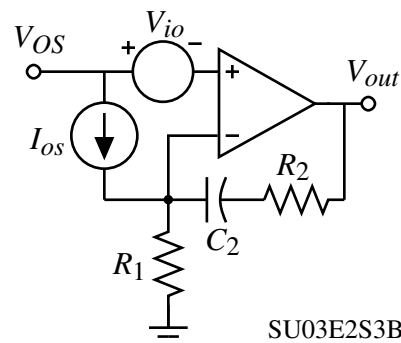


Problem 3 - (25 points)


Find the oscillation frequency, ω_{osc} and the value of $g_m r_{ds}$ necessary to oscillate in terms of L , C_1 , and C_2 for the LC oscillator shown.

Solution

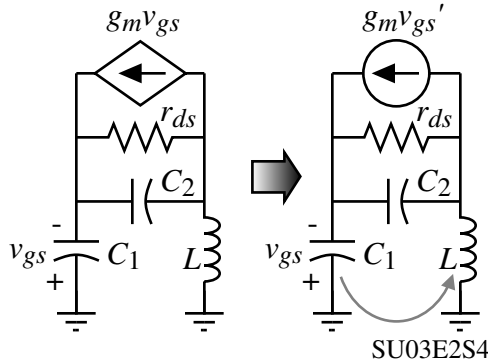The small-signal model for solving this problem is shown below.



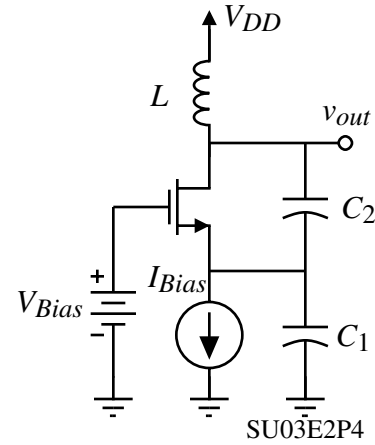Note that the current from the independent source has two paths. One is through the parallel combination of r_{ds} and C_2 , and the other is through C_1 and L .



The open-loop gain, V_{gs}'/V_{gs} can be found as,

$$\frac{V_{gs}(s)}{V_{gs}'(s)} = - \left(\frac{1}{sC_1} \right) \left[\frac{g_m [r_{ds} \parallel (1/sC_2)]}{sL + (1/sC_1) + r_{ds} \parallel (1/sC_2)} \right] = - \left(\frac{1}{sC_1} \right) \left[\frac{g_m \left(\frac{r_{ds}}{sC_2 r_{ds} + 1} \right)}{\frac{s^2 L C_1 + 1}{sC_1} + \frac{r_{ds}}{sC_2 r_{ds} + 1}} \right]$$

$$LG(s) = \frac{V_{gs}(s)}{V_{gs}'(s)} = - \left[\frac{g_m r_{ds}}{(s^2 L C_1 + 1)(sC_2 r_{ds} + 1) + sC_1 r_{ds}} \right]$$

$$= - \left[\frac{g_m r_{ds}}{s^3 L C_1 C_2 r_{ds} + s^2 L C_1 + s r_{ds} (C_1 + C_2) + 1} \right]$$

$$LG(j\omega) = \left[\frac{-g_m r_{ds}}{1 - \omega^2 L C_1 + j\omega [r_{ds}(C_1 + C_2) - \omega^2 L C_1 C_2 r_{ds}]} \right] = 1 + j0$$

$$\therefore \omega_{osc}^2 = \frac{C_1 + C_2}{L C_1 C_2} \rightarrow \boxed{\omega_{osc} = \frac{1}{\sqrt{L C_1 C_2 / (C_1 + C_2)}}}$$

At the oscillation frequency, we can write that,

$$-g_m r_{ds} = 1 - \omega_{osc}^2 L C_1 = 1 - \frac{C_1 + C_2}{C_2} = 1 - 1 - \frac{C_1}{C_2} = -\frac{C_1}{C_2}$$

$$\therefore \boxed{g_m r_{ds} = \frac{C_1}{C_2}}$$

Problem 4 – (25 points)

A model for single sideband noise using the time-invariant theory is given by

$$\mathcal{L}\{f_m\} = 10 \log \left\{ \frac{2FkT}{P_s} \left[1 + \frac{1}{4Q^2} \left(\frac{f_o}{f_m} \right)^2 \right] \left(1 + \frac{f_c}{f_m} \right) \right\}$$

- (a.) Describe each term in this equation and give the units of the term.
 (b.) If $F = 2\text{dB}$, what is the noise floor if the carrier power is 10 dBm at room temperature (27°C) and $k = 1.381 \times 10^{-23}$ Joules/ K° ?
 (c.) Make an approximate sketch of $\mathcal{L}\{f_m\}$ in dBc as a function of $\log_{10}(f_m)$ and identify the various regions.

Solution

(a.)

F = the noise figure or factor depending upon terminology. It is unitless.

k = Boltzmann's constant and is equal to 1.381×10^{-23} Joules/ K° .

T = temperature in $^\circ\text{K}$

P_s = power in the carrier in watts.

Q = open-loop Q of the oscillator. It is unitless.

f_o = carrier frequency in Hz.

f_m = deviation frequency from the carrier in Hz.


f_c = corner frequency in Hz associate where the $1/f$ noise is no longer significant.

- (b.) The noise floor is $10 \log \left(\frac{2FkT}{P_s} \right)$. We need to perform some "preprocessing" first before using the equation.

$$F = 2\text{dB} \rightarrow F = 10^{2/10} = 1.585 \quad \text{and} \quad P_s = 10\text{dBm} \rightarrow P_s = 10^{10/10} = 10\text{mW}$$

$$\mathcal{L}\{f_m\} = 10 \log \left(\frac{2 \cdot 1.585 \cdot 1.381 \times 10^{-23} \cdot 300}{10 \times 10^{-3}} \right) = -178.8 \text{ dBc}$$

(c.)

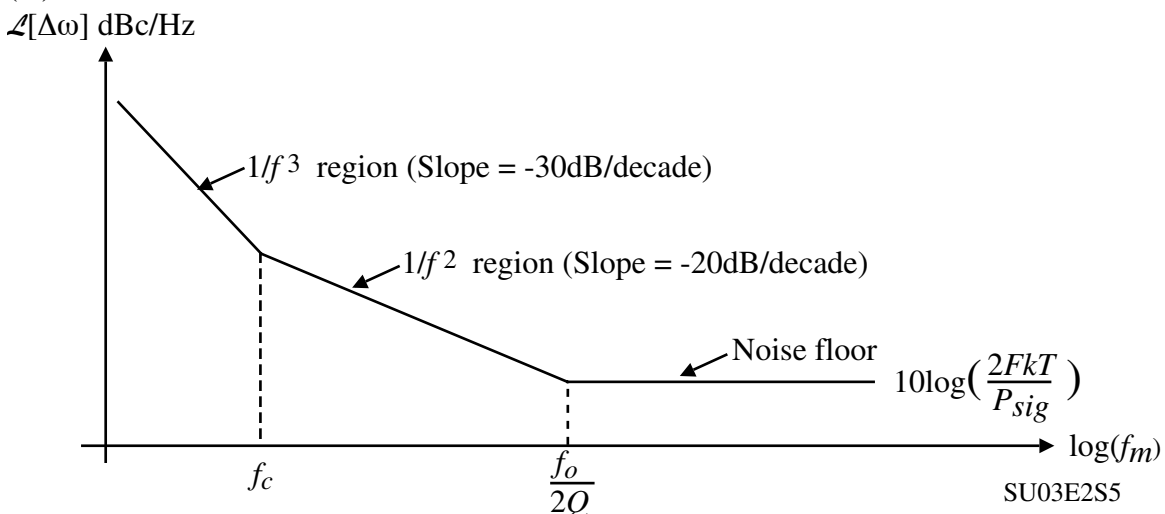

SU03E2S5