

# LECTURE 050 – LINEAR PHASE LOCK LOOPS - I

## (References [2])

### INTRODUCTION TO PHASE LOCK TECHNIQUES

#### Introduction

Objective:

Understand the principles and applications of phase locked loops using integrated circuit technology with emphasis on CMOS technology.

Organization:

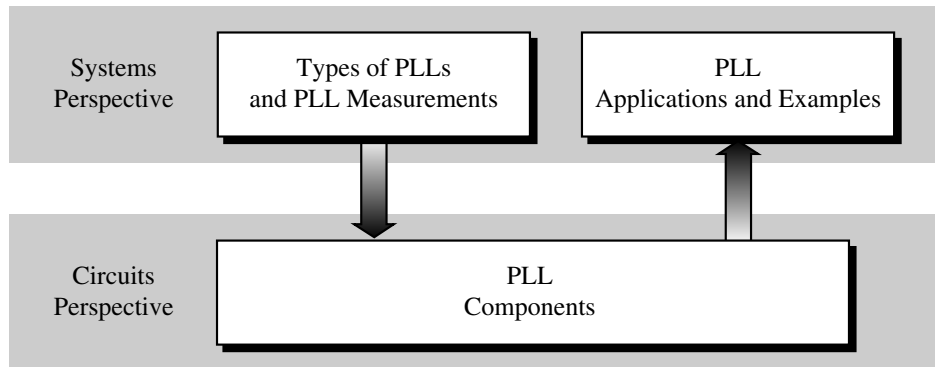


Fig. 050-01

#### Introduction - Continued

Outline:

- Operating Principles of PLLs
- Classification of PLL Types


Pertinent References:

1. F.M Gardner, *Phaselock Techniques*, 2<sup>nd</sup> edition, John-Wiley & Sons, Inc., New York, 1979.
2. B. Razavi (ed.), *Monolithic Phase-Locked Loops and Clock Recovery Circuits*, IEEE Press, 1997.
3. R.E. Best, *Phase-Locked Loops: Design, Simulation, and Applications*, 4<sup>th</sup> edition, McGraw-Hill, 1999.
4. Recent publications of the *IEEE Journal of Solid-State Circuits*.

## OPERATING PRINCIPLES OF PLLs

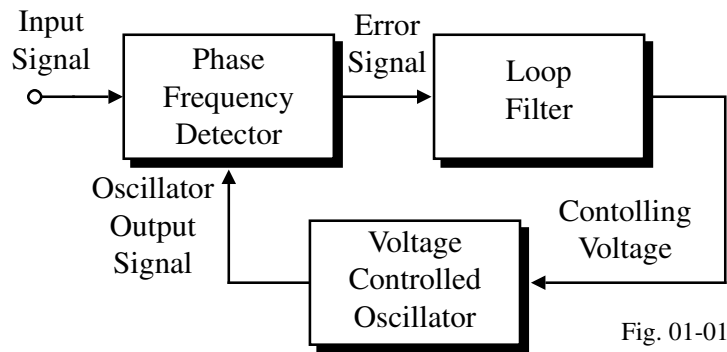
### What is a PLL?

A PLL contains three basic components as shown below:



- Phase/frequency detector determines the difference between the phase or frequency of two signals
- The loop filter removes the high-frequencies from the voltage-controlled oscillator (VCO) controlling voltage
- The VCO produces an output frequency controlled by a voltage

### More Detailed PLL Block Diagram

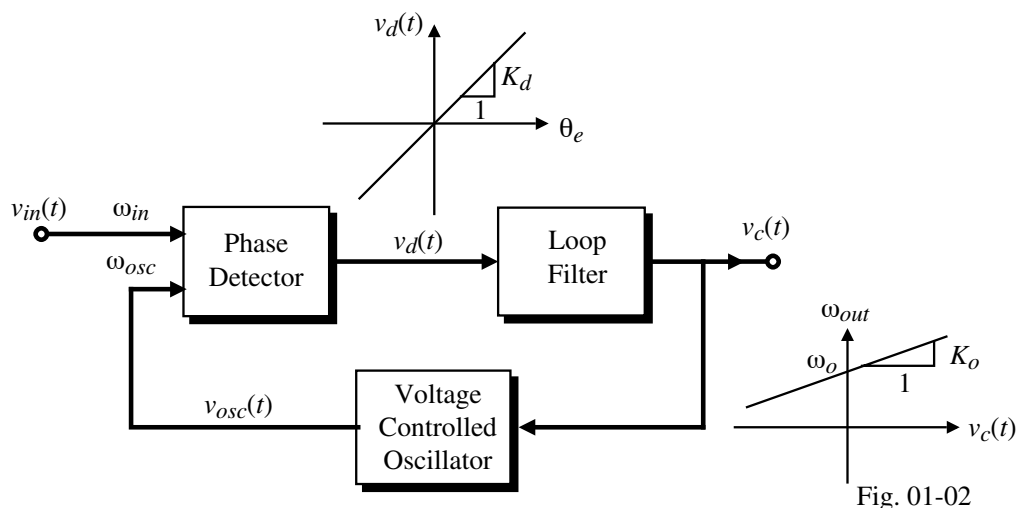

$v_{in}(t)$  – The input or reference signal

$\omega_{in}$  – The radian frequency of the input signal

$v_{osc}(t)$  – The output of the VCO

$\omega_{osc}$  – The radian frequency of the VCO

$v_d(t)$  – The detector output voltage =  $K_d\theta_e$

$\theta_e$  – Phase error between  $v_{in}(t)$  and  $v_{out}(t) = \theta_{in} - \theta_{osc}$

$v_c(t)$  – The output voltage of the loop filter and the control voltage for the VCO

## The Phase Detector and VCO in more Detail

Phase Detector:

$$v_d(t) = K_d \theta_e = K_d (\theta_{in} - \theta_{osc})$$

where  $K_d$  is the gain of the phase detector.

The units of  $K_d$  are volts/radians or simply volts assuming all phase shifts are in radians and not degrees.

Voltage Controlled Oscillator:

$$\omega_{osc} = \omega_o + K_o v_c(t)$$

where  $K_o$  is the VCO gain and  $\omega_o$  is the free-running radian frequency.

The units of  $K_o$  are rads/sec·V or simply (sec·V)<sup>-1</sup> assuming all phase shifts are in radians and not degrees.

## PLL Operation

Locked Operation:

- The loop is *locked* when the frequency of the VCO is exactly equal to the average frequency of the input signal.
- If the input signal has noise, the phase locked loop will remove much of the noise on the input signal.
- To maintain the control voltage needed for locked conditions, it is generally necessary for the output of the phase/frequency detector to be nonzero.

Unlocked Operation:

- The VCO runs at a frequency called the *free running frequency*,  $\omega_o$ , which corresponds to no control voltage.
- The capture process is the means by which the loop goes from unlocked, free-running state to that of the locked state.

## Transient Response of the PLL

Assume the input frequency is increased by an amount  $\Delta\omega$ .

- 1.)  $\omega_{in}$  increases by  $\Delta\omega$  at  $t_o$ .
- 2.) The input signal leads the VCO and  $v_d$  begins to increase.
- 3.) After a delay due to the loop filter, the VCO increases  $\omega_{osc}$ .
- 4.) As  $\omega_{osc}$  increases, the phase error reduces.
- 5.) Depending on the loop filter, the final phase error will be reduced to zero or to a finite value.

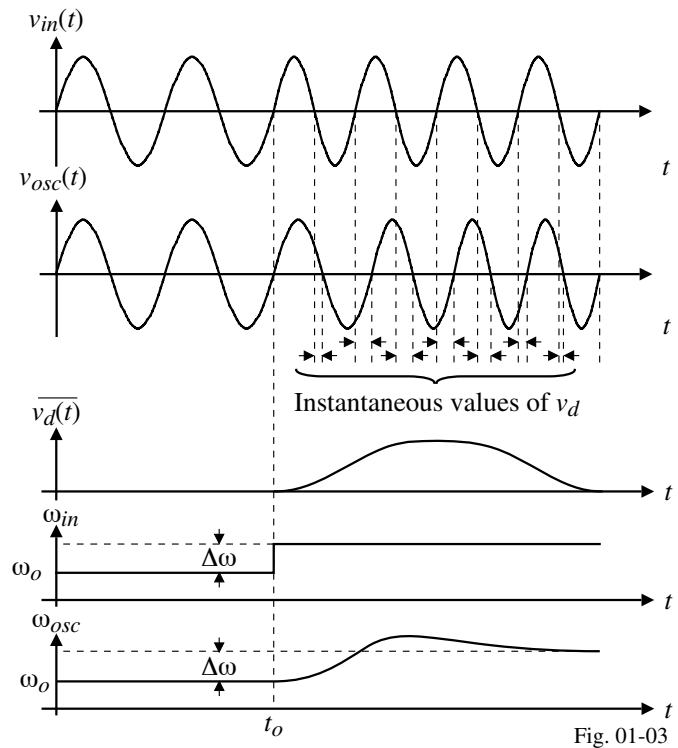


Fig. 01-03


## CLASSIFICATION OF PLL TYPES

### Types of PLLs


PLL Type	Phase Detector	Loop Filter	Controlled Oscillator
Linear PLL (LPLL)	Analog multiplier	RC passive or active	Voltage
Digital PLL (DPLL)	Digital detector	RC passive or active	Voltage
All digital PLL (ADPLL)	Digital detector	Digital filter	Digitally controlled
Software PLL (SPLL)	Software multiplier	Software filter	Software oscillator

The digital PLL (DPLL) has been the mainstay of most PLLs and is called the “classical” digital PLL.

## The Linear PLL (LPLL)

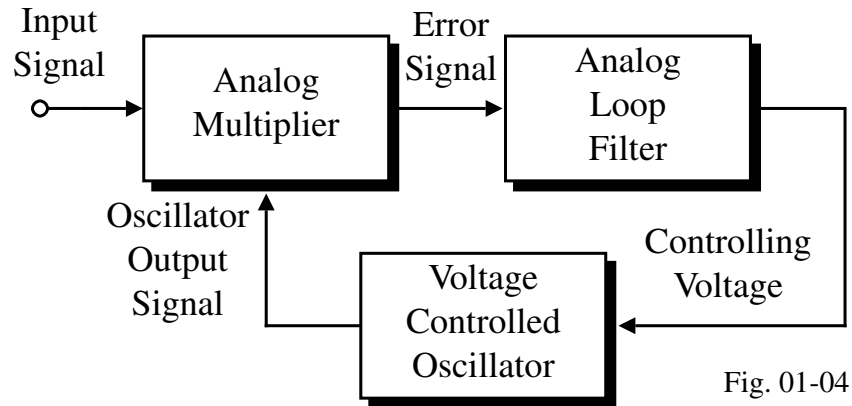

## The Digital PLL (DPLL)

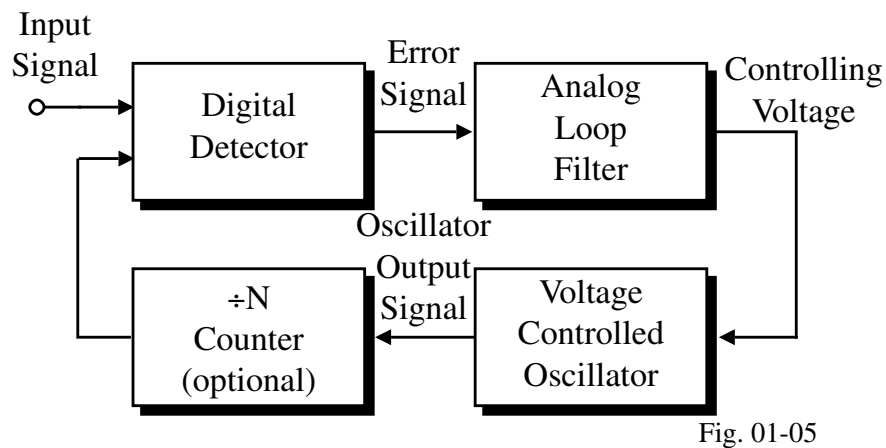

## The All-Digital PLL (ADPLL)

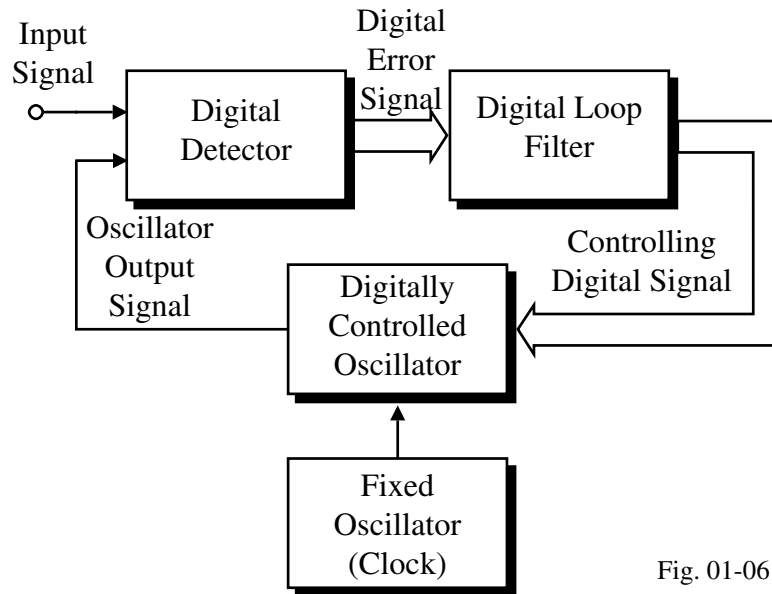


Fig. 01-06

## The Software PLL (SPLL)

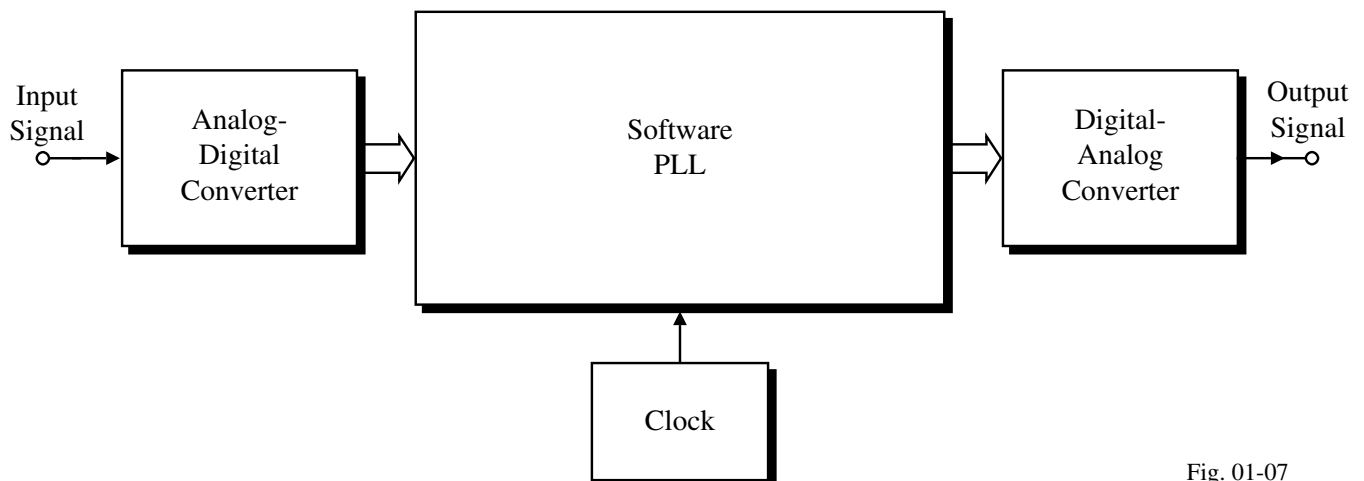


Fig. 01-07

## SYSTEMS PERSPECTIVE OF PLLs

### Outline

- Linear PLL
- Classical Digital PLL
- All-Digital PLL
- Measurement of PLLs

### Roadmap

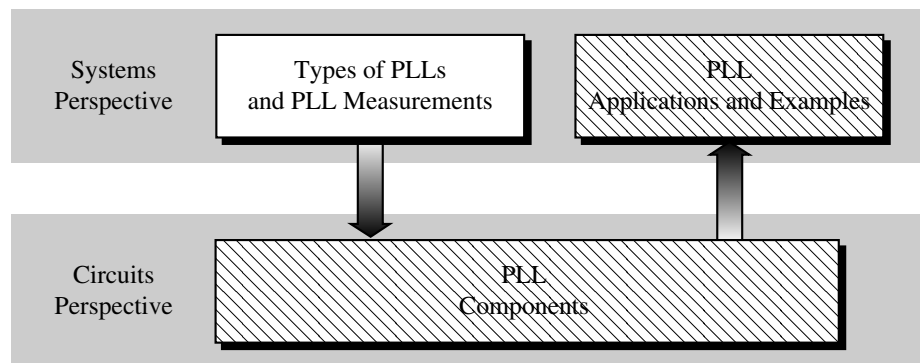


Fig. 050-02

## LINEAR PHASE LOCKED LOOPS

### Outline

- PLL Components
- Locked State
- Order of the LPLL System
- The Acquisition Process - Unlocked State
- Noise in the LPLL
- LPLL System Design
- Simulation of LPLLs

## PLL COMPONENTS

### Building Block of the LPLL

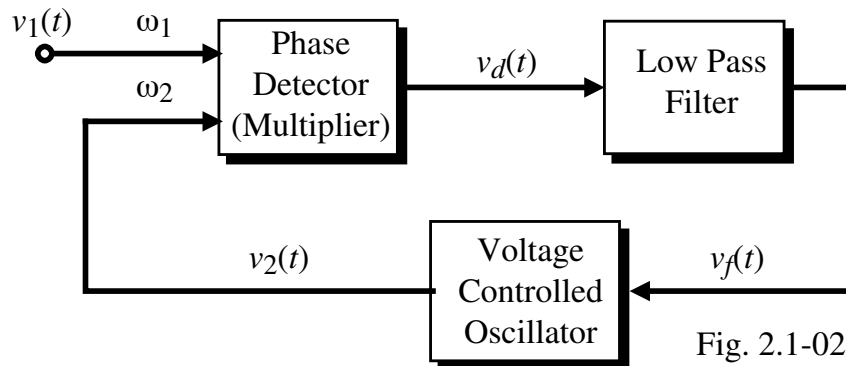


Fig. 2.1-02

$v_1(t)$  = Input signal, generally sinusoidal

$v_2(t)$  = VCO output signal, may be sinusoidal or square wave

$v_d(t)$  = Phase detector output signal

$v_f(t)$  = Loop filter output signal and controlling signal to the VCO

$\omega_1$  = Frequency of the input signal

$\omega_2$  = Frequency of the VCO

## Loop Filters

In the PLL, there are many high frequencies including noise that must be removed by the use of a low pass filter in order to achieve optimum performance.

Types of Loop Filters:

1.) Passive lag filter (*lag-lead*)

$$F(s) = \frac{1 + s\tau_2}{1 + s(\tau_1 + \tau_2)} \quad \text{where} \quad \tau_1 = R_1C \quad \text{and} \quad \tau_2 = R_2C$$


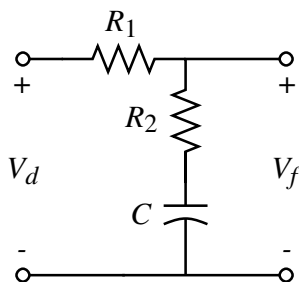


Fig. 2.1-03

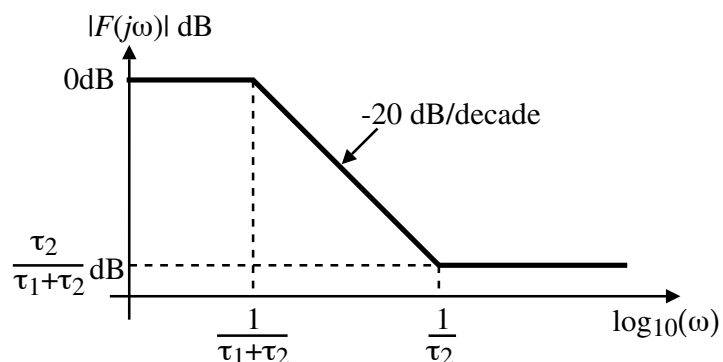

Pole is at  $1/(\tau_1 + \tau_2)$  and the zero at  $1/\tau_2$ .

- Since the pole is smaller than the zero, the filter is lag-lead
- Passive filters should have no amplitude nonlinearity



## Loop Filters - Continued

### 2.) Active Lag filter

$$F(s) = K_a \frac{1 + s\tau_2}{1 + s\tau_1} \quad \text{where} \quad \tau_1 = R_1 C_1, \quad \tau_2 = R_2 C_2 \quad \text{and} \quad K_a = -\frac{C_1}{C_2}$$


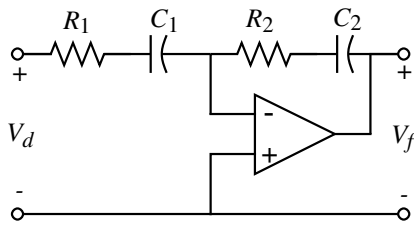


Fig. 2.1-04

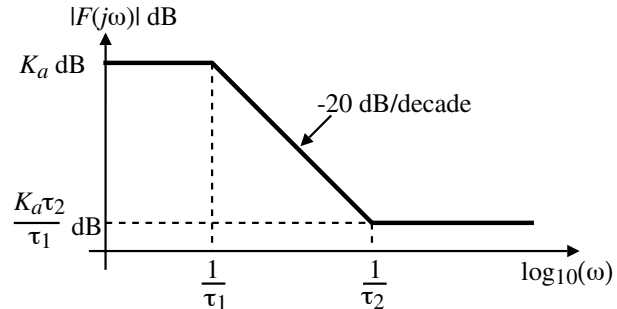

- Easier to make lead-lag
- Can have gain (not necessarily desirable)
- Limited by the linearity and noise of the op amp

## Loop Filters - Continued

### 3.) Active Proportional-Integral (PI) Filter

$$F(s) = \frac{1 + s\tau_2}{s\tau_1} \quad \text{where} \quad \tau_1 = R_1 C \quad \text{and} \quad \tau_2 = R_2 C$$


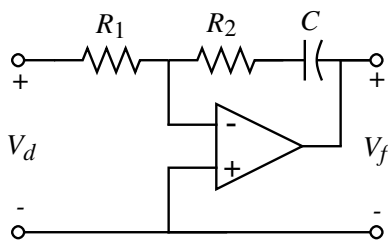


Fig. 2.1-05

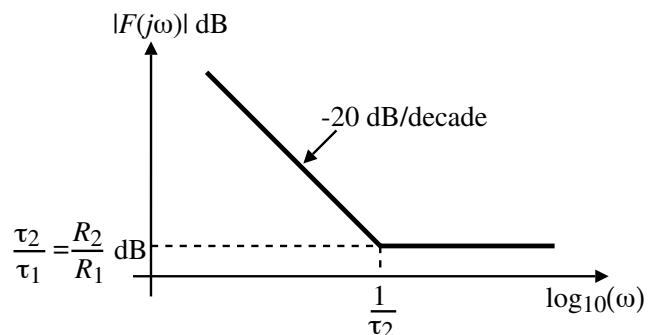

- Has large open loop gain at low frequencies  $\Rightarrow$  Large hold range
- Limited by the linearity and noise of the op amp
- Gain limits at the op amp open loop gain

### Stability:

To keep the loop stable, it is important to pick the loop filter so that it does not introduce more than a  $90^\circ$  phase shift in the loop.

## Phase Signals

It is important to remember that frequency and phase are related as

$$\frac{d\theta}{dt} = \omega \quad \rightarrow \quad \theta = \int \omega \cdot dt$$

Transfer functions:

$$H(s) = \frac{V_2(s)}{V_1(s)}$$

where  $V_2(s)$  and  $V_1(s)$  are the Laplace transforms of  $v_2(t)$  and  $v_1(t)$ .

To examine phase signals, let us assume that,

$$v_1(t) = V_{10} \sin[\omega_1 t + \theta_1(t)] \quad \text{and} \quad v_2(t) = V_{20} \sin[\omega_2 t + \theta_2(t)]$$


For phase signals, the information is carried only in  $\theta(t)$ .

Next, we consider some simple phase signals that are used to excite a PLL.

## Phase Signals – Continued

1.) A step phase shift which is an example of phase modulation.

$$\theta_1(t) = \Delta\Phi u(t)$$

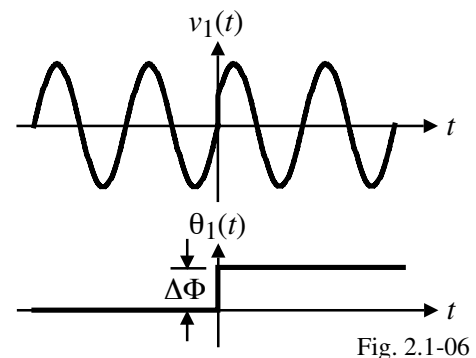


2.) A step frequency change assuming that  $\omega_1(t) = \omega_o$  for  $t < 0$ . We may express  $v_1(t)$  as,

$$\begin{aligned} v_1(t) &= V_{10} \sin[\omega_o t + \Delta\omega \cdot t] \\ &= V_{10} \sin[\omega_o t + \theta_1(t)] \end{aligned}$$

$$\therefore \theta_1(t) = \Delta\omega \cdot t$$

(the phase becomes a ramp signal)

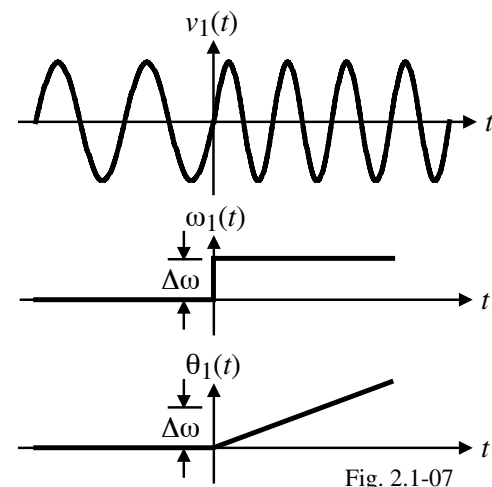

## Phase Signals – Continued

### 3.) Frequency ramp

$$\omega_1(t) = \omega_o + \Delta\dot{\omega} \cdot t$$

where  $\Delta\dot{\omega}$  is the rate of change of the angular frequency.

$$\therefore v_1(t) = V_{10} \sin \left[ \int_0^t (\omega_o + \Delta\dot{\omega}\tau) d\tau \right]$$

$$= V_{10} \sin \left( \omega_o t + \Delta\dot{\omega} \frac{t^2}{2} \right)$$

$$\theta_1(t) = \Delta\dot{\omega} \frac{t^2}{2}$$

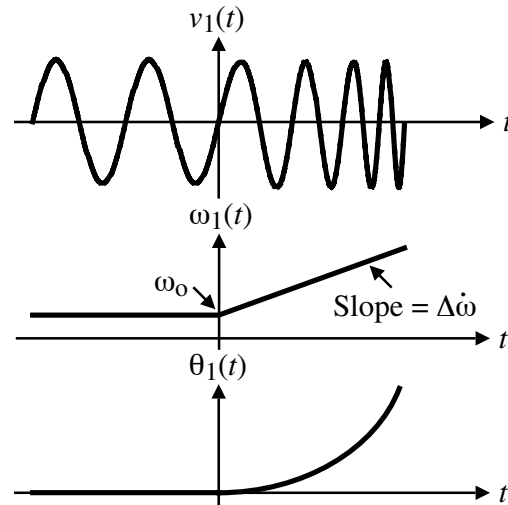


Fig. 2.1-08

## LOCKED STATE OF THE LPLL

### Transfer Function of the Phase Detector

Input sinusoidal and VCO sinusoidal:

$$v_1(t) = V_{10} \sin[\omega_1 t + \theta_1(t)] \quad \text{and} \quad v_2(t) = V_{20} \cos[\omega_2 t + \theta_2(t)]$$

$$\therefore v_d(t) = v_1(t) \cdot v_2(t) = V_{10} V_{20} \sin[\omega_1 t + \theta_1(t)] \cos[\omega_2 t + \theta_2(t)]$$

$$= \frac{V_{10} V_{20}}{2} \sin[\omega_1 t + \theta_1(t) - \omega_2 t - \theta_2(t)] - \frac{V_{10} V_{20}}{2} \sin[\omega_1 t + \theta_1(t) + \omega_2 t + \theta_2(t)]$$

If the loop is locked, then  $\omega_1 = \omega_2$  and

$$v_d(t) = \frac{V_{10} V_{20}}{2} \sin[\theta_1(t) - \theta_2(t)] - \frac{V_{10} V_{20}}{2} \sin[2\omega_1 t + \theta_1(t) + \theta_2(t)]$$

Ignoring the high-frequency terms gives,

$$v_d(t) \approx \frac{V_{10} V_{20}}{2} \sin[\theta_1(t) - \theta_2(t)] = \frac{V_{10} V_{20}}{2} \sin\theta_e(t) = K_d \sin\theta_e(t) \approx K_d \theta_e(t)$$

if  $\theta_e(t)$  is small.

$$K_d = \text{detector gain} = \frac{V_{10} V_{20}}{2}$$

$$\therefore v_d(t) \approx K_d \theta_e(t) \quad \Rightarrow \quad V_d(s) \approx K_d \Theta_e(s)$$

## **Transfer Function of the Phase Detector – Continued**

Input signals when VCO output is a square wave:

$$v_1(t) = V_{10} \sin[\omega_1 t + \theta_1(t)]$$

$$v_2(t) = V_{20} \operatorname{sgn}[\omega_2 t + \theta_2(t)] = V_{20} \left[ \frac{4}{\pi} \cos[\omega_2 t + \theta_2(t)] + \frac{4}{3\pi} \cos[3\omega_2 t + \theta_2(t)] + \dots \right]$$

$$\therefore v_d(t) = v_1(t) \cdot v_2(t)$$

$$= V_{10} V_{20} \sin[\omega_1 t + \theta_1(t)] \left[ \frac{4}{\pi} \cos[\omega_2 t + \theta_2(t)] + \frac{4}{3\pi} \cos[3\omega_2 t + \theta_2(t)] + \dots \right]$$

$$= \frac{4V_{10}V_{20}}{\pi} \left[ \sin[\omega_1 t + \theta_1(t)] \cos[\omega_2 t + \theta_2(t)] + \frac{1}{3} \cos[\omega_2 t + \theta_2(t)] \cos[3\omega_2 t + \theta_2(t)] + \dots \right]$$

When the loop is locked,

$$v_d(t) = \frac{2V_{10}V_{20}}{\pi} [\sin[\theta_1(t) - \theta_2(t)] + \sin[2\omega_1 t + \theta_1(t) + \theta_2(t)] + \dots]$$

$$\approx \frac{2V_{10}V_{20}}{\pi} \sin\theta_e(t) = K_d \sin\theta_e(t) \quad \rightarrow \quad v_d(t) \approx K_d \theta_e(t)$$

where the detector gain is  $K_d = \frac{2V_{10}V_{20}}{\pi}$  (a little better than sinusoidal inputs only)

$$\text{The transfer function is } V_d(s) \approx K_d \Theta_e(s) \quad \text{or} \quad \frac{V_d(s)}{\Theta_e(s)} = K_d$$

## **VCO Transfer Function**

The angular frequency of the VCO was expressed as,

$$\omega_2(t) = \omega_o + \Delta\omega_2(t) = \omega_o + K_o v_f(t)$$

where  $K_o$  is the VCO gain in units of radians/sec or simply  $\text{sec}^{-1}$ .


However, what we want is the phase of the VCO output.

$$\therefore \theta_2(t) = \int \Delta\omega_2 dt = K_o \int v_f(t) dt$$

Taking the Laplace transform gives,

$$\Theta_2(s) = \mathcal{L}[\theta_2(t)] = \frac{K_o}{s} V_f(s) \quad \rightarrow \quad \frac{\Theta_2(s)}{V_f(s)} = \frac{K_o}{s}$$

## Linear Model of the LPLL

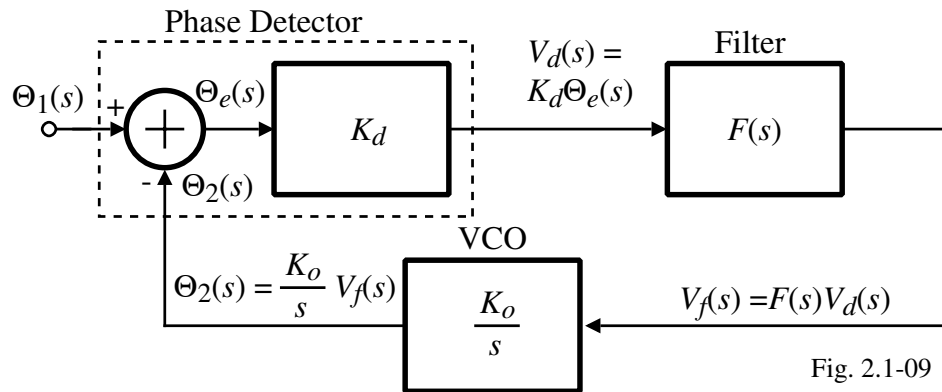

Phase transfer function:

$$H(s) = \frac{\Theta_2(s)}{\Theta_1(s)} = ?$$

$$\Theta_2(s) = \frac{K_o}{s} V_f(s) = \frac{K_o}{s} F(s) V_d(s) = \frac{K_o K_d}{s} F(s) \Theta_e(s) = \frac{K_o K_d}{s} F(s) [\Theta_1(s) - \Theta_2(s)]$$

$$s \Theta_2(s) = K_o K_d F(s) [\Theta_1(s) - \Theta_2(s)] \quad \rightarrow \quad \Theta_2(s) [s + K_o K_d F(s)] = K_o K_d F(s) \Theta_1(s)$$

$$\therefore H(s) = \frac{\Theta_2(s)}{\Theta_1(s)} = \frac{K_o K_d F(s)}{s + K_o K_d F(s)} \quad \text{Also, } H_e(s) = 1 - H(s) = \frac{s}{s + K_o K_d F(s)}$$

## LPLL Transfer Function for Various Loop Filters

1.) Passive lag filter.

$$F(s) = \frac{1 + s\tau_2}{1 + s(\tau_1 + \tau_2)} \quad \rightarrow \quad H(s) = \frac{K_o K_d \left( \frac{1 + s\tau_2}{\tau_1 + \tau_2} \right)}{s^2 + s \left( \frac{1 + K_o K_d \tau_2}{\tau_1 + \tau_2} \right) + \frac{K_o K_d}{\tau_1 + \tau_2}}$$

2.) The active lag filter.

$$F(s) = K_a \frac{1 + s\tau_2}{1 + s\tau_1} \quad \rightarrow \quad H(s) = \frac{K_o K_d K_a \left( \frac{1 + s\tau_2}{\tau_1} \right)}{s^2 + s \left( \frac{1 + K_o K_d K_a \tau_2}{\tau_1} \right) + \frac{K_o K_d K_a}{\tau_1}}$$

3.) The active PI filter.

$$F(s) = \frac{1 + s\tau_2}{s\tau_1} \quad \rightarrow \quad H(s) = \frac{K_o K_d \left( \frac{1 + s\tau_2}{\tau_1} \right)}{s^2 + s \left( \frac{K_o K_d \tau_2}{\tau_1} \right) + \frac{K_o K_d}{\tau_1 + \tau_2}}$$

## **Normalized Form of the Transfer Functions**

The normalized form of the denominator of a second-order transfer function is

$$D(s) = s^2 + 2\zeta\omega_n s + \omega_n^2$$

where  $\omega_n$  is the natural frequency and  $\zeta$  is the damping factor.

1.) Passive lag filter.

$$\omega_n = \sqrt{\frac{K_o K_d}{\tau_1 + \tau_2}} \quad \text{and} \quad \zeta = \frac{\omega_n}{2} \left( \tau_2 + \frac{1}{K_o K_d} \right)$$

2.) Active lag filter.

$$\omega_n = \sqrt{\frac{K_o K_d K_a}{\tau_1}} \quad \text{and} \quad \zeta = \frac{\omega_n}{2} \left( \tau_2 + \frac{1}{K_o K_d K_a} \right)$$

3.) Active PI filter.

$$\omega_n = \sqrt{\frac{K_o K_d}{\tau_1}} \quad \text{and} \quad \zeta = \frac{\omega_n \tau_2}{2}$$

## **Normalized Phase Functions**

1.) Passive lag filter.

$$H(s) = \frac{s\omega_n \left( 2\zeta - \frac{\omega_n}{K_o K_d} \right) + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

2.) Active lag filter.

$$H(s) = \frac{s\omega_n \left( 2\zeta - \frac{\omega_n}{K_o K_d K_a} \right) + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


3.) Active PI filter.

$$H(s) = \frac{2s\zeta\omega_n + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

If  $K_d K_o \gg \omega_n$  or  $K_d K_o K_a \gg \omega_n$ , then all of the above transfer functions simplify to,

$$H(s) = \frac{2s\zeta\omega_n + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad \text{and} \quad H_e(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

## Frequency Response of $H(s)$

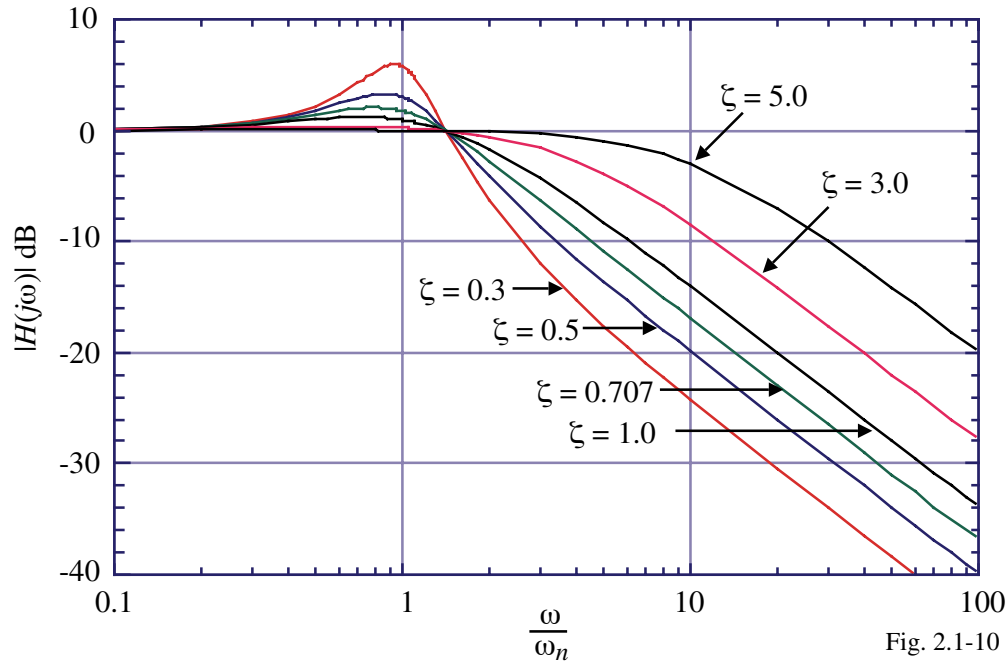

## Phase Step Response

Assume that  $\theta_1(t) = \Delta\Phi \cdot u(t) \quad \rightarrow \quad \Theta_1(s) = \frac{\Delta\Phi}{s}$

Phase error:

$$\Theta_e(s) = H_e(s) \frac{\Delta\Phi}{s} = \frac{\Delta\Phi s^2}{s(s^2 + 2\xi\omega_n s + \omega_n^2)}$$

$$\theta_e(t) = \mathcal{L}^{-1}[\Theta_e(s)] = \Delta\Phi \left( \cos\sqrt{1-\xi^2}\omega_n t - \frac{\xi}{\sqrt{1-\xi^2}} \sin\sqrt{1-\xi^2}\omega_n t \right) e^{-\xi\omega_n t}, \quad \xi < 1$$

$$= \Delta\Phi(1 - \omega_n t) e^{-\xi\omega_n t}, \quad \xi = 1$$

$$= \Delta\Phi \left( \cosh\sqrt{\xi^2-1}\omega_n t - \frac{\xi}{\sqrt{\xi^2-1}} \sinh\sqrt{\xi^2-1}\omega_n t \right) e^{-\xi\omega_n t}, \quad \xi > 1$$

Steady state error:

$$\theta_e(\infty) = \lim_{s \rightarrow 0} s\Theta_e(s) = 0$$

## Frequency Step Response

Assume that  $\omega_1(t) = \omega_o + \Delta\omega \cdot u(t)$

However,  $\theta_1(t) = \Delta\omega \cdot t \quad \rightarrow \quad \Theta_1(s) = \frac{\Delta\omega}{s^2}$

Phase error:

$$\Theta_e(s) = H_e(s) \frac{\Delta\omega}{s^2} = \frac{\Delta\omega s^2}{s^2(s^2 + 2\xi\omega_n s + \omega_n^2)} = \frac{\Delta\omega}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\theta_e(t) = \mathcal{L}^{-1}[\Theta_e(s)] = \frac{\Delta\omega}{\omega_n} \left( \frac{1}{\sqrt{1-\xi^2}} \sin\sqrt{1-\xi^2} \omega_n t \right) e^{-\xi\omega_n t}, \quad \xi < 1$$

$$= \frac{\Delta\omega}{\omega_n} (\omega_n t) e^{-\xi\omega_n t}, \quad \xi = 1$$

$$= \frac{\Delta\omega}{\omega_n} \left( \frac{1}{\sqrt{\xi^2-1}} \sinh\sqrt{\xi^2-1} \omega_n t \right) e^{-\xi\omega_n t}, \quad \xi > 1$$

Steady state error:

$$\theta_e(\infty) = \lim_{s \rightarrow 0} s\Theta_e(s) = 0 \text{ (high gain loops)} \quad \theta_e(\infty) = \frac{\Delta\omega}{K_d K_o F(0)} \text{ (low gain loops)}$$

## Frequency Ramp Response

Assume that  $\omega_1(t) = \omega_o + \Delta\dot{\omega} \cdot t$

However,  $\theta_1(t) = \Delta\dot{\omega} \frac{t^2}{2} \quad \rightarrow \quad \Theta_1(s) = \frac{\Delta\dot{\omega}}{s^3}$

Phase error:

$$\Theta_e(s) = H_e(s) \frac{\Delta\dot{\omega}}{s^3} = \frac{\Delta\dot{\omega} s^2}{s^3(s^2 + 2\xi\omega_n s + \omega_n^2)} = \frac{\Delta\dot{\omega}}{s(s^2 + 2\xi\omega_n s + \omega_n^2)}$$

$$\theta_e(t) = \mathcal{L}^{-1}[\Theta_e(s)] = \frac{\Delta\dot{\omega}}{\omega_n^2} - \frac{\Delta\dot{\omega}}{\omega_n^2} \left( \cos\sqrt{1-\xi^2} \omega_n t + \frac{\xi}{\sqrt{1+\xi^2}} \sin\sqrt{1-\xi^2} \omega_n t \right) e^{-\xi\omega_n t}, \quad \xi < 1$$

$$= \frac{\Delta\dot{\omega}}{\omega_n^2} - \frac{\Delta\dot{\omega}}{\omega_n^2} (1 + \omega_n t) e^{-\xi\omega_n t}, \quad \xi = 1$$

$$= \frac{\Delta\dot{\omega}}{\omega_n^2} - \frac{\Delta\dot{\omega}}{\omega_n^2} \left( \cosh\sqrt{\xi^2-1} \omega_n t + \frac{\xi}{\sqrt{\xi^2-1}} \sinh\sqrt{\xi^2-1} \omega_n t \right) e^{-\xi\omega_n t}, \quad \xi > 1$$

Steady state error:

$$\theta_e(\infty) = \lim_{s \rightarrow 0} s\Theta_e(s) = \frac{\Delta\dot{\omega}}{\omega_n^2} \text{ (High loop gain)} \quad \theta_e(\infty) = \frac{\Delta\dot{\omega} t}{K_d K_o F(0)^2} + \frac{\Delta\dot{\omega}}{\omega_n^2} \text{ (Low loop gain)}$$



## **THE ORDER OF A LPLL SYSTEM**

### **Definition of Order**

The number of roots in the denominator (poles) of the PLL transfer function determines the order.

Generally, the order of a PLL is one greater than the order of  $F(s)$ .

Implication of the order:

- Greater than 2 will be unstable unless corrected by zeros
- Less than 2 will have poor noise suppression.

### **First-Order PLL**

A first-order PLL occurs when  $F(s) = 1$ . From previous results we have,

$$H(s) = \frac{\Theta_2(s)}{\Theta_1(s)} = \frac{K_o K_d}{s + K_o K_d} \quad \text{Also, } H_e(s) = 1 - H(s) = \frac{s}{s + K_o K_d}$$

The  $-3\text{dB}$  bandwidth of  $H(s)$  is  $K_o K_d$ .


Comments:

- $F(s)$  causes the  $-3\text{dB}$  bandwidth to be reduced in higher-order systems which means that the first-order PLL has a wider bandwidth
- The hold range of the first-order PLL will be larger than for higher-order PLLs
- The first-order PLL will track the signal variations more quickly than higher-order PLLs
- The first-order PLL does not suppress noise superimposed on the input signal to the extent of higher-order PLLs.

## Higher-Order PLLs
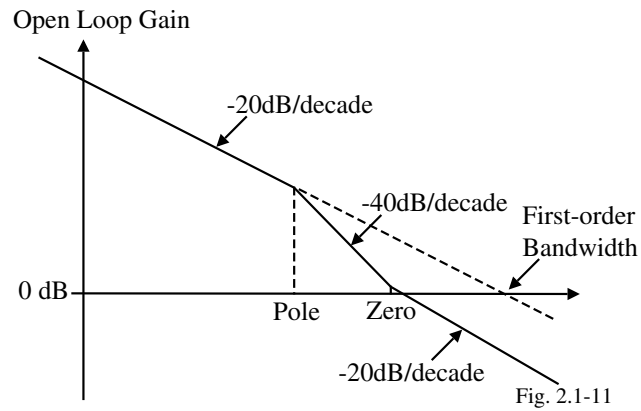
### Comments:

- Generally  $F(s)$  has a pole and a zero in order to get better noise rejection without sacrificing speed.



- If the phase shift of the open loop system is more than  $90^\circ$ , the stability of the loop may be poor ( $\zeta$  is small).

(To be continued in Lecture 060)