

LECTURE 130 – VOLTAGE-CONTROLLED OSCILLATORS

(READING: [4,6,9])

Objective

The objective of this presentation is examine and characterize the types of voltage-controlled oscillators compatible with both discrete and integrated technologies.

Outline

- Characterization of VCO's
- Oscillators
 - RC
 - LC
 - Relaxation oscillators
 - Ring oscillators
 - Direct digital synthesis (DDS)
- Varactors
- Summary

CHARACTERIZATION OF VOLTAGE-CONTROLLED OSCILLATORS

Introduction to Voltage-Controlled Oscillators

What is an oscillator?

An oscillator is a circuit capable of maintaining electric oscillations.

An oscillator is a periodic function, i.e. $f(x) = f(x+nk)$ for all x and for all integers, n , and k is a constant.

All oscillators use positive feedback of one form or another.

Classification of oscillators:

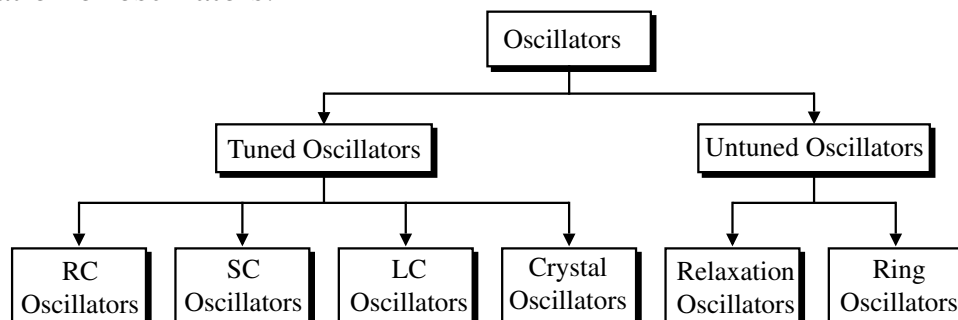


Fig. Osc-01

What are tuned oscillators?

A tuned oscillator uses a frequency-selective or tuned-circuit in the feedback path and is generally sinusoidal.

An untuned or oscillator uses nonlinear feedback and is generally non-sinusoidal

Types of Oscillators

Ring Oscillator:

Cascade of inverters

Frequency of oscillation = $\frac{1}{\Sigma \text{ of stage delays}}$

Controlled by current or power supply

Higher power

LC Oscillator:

Frequency of oscillation = $\frac{1}{\sqrt{LC}}$

Controlled by voltage dependent capacitance (varactor)

Medium power

Relaxation Oscillator:

Frequency determined by circuit time constants

Controlled by current

Medium power

RC Oscillators:

Don't require inductors


Operate at lower frequencies (1-100MHz)

Characteristics of Oscillators

- Frequency of oscillation
- Frequency tuning range as a function of the controlling variable (either voltage or current)
- Frequency stability – phase noise and jitter
- Amplitude stability (adjustable?)
- Purity (harmonics)

Linear Feedback Oscillator System

Simplified block diagram:

 

The loop gain of this diagram is,

$$LG(j\omega) = A(j\omega)F(j\omega)$$

When the loop gain is equal to 1, oscillation occurs.

$$Re[LG(j\omega)] + Im[LG(j\omega)] = 1 + j0$$

The frequency of oscillation is found from,

$$Im[LG(j\omega)] = 0$$

and the gain necessary for oscillation is found from,

$$Re[LG(j\omega)] = 1$$

Linear Oscillator Amplitude Stabilization


What determines the amplitude of the oscillator? Good question.

$A(j\omega)$ and/or $F(j\omega)$ must have an output-input characteristic that looks like an s shape.

For small amplitudes, the magnitude of the loop gain is greater than one and the oscillation grows.



As the amplitude grows, the effective gain decreases and stabilizes at just the right amplitude to give an effective loop gain of unity.

Illustration:

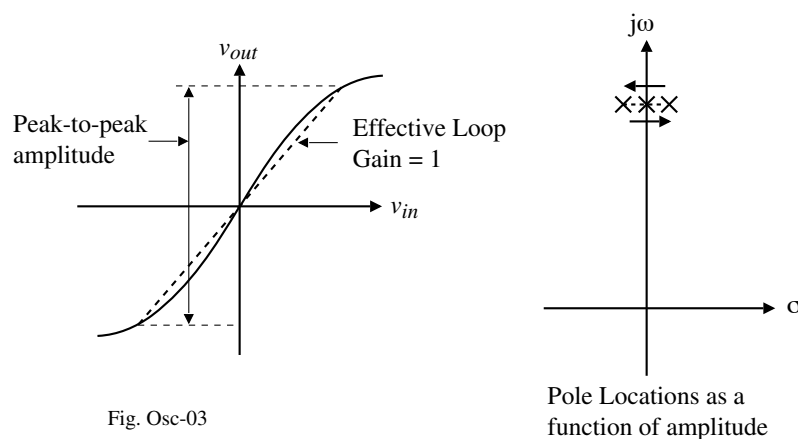

Van der Pol Equations for Oscillators

  Basic RLC oscillator and negative resistance circuit:



$$i_L + i_C + i_R + i = 0 \quad \text{and}$$

$$i = f(v) = -a_1v + a_3v^3$$

$$v_L = L \frac{di_L}{dt} \rightarrow \frac{di_L}{dt} = \frac{v}{L}$$

$$\frac{di}{dv} = -a_1 + 3a_3v^2$$

$$i_C = C \frac{dv}{dt} \rightarrow \frac{di_C}{dt} = C \frac{d^2v}{dt^2}$$

$$\left. \frac{di}{dv} \right|_{v=0} = -a_1 = -\frac{1}{R_n}$$

$$i_R = \frac{v}{R_p} \rightarrow \frac{di_{R_p}}{dt} = \frac{1}{R_p} \frac{dv}{dt}$$

$$\frac{di}{dt} = -a_1 \frac{dv}{dt} + 3a_3v^2 \frac{dv}{dt}$$

$$\frac{di_L}{dt} + \frac{di_C}{dt} + \frac{di_{R_p}}{dt} + \frac{di}{dt} = 0 \rightarrow \frac{v_L}{L} + C \frac{d^2v}{dt^2} + \frac{1}{R_p} \frac{dv}{dt} + \left[-a_1 \frac{dv}{dt} + 3a_3v^2 \frac{dv}{dt} \right] = 0$$

$$C \frac{d^2v}{dt^2} + \left[\frac{1}{R_p} - a_1 + 3a_3v^2 \right] \frac{dv}{dt} + \frac{v}{L} = 0$$

$$\frac{d^2v}{dt^2} + \left[\frac{1}{CR_p} - \frac{a_1}{C} + \frac{3a_3v^2}{C} \right] \frac{dv}{dt} + \frac{v}{LC} = 0$$

Van der Pol Equations

At start up, v is very small so that $3a_3v^2 \approx 0$

$$\therefore s^2V(s) + \left(\frac{1}{R_p} - a_1 \right) sV(s) + \frac{V(s)}{LC} = 0 \quad \rightarrow \quad s^2 + ms + \frac{1}{LC} = 0$$

$$\text{Poles} = -0.5m \pm 0.5\sqrt{m^2 - \frac{4}{LC}} = -0.5m \pm j0.5\sqrt{\frac{4}{LC} - m^2}$$

For $j\omega$ axis poles, $m = 0$.

In steady-state, the following relationship must hold.

$$m = \left[\frac{1}{CR_p} - \frac{a_1}{C} + \frac{3a_3v^2}{C} \right] = 0$$


We see that the amplitude of oscillation ($\omega_{osc} = \frac{1}{\sqrt{LC}}$) will be,

$$V = \sqrt{\frac{a_1 - \frac{1}{R_p}}{3a_3}} = \sqrt{\frac{\frac{1}{R_n} - \frac{1}{R_p}}{3a_3}}$$

For $V = 1V$, $\frac{1}{R_n} = \frac{1}{R_p} - 3a_3$

Open-Loop Concept of an Oscillator

Basic closed-loop oscillator:

 


Oscillator oscillates when $H(j\omega) = 1+j0$

Open-loop Q :

The open-loop Q is a measure of how much the closed loop system opposes variations in the oscillation frequency. The higher the Q , the lower the phase noise.

Definitions of Q :

 
- 1.) $Q = \frac{\omega_o}{\Delta\omega}$ where ω_o is the frequency of oscillation.
- 2.) $Q = \frac{2\pi \cdot \text{Energy Stored}}{\text{Energy Dissipated per Cycle}}$
- 3.) $Q = \frac{\omega_o}{2} \frac{d}{d\omega} \left(\text{Arg}[H(j\omega)] \right)$



Voltage Controlled Oscillators - Tuning

A voltage controlled oscillator (VCO) is an oscillator whose frequency can be varied by a voltage (or current).

 In local oscillator applications, the VCO frequency must be able to be varied over the Rx or Tx range (quickly).



Tuning variables:


- Capacitance (varactor)
- Current
- Power supply

Speed of tuning will be determined by the bandwidth of the phase lock loop.

OSCILLATORS

RC Oscillators - Wien-Bridge Oscillator

Circuit:

 

Open-Loop Gain:

For simplicity, let $R_1 = R_2 = R$ and $C_1 = C_2 = C$.

$$\therefore LG(s) = \frac{K \frac{s}{RC}}{s^2 + \frac{3}{RC}s + \frac{1}{(RC)^2}} \rightarrow LG(j\omega) = \frac{K \frac{j\omega}{RC}}{\frac{1}{(RC)^2} - \omega^2 + \frac{3}{RC}j\omega}$$

Equating the loop gain to 1+j0 gives


$$\frac{K \frac{j\omega_o}{RC}}{\frac{1}{(RC)^2} - \omega_o^2 + \frac{3}{RC}j\omega_o} = 1 + j0$$

The only way this equation can be satisfied is if $\omega_o^2 = \frac{1}{RC}$ and $K = 3$.

Wien-Bridge Oscillator – Continued

How do you realize the amplifier of $K = 3$?

 
$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$



How does the amplitude stabilize?


- Thermistor (a resistor whose resistance decreases with increasing temperature)
- Nonlinear transfer function

Example:

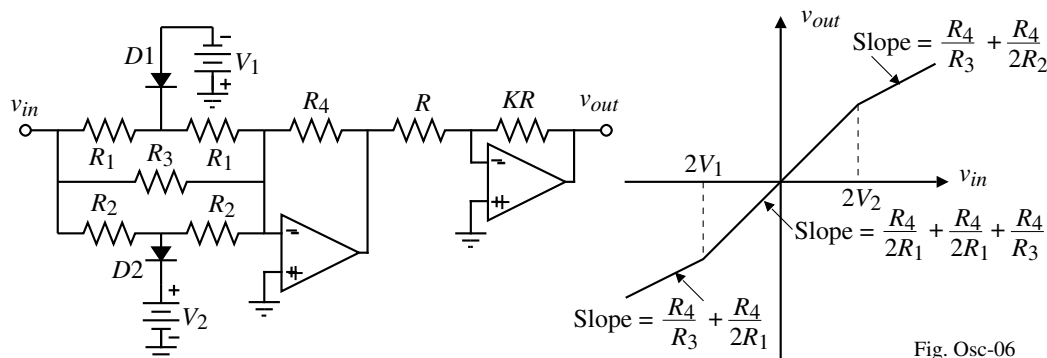

Other RC Oscillators

RC Phase-Shift Oscillator:

 


If $R_1 = R_2 = R_3 = R$ and $C_1 = C_2 = C_3 = C$, then

$$LG(j\omega) = \frac{(R_4 R_3)(j\omega RC)(\omega RC)^2}{[1 - 6(\omega RC)^2] + j\omega RC [5 - (\omega RC)^2]}$$

$$\therefore \omega_{osc} = \frac{1}{\sqrt{6} RC} \quad \text{and} \quad K = \frac{R_4}{R_3} = 29$$

Quadrature Oscillator:

 

$$LG(j\omega) = \frac{-1}{(j\omega)^2 R_1 C_2 R_3 C_4}$$

$$\therefore \omega_{osc} = \frac{1}{\sqrt{R_1 C_2 R_3 C_4}}$$


Other RC oscillators: Twin-tee RC oscillator, Sallen-Key bandpass filter with $Q = \infty$, Infinite gain, bandpass filter with $Q = \infty$

How do you tune the RC oscillator?

Must vary either R or C or both.

 Example

The circuit shown is a RC oscillator. Find the frequency of oscillation in Hertz and the voltage gain, K , of the voltage amplifiers necessary for oscillation. The voltage amplifiers have infinite input resistance and zero output resistance.



Solution

The loop gain can be found from the schematic shown:

$$T(s) = \frac{V_r}{V_x} = K^2 \left(\frac{1}{sRC + 1} \right) \left(\frac{sRC}{sRC + 1} \right)$$

$$= \frac{K^2 sRC}{s^2 R^2 C^2 + 2sRC + 1} \rightarrow T(j\omega) = \frac{K^2 j\omega RC}{1 - \omega^2 R^2 C^2 + j\omega 2RC} = 1 + j0$$

We see from this equation that for oscillation to occur, the following conditions must be satisfied:

$$1 - \omega^2 R^2 C^2 = 0 \quad \text{and} \quad K^2 = 2$$

or

$$\omega_{osc} = \frac{1}{RC} = \frac{1}{10^4 \cdot 10^{-9}} = 10^5 \text{ radians/sec.} \rightarrow f_{osc} = \underline{15.9 \text{ kHz}} \quad \text{and} \quad K = \sqrt{2} = \underline{1.414}$$

Gm-C Oscillators

Same the quadrature oscillator only implemented in a more IC friendly manner.

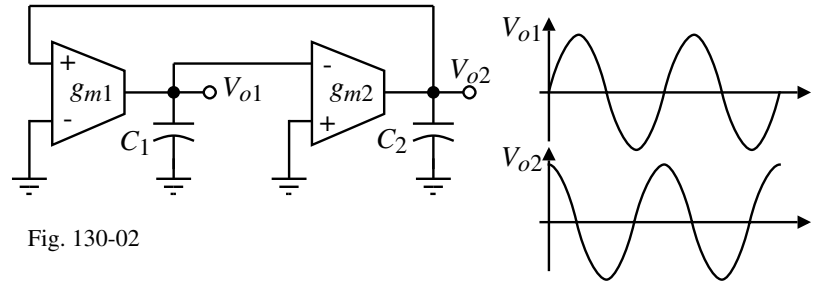


Fig. 130-02

$$\text{Open Loop Gain} = L(s) = \left(\frac{gm1}{sC1}\right) \left(\frac{-gm2}{sC2}\right) = \frac{-gm1gm2}{s^2C1C2}$$

Letting $s = j\omega$ and setting $L(j\omega) = 1$ gives,

$$\omega_{osc} = \sqrt{\frac{gm1gm2}{C1C2}} = \frac{gm1}{C1} = \frac{gm2}{C2} \quad \text{if } gm1 = gm2 \text{ and } C1 = C2$$

This circuit is much easier to tune. If the transconductors are MOS transistors, then

$$gm = \sqrt{\frac{2K'I_D W}{L}}$$

Varying the bias current will vary g_m and tune the frequency.

Switched Capacitor Oscillators

Concept

Theoretically, the R 's of any RC oscillator can be replaced by switches and capacitors to create an SC oscillator.

Quadrature SC Oscillator

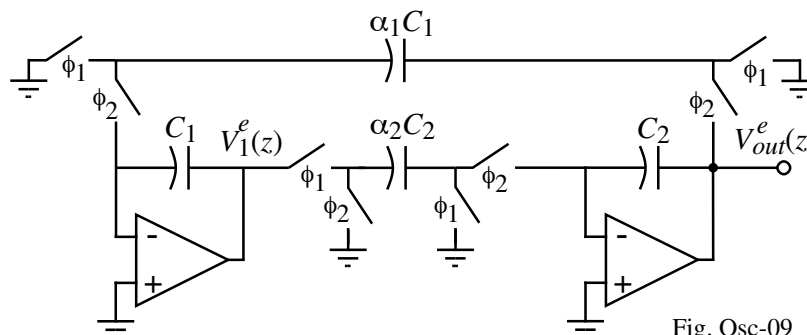


Fig. Osc-09


$$\omega_{osc} = \sqrt{\frac{\alpha_1 \alpha_2}{T^2}} = \sqrt{\alpha_1 \alpha_2} f_{clock} \quad (\text{really a frequency translator})$$

The output is a sinusoid at frequency of $\sqrt{\alpha_1 \alpha_2} f_{clock}$.


LC Oscillator

All LC oscillators require feedback for oscillation to occur.

1.) Hartley or Colpitts oscillators

 

Colpitts

 

Hartley Fig. 12.4-9

$$\omega_o = \frac{1}{\sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}} \text{ and } \frac{C_2}{C_1} = g_m R$$

$$\omega_o = \frac{1}{\sqrt{(L_1 + L_2) C}} \text{ and } \frac{L_2}{L_1} = g_m R$$

2.) Negative resistance LC tank

$$\omega_o = \frac{1}{\sqrt{LC}}$$

 


Fig. 12.4-10

Example – Clapp LC Oscillator

A Clapp oscillator which is a version of the Colpitt's oscillator is shown. Find an expression for the frequency of oscillation and the value of $g_m R_L$ necessary for oscillation. Assume that the output resistance of the FET, r_{ds} , and R_{Large} can be neglected (approach infinity).

Solution


The small-signal model for this problem is shown below.

The loop gain will be defined as V_{gs}/V_{gs}' . Therefore,


$$V_{gs} = \frac{-g_m V_{gs}' R_L \parallel (1/sC_3)}{R_L \parallel (1/sC_3) + \frac{1}{sC_1} + \frac{1}{sC_2} + sL} \left(\frac{1}{sC_2} \right)$$

$$= \frac{-g_m V_{gs}' \frac{R_L (1/sC_3)}{R_L + (1/sC_3)} \frac{1}{sC_2}}{\frac{R_L (1/sC_3)}{R_L + (1/sC_3)} + \frac{1}{sC_1} + \frac{1}{sC_2} + sL}$$
 
$$T(s) = \frac{V_{gs}}{V_{gs}'} = \frac{\frac{-g_m R_L}{s R_L C_3 + 1} \frac{1}{s C_2}}{\frac{R_L}{s R_L C_3 + 1} + \frac{1}{s C_1} + \frac{1}{s C_2} + s L} = \frac{\frac{-g_m R_L}{s C_2}}{R_L + (s R_L C_3 + 1) \left(\frac{1}{s C_1} + \frac{1}{s C_2} + s L \right)}$$



F02FEP5

 

F02FES5

Example – Continued

$$T(s) = \frac{-g_m R_L}{sC_2R_L + (sR_LC_3+1)(s^2LC_2+\frac{C_2}{C_1}+1)}$$

$$T(s) = \frac{-g_m R_L}{sC_2R_L + s^3R_LC_3LC_2 + sR_L\frac{C_2C_3}{C_1} + sC_3R_L + s^2LC_2 + \frac{C_2}{C_1} + 1}$$


$$T(j\omega) = \frac{-g_m R_L}{[1 + \frac{C_2}{C_1} - \omega^2LC_2] + j\omega[R_L(C_2+C_3) + R_L\frac{C_2C_3}{C_1} - \omega^2R_LC_3LC_2]} = 1 + j0$$

$$\therefore C_2+C_3 + \frac{C_2C_3}{C_1} = \omega_{osc}^2 C_3LC_2 \rightarrow \omega_{osc} = \sqrt{\frac{1}{L}\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}\right)}$$


$$\text{Also, } g_m R_L = \omega_{osc}^2 LC_2 - 1 - \frac{C_2}{C_1} = C_2\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}\right) - \frac{C_2}{C_1} - 1 = \frac{C_2}{C_3} \rightarrow g_m R_L = \frac{C_2}{C_3}$$

LC Oscillators


Circuits:

 

PMOS LC Oscillator

 

NMOS LC Oscillator

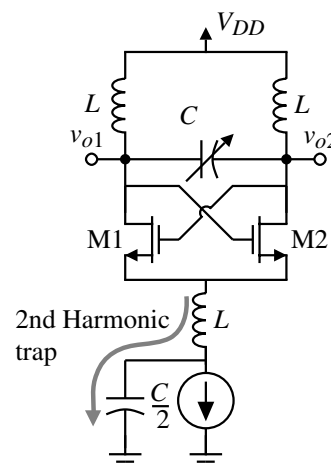

Improved NMOS LC Oscillator

Fig. 12.4-10A


Conditions for oscillation:

$$H(s) = \left[\frac{\frac{g_m}{C} s}{s^2 + \frac{s}{RC} + \frac{1}{LC}} \right]^2 \Rightarrow H(j\omega) = \left[\frac{\frac{g_m}{C} j\omega}{-\omega^2 + \frac{j\omega}{RC} + \frac{1}{LC}} \right]^2 = 1 + j0 \Rightarrow \omega_{osc}^2 = \frac{1}{LC} \ \& \ \frac{g_m}{C} = 1$$

Output swing of the improved circuit is twice that of the other circuits plus the second harmonic is removed.

 Example – LC Oscillator

An LC oscillator is shown. The value of the inductors, L , are 5nH and the capacitor, C , is 2.5pF. If the Q of each inductor is 5, find (a.) the value of negative resistance that should be available from the cross-coupled, source-coupled pair (M1 and M2) for oscillation and (b.) design the W/L ratios of M1 and M2 to realize this negative resistance (if you can't find the negative resistance of part (a.) assume that the desired negative resistance is -100Ω).



Solution

(a.) The equivalent circuit seen by the negative resistance circuit is:


The frequency of oscillation is given as $1/\sqrt{2LC}$ or $\omega_o = 2\pi \times 10^9$ radians/sec.

Therefore the series resistance, R_s , is found as

$$R_s = \frac{\omega L}{Q} = \frac{2\pi \times 10^9 \cdot 5 \times 10^{-9}}{5} = 2\pi \Omega$$

Converting the series impedance of $2L$ and $2R_s$ into a parallel impedance gives,
 
$$Y = \frac{1}{2R_s + j\omega 2L} = \frac{0.5}{R_s + j\omega L} \cdot \frac{R_s - j\omega L}{R_s - j\omega L} = \frac{0.5R_s}{R_s^2 + \omega^2 L^2} - \frac{j0.5\omega L_s}{R_s^2 + \omega^2 L^2}$$



LC Oscillator Example - Continued

The reciprocal of the conductance is the parallel resistance, R_p , given as

$$R_p = \frac{R_s^2 + \omega^2 L^2}{0.5R_s} = \frac{4\pi^2 + 4\pi^2 \cdot 25}{\pi} = 4\pi(26) = 326.7\Omega$$

$$\therefore \underline{R_{neg} = -104\pi \Omega = -326.7\Omega}$$

(b.) The negative resistance seen by the RLC circuit is found as follows.


$$i_{in} = g_{m1}v_{gs1} = -g_{m2}v_{gs2}$$

$$\therefore R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{gs2} - v_{gs1}}{i_{in}} = \frac{-1}{g_{m2}} - \frac{1}{g_{m1}} = \frac{-2}{g_m}$$

Assuming the 2mA splits evenly between M1 and M2 for the negative resistance calculation gives,

$$\text{Thus, } g_m = g_{m1} = g_{m2} = \sqrt{2 \cdot 2\text{mA} \cdot 110 \times 10^{-6} (W/L)} = \frac{\sqrt{W/L}}{1508} = \frac{2}{104\pi}$$
 
$$\therefore W/L = \left(\frac{1508}{52\pi}\right)^2 = 841 \quad \Rightarrow \quad \underline{W/L = 841}$$



LC Oscillator

VCO with PMOS pair:

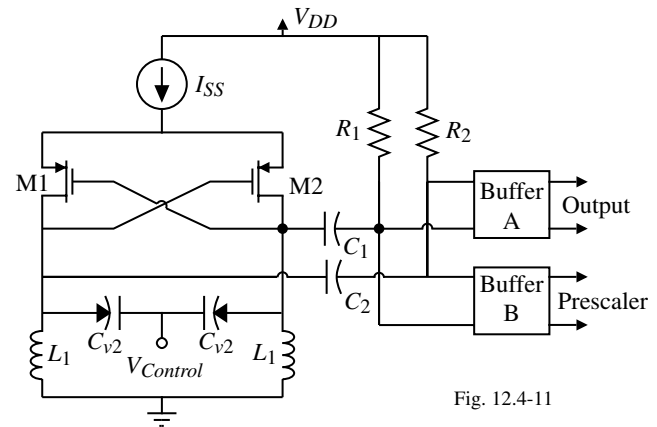


Fig. 12.4-11

Design:

- Inductors - $L_1 = L_2 = 7.1\text{nH}$, $Q = 8.5$ at 910MHz (Metal 3 with spacing of $2.1\mu\text{m}$ and width of $16.1\mu\text{m}$ and 5 turns)
- R_1, C_1 and R_2, C_2 form ac coupling filters
- Buffers A and B isolate the VCO from the next stages to avoid the pulling effect of the center frequency due to injection from the external load or the prescaler fed by the VCO. Buffer A provides a matched 50Ω output impedance and buffer B drives the large capacitance of the prescaler.
- $I_{SS} = 1.5\text{mA}$

 


Fig. 12.4-12

Relaxation Oscillators

Circuit:

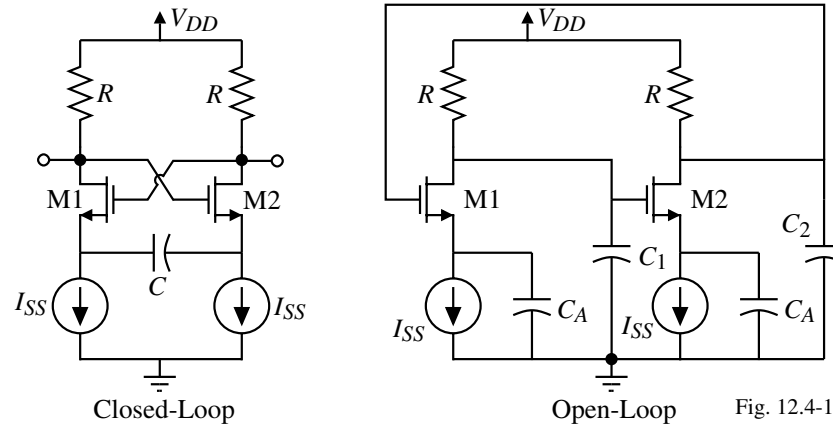


Fig. 12.4-13

Open Loop:

Assume that C in the closed loop circuit is really two $2C$ capacitors in series and ground the midpoint to obtain the open-loop circuit. C_1 and C_2 are capacitances to ground from the drains of M1 and M2.


$$H(s) = \left[\frac{-g_m R C_A s}{(g_m + C_A s)(R C_D s + 1)} \right]^2$$

where g_m = transconductance of each transistor and $C_D = C_1 = C_2$.

It can be shown that,

$$\omega_o = \frac{g_m}{R C_A C_D} \quad \text{and} \quad Q = 4 \left(1 - \frac{C_D}{C_A} \right) \frac{C_D}{C_A} \Rightarrow Q_{max} = 1 \Rightarrow S_{o\theta}(f_m) = \frac{1}{4} \left(\frac{f_o}{f_m} \right)^2 S_{\theta}(f_m)$$

 Relaxation Oscillator - Experimental Results



$W/L = 100\mu\text{m}/0.5\mu\text{m}$
 $g_m = 1/84\mu\text{S}$
 $R = 275\Omega$
 $C = 0.6\text{pF}$
 $I_{SS} = 3\text{mA}$


Fig. 12.4-14

$f_o = 920 \text{ MHz}$

Phase noise = -105 dBc/Hz for $f_m = 1\text{MHz}$ and -115dBc/Hz for $f_m = 5\text{MHz}$

Ring Oscillator VCO

Three-stage ring oscillator:

 

Comparison of a Three-Stage and Four-Stage Ring Oscillator:

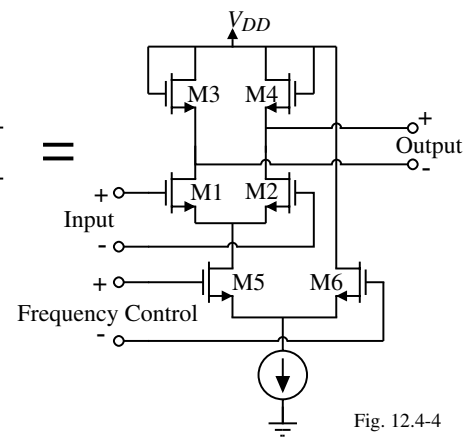


Fig. 12.4-4

Characteristic	3-Stage Ring Oscillator	4-Stage Ring Oscillator
Min. Required Gain	2	$\sqrt{2}$
Noise Shaping Function	$\frac{1}{27} \left(\frac{f_o}{f_m}\right)^2$	$\frac{1}{16} \left(\frac{f_o}{f_m}\right)^2$
Open-Loop Q	$0.75\sqrt{2}$	$\sqrt{2}$
Power Dissipation	1.8mW	3.6mW

Quadrature VCO's

Polyphase Oscillator:

 


Fig. 12.5-14

- Two cross-coupled oscillators synchronize in exact quadrature
- Phase inaccuracy insensitive to mismatch in resonators
- Large amplitudes available, balanced oscillation available to drive mixer FETs

Performance:

830 MHz

Unwanted sideband -46 dB below wanted sideband

Leakage 49 dB below wanted sideband

Quadrature Oscillators

Frequency Division Approach:

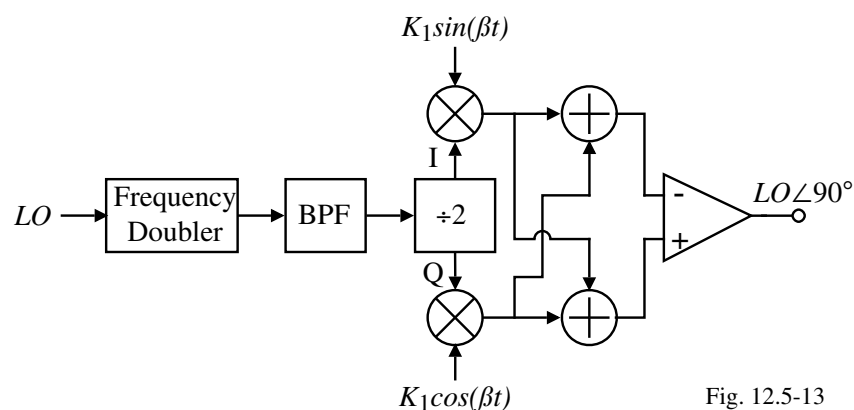


Fig. 12.5-13

Comments:

- Start with a single phase local oscillator at twice the desired frequency
- Divide by 2 is done by positive and negative edge triggered flip-flops
- Phase accuracy depends on timing skews between the flip-flop channels (typically 1-2°)

VARACTORS – VARIABLE CAPACITORS

One of the components that can be used to vary the frequency is the capacitor.

Types of Capacitors Considered

- pn junction capacitors
- Standard MOS capacitors
- Accumulation mode MOS capacitors
- Poly-poly capacitors
- Metal-metal capacitors

Characterization of Capacitors

Assume C is the desired capacitance:

- 1.) Dissipation (quality factor) of a capacitor is

$$Q = \omega CR_p$$

where R_p is the equivalent resistance in parallel with the capacitor, C .

- 2.) C_{max}/C_{min} ratio is the ratio of the largest value of capacitance to the smallest when the capacitor is used as a variable capacitor.
- 3.) Variation of capacitance with the control voltage.
- 4.) Parasitic capacitors from both terminal of the desired capacitor to ac ground.

Desirable Characteristics of Varactors

- 1.) A high quality factor
- 2.) A control voltage range compatible with supply voltage
- 3.) Good tunability over the available control voltage range
- 4.) Small silicon area (reduces cost)
- 5.) Reasonably uniform capacitance variation over the available control voltage range
- 6.) A high C_{max}/C_{min} ratio

Some References for Further Information

- 1.) P. Andreani and S. Mattisson, "On the Use of MOS Varactors in RF VCO's," *IEEE J. of Solid-State Circuits*, vol. 35, no. 6, June 2000, pp. 905-910.
- 2.) A-S Porret, T. Melly, C. Enz, and E. Vittoz, "Design of High- Q Varactors for Low-Power Wireless Applications Using a Standard CMOS Process," *IEEE J. of Solid-State Circuits*, vol. 35, no. 3, March 2000, pp. 337-345.
- 3.) E. Pedersen, "RF CMOS Varactors for 2GHz Applications," *Analog Integrated Circuits and Signal Processing*, vol. 26, pp. 27-36, Jan. 2001

Digitally Varied Capacitances

In a digital process, high-quality capacitors are very difficult to achieve. A high-quality variable capacitor is even more difficult to realize.

Therefore, digitally controlled capacitances are becoming more popular.

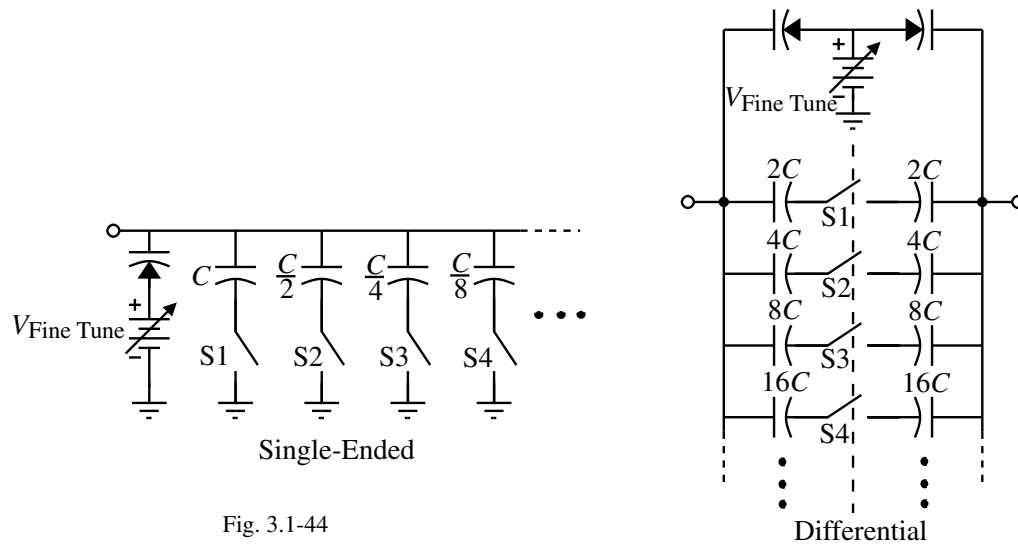


Fig. 3.1-44

Concerns:

- Switch parasitics
- Switch ON resistance (will lower Q)

$K_{V\omega}$ of Digitally Tuned VCOs

The value of the VCO gain constant can be made smaller which is desirable in many applications of the VCO.

 



Fig. 3.1-45

Capacitor Errors

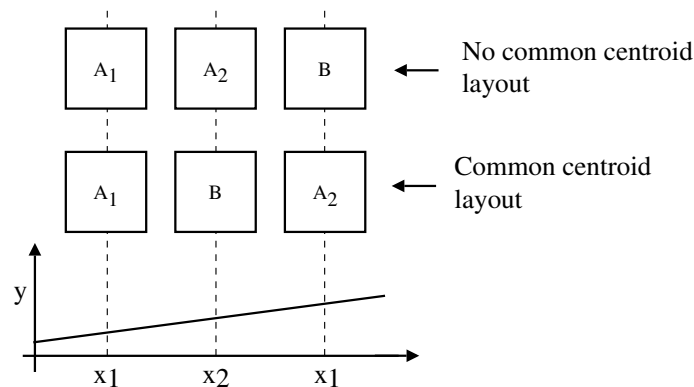- 1.) Oxide gradients
- 2.) Edge effects
- 3.) Parasitics
- 4.) Voltage dependence
- 5.) Temperature dependence


Capacitor Errors - Oxide Gradients

Error due to a variation in oxide thickness across the wafer.



Only good for one-dimensional errors.

 An alternate approach is to layout numerous repetitions and connect them randomly to achieve a statistical error balanced over the entire area of interest.



0.2% matching of poly resistors was achieved using an array of 50 unit resistors.


Capacitor Errors - Edge Effects

There will always be a randomness on the definition of the edge.


However, etching can be influenced by the presence of adjacent structures.

For example,

 Matching of A and B are disturbed by the presence of C.



 Improved matching achieved by matching the surroundings of A and B.



Capacitor Errors - Area/Periphery Ratio

The best match between two structures occurs when their area-to-periphery ratios are identical.

Let $C'_1 = C_1 \pm \Delta C_1$ and $C'_2 = C_2 \pm \Delta C_2$

where

C' = the actual capacitance

C = the desired capacitance (which is proportional to *area*)

ΔC = edge uncertainty (which is proportional to the *periphery*)

Solve for the ratio of C'_2/C'_1 ,

$$\frac{C'_2}{C'_1} = \frac{C_2 \pm \Delta C_2}{C_1 \pm \Delta C_1} = \frac{C_2}{C_1} \left(\frac{1 \pm \frac{\Delta C_2}{C_2}}{1 \pm \frac{\Delta C_1}{C_1}} \right) \approx \frac{C_2}{C_1} \left(1 \pm \frac{\Delta C_2}{C_2} \right) \left(1 \mp \frac{\Delta C_1}{C_1} \right) \approx \frac{C_2}{C_1} \left(1 \pm \frac{\Delta C_2}{C_2} \mp \frac{\Delta C_1}{C_1} \right)$$


If $\frac{\Delta C_2}{C_2} = \frac{\Delta C_1}{C_1}$, then $\boxed{\frac{C'_2}{C'_1} = \frac{C_2}{C_1}}$

Therefore, the best matching results are obtained when the area/periphery ratio of C_2 is equal to the area/periphery ratio of C_1 .

Capacitor Errors - Relative Accuracy


Capacitor relative accuracy is proportional to the area of the capacitors and inversely proportional to the difference in values between the two capacitors.

For example,

 

Capacitor Errors - Parasitics

 Parasitics are normally from the top and bottom plate to ac ground which is typically the substrate.



Top plate parasitic is 0.01 to 0.001 of C_{desired}

Bottom plate parasitic is 0.05 to 0.2 C_{desired}

Capacitor Errors - Temperature and Voltage Dependence

Polysilicon-Oxide-Semiconductor Capacitors

Absolute accuracy $\approx \pm 10\%$

Relative accuracy $\approx \pm 0.2\%$

Temperature coefficient $\approx +25 \text{ ppm}/\text{C}^\circ$

Voltage coefficient $\approx -50 \text{ ppm}/\text{V}$

Polysilicon-Oxide-Polysilicon Capacitors

Absolute accuracy $\approx \pm 10\%$

Relative accuracy $\approx \pm 0.2\%$

Temperature coefficient $\approx +25 \text{ ppm}/\text{C}^\circ$

Voltage coefficient $\approx -20 \text{ ppm}/\text{V}$

Accuracies depend upon the size of the capacitors.

SUMMARY

- Characterization of VCO's
 - Frequency,
 - Frequency tuning range
 - Frequency stability
 - Amplitude stability
 - Spectral purity
- Oscillators
 - RC
 - LC
 - Relaxation oscillators
 - Ring oscillators
 - Direct digital synthesis (DDS)
- Varactors
 - Used to vary the frequency of RC and LC oscillators