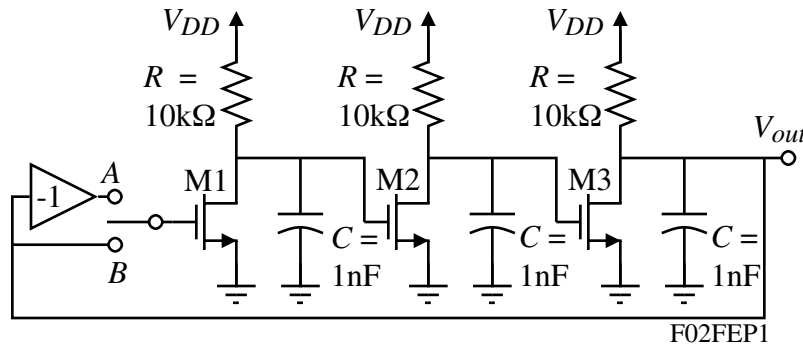


**FINAL EXAMINATION - SOLUTIONS**

(Average Score = 58/100)

**Problem 1 - (20 points - This problem must be attempted)**

The circuit shown is to be an oscillator. The transistors are identical with a  $g_m = 1\text{mS}$  and  $r_{ds} = \infty$ . (a.) Should the switch at the gate of M1 be connected to point A or B in order to oscillate? (b.) Find the frequency of oscillation in Hertz and the value of  $g_m R$  necessary for oscillation.

**Solution**

(a.) Assuming the switch is connected to B, the gain from the gate of M1 to  $V_{out}$  can be expressed as,

$$\frac{V_{out}}{V_{g1}} = T(s) = \left( \frac{-g_m R}{sRC + 1} \right)^3 = \frac{(-g_m R)^3}{(sRC)^3 + 3s^2 R^2 C^2 + 3sRC + 1}$$

$$T(j\omega) = \frac{-(g_m R)^3}{[1 - 3\omega^2 R^2 C^2] + j\omega RC [3 - 3\omega^2 R^2 C^2]} = 1 + j0$$

(b.) From the above equation, we get,

$$\omega_{osc} = \frac{\sqrt{3}}{RC} = \frac{1.732}{10 \times 10^3 \cdot 1 \times 10^{-9}} = 173.2 \text{Krad/sec} \quad \rightarrow \quad \underline{\underline{f_{osc} = 27.57 \text{kHz}}}$$

Also, from the above equation, we get


$$-(g_m R)^3 = 1 - 3\omega^2 R^2 C^2 = 1 - 9 = -8$$

$$\therefore (g_m R)^3 = 8 \quad \rightarrow \quad \underline{\underline{g_m R = 8^{0.33} = 2}}$$

We see that the switch should be connected to B. Otherwise,  $g_m R$  would be negative.

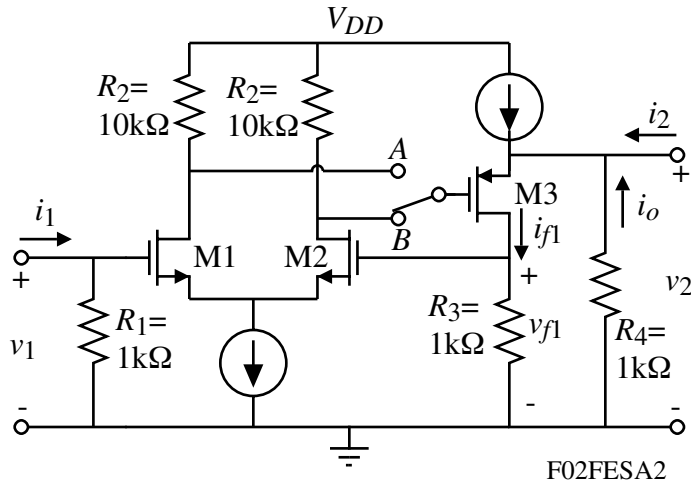Problem 2 – (20 points – This problem must be attempted)

The simplified schematic of a feedback amplifier is shown. Assume that all transistors are matched and  $g_m = 1\text{mA/V}$  and  $r_{ds} = \infty$ . (a.) Where should the switch be connected for negative feedback? (b.) Use the method of feedback analysis to find  $v_2/v_1$ ,  $R_{in} = v_1/i_1$ , and  $R_{out} = v_2/i_2$ .




Solution

(a.) A quick check of the ac voltage changes around the loop show that the switch should be connected to A.

(b.) This feedback circuit is series-series. The units of  $A$  are A/V and the units of  $\beta$  are V/A.

$$\beta = z_{12f} = \frac{v_{1f}}{i_{2f}} \Big|_{i_{1f}=0} = R_3 = 1\text{k}\Omega$$

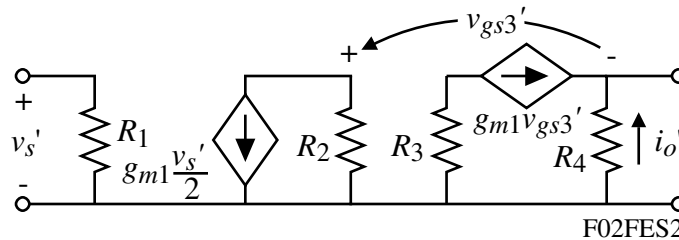The circuit for calculating the small-signal open-loop gain is,



$$A = \frac{i_o'}{v_s'} = \left(\frac{i_o'}{v_{gs3'}}\right) \left(\frac{v_{gs3'}}{v_s'}\right) \left(\frac{v_{id'}}{v_s'}\right) = (-g_{m3}) \left(\frac{1}{1+g_{m3}R_4}\right) \left(\frac{-g_{m1}R_2}{2}\right)$$

$$A = \frac{i_o'}{v_s'} = (1\text{mS})(0.5)(5) = 2.5\text{mS} \rightarrow A_F = \frac{i_o}{v_s} = \frac{A}{1+A\beta} = \frac{2.5\text{mS}}{1+2.5 \cdot 1} = 0.714 \text{ mS}$$

$$\frac{v_2}{v_1} = \frac{v_2}{v_s} = \left(\frac{v_2}{i_o}\right) \left(\frac{i_o}{v_s}\right) = -R_4(0.714\text{mS}) = -0.714 \text{ V/V}$$

$\frac{v_2}{v_s} = -0.714 \text{ V/V}$

$R_1$  is not influenced by feedback so  $\frac{v_1}{i_1} = R_1 = 1\text{k}\Omega$

$$R_o = R_4 + (1/g_{m3}) = 1\text{k}\Omega + 1\text{k}\Omega = 2\text{k}\Omega \rightarrow R_{oF} = 2\text{k}\Omega(1+2.5) = 7\text{k}\Omega$$

$$R_{out} = \frac{v_2}{i_2} = (R_{oF} - R_4) \parallel R_4 = 7\text{k}\Omega \parallel 1\text{k}\Omega = 875\Omega$$



$\frac{v_2}{i_2} = 875\Omega$

Problem 3 - (20 points - This problem is optional)

The simplified schematic of a feedback amplifier is shown. Use the method of feedback analysis to find  $v_2/v_1$ ,  $R_{in} = v_1/i_1$ , and  $R_{out} = v_2/i_2$ . Assume that all transistors are matched and that  $g_m = 1\text{mA/V}$  and  $r_{ds} = \infty$ .

Solution

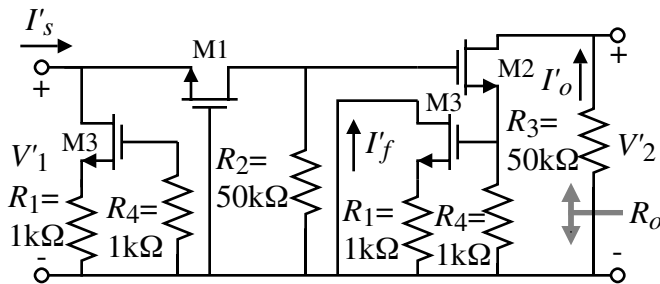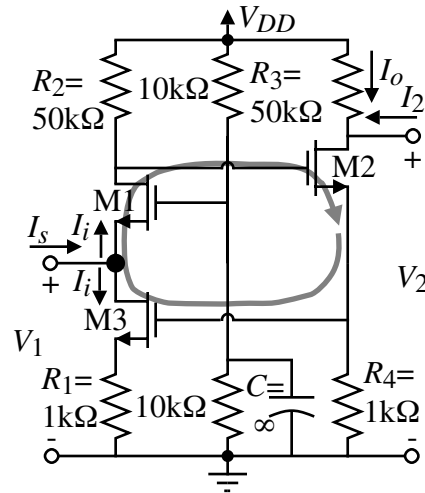This feedback circuit is shunt-series. We begin with the open-loop, quasi-ac model shown below.



The small-signal, open-loop model is:

$$\frac{I'_o}{I'_s} = \left( \frac{I'_o}{V_{gs2}} \right) \left( \frac{V_{gs2}}{V_{gs1}} \right) \left( \frac{V_{gs1}}{I'_s} \right)$$

$$V_{gs2} = -g_{m1} V_{gs1} R_2 - g_{m2} V_{gs2} R_4$$

or

$$\frac{V_{gs2}}{V_{gs1}} = \frac{-g_{m1} R_2}{1 + g_{m2} R_4} = -\frac{50}{2} = -25 \quad \therefore \frac{I'_o}{I'_s} = (g_{m2})(-25) \left( \frac{-1}{g_{m1}} \right) = 25\text{A/A}$$

$$\beta = \frac{I'_f}{I'_o} = \left( \frac{I'_f}{V_{gs3}} \right) \left( \frac{V_{gs3}}{I'_o} \right) = (g_{m3}) \left( \frac{R_1}{1 + g_{m3} R_4} \right) = (1\text{mA/V})(0.5\text{k}\Omega) = 0.5$$

$$\therefore A\beta = 25 \cdot 0.5 = 12.5$$


$$R_i = \frac{v_1}{I'_s} = \frac{1}{g_{m1}} = 1\text{k}\Omega \rightarrow R_{in} = R_{if} = \frac{R_i}{1 + A\beta} = \frac{1000}{13.5} = 74.07\Omega$$

$$R_{out} = 50\text{k}\Omega \text{ (} R_3 \text{ is outside the feedback loop)}$$

$$\frac{I_o}{I_s} = \frac{A}{1 + A\beta} = \frac{25}{1 + 12.5} = 1.852 \text{ A/A} \rightarrow \frac{v_2}{v_1} = \frac{I_o(-50\text{k}\Omega)}{I_s(74.07\Omega)} = -1240.1 \text{ V/V}$$

Problem 4 - (20 points - This problem is optional)

If the op amps shown are ideal (infinite voltage gain, infinite differential input resistance, and zero output resistance) find the voltage transfer function,  $V_{out}(s)/V_{in}(s)$ , the input impedance,  $Z_{in}(s)$ , and the output impedance,  $Z_{out}(s)$ . Sketch an asymptotic plot for the magnitude and phase shift of the voltage transfer function,  $V_{out}(j\omega)/V_{in}(j\omega)$  as a function of  $\log_{10}\omega$ .

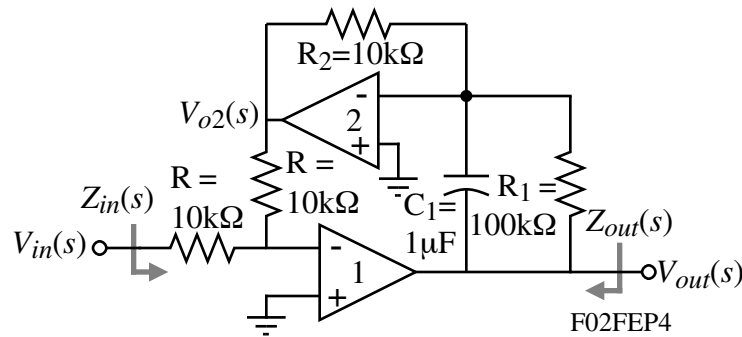Solution


$V_{o2}(s)$  can be written as  $V_{o2}(s) = -\frac{R_2}{Z_1}v_{out}(s)$ . Thus, the currents flowing toward the inverting terminal of the 1st op amp are,  $\frac{V_{in}(s)}{R} + \frac{V_{o2}(s)}{R} = \frac{V_{in}(s)}{R} - \frac{R_2}{Z_1} \frac{V_{out}(s)}{R} = 0$

$$\therefore \frac{V_{out}(s)}{V_{in}(s)} = \frac{Z_1(s)}{R_2} = \frac{1}{R_2} \frac{R_1(1/sC_1)}{R_1 + (1/sC_1)} = \frac{R_1}{R_2} \frac{1}{sR_1C_1 + 1} \quad \boxed{\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_1}{R_2} \frac{1}{sR_1C_1 + 1}}$$


By inspection,  $\boxed{Z_{in}(s) = R = 10k\Omega \text{ and } Z_{out}(s) = 0}$

For the Bode plot we want to plot the magnitude and phase of  $\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{10}{1+j\omega/10}$ .

Magnitude, dB

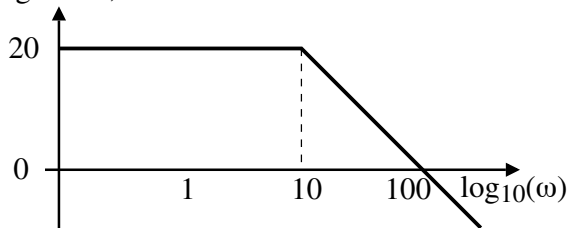

Phase Shift

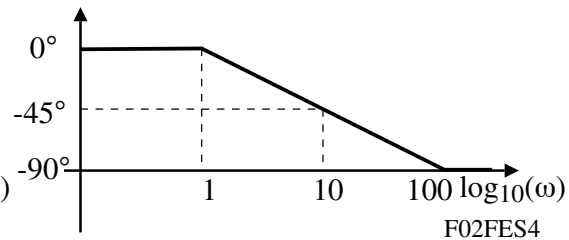



F02FES4

Problem 5 - (20 points - This problem is optional)

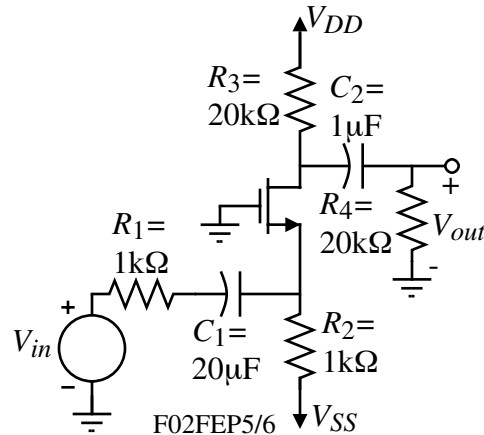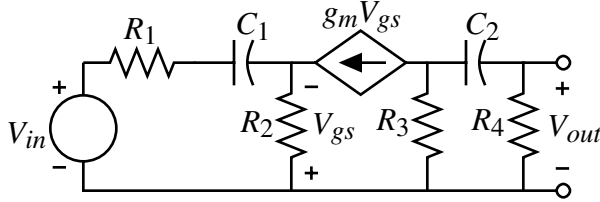- 1.) If  $g_m = 2\text{mA/V}$ , what is the midband voltage gain of the amplifier shown? Assume  $r_d = \infty$ .
- 2.) Find the lower -3dB frequency ( $f_L$ ) of the amplifier shown.

Solution

The small signal model for this problem is:



$$\frac{V_{out}(s)}{V_{in}(s)} = \left(\frac{V_{out}}{V_{gs}}\right) \left(\frac{V_{gs}}{V_{in}}\right)$$

$$\therefore \frac{V_{out}}{V_{gs}} = \frac{-g_m R_3 R_4}{R_3 + R_4 + \frac{1}{sC_2}} = \left(\frac{-g_m R_3 R_4}{R_3 + R_4}\right) \left(\frac{s}{s + \frac{1}{C_2(R_3 + R_4)}}\right) = (-20) \left(\frac{s}{s + 25}\right)$$

Next, find  $V_{gs}/V_{in}$ :

$$\frac{V_{in} + V_{gs}}{R_1 + \frac{1}{sC_1}} + \frac{V_{gs}}{R_2} + g_m V_{gs} = 0 \rightarrow \frac{-V_{in}}{R_1 + \frac{1}{sC_1}} = V_{gs} \left( \frac{1}{R_1 + \frac{1}{sC_1}} + \frac{1}{R_2 \parallel (1/g_m)} \right)$$

or

$$-V_{in} \left( R_2 \parallel \frac{1}{g_m} \right) = V_{gs} \left( R_2 \parallel \frac{1}{g_m} + R_1 \parallel \frac{1}{sC_1} \right) \rightarrow \frac{V_{gs}}{V_{in}} = \left( \frac{R_2 \parallel \frac{1}{g_m}}{R_1 + R_2 \parallel \frac{1}{g_m}} \right) \left( \frac{s}{s + \frac{1}{C_1 \left[ R_1 + R_2 \parallel \frac{1}{g_m} \right]}} \right)$$

$$\frac{V_{gs}}{V_{in}} = \frac{-0.33}{1 + 0.33} \left( \frac{s}{s + 37.5} \right) = (-0.25) \left( \frac{s}{s + 37.5} \right)$$

$$\text{Thus, } \frac{V_{out}(s)}{V_{in}(s)} = 5 \left( \frac{s}{s + 25} \right) \left( \frac{s}{s + 37.5} \right)$$



$$\therefore \text{MBG} = 5, \omega_L \approx \sqrt{(25)^2 + (37.5)^2} = 45.07 \text{ rads/sec} \rightarrow f_L = 7.17 \text{ Hz}$$

Problem 6 - (20 points - This problem is optional)

The FET in the amplifier shown has  $g_m = 1\text{mA/V}$ ,  $r_d = \infty$ ,  $C_{gd} = 0.5\text{pF}$ , and  $C_{gs} = 10\text{pF}$ . (a.) Find the midband gain,  $V_{out}/V_{in}$ . (b.) Find the upper -3dB frequency,  $f_H$ , in Hz. (Note: You cannot use the Miller's theorem on this problem because there is no bridging capacitor.)

Solution

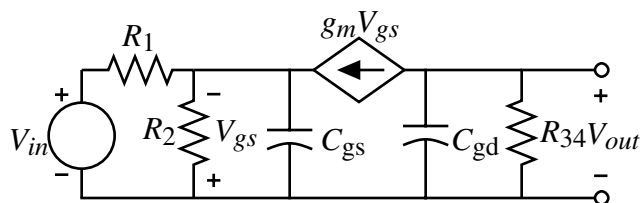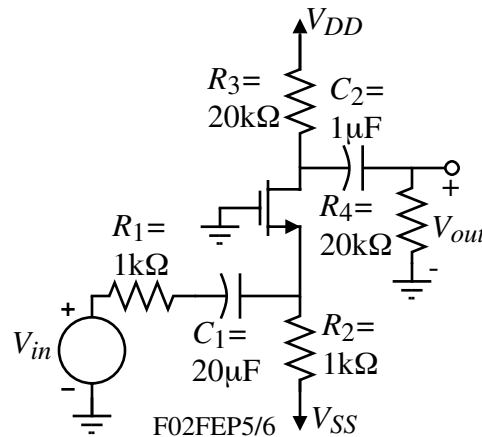The small signal model for the high frequency range is shown where  $R_{34} = R_3 \parallel R_4 = 10\text{k}\Omega$ .



Because the capacitors are independent, probably the best way to work this problem is by superposition (open-circuit time constants). Therefore,

$C_{gs}$ :

$$R_{C_{gs}} = R_1 \parallel R_2 \parallel (1/g_m) = 1\text{K} \parallel 1\text{K} \parallel 1\text{K} = 333\Omega \rightarrow \omega_{C_{gs}} = \frac{1}{C_{gs} \cdot 333\Omega} = 300 \text{ Mrads/sec.}$$

$C_{gd}$ :

$$R_{C_{gd}} = R_{34} = 10\text{k}\Omega \rightarrow \omega_{C_{gd}} = \frac{1}{C_{gd} \cdot 10\text{k}\Omega} = 200 \text{ Mrads/sec.}$$

$$\therefore \omega_H \approx \frac{1}{\sqrt{\left(\frac{1}{300\text{Mrads/sec}}\right)^2 + \left(\frac{1}{200\text{Mrads/sec}}\right)^2}} = 166 \text{ Mrads/sec.}$$

$$f_L = 26.48\text{MHz}$$


The midband gain is given as

$$\text{MBG} = \left( \frac{R_2 \parallel \frac{1}{g_m}}{R_1 + R_2 \parallel \frac{1}{g_m}} \right) \left( \frac{-g_m R_3 R_4}{R_3 + R_4} \right) = \left( \frac{-0.5}{1.5} \right) (-10) = 3.33 \text{ V/V}$$

Problem 7 - (20 points - This problem is optional).


A BJT amplifier is shown. Assume that the BJT has the small signal parameters of  $g_m = 50\text{mA/V}$ ,  $r_{\pi} = 2\text{k}\Omega$ , and  $r_o = \infty$ .

- Find the midband voltage gain of this amplifier,  $V_{out}/V_{in}$ .
- Find the numerical value of all poles and zeros of the low frequency response.
- Find the value of the lower -3dB frequency,  $f_L$ , in Hz.

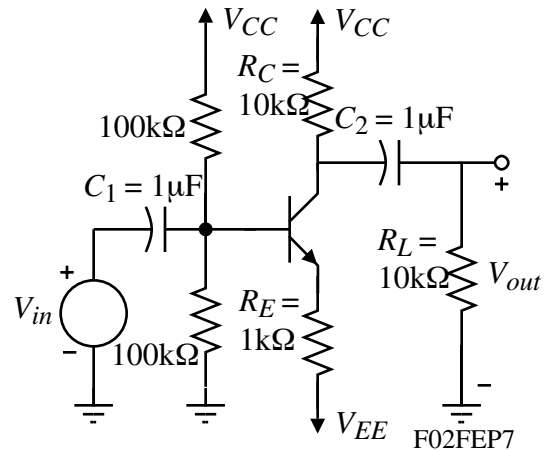Solution

The low-frequency, small signal model for this problem is shown where  $R_B = 50\text{k}\Omega$ .

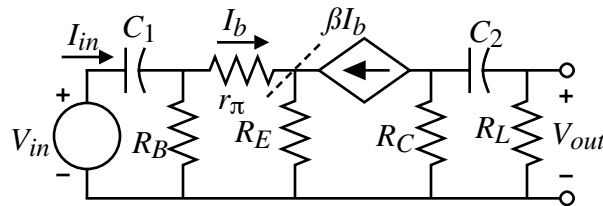The algebraic approach to this problem is:



$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{V_{out}}{I_b}\right) \left(\frac{I_b}{I_{in}}\right) \left(\frac{I_{in}}{V_{in}}\right) = \left(\frac{-\beta R_L R_C}{R_C + R_L + \frac{1}{sC_2}}\right) \left(\frac{R_B}{R_B + r_{\pi} + (1+\beta)R_E}\right) \left(\frac{1}{\frac{1}{sC_1} + R_B \parallel [r_{\pi} + (1+\beta)R_E]}\right) \\ &= \left(\frac{-\beta R_L R_C}{(R_C + R_L)[r_{\pi} + (1+\beta)R_E]}\right) \left(\frac{s}{s + \frac{1}{C_2(R_C + R_L)}}\right) \left(\frac{s}{s + \frac{1}{C_1(R_B \parallel [r_{\pi} + (1+\beta)R_E])}}\right) \\ &= \frac{-100 \cdot 10\text{K} \cdot 10\text{K}}{20\text{K} \cdot 103\text{K}} \left(\frac{s}{s+50}\right) \left(\frac{s}{s+29.7}\right) = -4.854 \left(\frac{s}{s+50}\right) \left(\frac{s}{s+29.7}\right) \end{aligned}$$

The midband gain is  $\boxed{MBG = 4.854 \text{ V/V}}$

$$\therefore \omega_L \approx \sqrt{(29.7)^2 + (50)^2} = 58.2 \text{ rads/sec.} \rightarrow \boxed{f_L = 9.26 \text{ Hz}}$$


The poles and zeros are,

$\boxed{\text{Two zeros at } s = 0, \text{ a pole at } s = -29.7 \text{ rads/sec. and a pole at } s = -50 \text{ rads/sec.}}$

**Problem 8 – (20 points, this problem is optional)**

A common-emitter BJT amplifier is shown. Assume that the BJT has a  $\beta = h_{fe} = 100$ ,  $C_{\mu} = 2\text{pF}$ ,  $V_t = 25\text{mV}$ ,  $f_T = 500\text{MHz}$ ,  $r_b = 0\Omega$ , and  $r_o = \infty$ .

- a.) Find the numerical values of  $r_{\pi}$ ,  $g_m$ , and  $C_{\pi}$   
 b.) If  $r_{\pi} = 1\text{k}\Omega$ ,  $g_m = 0.01\text{A/V}$  and  $C_{\pi} = 10\text{pF}$  for the above amplifier, find the value of the upper -3dB frequency,  $f_H$ , in Hz.

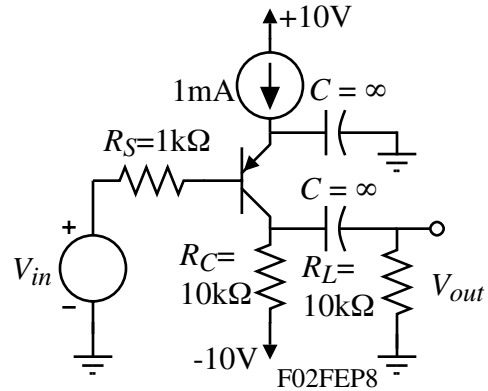**Solution**


$$a.) \quad g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{25\text{mV}} = 0.04 \text{ A/V}$$

$$r_{\pi} = \frac{\beta_o}{g_m} = \frac{100}{0.04} = 2500\Omega$$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu} = \frac{0.04}{2\pi \cdot 500 \times 10^6} - 2\text{pF} = 12.732\text{pF} - 2\text{pF} = 10.732 \text{ pF}$$

- b.) The high-frequency, small-signal model for this problem is shown where  $R_{CL} = R_C \parallel R_L = 5\text{k}\Omega$ .

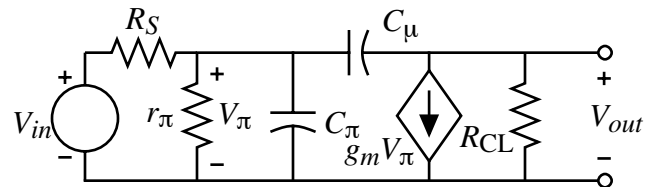The midband gain of this amplifier is given by



$$\frac{V_{out}}{V_{in}} = \left( \frac{V_{out}}{V_{\pi}} \right) \left( \frac{V_{\pi}}{V_{in}} \right) = -g_m R_{CL} \left( \frac{r_{\pi}}{r_{\pi} + R_S} \right) = (-0.01 \cdot 5\text{k}\Omega)(0.5) = -25\text{V/V}$$

$$\therefore \text{MBG} = -25 \text{ V/V}$$

Using Miller's theorem on this problem:

$$\text{If } \frac{1}{\omega_H C} \gg R_C \parallel R_L, \text{ then } C_{eq} \approx C_{\pi} + C_{\mu} (1 + g_m R_C \parallel R_L) = 10\text{pF} + 2\text{pF}(1+50) = 112\text{pF}$$

$$\text{We know that, } \omega_H = \frac{1}{C_{eq}(r_{\pi} \parallel R_S)} = \frac{1}{(112\text{pF} \cdot 500\Omega)} = 17.86 \text{ Mrads/sec.}$$

$$\therefore f_H = \frac{\omega_H}{2\pi} = 2.842 \text{ MHz}$$

Note that:

$$\frac{1}{\omega_H C} = \frac{10^6}{17.86 \cdot 2} = 28.06\text{k}\Omega > 5\text{k}\Omega \text{ so that the Miller approximation (neglecting } C_{\mu})$$

is valid.