

FINAL EXAMINATION


NAME _____ P.O. Box No. _____ SCORE _____ /100

| Problem | ① | ② | 3 | 4 | 5 | 6 | 7 | 8 | Sum |
|---------|---|---|---|---|---|---|---|---|-----|
| Points | | | | | | | | | |

INSTRUCTIONS: This exam is closed book with two sheets of notes permitted. The exam consists of 8, 20-point problems of which you are to work only 5 for a total of 100 points. Problems 1 and 2 must be worked and you may choose any three of the last six problems for a total of five problems. Please circle the number in the table above of the five problems you wish graded. If you do not indicate the problems to be graded, then problems 1 through 5 will be graded regardless of whether they are worked or not. Be sure to turn in only the 5 problems you wish graded in proper numerical order. Please show your work leading to your answers so that maximum partial credit may be given where appropriate.


Problem 1 - (20 points - This problem must be attempted)

The circuit shown is to be an oscillator. The transistors are identical with a $g_m = 1\text{mS}$ and $r_{ds} = \infty$. (a.) Should the switch at the gate of M1 be connected to point *A* or *B* in order to oscillate? (b.) Find the frequency of oscillation in Hertz and the value of $g_m R$ necessary for oscillation.

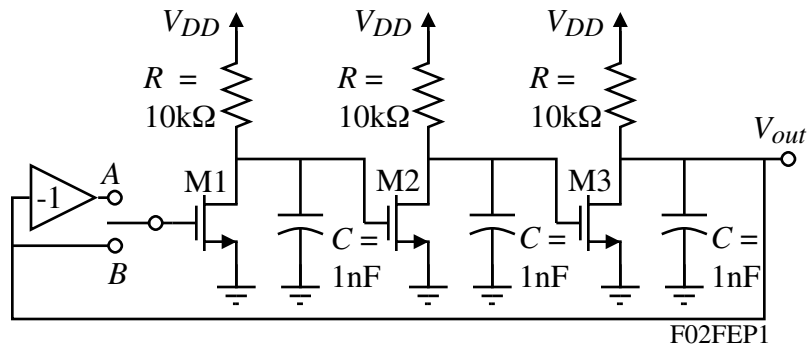


Problem 2 – (20 points – This problem must be attempted)

The simplified schematic of a feedback amplifier is shown. Assume that all transistors are matched and $g_m = 1\text{mA/V}$ and $r_{ds} = \infty$. (a.) Where should the switch be connected for negative feedback? (b.) Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$.

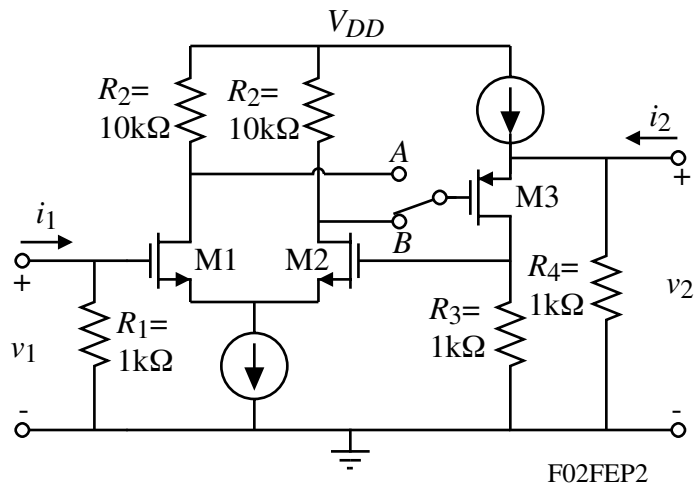


Problem 3 - (20 points - This problem is optional)

The simplified schematic of a feedback amplifier is shown. Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$. Assume that all transistors are matched and that $g_m = 1\text{mA/V}$ and $r_{ds} = \infty$.

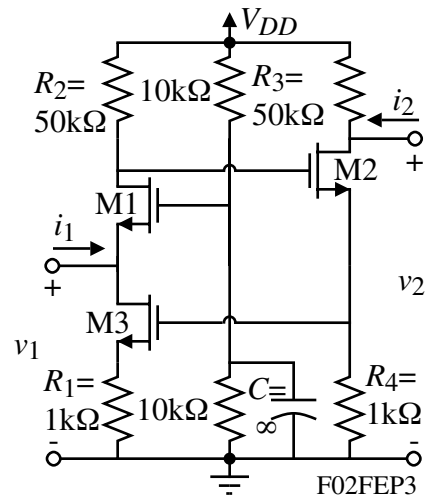


Problem 4 - (20 points - This problem is optional)

If the op amps shown are ideal (infinite voltage gain, infinite differential input resistance, and zero output resistance) find the voltage transfer function, $V_{out}(s)/V_{in}(s)$, the input impedance, $Z_{in}(s)$, and the output impedance, $Z_{out}(s)$. Sketch an asymptotic plot for the magnitude and phase shift of the voltage transfer function, $V_{out}(j\omega)/V_{in}(j\omega)$ as a function of $\log_{10}\omega$.

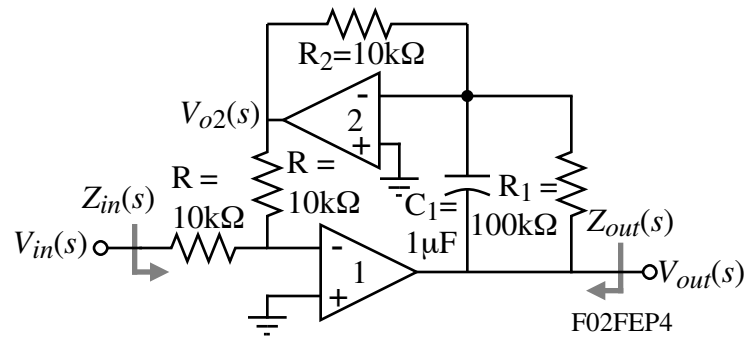


Problem 5 - (20 points - This problem is optional)

- 1.) If $g_m = 2\text{mA/V}$, what is the midband voltage gain of the amplifier shown? Assume $r_d = \infty$.
- 2.) Find the lower -3dB frequency (f_L) of the amplifier shown.

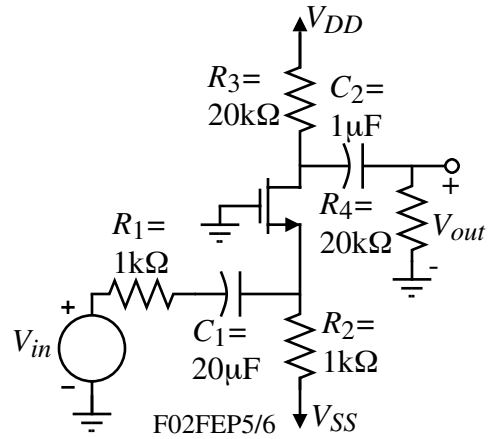

Problem 6 - (20 points - This problem is optional)


The FET in the amplifier shown has $g_m = 1\text{mA/V}$, $r_d = \infty$, $C_{gd} = 0.5\text{pF}$, and $C_{gs} = 10\text{pF}$. (a.) Find the midband gain, V_{out}/V_{in} . (b.) Find the upper -3dB frequency, f_H , in Hz. (Note: You cannot use the Miller's theorem on this problem because there is no bridging capacitor.)

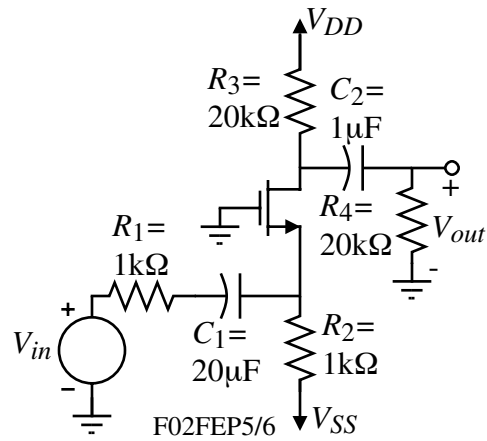

Problem 7 - (20 points - This problem is optional).

A BJT amplifier is shown. Assume that the BJT has the small signal parameters of $g_m = 50\text{mA/V}$, $r_{\pi} = 2\text{k}\Omega$, and $r_o = \infty$.


- Find the midband voltage gain of this amplifier, V_{out}/V_{in} .
- Find the numerical value of all poles and zeros of the low frequency response.
- Find the value of the lower -3dB frequency, f_L , in Hz.

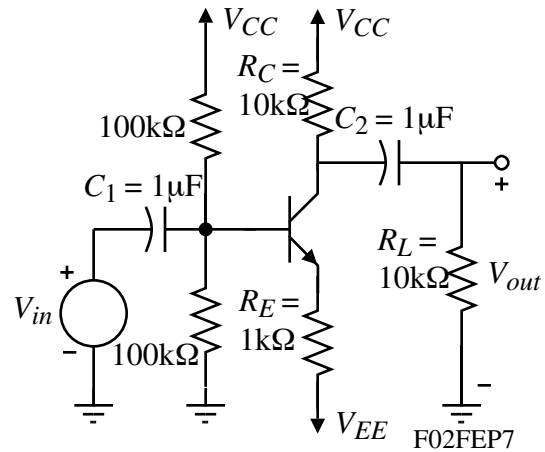

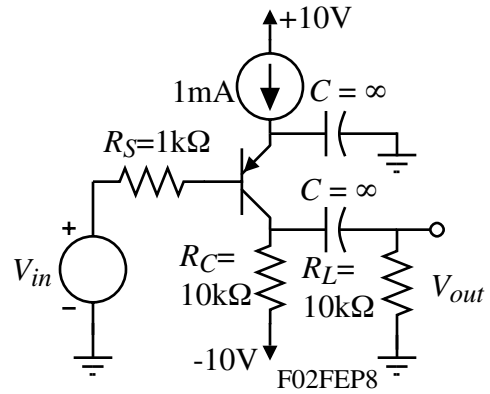Problem 8 – (20 points, this problem is optional)

A common-emitter BJT amplifier is shown. Assume that the BJT has a $\beta = h_{fe} = 100$, $C_{\mu} = 2\text{pF}$, $V_t = 25\text{mV}$, $f_T = 500\text{MHz}$, $r_b = 0\Omega$, and $r_o = \infty$.

- Find the numerical values of r_{π} , g_m , and C_{π} .
- If $r_{\pi} = 1\text{k}\Omega$, $g_m = 0.01\text{A/V}$ and $C_{\pi} = 10\text{pF}$ for the above amplifier, find the value of the upper -3dB frequency, f_H , in Hz.



Extra Sheet