

**Homework Assignment No. 9 - Solutions****17.1**

$$A_V(s) = 25 \frac{s^2}{(s+1)(s+20)} \quad | \quad A_{mid} = 25 \quad | \quad F_L(s) = \frac{s^2}{(s+1)(s+20)} \quad | \quad \text{Poles: } -1, -20 \quad | \quad \text{Zeros: } 0, 0$$

$$\text{yes, } s = -20 \quad | \quad A_V(s) \approx 25 \frac{s}{(s+20)} \quad | \quad \omega_L = 20 \frac{\text{rad}}{s} \quad | \quad f_L = \frac{\omega_L}{2\pi} \approx \frac{20}{2\pi} = 3.18 \text{ Hz}$$

$$f_L = \frac{1}{2\pi} \sqrt{20^2 + 1^2 - 2(0)^2 - 2(0)^2} = 3.19 \text{ Hz}$$

$$|A_V(j\omega)| = \frac{25\omega^2}{\sqrt{\omega^2 + 1^2} \sqrt{\omega^2 + 20^2}} \quad | \quad \text{MATLAB: } -3.19 \text{ Hz}$$


**17.4**

$$A_V(s) = \frac{(2 \times 10^{11})(10^{-4})(10^{-5})}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)} = \frac{200}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)} \quad | \quad A_{mid} = 200 \quad | \quad F_H(s) = \frac{1}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)}$$


$$\text{Poles: } -10^4, -10^5 \frac{\text{rad}}{s} \quad | \quad \text{Yes: } A_V(s) \approx \frac{200}{\frac{s}{10^4} + 1} \quad | \quad \omega_H = 10^4 \frac{\text{rad}}{s} \quad | \quad f_H \approx \frac{10^4}{2\pi} = 1.59 \text{ kHz}$$

$$f_H \approx \frac{1}{2\pi} \left( \sqrt{\left(\frac{1}{10^4}\right)^2 + \left(\frac{1}{10^5}\right)^2 - 2\left(\frac{1}{\infty}\right)^2 - 2\left(\frac{1}{\infty}\right)^2} \right)^{-1} = 1.58 \text{ kHz}$$

$$|A_V(j\omega)| = \frac{2 \times 10^{11}}{\sqrt{\omega^2 + (10^4)^2} \sqrt{\omega^2 + (10^5)^2}} \quad | \quad \text{MATLAB: } 1.58 \text{ kHz}$$

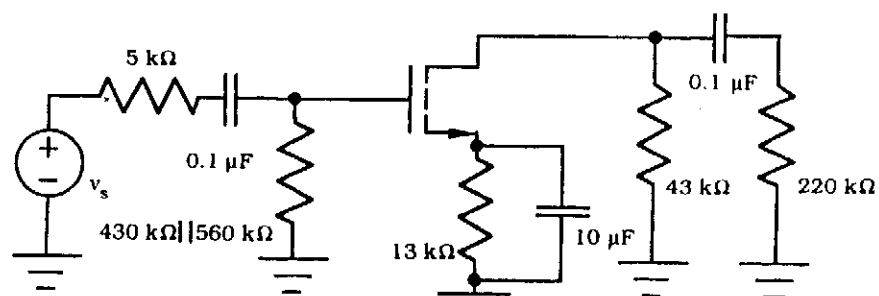**17.10**

Low frequency:

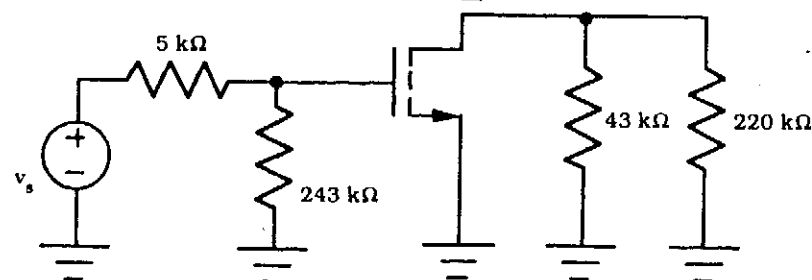

**17.10 Continued**

Mid-band:


$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}} = \frac{2(0.2\text{mA})}{1\text{V}} = 0.400\text{mS}$$

$$A_{\text{mid}} = -\frac{243\text{k}\Omega}{243\text{k}\Omega + 5\text{k}\Omega} (0.400\text{mS})(43\text{k}\Omega \parallel 220\text{k}\Omega) = -14.1$$

$$\omega_1 = \frac{1}{(10^{-7}\text{F})(243\text{k}\Omega + 5\text{k}\Omega)} = 40.3 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_2 = \frac{1}{(10^{-7}\text{F})(43\text{k}\Omega + 220\text{k}\Omega)} = 38.0 \frac{\text{rad}}{\text{s}}$$

$$\omega_3 = \frac{1}{(10^{-5}\text{F})\left(13\text{k}\Omega \parallel \frac{1}{g_m}\right)} = \frac{1}{(10^{-5}\text{F})(13\text{k}\Omega \parallel 2.5\text{k}\Omega)} = 47.7 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_z = \frac{1}{(10^{-5}\text{F})(13\text{k}\Omega)} = 7.69 \frac{\text{rad}}{\text{s}}$$

$$\text{Using Eq. (17.16): } f_L \approx \frac{1}{2\pi} \sqrt{(40.3)^2 + (38.0)^2 + (47.7)^2 - 2(7.69)^2} = 11.5 \text{ Hz}$$

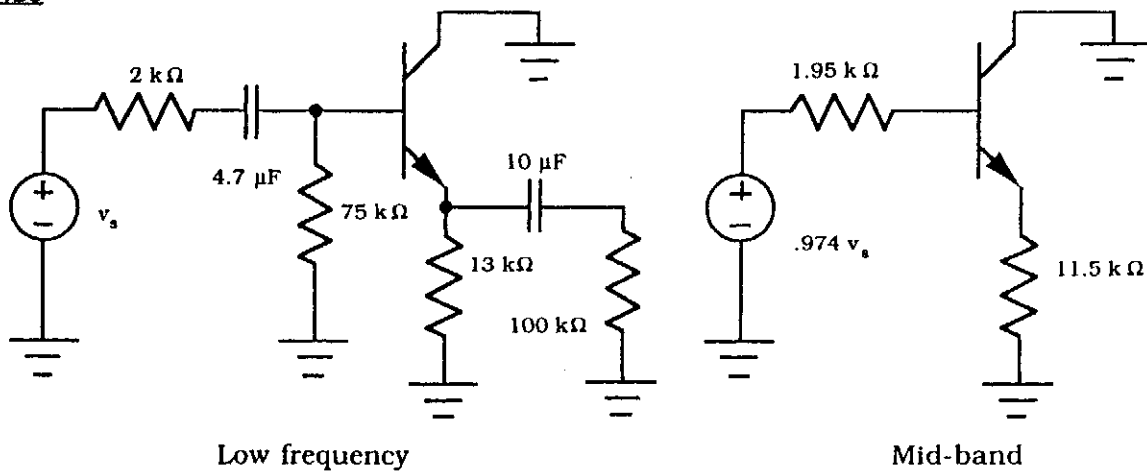**17.16**

$$(b) \ v_{\text{th}} = \frac{75\text{k}\Omega}{75\text{k}\Omega + 2\text{k}\Omega} v_s = 0.974 v_s \quad | \quad R_{\text{th}} = 75\text{k}\Omega \parallel 2\text{k}\Omega = 1.95\text{k}\Omega \quad | \quad R_L = 13\text{k}\Omega \parallel 100\text{k}\Omega = 11.5\text{k}\Omega$$

$$r_\pi = \frac{100}{40(0.25\text{mA})} = 10.0\text{k}\Omega \quad | \quad A_{\text{mid}} = 0.974 \frac{101(11.5\text{k}\Omega)}{[1.95 + 10.0 + 101(11.5)]\text{k}\Omega} = 0.964$$

$$R_{\text{IS}} = R_S + R_B \parallel [r_\pi + (\beta_o + 1)R_L] = 2\text{k}\Omega + 75\text{k}\Omega \parallel [10.0\text{k}\Omega + (101)11.5\text{k}\Omega] = 72.5\text{k}\Omega$$

$$\omega_1 = \frac{1}{(72.5\text{k}\Omega)4.7 \times 10^{-6}} = 2.94 \frac{\text{rad}}{\text{s}}$$

$$R_{\text{3S}} = R_7 + R_4 \parallel \frac{R_{\text{th}} + r_\pi}{(\beta_o + 1)} = 100\text{k}\Omega + 13\text{k}\Omega \parallel \frac{1.95\text{k}\Omega + 10.0\text{k}\Omega}{101} = 100\text{k}\Omega$$

$$\omega_3 = \frac{1}{10^{-5}(10^5)} = 1 \frac{\text{rad}}{\text{s}} \quad f_L \approx \frac{(2.94 + 1)}{2\pi} = 0.627\text{Hz}$$