

Continue Chapter 11


## 1.) Bandpass

$$A_v(s) = \frac{A_0 s}{s + w_L} \times \frac{w_H}{s + w_H} \xrightarrow{\text{Assume}} A_v(s) = \frac{-10 s 10^4}{(s + 10)(s + 10^4)}$$

Plot the magnitude and phase -

$$A_v(j\omega) = \frac{-10^5 j\omega}{(j\omega + 10)(j\omega + 10^4)} = \frac{(j\frac{\omega}{10})}{(1 + j\frac{\omega}{10})(1 + j\frac{\omega}{10^4})}$$

$$\text{dB} \quad 20 \log_{10} |A_v(j\omega)| = 20 \log_{10}(\omega) - 20 \log_{10} \sqrt{1 + (\frac{\omega}{10})^2} - 20 \log_{10} \sqrt{1 + (\frac{\omega}{10^4})^2}$$

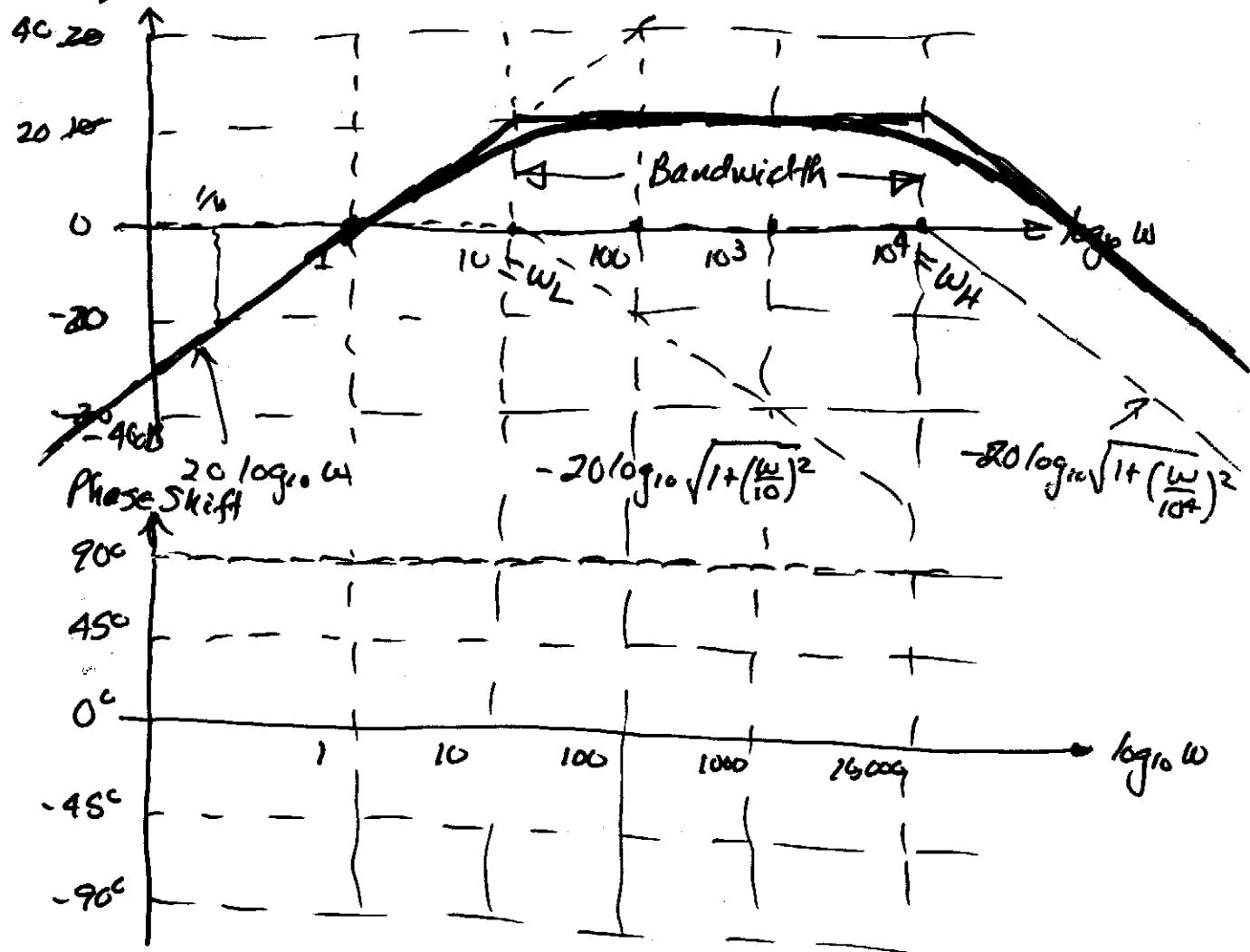


$$\text{Arg}[A_v(j\omega)] = \pm 180^\circ + 90^\circ - \tan^{-1}\left(\frac{\omega}{10}\right) - \tan^{-1}\left(\frac{\omega}{10^4}\right)$$

9/04/02

6  
Page 2Lecture 6 - Frequency Response Continued
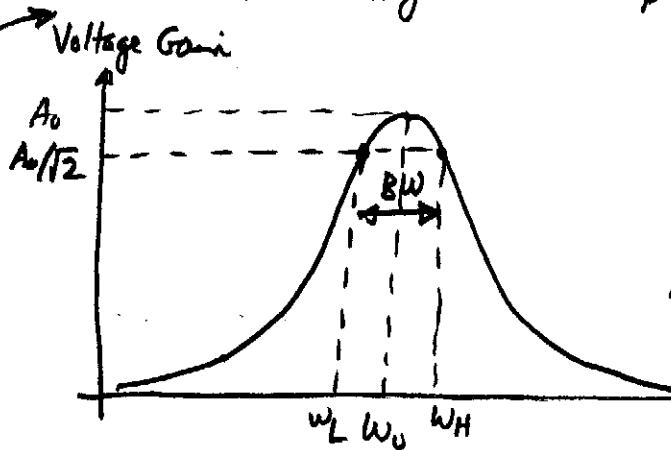
## 1.) Narrow-Band or High-Q Bandpass Amplifier




$$|A_v(jw)| = \frac{\frac{1}{Q} \frac{w}{w_0}}{\sqrt{\left[1 - \left(\frac{w}{w_0}\right)^2\right]^2 + \left(\frac{w}{Qw_0}\right)^2}}$$

$$\begin{aligned} \text{Arg}[A_v(jw)] &= \pm 180^\circ + 90^\circ - \tan^{-1} \left[ \frac{w w_0}{Q(w_0^2 - w^2)} \right] \\ &= \pm 180^\circ + 90^\circ - \tan^{-1} \left[ \frac{w w_0 Q}{1 - \left(\frac{w}{w_0}\right)^2} \right] \end{aligned}$$

Complex Poles -
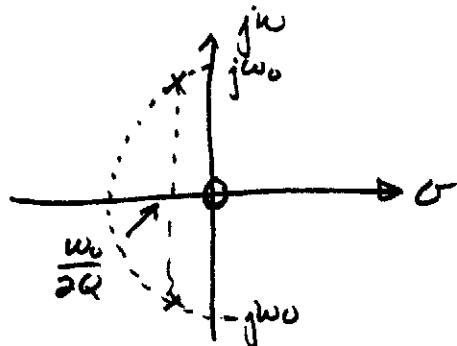
$$A_v(s) = A_0 \frac{s \frac{w_0}{Q}}{s^2 + \frac{w_0}{Q}s + w_0^2}$$





## 2.) Band-Rejection Amplifiers

jw axis zeros

$$A_v(s) = A_0 \frac{s^2 + w_0^2}{s^2 + \frac{w_0}{Q}s + w_0^2}$$

Voltage Gain

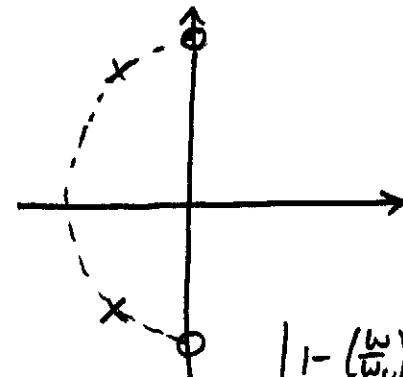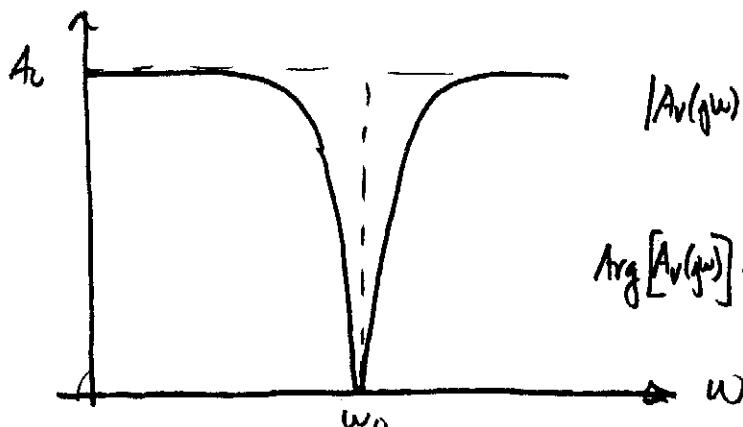


$$|A_v(jw)| = \frac{1}{\sqrt{\left(1 - \left(\frac{w}{w_0}\right)^2\right)^2 + \left(\frac{w}{Qw_0}\right)^2}}$$

$$\text{Arg}[A_v(jw)] = \angle A_0 + \angle \left[ \frac{(w_0^2 - w^2)}{Qw_0} \right] - \tan^{-1} \left[ \frac{\frac{w}{Qw_0}}{1 - \left(\frac{w}{w_0}\right)^2} \right]$$

## LECTURE 7 - OPERATIONAL AMPLIFIERS (OPAMPS)

### 1.) Differential Amplifier

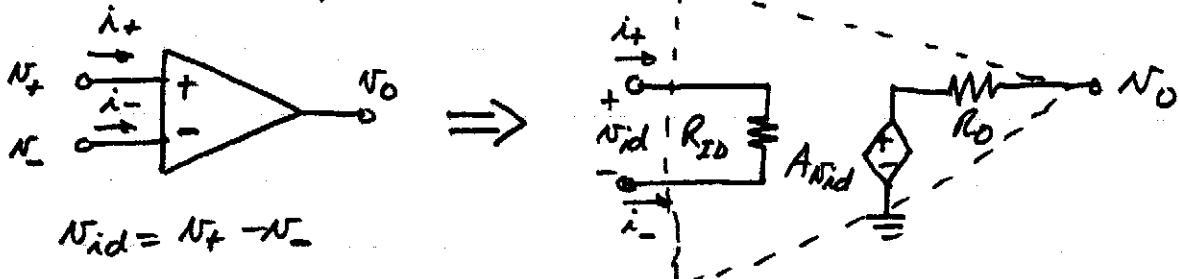


### 2.) Ideal Op Amp

- 1.)  $N_{id} = 0$

- 2.)  $i_+ = i_- = 0$

### 3.) Inverting Amplifier

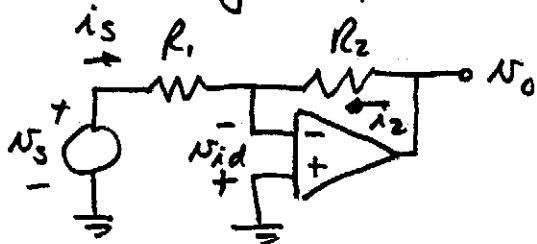

$$i_s = \frac{N_s + N_{id}}{R_1} = \frac{N_s}{R_1}$$

$$i_2 = \frac{N_o + N_{id}}{R_2} = \frac{N_o}{R_2}$$


$$i_s + i_2 = 0$$

$$R_{in} = \frac{N_s}{i_s} = \frac{N_s}{N_s/R_1} = \underline{\underline{R_1}}$$

$$\therefore \frac{N_o}{R_2} = -\frac{N_s}{R_1} \rightarrow \underline{\underline{\frac{N_o}{N_s} = -\frac{R_2}{R_1}}}$$

$$R_{out} = \underline{\underline{0}} \text{ (because } R_o = 0)$$

### 4.) Noninverting Amplifier

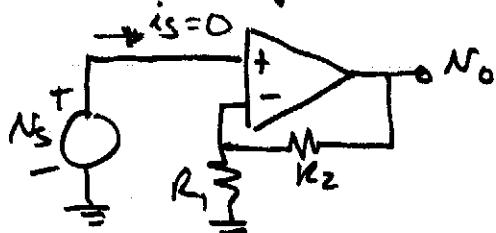

$$N_+ = N_s \quad \& \quad N_- = N_o \frac{R_1}{R_1 + R_2}$$


$$\text{but } N_+ = N_- \text{ so } N_o = \frac{R_1 + R_2}{R_1} N_s$$

$$R_{in} = \frac{N_s}{i_s} = \underline{\underline{\infty}} \quad R_{out} = \underline{\underline{0}}$$

9/4/02

~~Page 4~~  
Page 4

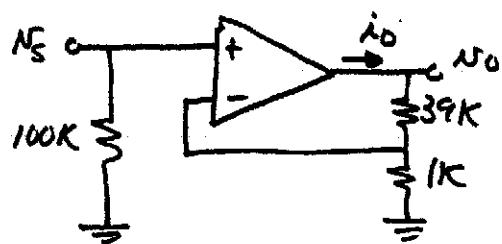5.) Example - What is the voltage gain in dB and  $R_{in}$ ?  
 If  $N_s = 0.25V$ , what is  $N_o$  and  $i_o$ ?



$$N_o = \frac{R_2 + R_1}{R_1} N_s = 40 N_s$$


$$A_v = 40 \rightarrow \underline{\underline{32 \text{dB}}}$$

$$R_{in} = \underline{\underline{100 \text{k}\Omega}}$$

$$N_s = \frac{1}{4} V \rightarrow N_o = \underline{\underline{10V}} \quad \text{and} \quad i_o = \frac{10}{40k} = \underline{\underline{0.25 \text{mA}}}$$


### 6.) Op Amp Circuits

a.) Buffer

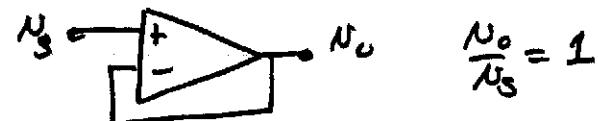


$$\frac{N_o}{N_s} = 1$$

b.) Summing Amplifier

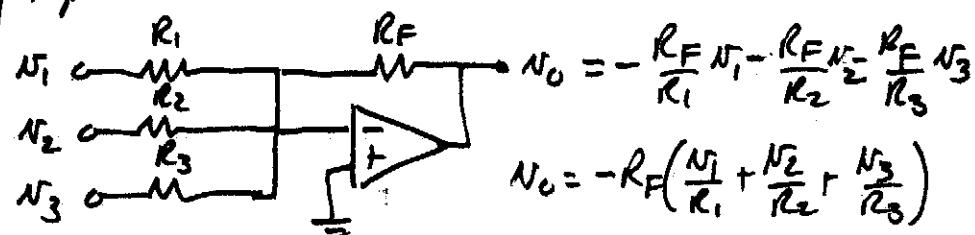

$$N_o = -R_F \left( \frac{N_1}{R_1} + \frac{N_2}{R_2} + \frac{N_3}{R_3} \right)$$

c.) Difference Amplifier

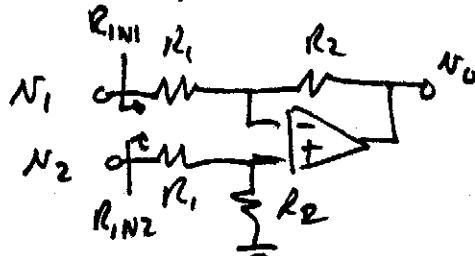

$$N_+ = \frac{N_2 R_2}{R_1 + R_2}$$

$$N_- = \frac{N_1 R_2}{R_1 + R_2} + \frac{N_0 R_1}{R_1 + R_2}$$

$$\therefore N_0 \frac{R_1}{R_1 + R_2} = \frac{N_2 R_2}{R_1 + R_2} - \frac{N_1 R_2}{R_1 + R_2} \rightarrow N_0 = \underline{\underline{\frac{R_2}{R_1} (N_2 - N_1)}}$$

$$R_{in1} = R_1 \quad \text{and} \quad R_{in2} = R_1 + R_2$$