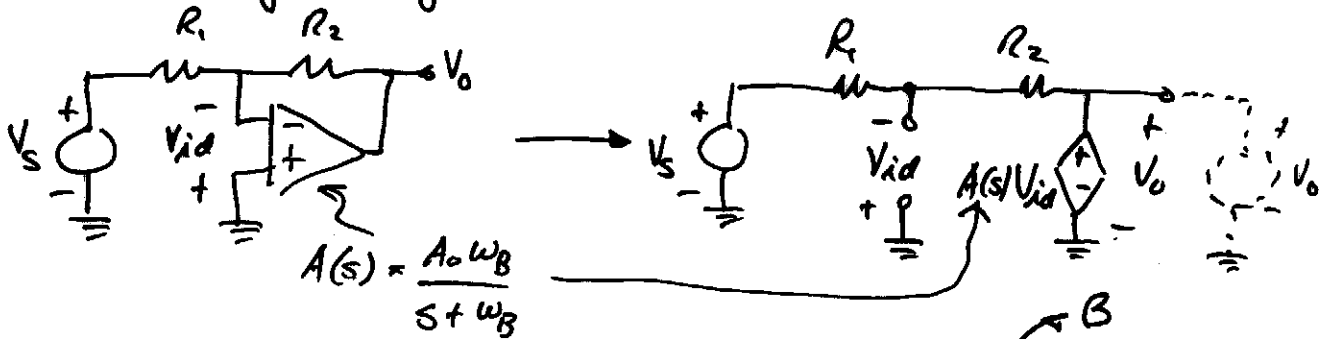


Frequency Response of OP Amps

1.) Inverting Configuration



$$V_o(s) = A(s) V_{id} = A(s) \left[-V_s \frac{R_2}{R_1 + R_2} - V_o \frac{R_1}{R_1 + R_2} \right]$$

$$V_o \left[1 + \frac{A(s) R_1}{R_1 + R_2} \right] = -\frac{A(s) R_2}{R_1 + R_2} V_s = -A(s) \frac{R_2}{R_1} \frac{R_1}{R_1 + R_2} V_s$$


$$A_v(s) = \frac{V_o(s)}{V_s(s)} = \frac{-\frac{R_2}{R_1} A(s) B}{1 + A(s) B} = \frac{-\frac{R_2}{R_1} B}{\frac{1}{A(s)} + B} \quad B = \frac{R_1}{R_1 + R_2}$$

$$A_v(s) = \frac{-\frac{R_2}{R_1} B}{\frac{s + \omega_B}{\omega_B A_0} + B} = \frac{-\frac{R_2}{R_1} B \omega_B A_0}{s + \omega_B (1 + A_0 B)}$$

$$= \frac{-\frac{R_2}{R_1} \frac{\omega_B A_0}{\omega_B (1 + A_0 B)}}{\frac{s}{\omega_B (1 + A_0 B)} + 1} = \frac{A_v(0)}{\frac{s}{\omega_H} + 1}$$

∴ $\omega_H = \omega_B (1 + A_0 B) \approx \omega_B A_0 B$
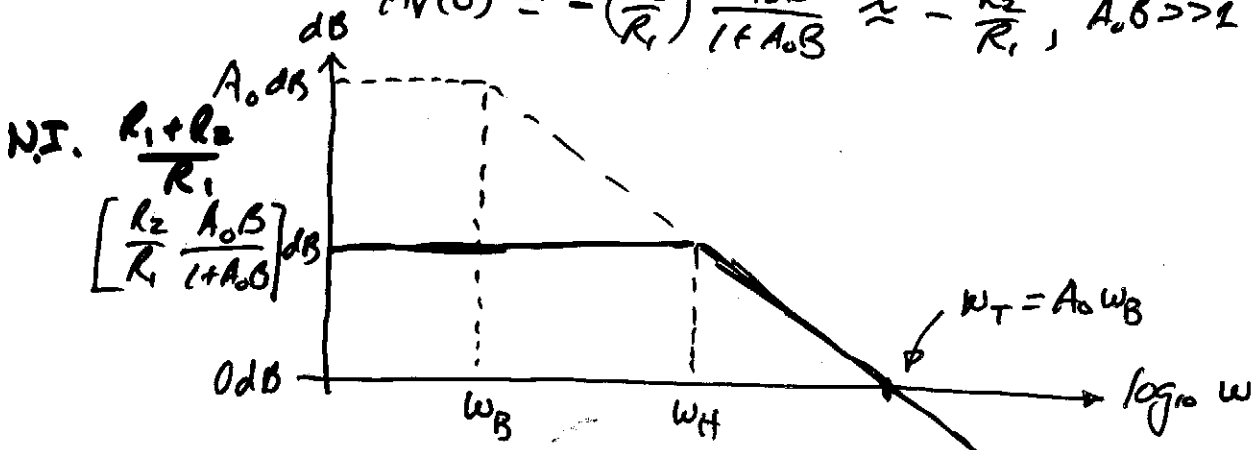
$$A_v(0) = -\left(\frac{R_2}{R_1}\right) \frac{A_0 B}{1 + A_0 B} \approx -\frac{R_2}{R_1}, \quad A_0 B \gg 1$$



2.) Summary

Config.	$A_v(0)$	ω_H
Non inverting	$\frac{R_1 + R_2}{R_1}$	$\omega_B (1 + A_0 B)$
Inverting	$-\frac{R_2}{R_1} \left(\frac{A_0 B}{1 + A_0 B} \right)$	$\omega_B (1 + A_0 B)$

$B = \frac{R_1}{R_1 + R_2}$


← Closed-loop gain

3.) Examples

- a.) An op amp ~~has~~ with $A_0 = 100 \text{ dB}$ and $f_T = 10 \text{ MHz}$ is used to build an amplifier with a gain of $+1$ and -1 . Find f_H .

Noninverting: ($R_1 = \infty$ and $R_2 = 0$)
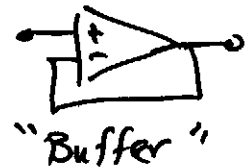
$$f_{-3\text{dB}} = f_B = \frac{f_T}{A_0} = \frac{10^7}{10^5} = 10^2$$



$$f_H = f_B (1 + A_0 B) = 10^2 (1 + 10^5 \cdot 1) \approx 10^7 \text{ or } \underline{\underline{10 \text{ MHz}}}$$

Inverting: ($R_1 = R_2 \rightarrow \text{Gain} = -1$)

Note that $B = \frac{1}{2}$

$$f_H = f_{-3\text{dB}} = 10^2 (1 + 10^5 \cdot \frac{1}{2}) = \underline{\underline{5 \text{ MHz}}}$$


- b.) Repeat the above but let the closed-loop amplifier gains be ± 100 .

Noninverting: $R_1 = 99R_2 \rightarrow B = \frac{1}{100}$

$$f_H = f_B (1 + A_0 B) = 100 (1 + 10^5 \cdot 10^{-2}) = 100 \text{ kHz}$$


Inverting: $R_1 = 100R_2 \rightarrow B = \frac{1}{101}$
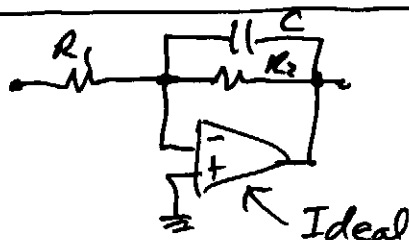
$$f_H = 100 (1 + 10^5 \cdot \frac{1}{101}) \approx \underline{\underline{99.5 \text{ kHz}}} \text{ (Guess)}$$



$$\frac{A_v(0)}{\frac{f}{\omega_H} + 1}$$

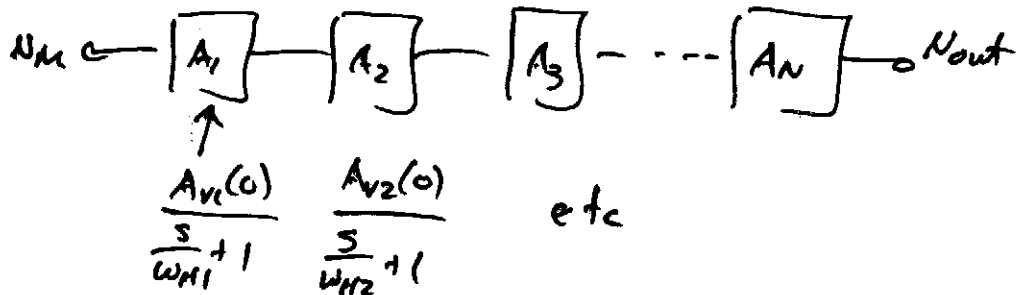4.) Frequency response of cascaded amplifiers



$$\frac{V_{out}(s)}{V_{in}(s)} = A_V(s) \stackrel{?}{=} \frac{A_V(0)}{\left(\frac{s}{\omega_{H1}} + 1\right) \left(\frac{s}{\omega_{H2}} + 1\right) \left(\frac{s}{\omega_{H3}} + 1\right) \cdots \left(\frac{s}{\omega_{HN}} + 1\right)}$$

$$A_V(0) = A_{V1}(0) A_{V2}(0) \cdots A_{VN}(0)$$

$$\omega_H = ? \quad |A_V(j\omega_H)| = \frac{|A_{V1}(0) A_{V2}(0) \cdots A_{VN}(0)|}{\sqrt{2}}$$

5.) Cascade of identical stages

$$A_V(s) = \left(\frac{A_{V1}(0)}{\frac{s}{\omega_{H1}} + 1} \right)^N \rightarrow A_V(0) = [A_{V1}(0)]^N$$

$$\boxed{\omega_H = \omega_{H1} \sqrt{2^{1/N} - 1}}$$

N	1	2	3	4
$\sqrt{2^{1/N} - 1}$	1	0.644	0.510	0.435

6.) Example - Given an op amp with $f_T = 10 \text{ MHz}$ and $A_0 = 100 \text{ dB}$, find the ω_H (-3dB freq.) of the gain of +100 amplifier using 1 op amp, ~~2 op amps~~ 2 cascaded op amps and 3 cascaded op amps

$$\omega_{H1} = (1 + A_0 B) \omega_B \rightarrow f_{H1} \approx A_0 B f_B = f_T B$$

a.) 1 op amp $\rightarrow B = \frac{1}{100} \rightarrow f_H = f_{H1} = \frac{10 \text{ MHz}}{100} = 100 \text{ kHz}$

b.) 2 op amps $\rightarrow B = \frac{1}{10} \rightarrow f_{H1} = 1 \text{ MHz} \rightarrow f_H = 644 \text{ kHz}$

c.) 3 op amps $\rightarrow B = \frac{1}{4.692} \rightarrow f_{H1} = 2.154 \text{ MHz} \rightarrow f_H = 6099 \text{ kHz}$