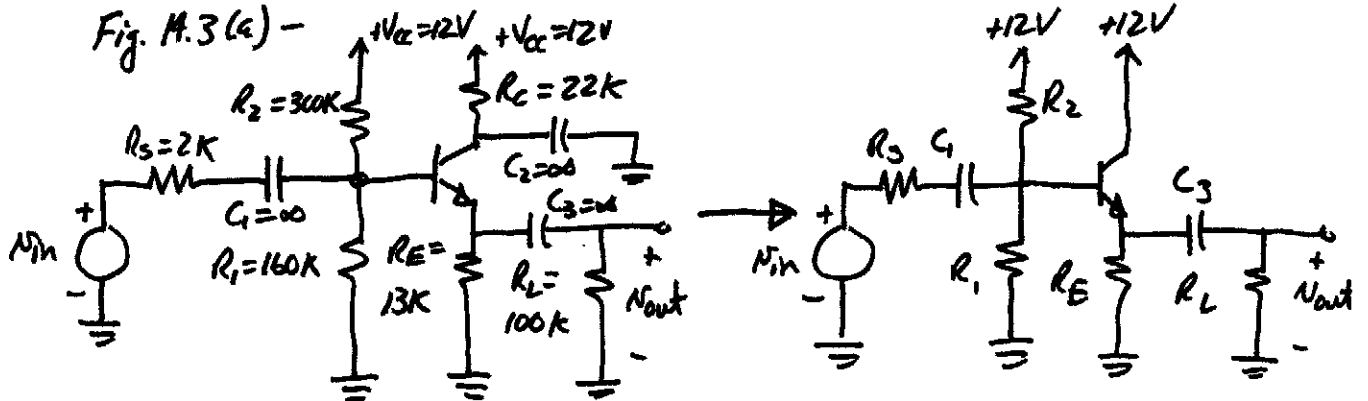



Lecture 17 - Amplifier Examples

1.) Common collector (Emitter follower)



Assume $\beta_F = 100$ and $V_A = 50$
 Q point: $I_C = 245\mu A$ and $V_{CE} = 3.64V$


Small signal model:

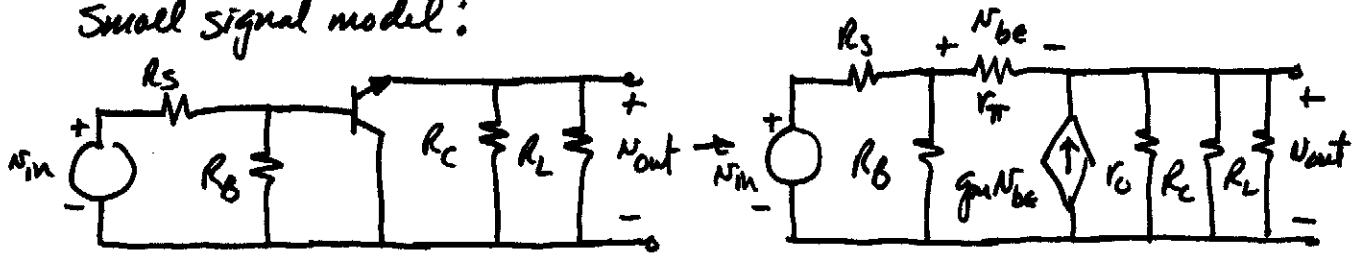

where $R_B = R_1 || R_2 = 104.35k\Omega$ $g_m = \frac{I_C}{V_T} = 9.8mS$

$r_{\pi} = \frac{\beta_F}{g_m} = 10.2k\Omega$ $r_o = \frac{V_A + V_{CE}}{I_C} = \frac{103.64}{245\mu A} = 423k\Omega$

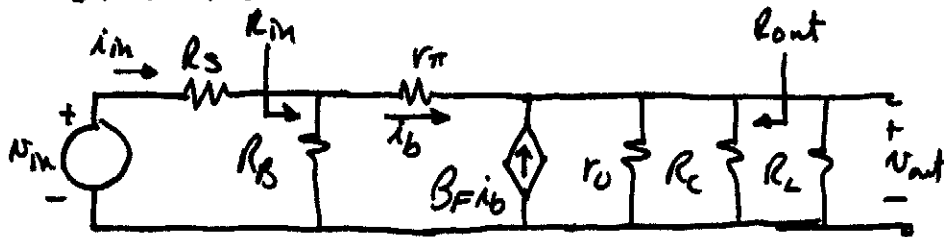It will be easier to use the current controlled model which is,



$R_{in} = R_B || [r_{\pi} + (1 + \beta_F)(r_o || R_C || R_L)] = 104.35k || [10.2k + 101(17.3k)]$

$R_{in} = 104.35k || 1.76M\Omega = \underline{\underline{98.5k\Omega}}$

1.) Common Collector - Cont'd


$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{i_b} \right) \left(\frac{i_b}{i_{in}} \right) \left(\frac{i_{in}}{N_{in}} \right) \quad \text{Let } R' = r_o \parallel R_c \parallel R_L = 17.3k$$

$$= \left[(1 + \beta_F) R' \right] \left[\frac{R_B}{R_B + r_{\pi} + (1 + \beta) R'} \right] \left[\frac{1}{R_S + r_{in}} \right]$$

$$= (101)(17.3k) \left(\frac{104.35k}{104.35k + 1760k} \right) \left(\frac{1}{2k + 98.5k} \right)$$

$$= (1747.3k) (0.05597) \left(\frac{1}{101.5k} \right) = \underline{\underline{0.963 \text{ V/V}}}$$

$R_{out} = ?$ Set $N_{in} = 0$,

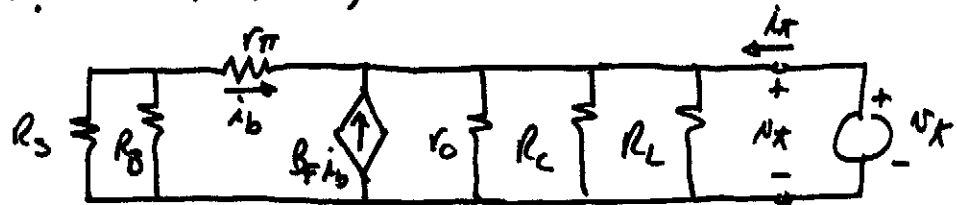

$$\sum i = 0 \Rightarrow i_x = g_o N_x + G_c N_x + G_L N_x - i_b (1 + \beta_F)$$

$$\text{But } i_b = - \frac{N_x}{r_{\pi} + R_S \parallel R_B}$$

$$\therefore i_x = \left[g_o + G_c + G_L + \frac{1 + \beta_F}{r_{\pi} + R_S \parallel R_B} \right] N_x$$

$$R_{out} = \frac{N_x}{i_x} = \frac{1}{\frac{1}{r_o} + \frac{1}{R_c} + \frac{1}{R_L} + \frac{101}{r_{\pi} + R_S \parallel R_B}} = \frac{1}{\frac{1}{423k} + \frac{1}{22k} + \frac{1}{100k} + \frac{101}{12.16k}}$$

$$R_{out} = \underline{\underline{119.6 \Omega}}$$