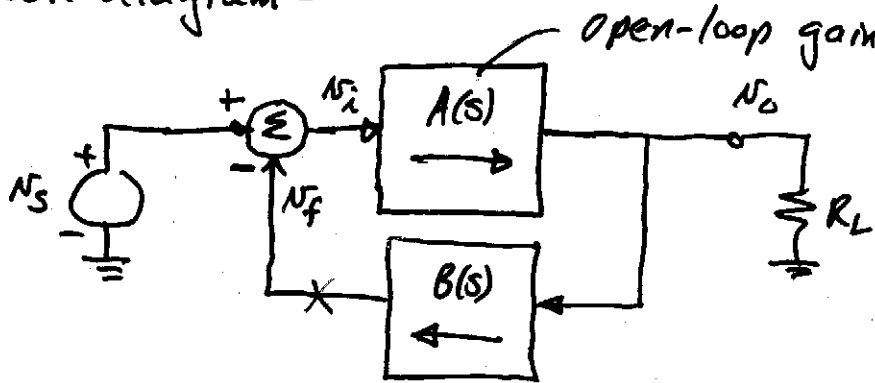


CHAPTER 18 - FEEDBACK CONCEPTS AND THEORY

(Feedback is a great concept but a terrible analysis tool.)

Classical Single Feedback (Negative)

Block diagram -



$$N_o = A(s) N_i = A(s) [N_s - N_f] = A(s) N_s - A(s) B(s) N_o$$

$$N_o [1 + A(s) B(s)] = A(s) N_s$$

Closed-loop transfer function = $\frac{N_o}{N_s} = \frac{A(s)}{1 + A(s) B(s)} = \frac{A(s)}{1 - T(s)}$


$T(s) = \text{Loop gain} = -A(s) B(s)$ $|T(s)| = A(s) B(s)$

Jaeger: $\frac{N_o}{N_s} = \frac{A(s)}{1 + T(s)} \rightarrow T(s) = A(s) B(s)$

KEY: If the magnitude of the loop gain $\gg 1$

then $\frac{N_o}{N_s} = \frac{A(s)}{1 + A(s) B(s)} \rightarrow \frac{A(s)}{\underbrace{A(s) B(s)}_{\text{Large} \gg 1}} = \frac{1}{B(s)}$

B(s):

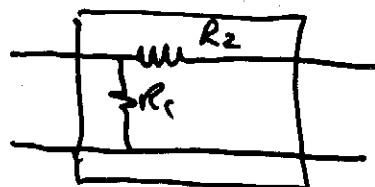

$\beta = \frac{R_1}{R_1 + R_2}$

C.L.G. $\equiv \frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$

$T(s) > 0 \rightarrow +FB$
 $T(s) < 0 \rightarrow -FB$

Types of Feedback Circuits -


Input variable: N_s, N_f or N_i

Output variable: N_o

$N =$ Voltage or current
 N_s, N_f & N_i must be the same type

Input Variables: (N_i, N_f, N_s)	Output Variable N_o	Type of Feedback (input-output)
Voltage	Voltage	Series-Shunt
Current	Voltage	Shunt-shunt
Current	Current	Shunt-Series
Voltage	Current	Series-Series

Series-shunt (Voltage Amplifiers)

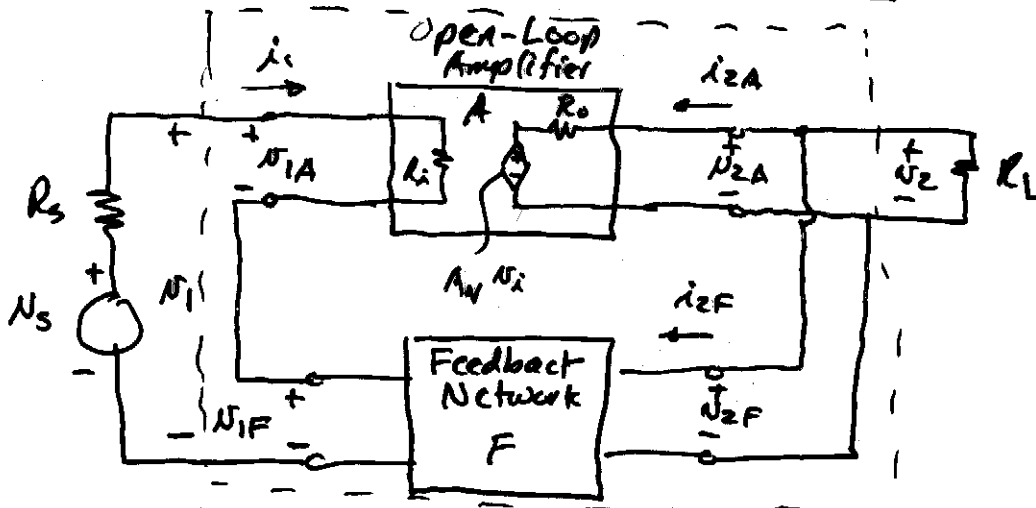

$$N_i = N_{iA} + N_{iF}$$

$$\text{or } N_{iA} = N_i - N_{iF}$$

$$(N_i = N_s - N_f)$$