
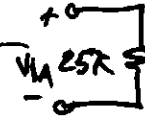


Example of Series-Shunt

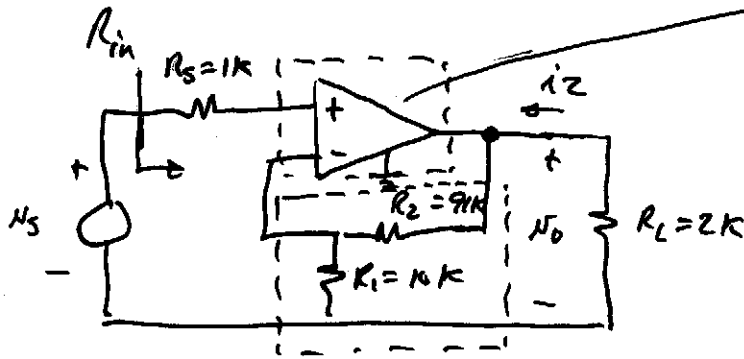

$$\frac{N_0}{N_S} = \frac{A}{1+AB} \approx \frac{1}{B} \text{ if } AB \gg 1$$

$$A = 4730 \frac{V}{V} \quad B = 0.099$$

Input Resistance for a series-shunt feedback network

$$\begin{aligned} N_1 &= h_{11T} i_1 + h_{21T} N_2 \\ i_2 &= h_{12T} i_1 + h_{22T} N_2 \end{aligned} \quad \begin{aligned} N_S &= i_1 R_S + N_1 \\ N_2 &= -i_2 R_L \end{aligned}$$

$$N_S = (R_S + h_{11T}) i_1 + h_{12F} N_2$$

$$h_{12T} = h_{12A} + h_{12F} \approx h_{12F}$$


$$0 = h_{21A} i_1 + (h_{22T} + G_L) N_2$$

$$R_{inF} = \frac{N_S}{i_1} = (R_S + h_{11T}) + \frac{-h_{21A} h_{12F}}{(h_{22T} + G_L)}$$

$$= (R_S + h_{11T}) \left[1 + \frac{-h_{21A} h_{12F}}{(R_S + h_{11T})(h_{22T} + G_L)} \right] = \underline{\underline{(R_S + h_{11T})(1 + AB)}}$$

$$B = h_{12F} \quad A = \frac{-h_{21A}}{(R_S + h_{11T})(h_{22T} + G_L)}$$


Back to Example -

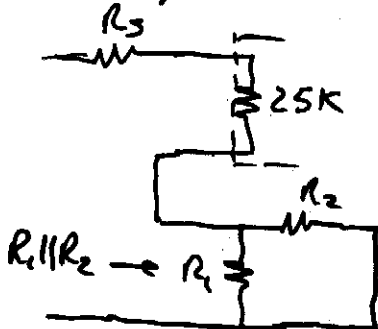

$$h_{11F} = \left. \frac{N_{1F}}{i_{1F}} \right|_{N_{2F}=0}$$

$$h_{11T} = 25K + R_1 \parallel R_2 = 25K + 9.01K$$

$$R_{in}(fb) = (35.01K)(1 + 4730 \times 0.099) = \underline{\underline{16.47M\Omega}}$$

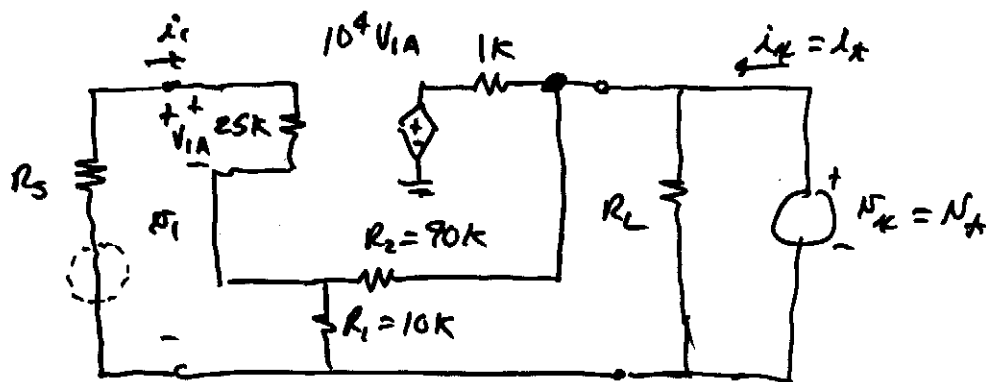Output Resistance for Series-Shunt Feedback

$$R_{out}(fb) = \frac{N_X}{i_X}$$

$$0 = (R_S + h_{11F}) i_1 + h_{12F} N_X$$

$$i_X = h_{12A} i_1 + (h_{22T} + G_L) N_X$$

$$R_{out}(fb) = \frac{1}{(h_{22T} + G_L) \left[1 + \frac{-h_{21A} h_{12F}}{(R_S + h_{11F})(h_{22T} + G_L)} \right]} = \frac{1}{(h_{22T} + G_L) [1 + AB]}$$

$$R_{out}(fb) = \frac{\left(\frac{1}{h_{22T} + G_L} \right)}{1 + AB}$$

Back to Example -

$$h_{22} = \frac{i_2}{V_2} \Big|_{i_1=0} \rightarrow h_{22A} = \frac{1}{1K} \quad \& \quad h_{22F} = \frac{1}{R_1 + R_2} = \frac{1}{100K}$$

$$h_{22T} = h_{22A} + h_{22F} = \frac{1}{1K} + \frac{1}{100K} = \frac{1}{1K \parallel 100K}$$

$$R_{out}(fb) = \frac{1}{\left(\frac{1}{1K} + \frac{1}{100K} + \frac{1}{2K} \right) (1 + 4730 \times 0.009)} = \frac{662\Omega}{474} = \underline{\underline{1.41\Omega}}$$

Summary

The general approach to analyzing neg. fb. ckts is:

- 1.) Find \$h_{11F}\$ (input resistance of the fb. ntwk with output S.C.)
- 2.) Find \$h_{22F}\$ (output conductance of the fb. ntwk with input O.C.)
- 3.) Find \$h_{12F} = B\$ (voltage gain from output to input with the input O.C.)


4.) Use the A circuit (including h_{11F} and h_{22F})
to find $A = \frac{V_o'}{V_s'}$

5.) $A(fb.) = \frac{A}{1+AB}$

6.) $R_{in}(fb.) = (R_s + h_{11\pi}) (1+AB)$

7.) $R_{out}(fb.) = \frac{1}{(h_{22\pi} + G_L)(1+AB)}$



Comment on Quiz 9

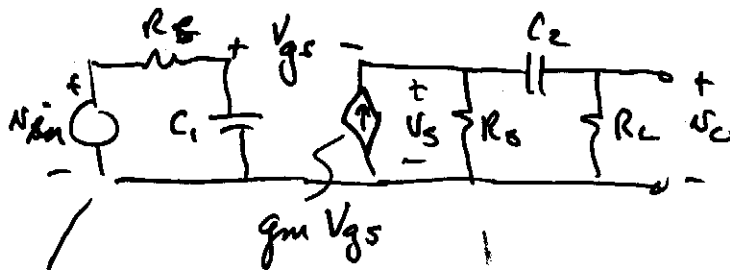


$$\frac{V_o}{V_{in}} = \left(\frac{V_o}{V_{gs}} \right) \left(\frac{V_{gs}}{V_g} \right) \left(\frac{V_g}{V_{in}} \right)$$

$V_{gs} = V_g - V_s$

$g_m V_{gs} = g_m V_g - g_m V_s$

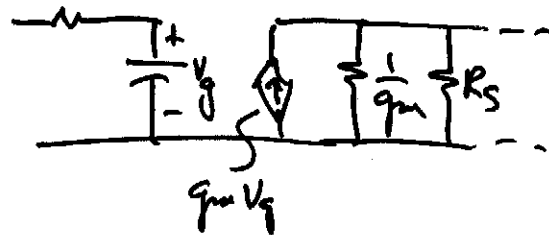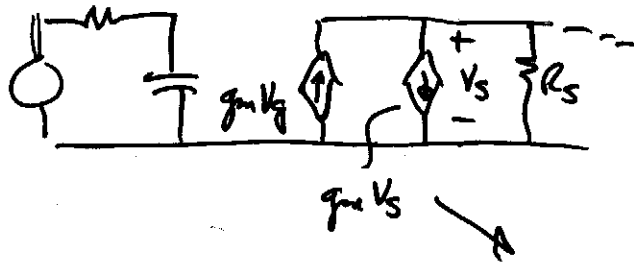

Example of Series-Shunt

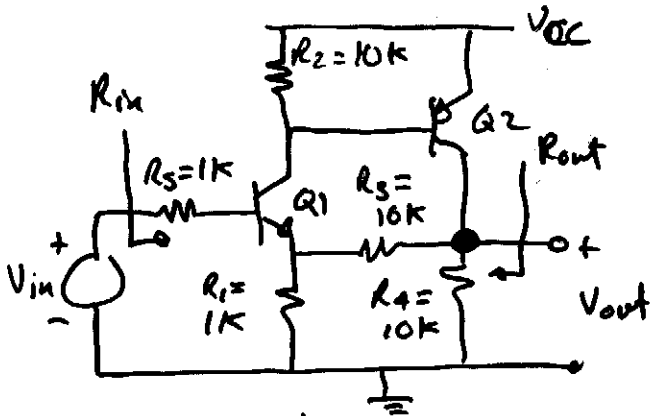

If $Q1 = Q2$, ~~β_{FE}~~ $h_{fe} = 100$

$r_c = \infty$, and $r_e = 10K$

Use feedback analysis methods to find $\frac{V_{out}}{V_{in}}$,

R_{in} , and R_{out} .

