


Bode Feedback Stability Conditions

1.) $\text{Arg}[T(j\omega_{0dB})] > -180^\circ \rightarrow$

The loop phase shift is greater than -180° when the loop magnitude = 1



2.) $|T(j\omega_{-180})| < 1 \rightarrow$

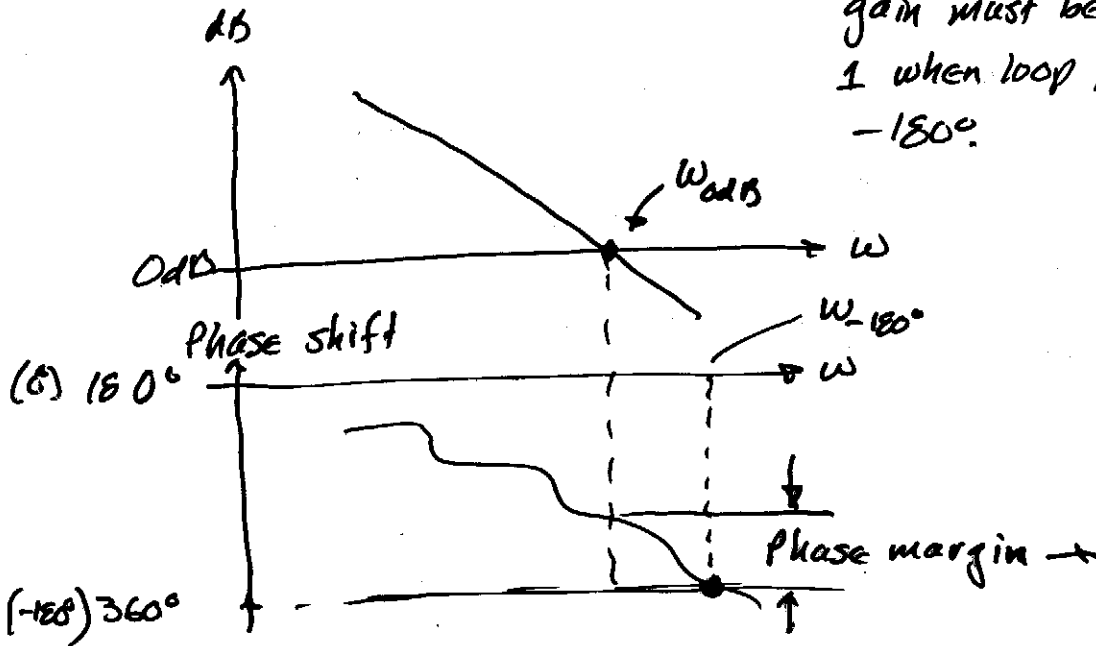The magnitude of the loop gain must be less than 1 when loop phase shift = -180° .



A good system has a phase margin $\geq 45^\circ$.


Consider a buffer -

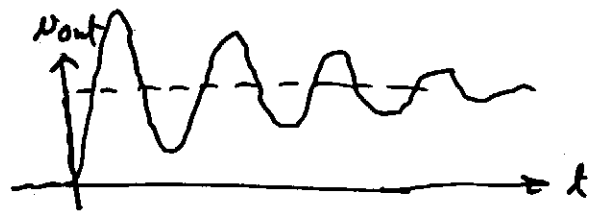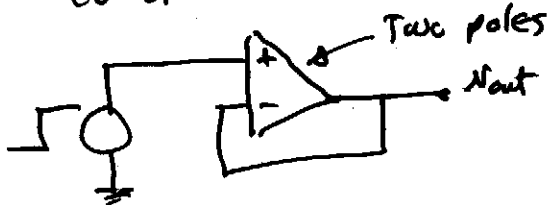

Self Example

$A(s) = \frac{A_0}{(s/\omega_1 + 1)(s/\omega_2 + 1)}$

$B(s) = B_0$

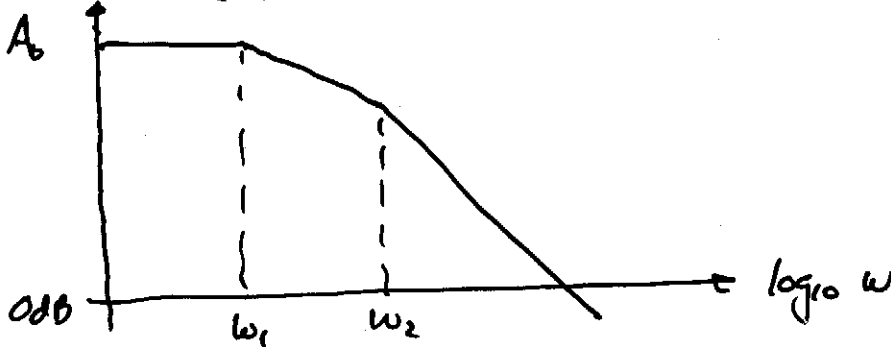

OSCILLATORS

Intro

• Oscillators all use some form of positive feedback along a frequency dependent transfer function to create periodic waveforms.

• Classification of oscillators

Tuned - sinusoidal

Untuned - sq. wave, triangle, etc.


Criteria for oscillation

$$\text{Loop gain} = T(j\omega) = 1 + j0 = 1 \angle 0^\circ$$


From this eq. you get:

- 1.) Freq. of oscillation
- 2.) Gain necessary for oscillation


Wien Bridge Oscillator

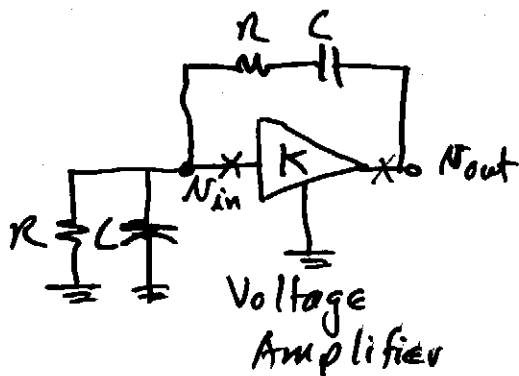

Open-loop

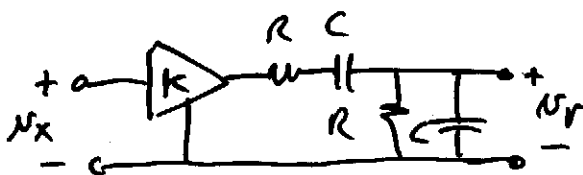

Phase shift

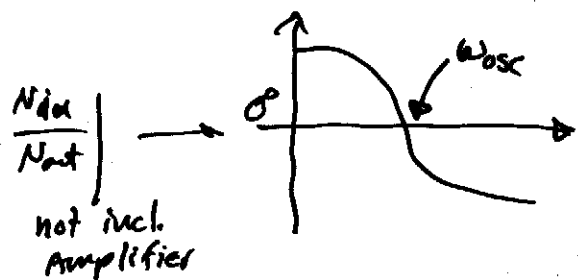

$$T(s) = \frac{N_r(s)}{V_x(s)} = K \frac{R \parallel \frac{1}{sC}}{R + \frac{1}{sC} + R \parallel \frac{1}{sC}}$$

$$R \parallel \frac{1}{sC} = \frac{R/sC}{R + \frac{1}{sC}} = \frac{R}{sRC + 1}$$

$$T(s) = \frac{K \frac{R}{sRC + 1}}{\frac{sRC + 1}{sC} + \frac{R}{sRC + 1}} \times \frac{sC(sRC + 1)}{sC(sRC + 1)}$$


Cont'd

$$T(s) = \frac{k sRC}{(sRC+1)^2 + sRC} = \frac{sKRC}{s^2R^2C^2 + s3RC + 1}$$




$$T(j\omega) = \frac{j\omega KRC}{[1 - \omega^2R^2C^2] + j\omega 3RC} = 1 + j0$$

a.) $1 - \omega^2R^2C^2 = 0 \rightarrow \boxed{\omega_{osc} = \frac{1}{RC}}$

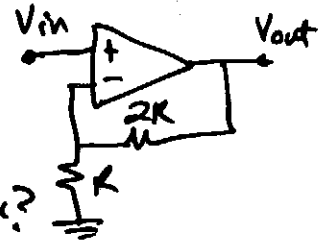
b.) $\frac{j\omega KRC}{j\omega 3RC} = 1 \rightarrow \boxed{K=3} \rightarrow$



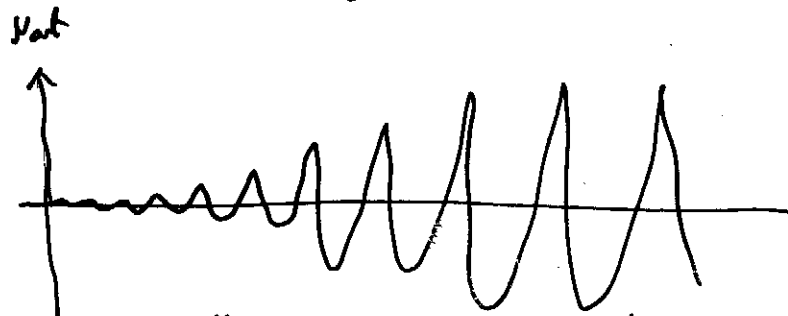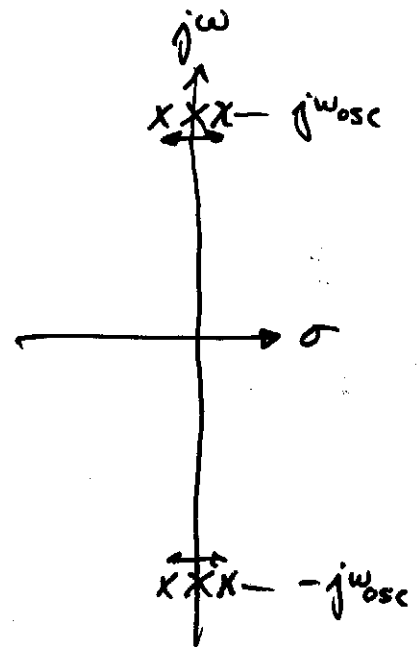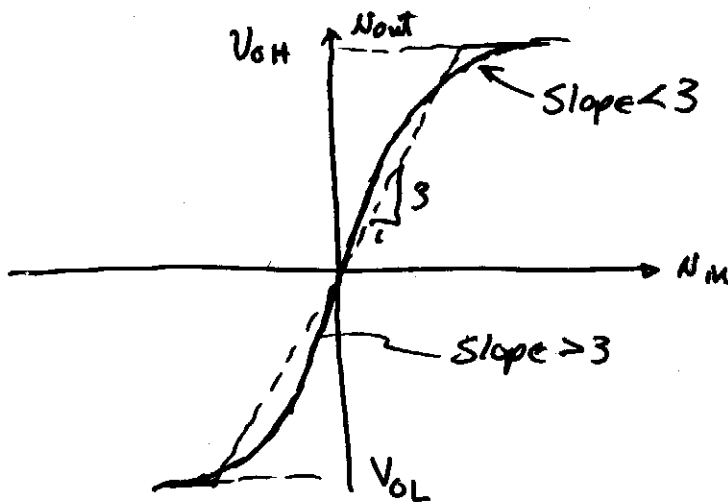What determines the amplitude of oscillation?




Output of a "sinusoidal" oscillator.

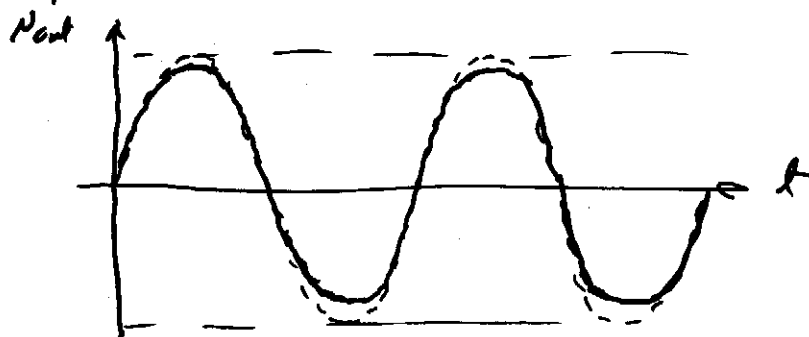

How do you accomplish the amplitude stabilization?

One possible approach -

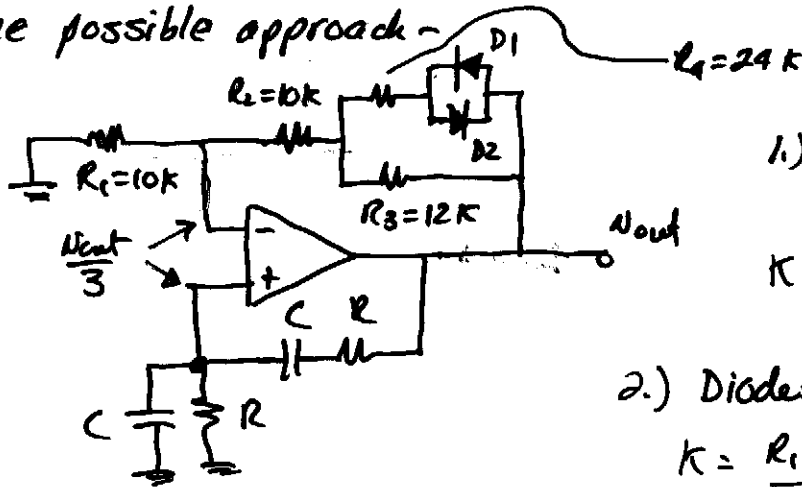

1.) Diodes OFF


$$R_4 = \infty$$

$$K = \frac{R_1 + R_2 + R_3}{R_1} = \frac{32K}{10K} = 3.2$$

2.) Diodes ON

$$K = \frac{R_1 + R_2 + R_3 \parallel R_4}{R_1} = \frac{20K}{10K} = 2.0$$

What amplitude does the diodes turn ON?

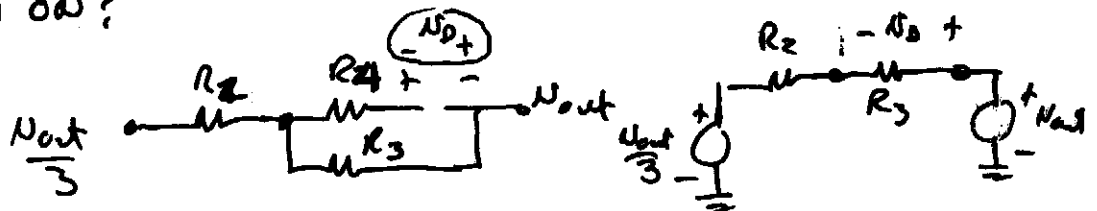


$$C = N_D = N_{out} \frac{R_3}{R_2 + R_3} = \frac{N_{out}}{3} \frac{R_3}{R_2 + R_3} = \frac{R_3}{R_2 + R_3} \left(\frac{R_3}{3} N_{out} \right)$$

Assume $N_D = 0.6V$, then

$$0.6V \times \frac{R_2 + R_3}{R_3} = N_{out} \frac{2}{3}$$

$$0.6 \times \frac{22K}{12K} \times \frac{3}{2} = N_{out} \approx 0.6 \times \frac{2 \times 3}{2} \approx 1.8V$$

Prob. 18.61

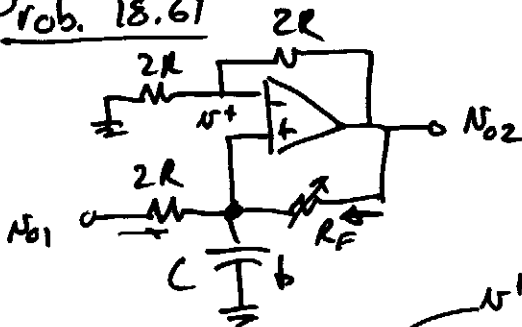

$\sum i$ at N^+ gives

$$\frac{N_{01} - N^+}{2R} + \frac{N_{02} - N^+}{R_F} = 5C N^+$$

$$N^+ \left[5C + \frac{1}{2R} + \frac{1}{R_F} \right] = \frac{N_{01}}{2R} + \frac{N_{02}}{R_F}$$

$$N_{02} = 2N^+ \left(\frac{N_{02}}{N_{01}} \right)$$