
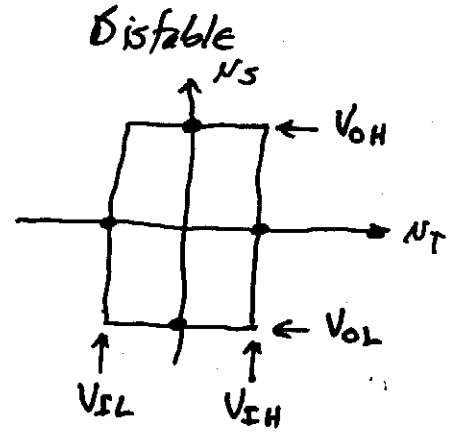





Prob. Session, 7pm Dec. 12th, Thursday

Waveform Generators



1.)

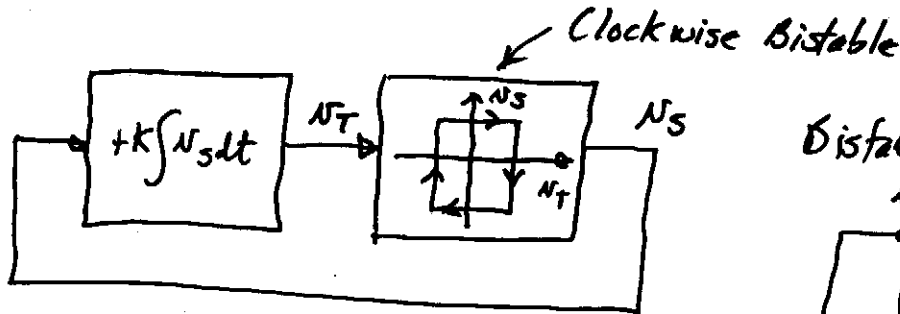

2.)

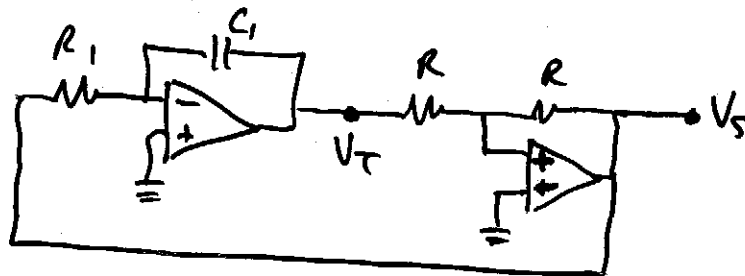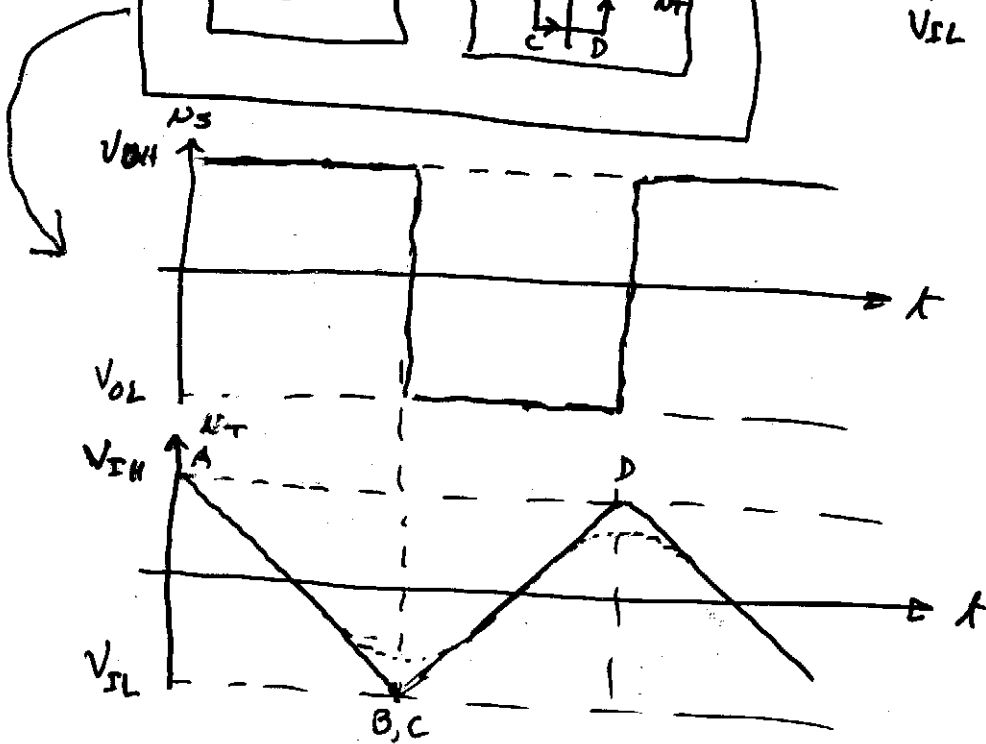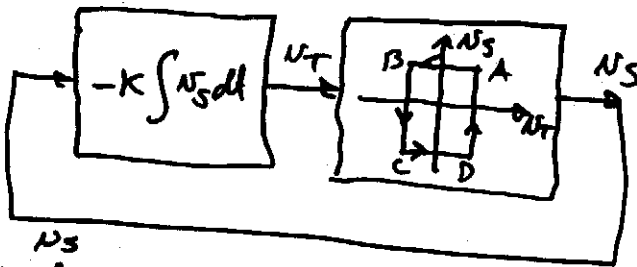

# Bistable Circuits

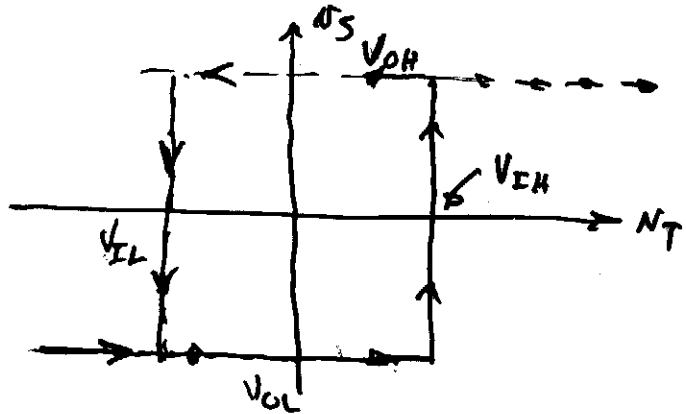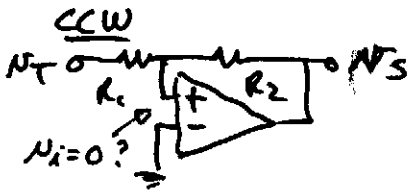

1.) Assume the  $N_T < 0$

2.)  $N_i < 0 \rightarrow N_{out} = V_{OL}$



3.)  $N_i = ? = \frac{V_{OL} R_1}{R_1 + R_2} + \frac{N_T R_2}{R_1 + R_2} \rightarrow 0 = \frac{V_{OL} R_1}{R_1 + R_2} + \frac{V_{IH} R_2}{R_1 + R_2}$

$\therefore \boxed{V_{IH} = -\frac{R_1}{R_2} V_{OL}} \rightarrow V_S = V_{OH}$

4.) Decrease  $V_T$  until  $N_i = 0$  again

$N_i = 0 = \frac{V_{OH} R_1}{R_1 + R_2} + \frac{V_{IL} R_2}{R_1 + R_2} \rightarrow \boxed{V_{IL} = -\frac{R_1}{R_2} V_{OH}}$


CW Bistable -

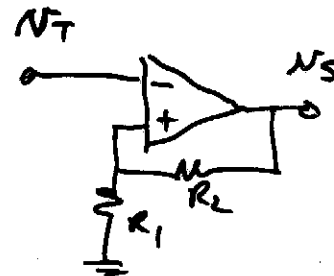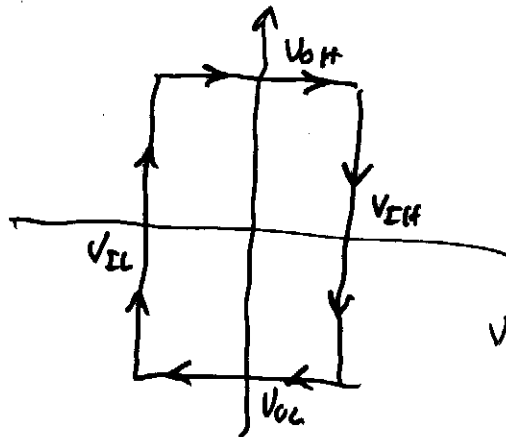

$V_{IH} = \frac{R_1}{R_1 + R_2} V_{OH}$

$V_{IL} = \frac{R_1}{R_1 + R_2} V_{OL}$

Back to the waveform generator -

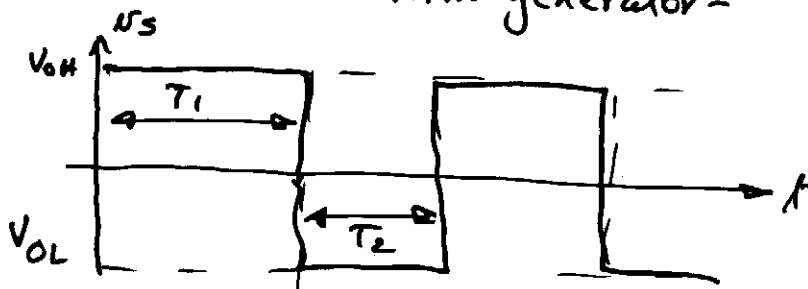

Find  $T = T_1 + T_2$


$f_{osc} = \frac{1}{T}$

General result -

$$T = T_1 + T_2 = \frac{V_{IH} - V_{IL}}{K} \left[ \frac{1}{V_{OH}} - \frac{1}{V_{OL}} \right]$$

If  $V_{OL} = -V_{OH}$  then  $V_{IL} = -V_{IH}$

$$T = \frac{4 V_{IH}}{K V_{OL}}$$

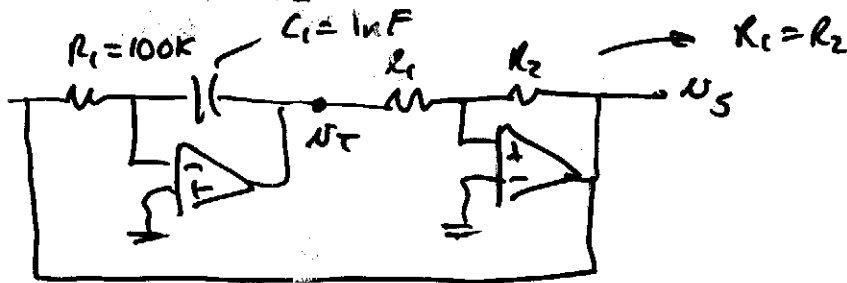

$$T = \frac{4}{K} = 4R_1C_1 \rightarrow f_{osc} = \frac{1}{4R_1C_1} = 2500\text{Hz}$$

✓