

QUIZ NO. 1 – SOLUTION


(Average Score = 8.0)

The following questions give the dc voltages at the terminals of an active device. You are to calculate the designated dc current.

- a.) Find the diode current, I_D , where $I_S = 100\text{fA}$ and $V_T = 0.025\text{V}$ (2 pts).

Obviously, the diode is forward biased. Therefore,

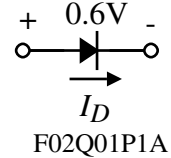
$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right) = 10^{-13} \exp\left(\frac{0.6}{0.025}\right) = \underline{2.65 \text{ mA}}$$



- b.) Find the drain-source current, I_{DS} , where $K_n' = 25\mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$ and $W/L = 10$ (2 pts).

We see that the enhancement, n-channel MOSFET is in the saturation region. Therefore,
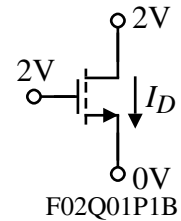
$$I_{DS} = \frac{K_n' W}{2L} (V_{GS} - V_{TN})^2 = \frac{25 \cdot 10}{2} (2-1)^2 = \underline{125 \mu\text{A}}$$




- c.) Find the collector, emitter, and base currents, I_C , I_E , and I_B if $I_S = 100\text{fA}$, $V_T = 0.025\text{V}$ and $\beta_F = 100$ (4 pts).

We see that the npn BJT is in the forward active region. Therefore,

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 10^{-13} \exp\left(\frac{0.7}{0.025}\right) = \underline{144.6 \text{ mA}}$$
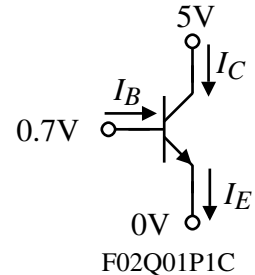
$$I_B = \frac{I_C}{\beta_F} = \underline{1.446 \text{ mA}} \quad \text{and} \quad I_E = I_C + I_B = \underline{146 \text{ mA}}$$



- d.) Repeat (b.) if $V_D = 1\text{V}$ and $V_G = 3\text{V}$ (2 pts).

We see that the enhancement, n-channel MOSFET is in the linear region. Therefore,

$$I_{DS} = K_n' \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \cdot 10 (3-1-0.5)(1) = \underline{375 \mu\text{A}}$$