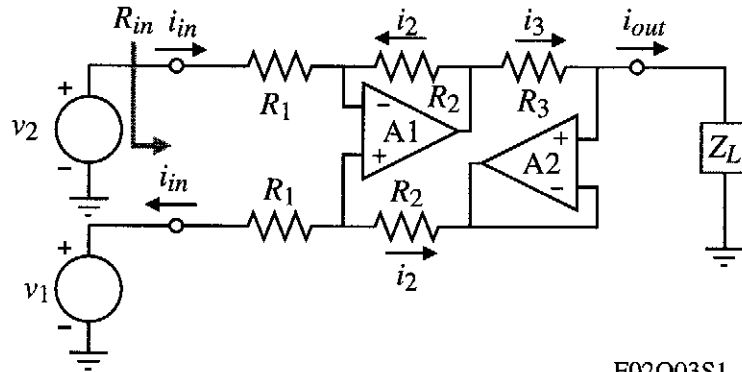


QUIZ NO. 3 - SOLUTION

(Average Score = 6.2/10)

Assume that the op amps are ideal and find i_{out} as a function of the inputs, v_1 and v_2 . Find the input resistance defined as $R_{in} = (v_2 - v_1)/i_{in}$.



F02Q03S1

Solution

From the circuit we can write the following equations based on an ideal op amp:

$$i_{out} = i_3, \quad v_2 - v_1 = 2R_1 i_{in}, \quad i_2 R_2 + i_2 R_2 = i_3 R_3, \quad i_{in} = -i_2$$

$$\therefore i_{out} = i_3 = \frac{2R_2 i_2}{R_3} = \frac{2R_2}{R_3} (-i_{in}) = \frac{2R_2}{R_3} \left(-\frac{v_2 - v_1}{2R_1} \right) = \frac{R_2}{R_1 R_3} (v_1 - v_2)$$

$$\boxed{i_{out} = \frac{R_2}{R_1 R_3} (v_1 - v_2)}$$

The input resistance, R_{in} is seen to be equal to $2R_1$. $\boxed{R_{in} = 2R_1}$