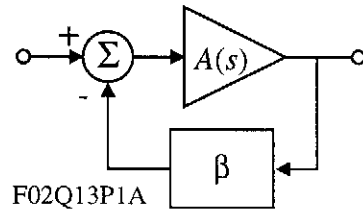


QUIZ NO. 13 - SOLUTION

(Average score = 7.1/10 of those who took the quiz)

1.) The amplifier in the feedback circuit shown has a transfer function of

$$A(s) = \frac{100}{\frac{s}{10^5} + 1}$$



What value of β will increase the upper -3dB frequency by a factor of 10 for the closed loop gain? What is the closed loop, low frequency gain?

Solution


$$A_F = \frac{A}{1+A\beta} = \frac{1}{\frac{1}{A} + \beta} = \frac{1}{\frac{s/10^5 + 1}{100} + \beta} = \frac{100}{\frac{s}{10^5} + 1 + 100\beta} = \left(\frac{100}{1+100\beta} \right) \frac{1}{\frac{s}{10^5(1+100\beta)} + 1}$$

$$\therefore 10^5(1+100\beta) = 10^6 \quad \rightarrow \quad 1+100\beta = 10 \quad \rightarrow \quad \underline{\underline{\beta = 9/100 = 0.09}}$$


The closed-loop, low frequency gain is,

$$A_F(0) = \frac{100}{1+100\beta} = \frac{100}{1+9} = 10 \quad \rightarrow \quad \underline{\underline{A_F(0) = 10}}$$

2.) Find the loop gain of the amplifier shown. Assume that $g_m = 1\text{mS}$ and $r_{ds} = \infty$ for all MOSFETs and that $R = 10\text{k}\Omega$ and $C = 100\text{nF}$.

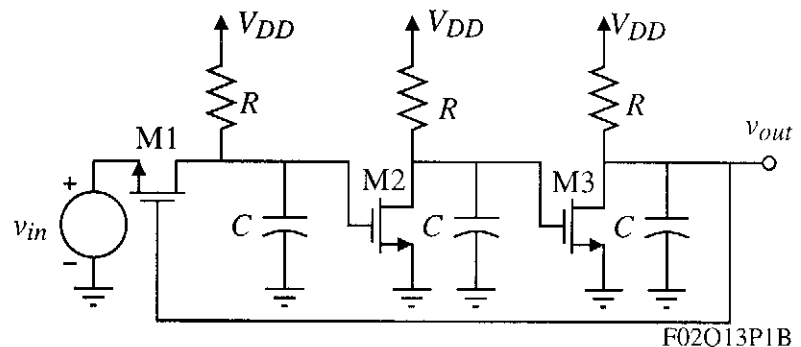Solution

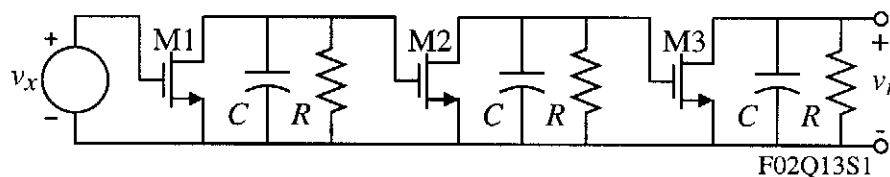Use the model shown to find the loop gain.



This circuit consists of three identical stages with each transfer function given as

$$A(s) = \frac{-g_m R}{sRC + 1}$$

Therefore,

$$T(s) = -\frac{v_r}{v_x} = -\left(\frac{-g_m R}{sRC + 1} \right)^3 = -\left(\frac{-10}{\frac{s}{10^3} + 1} \right)^3 = \frac{1000}{\left(\frac{s}{10^3} + 1 \right)^3} \rightarrow \boxed{T(s) = \frac{1000}{\left(\frac{s}{10^3} + 1 \right)^3}}$$