

EXAMINATION NO. 1 – SOLUTIONS

(Average score = 60/100)

Problem 1 - (25 points)

Find an algebraic expression for the voltage gain, v_{out}/v_{in} , and the output resistance, R_{out} , of the source follower shown in terms of the small-signal model parameters, g_m and R_L (ignore r_{ds}). If the bias current is 1mA find the numerical value of the voltage gain and the output resistance. Assume that $K_N' = 110\mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$, and $K_P' = 50\mu\text{A}/\text{V}^2$, $V_{TP} = -0.7\text{V}$.

Solution

A small-signal model for this circuit is shown below neglecting r_{ds} of the transistors.

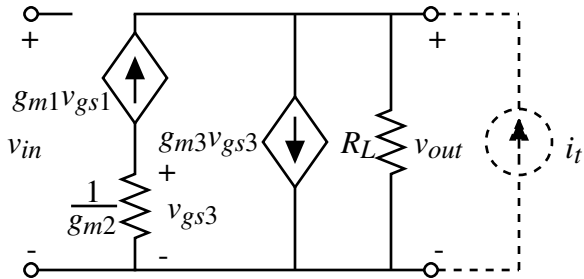


Fig. S03E1S1

$$g_{m1}(v_{out} - v_{in}) \left(1 + \frac{g_{m3}}{g_{m2}}\right) = G_L v_{out}$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{g_{m1} \left(1 + \frac{g_{m3}}{g_{m2}}\right)}{g_{m1} \left(1 + \frac{g_{m3}}{g_{m2}}\right) + G_L}$$

Setting $v_{in} = 0$ and applying i_t and solving for v_{out} and ignoring R_L gives,

$$i_t = g_{m3}v_{gs3} + g_{m1}v_{out} = g_{m3} \left(\frac{g_{m1}}{g_{m2}}\right)v_{out} + g_{m1}v_{out}$$

$$\therefore \frac{v_{out}}{i_t} = R_{out} = \frac{1}{g_{m1} \left(1 + \frac{g_{m3}}{g_{m2}}\right)}$$


Note that the 1mA splits between M1(M2) and M3 in a ratio of 1 to 100. Therefore, $I_{D1} = I_{D2} = 9.9\mu\text{A}$ and $I_{D3} = 990.1\mu\text{A}$.

$$\therefore g_{m1} = \sqrt{2 \cdot 110 \cdot 100 \cdot 9.9} = 466.71\mu\text{S}, \quad g_{m2} = \sqrt{2 \cdot 50 \cdot 1 \cdot 9.9} = 31.47\mu\text{S}$$

$$\text{and } g_{m3} = \sqrt{2 \cdot 110 \cdot 100 \cdot 990.1} = 3146.7\mu\text{S}$$

$$\frac{v_{out}}{v_{in}} = \frac{466.71 \cdot 101}{466.71 \cdot 101 + 1/50} = \frac{47.137}{47.137 + 20} = \underline{\underline{0.702 \text{ V/V}}}$$
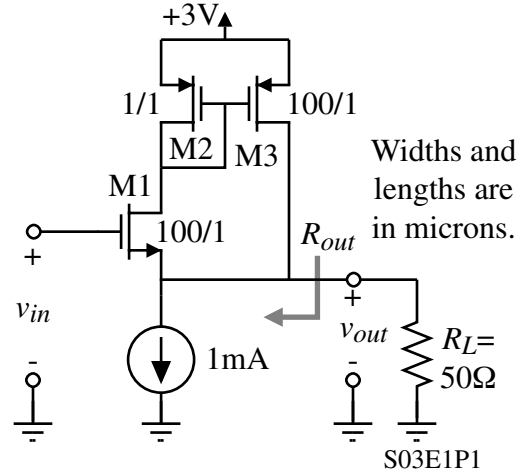
$$R_{out} = \frac{1000}{47.137} = \underline{\underline{21.2\Omega}}$$



Summing currents at the output node gives,

$$g_{m1}v_{gs1} = g_{m3}v_{gs3} + G_L v_{out}$$


$$\text{Also, } v_{gs3} = -g_{m1}v_{gs1}(1/g_{m2})$$

$$\therefore g_{m1}v_{gs1} = g_{m3} \left(-\frac{g_{m1}}{g_{m2}}\right)v_{gs1} + G_L v_{out}$$

$$g_{m1}v_{gs1} \left(1 + \frac{g_{m3}}{g_{m2}}\right) = G_L v_{out} \rightarrow$$

Problem 2 - (25 points)

Using the open-circuit and short-circuit time constant methods, find the two poles of the circuit shown below (assuming that the two poles are far apart from each other). $\beta_0=100$, $I_C=0.5\text{mA}$, $f_T=1\text{GHz}$, $C_\mu=0.2\text{pF}$, $V_T=26\text{mV}$.

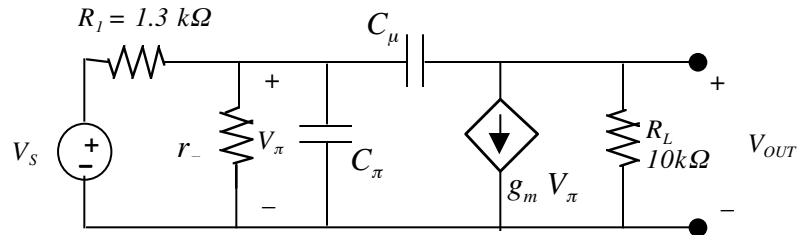Solution

$$r_\pi = \beta_0 / g_m = 100 \times 26 / 0.5 = 5.2 \text{ k}\Omega$$

$$\tau_T = 1 / (2\pi f_T) = 159 \text{ ps}$$

$$C_\pi = g_m \tau_T - C_\mu = (0.5/26) \times 159 \text{ pF} - 0.2 \text{ pF} = 2.86 \text{ pF}$$

$$R_I = R_I \parallel r_\pi = 1.04 \text{ k}\Omega$$

Open circuit time constant method:

$$P_1 \approx 1 / \Sigma \tau = [R_I C_\pi + (R_I + R_L + g_m R_I R_L) C_\mu]^{-1} = 22.13 \times 10^6 \text{ rad/s} = 3.52 \text{ MHz}$$

Short circuit time constant method:

$$P_2 \approx \Sigma (1/\tau) = [(R_I \parallel 1/g_m \parallel R_L) C_\pi]^{-1} + [R_L C_\mu]^{-1} = 7.224 \times 10^9 \text{ rad/s} = 1.15 \text{ GHz}$$

Problem 3 - (25 points)

a) For the emitter follower output stage shown below, find the value of R_I for maximum efficiency and find the value of that efficiency. $V_{CC} = -V_{EE} = 2.5V$, $V_{CE}(sat) = 0.2V$, $R_L = 10k\Omega$, $V_{BE}(on) = 0.7V$.

b) A load capacitor of 100pF is attached to the output voltage. If the input voltage suddenly drops from 2.5V to -2.5V, explain what happens at the output and accurately sketch the output voltage as a function of time, specifying its initial and final values and times.

Solution

The I_Q for maximum efficiency is found as,

$$I_Q = \left(\frac{V_{CC} - V_{CE}(sat)}{R_L} \right) = 230\mu A$$

$$R_I = \left(\frac{-V_{EE} - V_{BE}}{I_Q} \right) = 7.826k\Omega$$


$$P_{L(max)} = \left(\frac{V_{CC} - V_{CE}(sat)}{\sqrt{2}} \right) \left(\frac{I_Q}{\sqrt{2}} \right) = 0.5(2.3V)(0.23mA) = 0.2645mW$$

$$P_{supply} = 2V_{CC}I_Q = 2(2.5)(0.23mA) = 1.15mW$$

$$\eta = \frac{P_{L(max)}}{P_{supply}} = \frac{1}{4} \left(1 - \frac{V_{CE}(sat)}{V_{CC}} \right) = 23\%$$

b) The output would slew under such condition. The current will be limited by the bias current:

$$\text{Slew rate} = 0.23mA / 100pF = 2.3V/\mu s$$

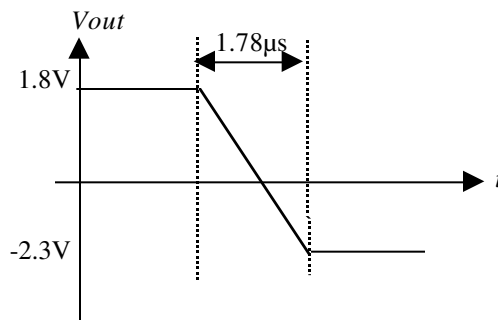

Problem 4 - (25 points)

Find the numerical values of all roots and the midband gain of the transfer function v_{out}/v_{in} of the differential amplifier shown. Assume that $K_N' = 110\mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$, and $\lambda_N = 0.04\text{V}^{-1}$. The values of $C_{gs} = 0.2\text{pF}$ and $C_{gd} = 20\text{fF}$.

Solution

A small-signal model appropriate for this circuit is shown.


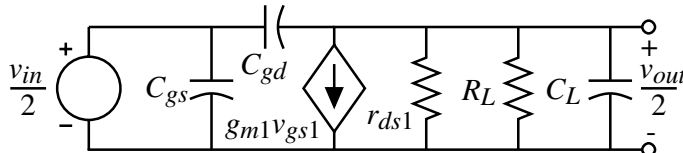


Fig. S03E1S4

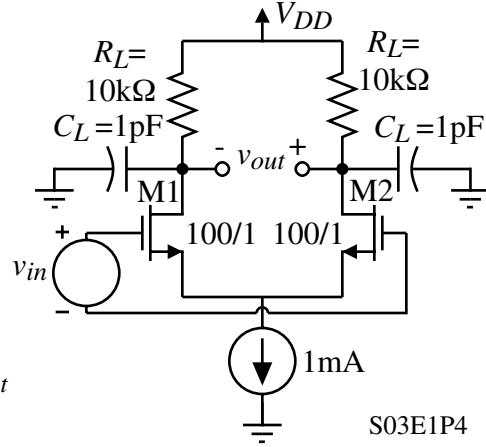

S03E1P4

Summing the currents at the output nodes gives,

$$g_{m1}v_{gs1} + sC_{gd}(v_{out} - v_{in}) + (g_{ds1} + G_L)v_{out} + sC_L v_{out} = 0$$

(Note: we are ignoring the fact that v_{out} and v_{in} should be divided by two since it makes no difference in the results and is easier to write.) Replacing v_{gs1} by v_{in} gives

$$-(g_{m1} - sC_{gd})v_{in} = [(g_{ds1} + G_L) + sC_L + sC_{gd}] v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{-(g_{m1} - sC_{gd})}{s(C_L + C_{gd}) + (g_{ds1} + G_L)} = \left(\frac{-g_{m1}}{g_{ds1} + G_L} \right) \left(\frac{1 - \frac{sC_{gd}}{g_m}}{1 + s \frac{C_L + C_{gd}}{g_{ds1} + G_L}} \right)$$

$$\therefore \text{MGB} = -g_{m1}(r_{ds} \parallel R_L), \quad \text{Zero} = \frac{g_m}{C_{gd}} \quad \text{and} \quad \text{Pole} = -\frac{g_{ds} + G_L}{C_{gd} + C_L}$$

$$g_m = \sqrt{2 \cdot 110 \cdot 100 \cdot 500} = 3316.7\mu\text{S} \quad \text{and} \quad r_{ds} = \frac{1}{\lambda_D} = \frac{25}{500\mu\text{A}} = 50 \text{ k}\Omega$$

$$\therefore \text{MGB} = -3.3167\text{mS} \cdot (10\text{k}\Omega \parallel 50\text{k}\Omega) = \underline{\underline{-27.64 \text{ V/V}}}$$

$$\text{Zero} = \frac{3.3167 \times 10^{-3}}{20 \times 10^{-15}} = \underline{\underline{1.658 \times 10^{11} \text{ radians/sec.}}}$$

$$\text{Pole} = \frac{-1}{1.02 \times 10^{-12} (10\text{k}\Omega \parallel 50\text{k}\Omega)} = \underline{\underline{-1.1176 \times 10^8 \text{ radians/sec.}}}$$