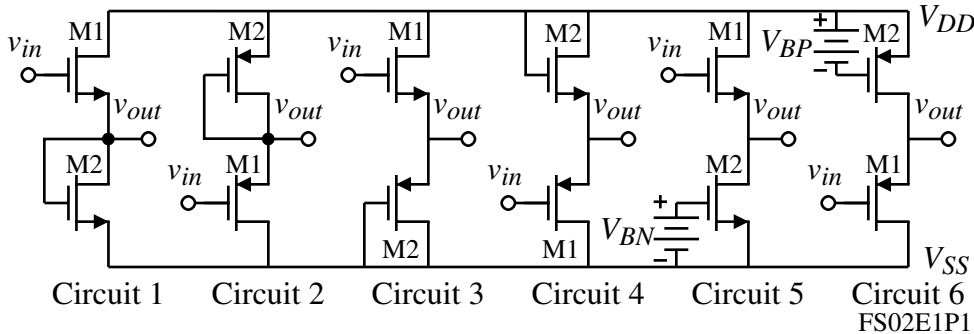


EXAMINATION NO. 1- SOLUTIONS

(Average = 60, High = 88, Low = 46)

Problem 1 - (25 points)


Six versions of a source follower are shown below. Assume that $K'_N = 2K'_P$, $\lambda_P = 2\lambda_N$, all W/L ratios of all devices are equal, and that all bias currents in each device are equal. Neglect bulk effects in this problem and assume no external load resistor. Identify which circuit or circuits have the following characteristics: (a.) highest small-signal voltage gain, (b.) lowest small-signal voltage gain, (c.) the highest output resistance, (d.) the lowest output resistance, (e.) the highest $v_{out(max)}$ and (f.) the lowest $v_{out(max)}$.



Solution

(a.) and (b.) - Voltage gain.

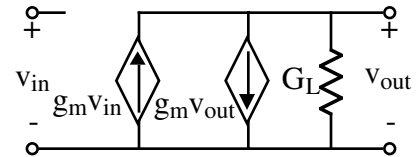The voltage gain is found as: $\frac{v_{out}}{v_{in}} = \frac{g_m}{g_m + G_L}$



where G_L is the load conductance. Therefore we get:

Circuit	1	2	3	4	5	6
$\frac{v_{out}}{v_{in}}$	$\frac{g_{mN}}{g_{mN} + g_{mN}}$	$\frac{g_{mP}}{g_{mP} + g_{mP}}$	$\frac{g_{mN}}{g_{mN} + g_{mP}}$	$\frac{g_{mP}}{g_{mP} + g_{mN}}$	$\frac{g_{mN}}{g_{mN} + g_{dsN} + g_{dsP}}$	$\frac{g_{mP}}{g_{mP} + g_{dsN} + g_{dsP}}$

But $g_{mN} = \sqrt{2} g_{mP}$ and $g_{dsN} = 0.5g_{dsP}$, therefore

Circuit	1	2	3	4	5	6
$\frac{v_{out}}{v_{in}}$	$\frac{1}{2}$	$\frac{1}{2}$	0.5858	0.4142	$\frac{g_{mP}}{g_{mP} + (g_{dsP} + g_{dsN})/\sqrt{2}}$	$\frac{g_{mP}}{g_{mP} + g_{dsP} + g_{dsN}}$

Thus, circuit 5 has the highest gain and circuit 4 the lowest gain

(c.) and (d.) - Output resistance.

The denominators of the first table show the following:

Ckt.6 has the highest output resistance and Ckt. 1 the lowest output resistance.

(e.) Assuming no current has to be provided by the output, circuits 2, 4, and 6 can pull the output to V_{DD} . \therefore Circuits 2, 4 and 6 have the highest output swing.


(f.) Assuming no current has to be provided by the output, circuits 1, 3, and 5 can pull the output to ground. \therefore Circuits 1, 3 and 5 have lowest output swing.

Summary

- (a.) Ckt. 5 has the highest voltage gain
- (b.) Ckt. 4 has the lowest voltage gain
- (c.) Ckt. 6 has the highest output resistance
- (d.) Ckt. 1 has the lowest output resistance
- (e.) Ckts. 2,4 and 6 have the highest output
- (f.) Ckts. 1,3 and 5 have the lowest output

Problem 3 - (25 points)

Find the midband voltage gain and the -3dB frequency in Hertz for the circuit shown.

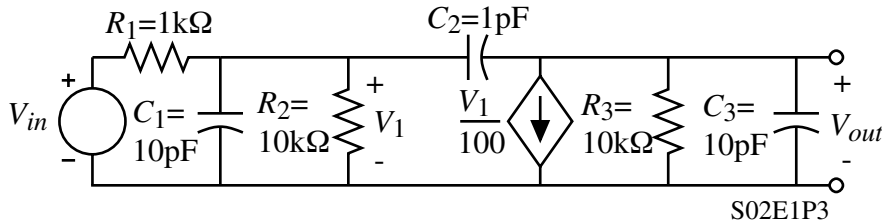Solution

The midband gain is given as,

$$\frac{V_{out}}{V_{in}} = - \left(\frac{10\text{k}\Omega}{100} \right) \left(\frac{10\text{k}\Omega}{11\text{k}\Omega} \right) = \underline{\underline{-90.91\text{V/V}}}$$


To find the -3dB frequency requires finding the 3 open-circuit time constants.

R_{C10} :

$$R_{C10} = 1\text{k}\Omega \parallel 10\text{k}\Omega = 0.9091\text{k}\Omega \quad \rightarrow \quad R_{C10}C_1 = 0.9091 \cdot 10\text{ns} = 9.09\text{ns}$$

R_{C20} :
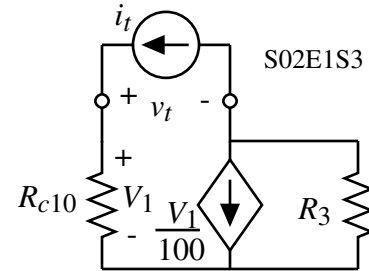
$$\begin{aligned} v_t &= i_t R_{C10} + R_3(i_t + 0.01V_1) \\ &= i_t(R_{C10} + R_3 + 0.01R_{C10}R_3) \\ \therefore R_{C20} &= R_{C10} + R_3 + 0.01R_{C10}R_3 \\ &= 0.9091 + 10(1 + 0.01 \cdot 0.9091)\text{k}\Omega = 101.82\text{k}\Omega \\ R_{C20}C_2 &= 101.82 \cdot 1\text{ns} = 101.82\text{ns} \end{aligned}$$



R_{C30} :


$$R_{C30} = 10\text{k}\Omega \quad \rightarrow \quad R_{C30}C_3 = 10 \cdot 10\text{ns} = 100\text{ns}$$

$$\Sigma T_0 = (9.091 + 101.82 + 100)\text{ns} = 210.91\text{ns} \quad \rightarrow \quad \omega_{-3\text{dB}} = \frac{1}{\Sigma T_0} = 4.74 \times 10^6 \text{ rad/s}$$

$$f_{-3\text{dB}} = \frac{4.74 \times 10^6}{2\pi} = \underline{\underline{754.6\text{kHz}}}$$


Problem 4 - (25 points)

Find the midband voltage gain and the exact value of the two poles of the voltage transfer function for the circuit shown. Assume that $R_I = 1\text{k}\Omega$, $R_L = 10\text{k}\Omega$, $g_m = 1\text{mS}$, $C_{gs} = 5\text{pF}$ and $C_{gd} = 1\text{pF}$. Ignore r_{ds} .

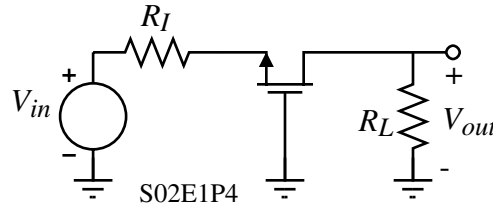Solution

The best approach to this problem is a direct analysis.

Small-signal model:

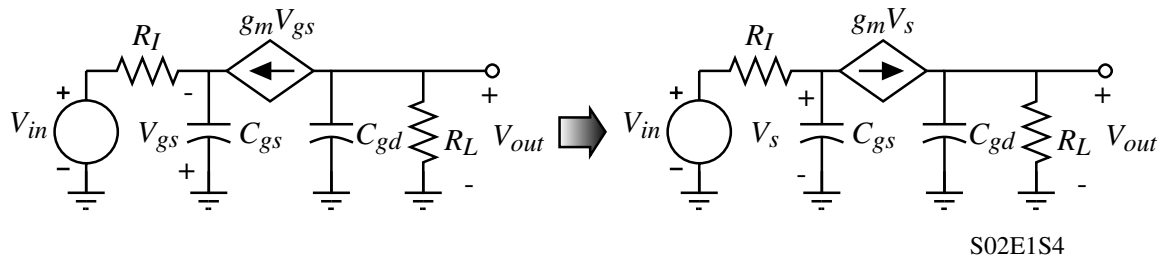

$$V_{out} = g_m Z_L V_s \quad \text{where} \quad Z_L = \frac{1}{sR_L C_{gd} + 1} \quad \text{and} \quad \frac{V_{in} - V_s}{R_I} = g_m V_s + sC_{gs} V_s$$

Solving for V_s from the second equation gives,

$$V_s = \frac{V_{in}}{1 + g_m R_I + sC_{gs} R_I}$$

Substituting V_s in the first equation gives,

$$\begin{aligned} V_{out} &= g_m Z_L \frac{V_{in}}{1 + g_m R_I + sC_{gs} R_I} \rightarrow \frac{V_{out}}{V_{in}} = g_m \left(\frac{1}{sR_L C_{gd} + 1} \right) \left(\frac{1}{1 + g_m R_I + sC_{gs} R_I} \right) \\ &= \left(\frac{g_m R_L}{1 + g_m R_I} \right) \left(\frac{1}{sR_L C_{gd} + 1} \right) \left(\frac{1}{\frac{sC_{gd} R_I}{1 + g_m R_I} + 1} \right) = \text{MBG} \left(\frac{1}{1 - \frac{s}{p_1}} \right) \left(\frac{1}{1 - \frac{s}{p_2}} \right) \end{aligned}$$

$$\therefore \text{MBG} = \left(\frac{g_m R_L}{1 + g_m R_I} \right) = \left(\frac{1 \cdot 10}{1 + 1 \cdot 1} \right) = \underline{\underline{5\text{V/V}}}$$

$$p_1 = -\frac{1}{R_L C_{gd}} = -\frac{1}{10 \cdot 1\text{ns}} = \underline{\underline{-10^8 \text{ rad/s}}} \quad \text{and} \quad p_2 = -\frac{1 + g_m R_I}{R_I C_{gs}} = -\frac{1 + 1}{1 \cdot 5\text{ns}} = \underline{\underline{-4 \times 10^8 \text{ rad/s}}}$$