

FINAL EXAMINATION


NAME _____ SCORE _____ /120

Problem	①	②	3	4	5	6	7	8
Score								

INSTRUCTIONS: This exam is closed book with four sheets of notes permitted. The exam consists of 8, 20-point problems of which you are to work only 6 for a total of 120 points. You must attempt problems 1 and 2. All other problems are optional. **Please circle the number in the table above of the remaining three problems you wish graded.** If you do not indicate the problems to be graded, then problems 1 through 6 will be graded regardless of whether they are worked or not. Be sure to turn in only the 6 problems you wish graded in proper numerical order. Please show your work leading to your answers so that maximum partial credit may be given where appropriate.


Problem 1 - (20 points - This problem is required)

If the folded-cascode op amp shown having a small-signal voltage gain of 7464V/V is used as a comparator, find the dominant pole if $C_L = 5\text{pF}$. If the input step is 10mV, determine whether the response is linear or slewing and find the propagation delay time. Assume the parameters of the NMOS transistors are $K_N' = 110\text{V}/\mu\text{A}^2$, $V_{TN} = 0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$ and for the PMOS transistors are $K_P' = 50\text{V}/\mu\text{A}^2$, $V_{TP} = -0.7\text{V}$, $\lambda_P = 0.05\text{V}^{-1}$.

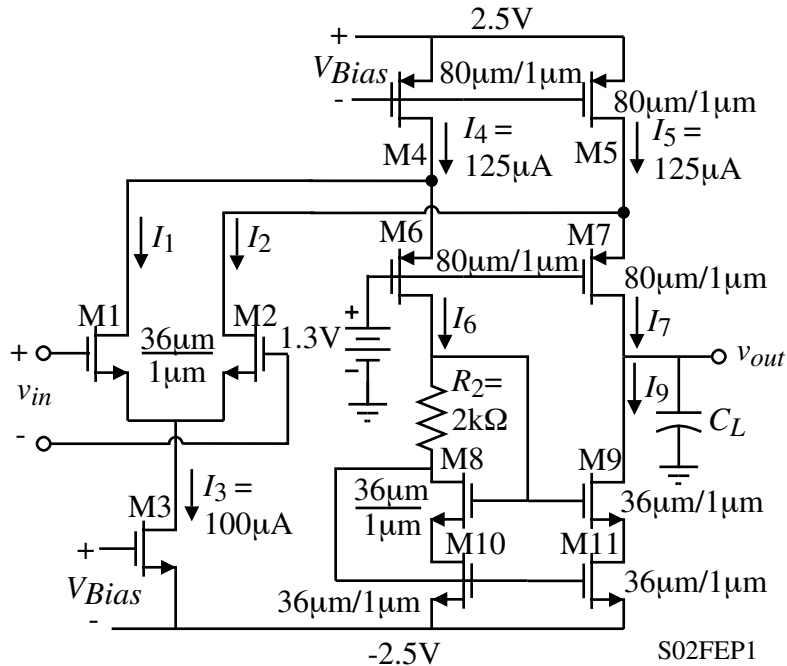


Problem 2 - (20 points - This problem is required)

A comparator consists of an amplifier cascaded with a latch as shown below. The amplifier has voltage gain of 10V/V and $-f_{-3\text{dB}} = 100\text{MHz}$ and the latch has a time constant of 10ns . The maximum and minimum voltage swings of the amplifier and latch are V_{OH} and V_{OL} . When should the latch be enabled after the application of a step input to the amplifier of $0.05(V_{OH}-V_{OL})$ to get minimum overall propagation time delay? What is the value of the minimum propagation time delay? It may be useful to recall that the propagation time delay of the latch is given as $t_p = \tau_L \ln\left(\frac{V_{OH}-V_{OL}}{2v_{il}}\right)$ where v_{il} is the latch input (ΔV_i of the text).

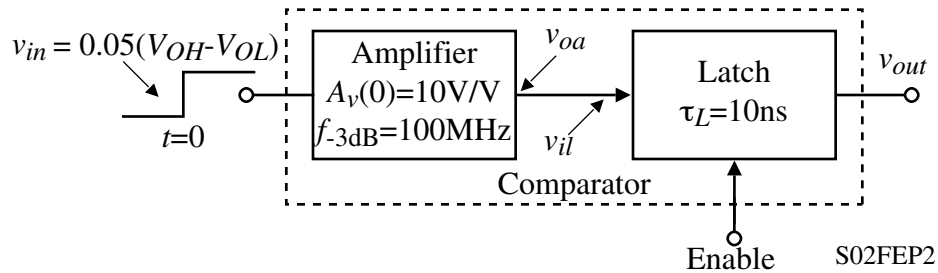


Problem 3 - (20 points - This problem is optional)

If $R_1 = R_2$ of the circuit shown, find an expression for the small-signal output resistance R_{out} ignoring R_L . Repeat including the influence of R_L on the output resistance. Let $R_1 = R_2$ and $R_L = 1\text{k}\Omega$, dc currents through M1 and M2 be $500\mu\text{A}$, $W_1/L_1 = 100\mu\text{m}/1\mu\text{m}$ and $W_2/L_2 = 200\mu\text{m}/1\mu\text{m}$. Find the value of R_{out} . Assume the parameters of the NMOS transistors are $K_N' = 110\text{V}/\mu\text{A}^2$, $V_{TN} = 0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$ and for the PMOS transistors are $K_P' = 50\text{V}/\mu\text{A}^2$, $V_{TP} = -0.7\text{V}$, $\lambda_P = 0.05\text{V}^{-1}$. Assume that $R_2 \gg r_{ds1}$ or r_{ds2} .

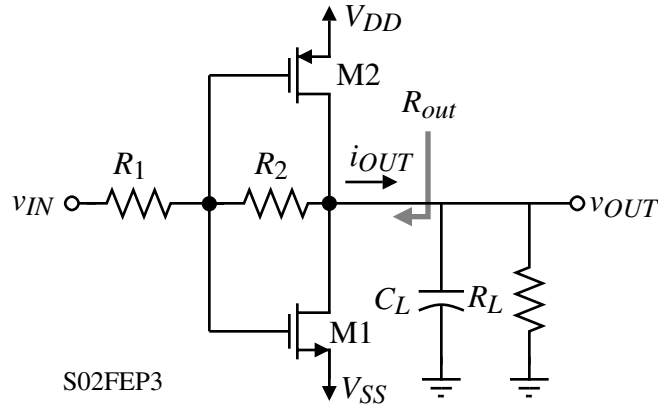

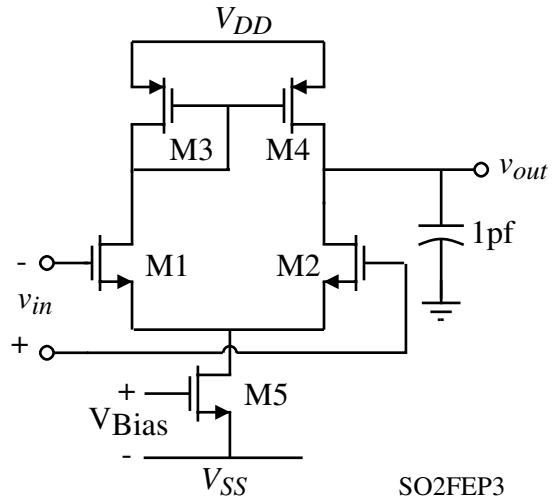Problem 4 - (20 points - This problem is optional)


A current mirror load, CMOS differential amplifier is shown. The current in M5 is $100\mu\text{A}$. Assume the parameters of the NMOS transistors are $K_N' = 110\text{V}/\mu\text{A}^2$, $V_{TN} = 0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$ and for the PMOS transistors are $K_P' = 50\text{V}/\mu\text{A}^2$, $V_{TP} = -0.7\text{V}$, $\lambda_P = 0.05\text{V}^{-1}$. (a.) Find the small-signal output resistance and voltage gain if the W/L ratio of M1 and M2 is $100\mu\text{m}/1\mu\text{m}$. (b.) If the W/L ratio of M3 and M4 is $50\mu\text{m}/1\mu\text{m}$ and $C_{ox} = 24.7 \times 10^{-4}\text{F}/\text{m}^2$, and the effective output capacitance is 1pF , find all roots of this amplifier (ignore the influence of C_{gd4}). Only include the capacitors in this problem that you can calculate from the information given. (c.) What is the -3dB frequency in Hertz?



SO2FEP3

Problem 5 - (20 points - This problem is optional)


The simplified schematic of a feedback amplifier is shown. Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$. Assume that all transistors are matched and that $\beta = 100$, $r_{\pi} = 5\text{k}\Omega$ and $r_o = \infty$.

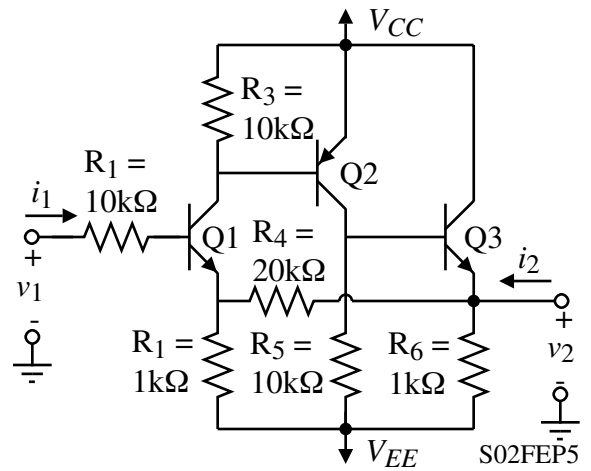

Problem 6 - (20 points - This problem is optional)


A voltage follower feedback circuit is shown. For the MOS transistor, $I_D = 0.5\text{mA}$, $K' = 180\mu\text{A}/\text{V}^2$, $r_{ds} = \infty$, and $W/L = 100$. Although, the bulk effect should be considered, g_{mbs} , for simplicity ignore the bulk effects in this problem. For the op amp, assume that $R_i = 1\text{M}\Omega$, $R_o = 10\text{k}\Omega$, and $a_v = 1000$. Calculate the input resistance and output resistance using Blackman's formula given below.

$$R_{out} = R_{out} (\text{Controlled source} = 0) \left[\frac{1 + RR(\text{output port shorted})}{1 + RR(\text{output port open})} \right]$$

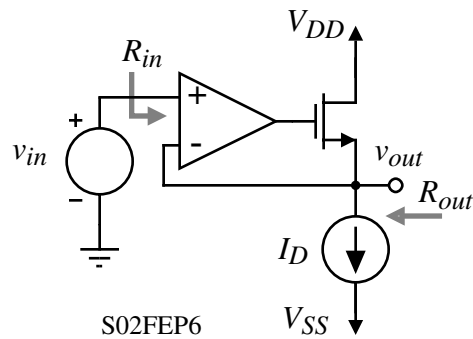

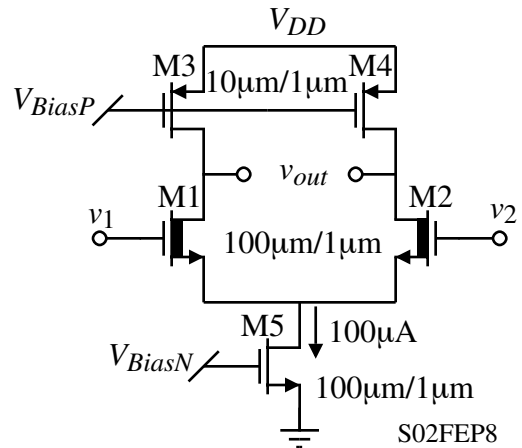Problem 8 – (20 points – This problem is optional)

A differential CMOS amplifier using depletion mode input devices is shown. Assume that the normal MOSFETs parameters are $K_N' = 110\text{V}/\mu\text{A}^2$, $V_{TN} = 0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$ and for the PMOS transistors are $K_P' = 50\text{V}/\mu\text{A}^2$, $V_{TP} = -0.7\text{V}$, $\lambda_P = 0.05\text{V}^{-1}$. For the depletion mode NMOS transistors, the parameters are the same as the normal NMOS except that $V_{TN} = -0.5\text{V}$. (a.) What is the maximum input common-mode voltage, $V_{icm}^+(\text{max})$? (b.) What is the minimum input common-mode voltage, $V_{icm}^-(\text{min})$? (c.) What value of V_{DD} gives an $ICMR = 0.5V_{DD}$?



Extra Page