

Homework Assignment No. 3 - Solutions

Problem 1 - (10 points) (Prob. 7.1 of 3rd and 4th edition)

(a) Transistor parameters are

$$r_{\pi} = \frac{\beta_o}{g_m} = 200 \times 52 = 10.4 \text{ k}\Omega$$

$$\tau_T = \frac{1}{2\pi f_T} = 318 \text{ ps}$$

$$C_{\pi} + C_{\mu} = g_m \tau_T = \frac{1}{52} \times 318 = 6.12 \text{ pF}$$

$$\therefore C_{\pi} = 6.1 - 0.3 = 5.8 \text{ pF}$$

$$C_M = (1 + g_m R_L) C_{\mu} \\ = \left(1 + \frac{3000}{52}\right) \times 0.3 = 17.6 \text{ pF}$$

In (7.12)

$$f_{-3dB} = \frac{1}{2\pi} \frac{5000 + 300 + 10400}{(5000 + 300) \times 10400} \frac{10^{12}}{5.8 + 17.6} \\ = 1.94 \text{ MHz}$$

(b) From (7.27)

$$P_2 = -\left(\frac{1}{R_L C_{\mu}} + \frac{1}{R C_{\pi}} + \frac{1}{R_L C_{\pi}} + \omega_T\right)$$

$$R = (R_S + r_b) \parallel r_{\pi}$$

$$= 5300 \parallel 10400 = 3511 \Omega$$

$$\therefore P_2 = -\left(\frac{10^{12}}{3000 \times 0.3} + \frac{10^{12}}{3511 \times 5.8} + \frac{10^{12}}{3000 \times 5.8}\right)$$

$$+ 2\pi \times 500 \times 10^6$$

$$= -(11.1 + 0.49 + 0.57 + 31.4) \times 10^8 \text{ rad/sec}$$

$$= -43.6 \times 10^8 \text{ rad/sec}$$

$$= -693 \text{ MHz}$$

COMMON EMITTER GAIN STAGE

```
VCC 1 0 5V
RL 1 2 3K
Q1 2 3 0 NPN
RS 4 3 5K
VI 4 0 0.7696 AC
.TF V(2) VI
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 10 100K 1GIG
.MODEL NPN NPN IS=1E-16A BF=200
+ RB=300 CJC=0.3PF CJS=0 TF=302PS
* ASSUME CJE SMALL COMPARED TO CB
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.END
```

0**** BIPOLAR JUNCTION TRANSISTORS

```
0 Q1
0MODEL NPN
IB 2.50E-06
IC 5.01E-04
VBE 0.757
VBC -2.740
VCE 3.497
BETADC 200.000
GM 1.94E-02
RPI 1.03E+04
RX 3.00E+02
RO 1.00E+12
CPI 5.85E-12
CMU 1.81E-13
CBX 0.00E+00
CCS -0.00E+00
BETAAC 200.000
FT 5.11E+08
```

0**** SMALL-SIGNAL CHARACTERISTICS


```
0 V(2)/VI = -3.840D+01
0 INPUT RESISTANCE AT VI = 1.563D+04
0 OUTPUT RESISTANCE AT V(2) = 3.000D+03
```

0**** AC ANALYSIS

```
FREQ VDB(2)
-4.0D+01 -2.0D+01 0.0D+00 2.0D+01 4.0D+01
-----
1.000D+05 3.168D+01 . . . . .
1.259D+05 3.168D+01 . . . . .
1.585D+05 3.167D+01 . . . . .
1.995D+05 3.166D+01 . . . . .
2.512D+05 3.165D+01 . . . . .
3.162D+05 3.163D+01 . . . . .
3.981D+05 3.160D+01 . . . . .
5.012D+05 3.154D+01 . . . . .
6.310D+05 3.146D+01 . . . . .
7.943D+05 3.133D+01 . . . . .
1.000D+06 3.114D+01 . . . . .
1.259D+06 3.085D+01 . . . . .
1.585D+06 3.043D+01 . . . . .
1.995D+06 2.983D+01 . . . . .
2.512D+06 2.903D+01 . . . . .
3.162D+06 2.800D+01 . . . . .
3.981D+06 2.674D+01 . . . . .
5.012D+06 2.529D+01 . . . . .
6.310D+06 2.367D+01 . . . . .
7.943D+06 2.193D+01 . . . . .
1.000D+07 2.011D+01 . . . . .
1.259D+07 1.822D+01 . . . . .
1.585D+07 1.629D+01 . . . . .
1.995D+07 1.434D+01 . . . . .
2.512D+07 1.237D+01 . . . . .
3.162D+07 1.038D+01 . . . . .
3.981D+07 8.391D+00 . . . . .
5.012D+07 6.392D+00 . . . . .
6.310D+07 4.388D+00 . . . . .
7.943D+07 2.377D+00 . . . . .
1.000D+08 3.558D-01 . . . . .
1.259D+08 -1.679D+00 . . . . .
```

7.1 - Cont'd

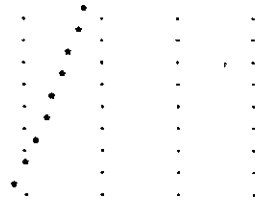1.585D+08 -3.734D+00.
 1.995D+08 -5.821D+00.
 2.512D+08 -7.955D+00.
 3.162D+08 -1.016D+01.
 3.981D+08 -1.247D+01.
 5.012D+08 -1.491D+01.
 6.310D+08 -1.754D+01.
 7.943D+08 -2.037D+01.
 1.000D+09 -2.343D+01.




Y
 0**** AC ANALYSIS
 FREQ VP(2)
 0.0D+00 5.0D+01 1.0D+02 1.5D+02 2.0D+02

1.000D+05 1.779D+02.
 1.259D+05 1.774D+02.
 1.585D+05 1.767D+02.
 1.995D+05 1.758D+02.
 2.512D+05 1.747D+02.
 3.162D+05 1.734D+02.
 3.981D+05 1.717D+02.
 5.012D+05 1.696D+02.
 6.310D+05 1.670D+02.
 7.943D+05 1.637D+02.
 1.000D+06 1.598D+02.
 1.259D+06 1.552D+02.
 1.585D+06 1.498D+02.
 1.995D+06 1.437D+02.
 2.512D+06 1.372D+02.
 3.162D+06 1.306D+02.
 3.981D+06 1.242D+02.
 5.012D+06 1.182D+02.
 6.310D+06 1.130D+02.
 7.943D+06 1.084D+02.
 1.000D+07 1.046D+02.
 1.259D+07 1.013D+02.
 1.585D+07 9.865D+01.
 1.995D+07 9.637D+01.
 2.512D+07 9.440D+01.
 3.162D+07 9.267D+01.
 3.981D+07 9.106D+01.
 5.012D+07 8.952D+01.
 6.310D+07 8.795D+01.
 7.943D+07 8.627D+01.
 1.000D+08 8.440D+01.
 1.259D+08 8.225D+01.
 1.585D+08 7.971D+01.
 1.995D+08 7.667D+01.
 2.512D+08 7.304D+01.
 3.162D+08 6.869D+01.
 3.981D+08 6.356D+01.
 5.012D+08 5.765D+01.
 6.310D+08 5.105D+01.
 7.943D+08 4.396D+01.
 1.000D+09 3.666D+01.

- * DOMINANT POLE @ (DC PHASE - 45 DEGREES) = 135 DEGREES
- * DOMINANT POLE = 2.5 MEGAHERTZ
- * SECOND POLE @ (DC PHASE - 135 DEGREES) = 45 DEGREES
- * SECOND POLE = 794 MEGAHERTZ

7.2

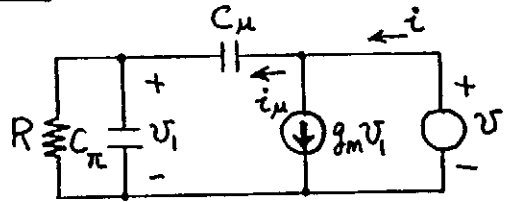

$$R = (R_s + r_b) \parallel r_{\pi}$$

$$V_i = \frac{Z_{\pi}}{Z_{\pi} + \frac{1}{C_{\mu} s}} V, \text{ where } Z_{\pi} = \frac{R}{1 + RC_{\pi} s}$$

$$g_m V_i = g_m \frac{RV}{R + (1 + RC_{\pi} s) \frac{1}{C_{\mu} s}}$$

$$= \frac{g_m RC_{\mu} s}{1 + RC_{\pi} s + RC_{\mu} s} V$$


$$i = i_{\mu} + g_m V_i$$

$$\therefore \frac{1}{Z_o} = \frac{i}{V} = \frac{i_{\mu}}{V} + \frac{g_m V_i}{V}$$

$$= \frac{i_{\mu}}{V} + \frac{g_m RC_{\mu} s}{1 + RC_{\pi} s + RC_{\mu} s}$$

But $\frac{i_{\mu}}{V} \approx C_{\mu} s$, because $C_{\pi} \gg C_{\mu}$

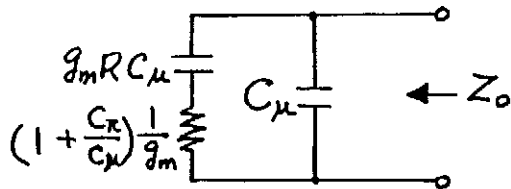
$$\therefore Z_o \approx \frac{1}{C_{\mu} s} \parallel \left(\frac{1}{g_m RC_{\mu} s} + \frac{C_{\pi}}{C_{\mu}} \frac{1}{g_m} + \frac{1}{g_m} \right)$$



$$C_{\mu} = 0.3 \text{ pF}$$

$$g_m RC_{\mu} = \frac{3511}{52} \times 0.3 = 20.3 \text{ pF}$$
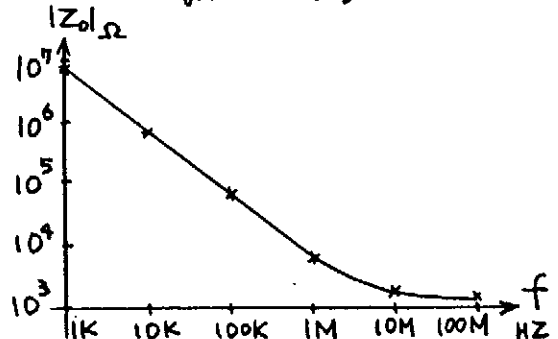
$$\left(1 + \frac{C_{\pi}}{C_{\mu}} \right) \frac{1}{g_m} = \left(1 + \frac{5.8}{0.3} \right) 52 = 1057 \Omega$$



7.8

At low freq.

$$\frac{V_o}{V_i} = -\frac{Y_\pi}{Y_\pi + R_s} g_m R_L$$

$$= -\frac{5.2K}{5.2K + 10K} \frac{5000}{26} = -65.8$$

Zero value time constant

$$R_{\pi o} = Y_\pi \parallel (R_s + Y_b)$$

$$= 5.2K \parallel 10K = 3.42K \Omega$$

$$R_{\mu o} = R_{\pi o} + R_L + g_m R_L R_{\pi o}$$

$$= 3.42 + 5 + \frac{5000}{26} \times 3.42$$

$$= 666K \Omega$$

$$R_{C_{s0}} = R_L = 5K \Omega$$

$$C_\pi + C_\mu = \frac{g_m}{2\pi f_T}$$

$$= \frac{1}{2\pi \times 26 \times 600 \times 10^6} = 10.2 \text{ pF}$$

$$\therefore C_\pi = 10 \text{ pF}$$

$$\therefore C_\pi R_{\pi o} = 10 \times 3.42 = 34.2 \text{ ns}$$

$$C_\mu R_{\mu o} = 0.2 \times 666 = 133.2 \text{ ns}$$

$$C_{s0} R_{C_{s0}} = 1 \times 5 = 5 \text{ ns}$$

$$\therefore \sum T_o = 34.2 + 133.2 + 5 = 172.4 \text{ ns}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \sum T_o} = 0.923 \text{ MHz}$$

$$\frac{V_o}{V_i} = -\frac{R_i}{R_s + R_i} G_m R_L$$

$$= -\frac{65.2}{10 + 65.2} \times 3.07 \times 10^3 \times 5000$$

$$= -13.31$$

$$R_{\mu o} = R_x + R_L + G_m R_x R_L$$

$$R_x = R_i \parallel R_s = 10 \parallel 65.2 = 8.67K \Omega$$

$$\therefore R_{\mu o} = 8.67 + 5 + 3.07 \times 5 \times 8.67$$

$$= 147K \Omega$$

$$\therefore C_\mu R_{\mu o} = 0.2 \times 147 = 29.4 \text{ ns}$$

$$C_{s0} R_{C_{s0}} = 1 \times 5 = 5 \text{ ns}$$

$$R_{\pi o} = Y_\pi \parallel \frac{R_s + Y_b + R_E}{1 + g_m R_E}$$

$$= 5.2K \parallel \frac{10 + 0.3}{1 + \frac{300}{26}} K = 709 \Omega$$

$$C_\pi R_{\pi o} = 10 \times 0.709 = 7.09 \text{ ns}$$

$$\therefore \sum T_o = 29.4 + 5 + 7.09 = 41.49 \text{ ns}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \sum T_o} = 3.84 \text{ MHz}$$


7.9

$$G_m = \frac{g_m}{1 + g_m R_E}$$

$$= \frac{1}{26} \frac{1}{1 + \frac{300}{26}} = 3.07 \times 10^{-3} \text{ A/V}$$


$$R_t = Y_\pi (1 + g_m R_E)$$

$$= 5.2 \left(1 + \frac{300}{26} \right) = 65.2K \Omega$$

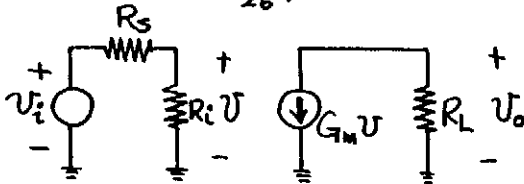

Problem 5 – (10 points)

Find the midband voltage gain and the -3dB frequency in Hertz for the circuit shown.

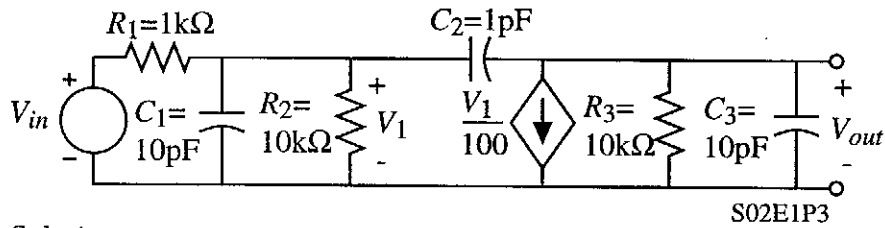Solution

The midband gain is given as,

$$\frac{V_{out}}{V_{in}} = - \left(\frac{10\text{k}\Omega}{100} \right) \left(\frac{10\text{k}\Omega}{11\text{k}\Omega} \right) = \underline{\underline{-90.91\text{V/V}}}$$

To find the -3dB frequency requires finding the 3 open-circuit time constants.

R_{C10} :

$$R_{C10} = 1\text{k}\Omega \parallel 10\text{k}\Omega = 0.9091\text{k}\Omega \quad \rightarrow \quad R_{C10}C_1 = 0.9091 \cdot 10\text{ns} = 9.09\text{ns}$$

R_{C20} :

$$\begin{aligned} v_t &= i_t R_{C10} + R_3(i_t + 0.01V_1) \\ &= i_t(R_{C10} + R_3 + 0.01R_{C10}R_3) \\ \therefore R_{C20} &= R_{C10} + R_3 + 0.01R_{C10}R_3 \\ &= 0.9091 \end{aligned}$$

$$10(1 + 0.01 \cdot 909.1)\text{k}\Omega = 101.82\text{k}\Omega$$

$$R_{C20}C_2 = 101.82 \cdot 1\text{ns} = 101.82\text{ns}$$

R_{C30} :

$$R_{C30} = 10\text{k}\Omega \quad \rightarrow \quad R_{C30}C_3 = 10 \cdot 10\text{ns} = 100\text{ns}$$

$$\Sigma T_0 = (9.091 + 101.82 + 100)\text{ns} = 210.91\text{ns} \quad \rightarrow \quad \omega_{-3\text{dB}} = \frac{1}{\Sigma T_0} = 4.74 \times 10^6 \text{ rad/s}$$

$$f_{-3\text{dB}} = \frac{4.74 \times 10^6}{2\pi} = \underline{\underline{754.6\text{kHz}}}$$

