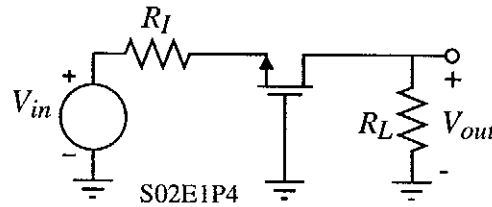


Homework Assignment No. 4 - Solutions

Problem 1 – (10 points)


Find the midband voltage gain and the exact value of the two poles of the voltage transfer function for the circuit shown. Assume that $R_I = 1\text{k}\Omega$, $R_L = 10\text{k}\Omega$, $g_m = 1\text{mS}$, $C_{gs} = 5\text{pF}$ and $C_{gd} = 1\text{pF}$. Ignore r_{ds} .



Solution

The best approach to this problem is a direct analysis.

Small-signal model:

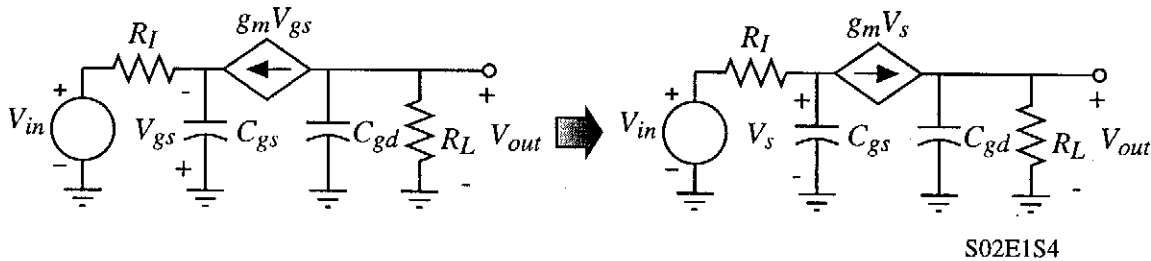

$$V_{out} = g_m Z_L V_s \quad \text{where} \quad Z_L = \frac{1}{sR_L C_{gd} + 1} \quad \text{and} \quad \frac{V_{in} - V_s}{R_I} = g_m V_s + sC_{gs} V_s$$

Solving for V_s from the second equation gives,

$$V_s = \frac{V_{in}}{1 + g_m R_I + sC_{gs} R_I}$$

Substituting V_s in the first equation gives,


$$\begin{aligned} V_{out} &= g_m Z_L \frac{V_{in}}{1 + g_m R_I + sC_{gs} R_I} \rightarrow \frac{V_{out}}{V_{in}} = g_m \left(\frac{1}{sR_L C_{gd} + 1} \right) \left(\frac{1}{1 + g_m R_I + sC_{gs} R_I} \right) \\ &= \left(\frac{g_m R_L}{1 + g_m R_I} \right) \left(\frac{1}{sR_L C_{gd} + 1} \right) \left(\frac{1}{\frac{sC_{gd} R_I}{1 + g_m R_I} + 1} \right) = \text{MBG} \left(\frac{1}{1 - \frac{s}{p_1}} \right) \left(\frac{1}{1 - \frac{s}{p_2}} \right) \end{aligned}$$

$$\therefore \text{MBG} = \left(\frac{g_m R_L}{1 + g_m R_I} \right) = \left(\frac{1 \cdot 10}{1 + 1 \cdot 1} \right) = \underline{\underline{5\text{V/V}}}$$

$$p_1 = -\frac{1}{R_L C_{gd}} = -\frac{1}{10 \cdot 1\text{ns}} = \underline{\underline{-10^8 \text{ rad/s}}} \quad \text{and} \quad p_2 = -\frac{1 + g_m R_I}{R_I C_{gs}} = -\frac{1 + 1}{1 \cdot 5\text{ns}} = \underline{\underline{-4 \times 10^8 \text{ rad/s}}}$$

7.11

(a)

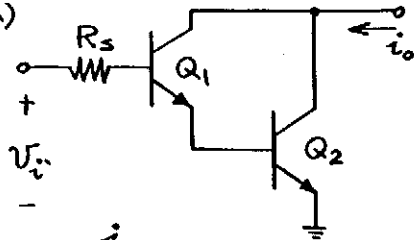

$$G_m = \frac{i_o}{V_i} \approx \frac{1}{2} g_{m2} = \frac{1}{2} \frac{1}{26}$$

$$= \frac{1}{52} \text{ A/V} \quad \text{--- both circuits}$$

$$R_i \approx r_{\pi 1} (1 + g_{m1} r_{\pi 2}) = 2 r_{\pi 1} = 2 \frac{\beta}{g_{m1}}$$

$$= 2 \times 100 \times 2.6 \text{ k} = 520 \text{ k} \Omega$$

--- both Circuits

$$\therefore \frac{V_o}{V_i} = - \frac{R_i}{R_i + R_s} G_m R_L$$

$$= - \frac{520}{620} \times \frac{1}{52} \times 3000$$

$$= -48.4 \quad \text{--- both circuits}$$

(b) Darlington

$$R_{C50} = R_L = 3 \text{ k} \Omega \quad \text{for } Q_1 \text{ and } Q_2$$

$$\therefore R_{C50} (C_{cs1} + C_{cs2}) = 3 \times 2 = 6 \text{ ns}$$

$$R_{\pi 01} = r_{\pi 1} \parallel \frac{R_s + R_E}{1 + g_{m1} R_E} = r_{\pi 1} \parallel \frac{R_s + r_{\pi 2}}{1 + g_{m1} r_{\pi 2}}$$

$$= 260 \text{ k} \parallel \frac{102.6 \text{ k}}{2} = 42.9 \text{ k} \Omega$$

$$C_{\pi} + C_{\mu} = \frac{g_m}{2\pi f_T} = \frac{1}{26} \frac{1}{2\pi \times 500 \times 10^6}$$

$$= 12.2 \text{ pF} \quad \text{at } I_C = 1 \text{ mA}$$

$$\therefore C_{\pi} = 11.8 \text{ pF} \quad \text{at } I_C = 1 \text{ mA}$$

$$C_b = 9.8 \text{ pF}$$

$$\therefore C_{b1} = 0.1 \text{ pF}, \therefore C_{\pi 1} = 2.1 \text{ pF}$$

$$\therefore C_{\pi 1} R_{\pi 01} = 2.1 \times 42.9 = 90.1 \text{ ns}$$

$$R_{\mu 01} = R_x + R_L + G_m R_x R_L$$

$$R_x = R_i \parallel R_s = 520 \text{ k} \parallel 100 \text{ k} = 83.9 \text{ k} \Omega$$

$$\therefore R_{\mu 01} = 83.9 + 3 + \frac{1}{52} \times 3000 \times 83.9$$

$$= 4.93 \text{ M} \Omega$$

$$\therefore C_{\mu 1} R_{\mu 01} = 0.4 \times 4.93 \times 10^3 = 1972 \text{ ns}$$

$$C_{\pi 2} = 11.8 \text{ pF}$$

$$R_{\pi 02} = r_{\pi 2} \parallel \left(\frac{1}{g_{m1}} + \frac{R_s}{\beta_1} \right)$$

$$= 2.6 \text{ k} \parallel \left(2.6 \text{ k} + \frac{100 \text{ k}}{100} \right)$$

$$= 2.6 \text{ k} \parallel 3.6 \text{ k} = 1.51 \text{ k} \Omega$$

$$\therefore C_{\pi 2} R_{\pi 02} = 17.8 \text{ ns}$$

$$R_{\mu 0} = R_{\pi 02} + R_L + g_{m2} R_L R_{\pi 02}$$

$$= 1.51 + 3 + \frac{3000}{26} \times 1.51$$

$$= 179 \text{ k} \Omega$$

$$\therefore C_{\mu 2} R_{\mu 02} = 0.4 \times 179 = 71 \text{ ns}$$

$$\therefore \Sigma T_o = 6 + 90 + 1972 + 18 + 71$$

$$= 2157 \text{ ns}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \Sigma T_o} = 73.8 \text{ kHz}$$

Common-collector - Common emitter

$$R_{C50} C_{C52} = 3 \text{ ns}$$

$$R_{C50} C_{C51} = 0$$

$$C_{\pi 1} R_{\pi 01} = 90.1 \text{ ns}$$

$$C_{\pi 2} R_{\pi 02} = 17.8 \text{ ns}$$

$$C_{\mu 2} R_{\mu 02} = 71 \text{ ns}$$

$$R_{\mu 01} = R_i \parallel R_s = 83.9 \text{ k} \Omega$$

$$\therefore C_{\mu 1} R_{\mu 01} = 0.4 \times 83.9 = 33.6 \text{ ns}$$


$$\therefore \Sigma T_o = 3 + 90.1 + 17.8 + 71 + 33.6$$

$$= 215.5 \text{ ns}$$


$$\therefore f_{-3dB} = \frac{1}{2\pi \Sigma T_o} = 738 \text{ kHz}$$

7.15

Half-circuits (ac)

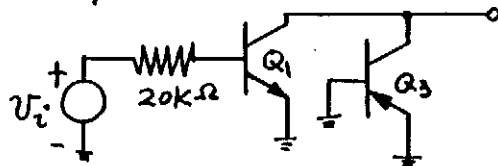

Equivalent

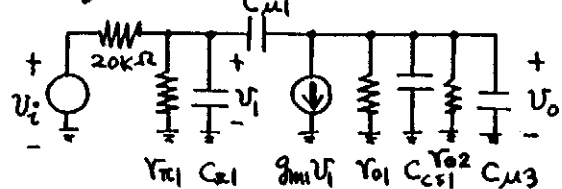

$$I_{C6} = \frac{9.4}{20} = 470 \mu\text{A}$$

$$I_{C5} = \frac{V_T}{R_E} \ln \frac{I_{C6}}{I_{C5}} = 2.6 \ln \frac{470}{I_{C5}} \mu\text{A}$$

$$= 10 \mu\text{A}$$

$$\therefore I_{C1} = I_{C3} = I_{C5}/2 = 5 \mu\text{A}$$

$$\text{Q1} \quad r_{o1} = \frac{V_A}{I_{C1}} = \frac{120}{5} = 24 \text{ M}\Omega$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = 200 \times \frac{26}{0.005} = 1.04 \text{ M}\Omega$$

$$C_{\mu 1} = \frac{0.7}{\sqrt{1 + \frac{5}{0.55}}} = 0.22 \text{ pF}$$

$$C_{cs1} = \frac{2}{\sqrt{1 + \frac{15}{0.55}}} = 0.38 \text{ pF}$$

$$C_{\pi 1} + C_{\mu 1} = \frac{g_m}{2\pi f_T} = \frac{1}{2\pi \times 26 \times 500 \times 10^6}$$

$$= 12.2 \text{ pF at } 1 \text{ mA}$$

$$\therefore C_{\pi 1} = 12 \text{ pF at } 1 \text{ mA}$$

$$C_{b1} = 9 \text{ pF at } 1 \text{ mA}$$

$$\approx 0 \text{ at } 5 \mu\text{A}$$

$$\therefore C_{\pi 1} = 3 \text{ pF at } 5 \mu\text{A}$$

$$\text{Q3} \quad r_{o3} = \frac{50}{5} = 10 \text{ M}\Omega$$

$$C_{\mu 3} = \frac{1}{\sqrt{1 + \frac{4.4}{0.55}}} = 0.33 \text{ pF}$$

$$\frac{v_o}{v_i} = - \frac{r_{\pi 1}}{r_{\pi 1} + R_S} g_{m1} r_o$$

$$r_o = r_{o1} \parallel r_{o3} = 24 \parallel 10 = 7.06 \text{ M}\Omega$$

$$\frac{v_o}{v_i} = - \frac{1.04}{1.06} \times \frac{0.005}{26} \times 7.06 \times 10^6$$

$$= -1332$$

$$R_{\pi o1} = r_{\pi 1} \parallel R_S = 1 \text{ M} \parallel 20 \text{ k} = 19.6 \text{ k}\Omega$$

$$\therefore C_{\pi 1} R_{\pi o1} = 3 \times 19.6 = 59 \text{ ns}$$

$$R_{\mu o1} = R_{\pi o1} + r_o + g_{m1} R_{\pi o1} r_o$$

$$R_{\mu o1} = 19.6 \text{ k} + 7.06 \text{ M} + \frac{0.005}{26} \times 19600 \times 7.06 \text{ M}$$

$$= 33.7 \text{ M}\Omega$$

$$\therefore C_{\mu 1} R_{\mu o1} = 0.22 \times 33.7 = 7.41 \mu\text{s}$$

$$(C_{cs1} + C_{\mu 3}) r_o = 0.71 \times 7.06 = 5.0 \mu\text{s}$$

$$\therefore \sum T_o = 0.06 + 7.41 + 5 = 12.47 \mu\text{s}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \sum T_o} = 12.8 \text{ kHz}$$

$$7.21 \quad (a)$$

$$V_0 = 2.5 \text{ V dc}$$

$$V_{GS2} = 2.5 \text{ V}$$

$$V_{t2} = V_{t0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$$

$$= 0.7 + 0.4 (\sqrt{0.6 + 2.5} - \sqrt{0.6})$$

$$= 1.09 \text{ V}$$

$$I_D = \frac{\mu_n C_{ox} (W/L)_2}{2} (V_{GS2} - V_{t2})^2$$

$$= \frac{60 \mu}{2} \frac{4}{1} (2.5 - 1.09)^2$$

$$= 237 \mu\text{A}$$

$$\frac{v_o}{v_i} = \frac{-g_{m1}}{g_{m2} + g_{mb2}} = \frac{-1.69 \text{ mA/V}}{337 \mu + 38.3 \mu}$$

$$= -4.5$$

$$g_{m1} = \sqrt{2 I_D \mu C_{ox} \frac{W}{L}}$$

$$= \sqrt{2 (237 \mu) (60 \mu) (100)}$$


$$= 1.69 \text{ mA/V}$$

$$g_{m2} = \sqrt{2 (237 \mu) (60 \mu) (4)}$$

$$= 337 \mu\text{A/V}$$

$$g_{mb2} = \frac{g_{m2} \gamma}{2\sqrt{2\phi_f + V_{SB}}} = \frac{g_{m2} \cdot 0.4}{2\sqrt{0.6 + 2.5}}$$

$$= 38.3 \mu\text{A/V}$$

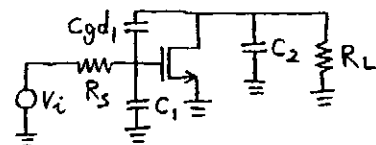

$$C_{ox} = 1.73 \frac{\text{fF}}{\mu\text{m}^2}$$

$$C_{gs1} = \frac{2}{3} WL C_{ox} + C_{ol} W$$

$$= 115 \text{ fF} + 30 \text{ fF} = 145 \text{ fF}$$

$$C_{gs2} = \frac{2}{3} WL C_{ox} + C_{ol} W$$

$$= 4.61 \text{ fF} + 1.2 \text{ fF}$$

$$= 5.8 \text{ fF}$$

7.21- Continued

$$C_{db1} = \frac{0.8 (100)}{\sqrt{1 + \frac{2.5}{0.6}}} = 35.2 \text{ fF}$$

$$C_{gd1} = C_{ol} W = 30 \text{ fF}$$

$$C_{sb2} = \frac{0.8 (4)}{\sqrt{1 + \frac{2.5}{0.6}}} = 1.41 \text{ fF}$$

$$C_1 = C_{gs1} = 145 \text{ fF}$$

$$C_2 = C_{db1} + C_{sb2} + C_{gs2} + C_L$$

$$= 142 \text{ fF}$$

$$C_1 R_S = 145 \text{ ps}$$

$$C_2 R_L = 142 \text{ fF} (2665 \Omega) = 378 \text{ ps}$$

$$C_{gd1} (R_S + R_L + g_m R_S R_L) = 30(1k + 2665 + 1.69m(1k)(2665)) \text{ f} = 245 \text{ ps}$$

$$f_{-3dB} = \frac{1}{2\pi} \frac{10^{12}}{145 + 378 + 245} = 207 \text{ MHz}$$

(b)

$$R_{sx} = \frac{1}{E_c \mu C_{ox} W}$$

$$m1 R_{sx} = \frac{1}{1.5M \cdot 60\mu \cdot 100\mu} = 111 \Omega$$

$$m2 R_{sx} = \frac{1}{1.5M \cdot 60\mu \cdot 4\mu} = 2.78 \text{ k}$$

$$R_L' = R_{sx2} + \frac{1}{g_{m2} + g_{mb2}}$$

$$= 2.78 \text{ k} + 2.66 \text{ k}$$

$$= 5.44 \text{ k}$$

$$g_{m1}' = \frac{g_{m1}}{1 + g_{m1} R_{sx1}}$$

$$= 1.42 \text{ mA/V}$$

$$\frac{V_o}{V_i} = -g_{m1}' R_L' = -7.74$$

$$C_1 R_S = 145 \text{ ps unchanged}$$

$$C_2 R_L' = C_2 R_L \frac{R_L'}{R_L}$$

$$= 378 \text{ ps} (2.04)$$

$$= 772 \text{ ps}$$

$$C_{gd1} (R_S + R_L' + g_{m1}' R_L' R_S)$$

$$= 30f(1k + 5.44k + 1.42m(5.44k)(1k))$$

$$= 425 \text{ ps}$$

$$f_{-3dB} = \frac{1}{2\pi} \frac{10^{12}}{145 + 772 + 425}$$

$$= 119 \text{ MHz}$$

```


NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100FF
RS 4 3 1K
VI 4 0 0.981V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=3.2FF CBS=3.2FF
OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.END
0**** SMALL SIGNAL BIAS SOLUTION
NODE VOLTAGE
( 1) 5.0000 ( 2) 2.5005 ( 3) 0.9810 ( 4) 0.9810
    
```

0**** MOSFETS			0**** AC ANALYSIS						
0	M2	M1	FREQ	VDB(2)					
ID					-2.0D+01	-1.0D+01	0.0D+00	1.0D+01	2.0D+01
VGS	2.499	0.981	1.000D+06	1.304D+01					
VDS	2.499	2.501	1.166D+06	1.304D+01					
VBS	-2.501	0.000	1.359D+06	1.304D+01					
VTH	1.094	0.700	1.585D+06	1.304D+01					
VDSAT	1.405	0.281	1.848D+06	1.304D+01					
GM	3.37E-04	1.69E-03	2.154D+06	1.304D+01					
GDS	-0.00E+00	-0.00E+00	2.512D+06	1.304D+01					
GMB	3.83E-05	4.35E-04	2.929D+06	1.304D+01					
CBD	1.19E-15	3.94E-14	3.415D+06	1.304D+01					
CBS	1.58E-15	8.00E-14	3.981D+06	1.304D+01					
CGSOVL	1.20E-15	3.00E-14	4.642D+06	1.304D+01					
CGDOVL	1.20E-15	3.00E-14	5.412D+06	1.304D+01					
CGBOVL	0.00E+00	0.00E+00	6.310D+06	1.304D+01					
CGS	4.60E-15	1.15E-13	7.356D+06	1.304D+01					
CGD	0.00E+00	0.00E+00	8.577D+06	1.304D+01					
CGB	0.00E+00	0.00E+00	1.000D+07	1.304D+01					
			1.166D+07	1.303D+01					
			1.359D+07	1.303D+01					
			1.585D+07	1.303D+01					
			1.848D+07	1.302D+01					
			2.154D+07	1.301D+01					
			2.512D+07	1.300D+01					
			2.929D+07	1.298D+01					
			3.415D+07	1.296D+01					
			3.981D+07	1.292D+01					
			4.642D+07	1.288D+01					
			5.412D+07	1.282D+01					
			6.310D+07	1.275D+01					

7.21-Continued

```

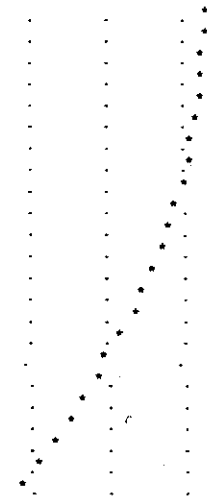7.356D+07 1.265D+01 .
8.577D+07 1.251D+01 .
1.000D+08 1.233D+01 .
1.166D+08 1.210D+01 .
1.359D+08 1.180D+01 .
1.585D+08 1.143D+01 .
1.848D+08 1.096D+01 .
2.154D+08 1.039D+01 .
2.512D+08 9.706D+00 .
2.929D+08 8.909D+00 .
3.415D+08 7.995D+00 .
3.981D+08 6.967D+00 .
4.642D+08 5.827D+00 .
5.412D+08 4.579D+00 .
6.310D+08 3.225D+00 .
7.356D+08 1.764D+00 .
8.577D+08 1.959D-01 .
1.000D+09 -1.482D+00 .
1.166D+09 -3.272D+00 .
1.359D+09 -5.172D+00 .
1.585D+09 -7.176D+00 .
1.848D+09 -9.276D+00 .
2.154D+09 -1.146D+01 .
    
```



- * DOMINANT POLE @ (DC PHASE - 45 DEGREES) = 135 DEGREES
- * DOMINANT POLE = 185 MEGAHERTZ
- * SECOND POLE @ (DC PHASE - 135 DEGREES) = 45 DEGREES
- * SECOND POLE = 1.36 GIGAHERTZ


NMOS AMP, EXAMINE SMALL SIGNAL BANDWIDTH AS DC VIN VARIES

```

0**** AC ANALYSIS
FREQ VP(2)
0.0D+00 5.0D+01 1.0D+02 1.5D+02 2.0D+02
    
```

```

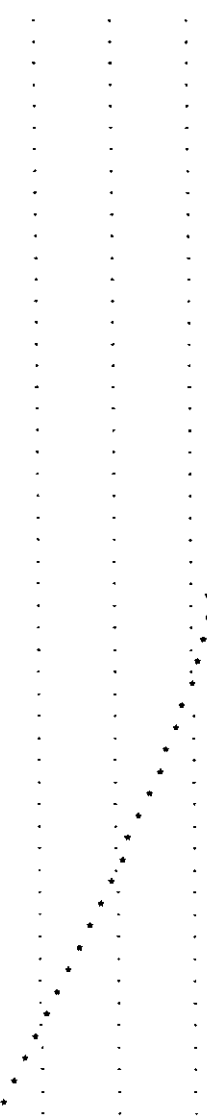1.000D+06 1.797D+02 .
1.166D+06 1.797D+02 .
1.359D+06 1.796D+02 .
1.585D+06 1.795D+02 .
1.848D+06 1.795D+02 .
2.154D+06 1.794D+02 .
2.512D+06 1.793D+02 .
2.929D+06 1.792D+02 .
3.415D+06 1.790D+02 .
3.981D+06 1.789D+02 .
4.642D+06 1.787D+02 .
5.412D+06 1.784D+02 .
6.310D+06 1.782D+02 .
7.356D+06 1.779D+02 .
8.577D+06 1.775D+02 .
1.000D+07 1.771D+02 .
1.166D+07 1.767D+02 .
1.359D+07 1.761D+02 .
1.585D+07 1.755D+02 .
1.848D+07 1.747D+02 .
2.154D+07 1.738D+02 .
2.512D+07 1.728D+02 .
2.929D+07 1.716D+02 .
3.415D+07 1.702D+02 .
3.981D+07 1.686D+02 .
4.642D+07 1.668D+02 .
5.412D+07 1.647D+02 .
6.310D+07 1.622D+02 .
7.356D+07 1.594D+02 .
8.577D+07 1.562D+02 .
1.000D+08 1.525D+02 .
1.166D+08 1.484D+02 .
1.359D+08 1.438D+02 .
1.585D+08 1.388D+02 .
1.848D+08 1.334D+02 .
2.154D+08 1.275D+02 .
2.512D+08 1.214D+02 .
2.929D+08 1.150D+02 .
3.415D+08 1.085D+02 .
3.981D+08 1.018D+02 .
4.642D+08 9.501D+01 .
5.412D+08 8.815D+01 .
6.310D+08 8.120D+01 .
7.356D+08 7.417D+01 .
8.577D+08 6.705D+01 .
1.000D+09 5.986D+01 .
1.166D+09 5.262D+01 .
1.359D+09 4.539D+01 .
1.585D+09 3.821D+01 .
1.848D+09 3.112D+01 .
2.154D+09 2.417D+01 .
    
```




```

VI 4 0 0.5V AC
0**** AC ANALYSIS
FREQ VDB(2)
-3.0D+01 -2.5D+01 -2.0D+01 -1.5D+01 -1.0D+01
    
```

```

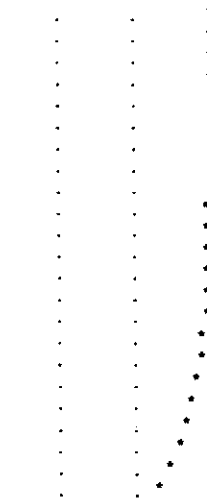3.981D+07 -1.510D+01 .
4.642D+07 -1.511D+01 .
5.412D+07 -1.511D+01 .
6.310D+07 -1.511D+01 .
7.356D+07 -1.512D+01 .
8.577D+07 -1.513D+01 .
1.000D+08 -1.514D+01 .
1.166D+08 -1.515D+01 .
1.359D+08 -1.517D+01 .
1.585D+08 -1.519D+01 .
1.848D+08 -1.523D+01 .
2.154D+08 -1.527D+01 .
2.512D+08 -1.534D+01 .
2.929D+08 -1.542D+01 .
3.415D+08 -1.553D+01 .
3.981D+08 -1.567D+01 .
4.642D+08 -1.586D+01 .
5.412D+08 -1.611D+01 .
6.310D+08 -1.642D+01 .
7.356D+08 -1.681D+01 .
8.577D+08 -1.730D+01 .
1.000D+09 -1.788D+01 .
1.166D+09 -1.856D+01 .
    
```




```

VI 4 0 1.5V AC
0**** AC ANALYSIS
FREQ VDB(2)
-1.5D+01 -1.0D+01 -5.0D+00 0.0D+00 5.0D+00
    
```

```

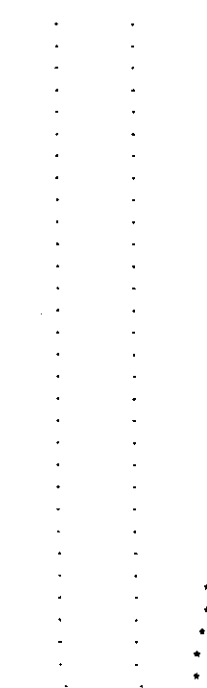2.929D+06 2.273D-01 .
3.415D+06 2.273D-01 .
3.981D+06 2.272D-01 .
4.642D+06 2.271D-01 .
5.412D+06 2.269D-01 .
6.310D+06 2.267D-01 .
7.356D+06 2.264D-01 .
8.577D+06 2.260D-01 .
1.000D+07 2.254D-01 .
1.166D+07 2.247D-01 .
1.359D+07 2.236D-01 .
1.585D+07 2.223D-01 .
1.848D+07 2.204D-01 .
2.154D+07 2.178D-01 .
2.512D+07 2.143D-01 .
2.929D+07 2.096D-01 .
3.415D+07 2.031D-01 .
3.981D+07 1.944D-01 .
4.642D+07 1.825D-01 .
5.412D+07 1.665D-01 .
6.310D+07 1.447D-01 .
7.356D+07 1.153D-01 .
8.577D+07 7.570D-02 .
1.000D+08 2.238D-02 .
1.166D+08 -4.909D-02 .
1.359D+08 -1.445D-01 .
1.585D+08 -2.709D-01 .
1.848D+08 -4.372D-01 .
2.154D+08 -6.539D-01 .
2.512D+08 -9.325D-01 .
2.929D+08 -1.286D+00 .
    
```



7.21 - Continued

3.415D+08 -1.725D+00
 3.981D+08 -2.261D+00
 4.642D+08 -2.901D+00

VI 4 0 2V AC
 0**** AC ANALYSIS
 FREQ VDB(2)

-2.5D+01 -2.0D+01 -1.5D+01 -1.0D+01 -5.0D+00

2.512D+07 -1.312D+01
 2.929D+07 -1.312D+01
 3.415D+07 -1.313D+01
 3.981D+07 -1.313D+01
 4.642D+07 -1.314D+01
 5.412D+07 -1.315D+01
 6.310D+07 -1.316D+01
 7.356D+07 -1.318D+01
 8.577D+07 -1.320D+01
 1.000D+08 -1.323D+01
 1.166D+08 -1.327D+01
 1.359D+08 -1.332D+01
 1.585D+08 -1.340D+01
 1.848D+08 -1.349D+01
 2.154D+08 -1.362D+01
 2.512D+08 -1.379D+01
 2.929D+08 -1.400D+01
 3.415D+08 -1.427D+01
 3.981D+08 -1.462D+01
 4.642D+08 -1.504D+01
 5.412D+08 -1.555D+01
 6.310D+08 -1.614D+01
 7.356D+08 -1.681D+01

VI 4 0 3V AC
 0**** AC ANALYSIS
 FREQ VDB(2)

-3.5D+01 -3.0D+01 -2.5D+01 -2.0D+01 -1.5D+01

4.642D+07 -2.380D+01
 5.412D+07 -2.381D+01
 6.310D+07 -2.382D+01
 7.356D+07 -2.383D+01
 8.577D+07 -2.384D+01
 1.000D+08 -2.386D+01
 1.166D+08 -2.389D+01
 1.359D+08 -2.392D+01
 1.585D+08 -2.397D+01
 1.848D+08 -2.403D+01
 2.154D+08 -2.412D+01
 2.512D+08 -2.423D+01
 2.929D+08 -2.437D+01
 3.415D+08 -2.455D+01
 3.981D+08 -2.477D+01
 4.642D+08 -2.504D+01
 5.412D+08 -2.536D+01
 6.310D+08 -2.573D+01
 7.356D+08 -2.613D+01
 8.577D+08 -2.657D+01
 1.000D+09 -2.701D+01

VI 4 0 4V AC
 0**** AC ANALYSIS
 FREQ VDB(2)

-3.6D+01 -3.4D+01 -3.2D+01 -3.0D+01 -2.8D+01

4.642D+07 -3.005D+01
 5.412D+07 -3.006D+01
 6.310D+07 -3.006D+01
 7.356D+07 -3.007D+01
 8.577D+07 -3.008D+01
 1.000D+08 -3.009D+01
 1.166D+08 -3.010D+01
 1.359D+08 -3.012D+01
 1.585D+08 -3.015D+01
 1.848D+08 -3.018D+01
 2.154D+08 -3.023D+01

2.512D+08 -3.029D+01
 2.929D+08 -3.037D+01
 3.415D+08 -3.046D+01
 3.981D+08 -3.058D+01
 4.642D+08 -3.072D+01
 5.412D+08 -3.088D+01
 6.310D+08 -3.106D+01
 7.356D+08 -3.125D+01
 8.577D+08 -3.144D+01
 1.000D+09 -3.163D+01
 1.166D+09 -3.181D+01
 1.359D+09 -3.197D+01
 1.585D+09 -3.211D+01
 1.848D+09 -3.224D+01
 2.154D+09 -3.235D+01
 2.512D+09 -3.246D+01
 2.929D+09 -3.256D+01
 3.415D+09 -3.267D+01
 3.981D+09 -3.279D+01
 4.642D+09 -3.293D+01
 5.412D+09 -3.310D+01
 6.310D+09 -3.332D+01
 7.356D+09 -3.359D+01

VI 4 0 5V AC
 0**** AC ANALYSIS
 FREQ VDB(2)

-5.0D+01 -4.5D+01 -4.0D+01 -3.5D+01 -3.0D+01

3.415D+08 -3.460D+01
 3.981D+08 -3.461D+01
 4.642D+08 -3.462D+01
 5.412D+08 -3.463D+01
 6.310D+08 -3.464D+01
 7.356D+08 -3.465D+01
 8.577D+08 -3.467D+01
 1.000D+09 -3.468D+01
 1.166D+09 -3.470D+01
 1.359D+09 -3.471D+01
 1.585D+09 -3.472D+01
 1.848D+09 -3.474D+01
 2.154D+09 -3.476D+01
 2.512D+09 -3.479D+01
 2.929D+09 -3.482D+01
 3.415D+09 -3.486D+01
 3.981D+09 -3.492D+01
 4.642D+09 -3.500D+01
 5.412D+09 -3.510D+01
 6.310D+09 -3.523D+01
 7.356D+09 -3.540D+01
 8.577D+09 -3.563D+01
 1.000D+10 -3.591D+01
 1.166D+10 -3.627D+01
 1.359D+10 -3.672D+01
 1.585D+10 -3.727D+01
 1.848D+10 -3.791D+01
 2.154D+10 -3.865D+01
 2.512D+10 -3.950D+01

7.2.2

$m_3, m_4 \quad I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_t)^2$

$100\mu = 15\mu \cdot 50 (V_{GS} - V_t)^2$

$V_{GS} = -1.065 V$

m_2, m_6, m_7

$100\mu = 30\mu \cdot 50 (V_{GS} - V_t)^2$

$V_{GS} = 0.958 V$

$V_{GS5} = 5 - 1.065 - 0.958$

$= 2.977 V$

$100\mu = 15\mu \frac{W}{L} (2.977 - 0.7)^2$

$m_5 \frac{W}{L} = 1.286 = \frac{2.57\mu}{2\mu}$

$2.5 = V_{GS1} + V_{GS2}$

$2.5 - 0.958 = 1.542 V = V_{GS1}$

$V_{t1} = V_{t0} + \gamma(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$



$= 0.7 + 0.4(\sqrt{0.6 + 0.958} - \sqrt{0.6})$

$= 0.89$

$I_{D1} = 100\mu = 30\mu \left(\frac{W}{L}\right)_1 (1.542 - 0.89)^2$

$\left(\frac{W}{L}\right)_1 = 7.83 = \frac{15.7\mu}{2\mu}$

signal path

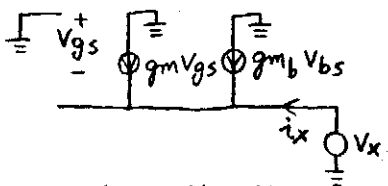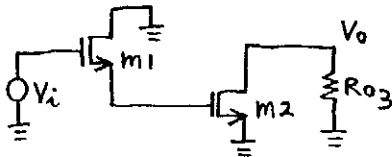

$V_{GS} = -V_x = V_{BS}$

$i_x = g_m V_x + g_{mb} V_x$

$R_{o1} = \frac{V_x}{i_x} = \frac{1}{g_m + g_{mb}}$

$r_{o2} = r_{o3} = \frac{1}{0.03(100\mu)} = 333 k$

$R_{o3} = r_{o2} || r_{o3} = 167 k$

$g_{m1} = \sqrt{2 I_D \mu C_{ox} \frac{W}{L}}$

$= \sqrt{200\mu \cdot 60\mu \cdot 7.83}$

$= 307 \mu A/V$

$g_{mb1} = g_{m1} \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}}$

$= 307\mu \frac{0.4}{2\sqrt{0.6 + 0.958}}$

$= 49.2 \mu A/V$


$R_{o1} = 2811 \Omega$

$g_{m2} = \sqrt{200\mu \cdot 60\mu \cdot 50}$

$= 775 \mu A/V$

Gain -

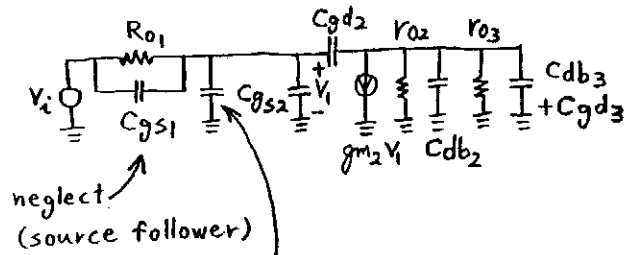$\frac{V_o}{V_i} = -g_{m1} R_{o1} g_{m2} R_{o3} = -112 V/V$



$C_{sb1} + C_{db7} + C_{gd7}$

$C_{sb1} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{\psi_0}}}$

$= \frac{0.8 f(7.83)}{\sqrt{1 + \frac{0.958}{0.6}}} = 3.89 fF$

$C_{db7} = \frac{0.8 f(100)}{\sqrt{1 + \frac{0.958}{0.6}}} = 49.6 fF$

$C_{gd7} = 0.3(100\mu) = 30 fF = C_{gd2}$

$C_{gs2} = \frac{2}{3} WL C_{ox} + 30 fF$

$= 231 + 30$

$= 261 fF$

$C_{db2} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{\psi_0}}} = \frac{0.8 f(100)}{\sqrt{1 + \frac{2.5}{0.6}}} = 35.2 fF$

$C_{db3} = C_{db2}$

7.22- Continued

$$R_0(C_{sb1} + C_{db7} + C_{gd7} + C_{gs2})$$

$$= 2811(3.89 + 49.6 + 30 + 261) f$$

$$= 0.968 ns$$

$$(r_{o2} || r_{o3})(C_{db2} + C_{db3} + C_{gd3})$$

$$= 167k(35.2 + 35.2 + 30) f$$

$$= 16.8 ns$$

$$C_{gd2}(R_{o1} + R_{o3} + g_{m2} R_{o1} R_{o3})$$

$$= 30f(2811 + 167k + 775 \mu 167k 2811)$$


$$= 16 ns$$

$$f_{-3dB} = \frac{1}{2\pi} \frac{10^9}{0.968 + 16.8 + 16} = 4.71 MHz$$

```
CMOS AMP
VDD 1 0 5V
M1 2 8 6 0 NMOS1 W=15.7U L=2U
M2 7 6 0 0 NMOS W=100U L=2U
M3 7 2 1 1 PMOS W=100U L=2U
M4 2 2 1 1 PMOS W=100U L=2U
M5 5 5 2 2 PMOS5 W=2.57U L=2U
M6 5 5 0 0 NMOS W=100U L=2U
M7 6 5 0 0 NMOS W=100U L=2U
VI 8 0 2.5746V AC
.PLOT AC VDB(7)
.AC DEC 20 100K 100MEG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0.03 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=80FF CBS=80FF
.MODEL NMOS1 NMOS KP=60U VTO=0.7 LAMBDA=0.03 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=12.6FF CBS=12.6FF
.MODEL PMOS PMOS KP=30U VTO=0.7 LAMBDA=0.03 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=80FF CBS=80FF
.MODEL PMOS5 PMOS KP=30U VTO=0.7 LAMBDA=0.03 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=2.06FF CBS=2.06FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.END
```

```
0**** SMALL SIGNAL BIAS SOLUTION
NODE VOLTAGE
( 1) 5.0000 ( 2) 3.8006 ( 5) 0.9504 ( 6) 1.0532
( 7) 2.4930 ( 8) 2.5746
```

```
0**** MOSFETS
0 M1 M2 M3 M4 M5 M6 M7
NMOS1 NMOS PMOS PMOS PMOS5 NMOS NMOS
ID 9.70E-05 2.01E-04 -2.01E-04 -1.94E-04 -9.67E-05 9.67E-05 9.70E-05
VGS 1.521 1.053 -1.199 -1.199 -2.850 0.950 0.950
VDS 2.747 2.493 -2.507 -1.199 -2.850 0.950 1.053
VBS -1.053 0.000 0.000 0.000 0.000 0.000 0.000
VTH 0.904 0.700 -0.700 -0.700 -0.700 0.700 0.700
VDSAT 0.617 0.353 -0.499 -0.499 -2.150 0.250 0.250
GM 3.15E-04 1.14E-03 8.05E-04 7.76E-04 9.00E-05 7.73E-04 7.75E-04
GDS 2.69E-06 5.61E-06 5.61E-06 5.61E-06 2.67E-06 2.82E-06 2.82E-06
GMB 4.89E-05 2.94E-04 2.08E-04 2.00E-04 2.32E-05 1.99E-04 2.00E-04
CBD 5.25E-15 3.94E-14 3.93E-14 5.06E-14 9.64E-16 5.41E-14 5.26E-14
CBS 8.28E-15 8.00E-14 8.00E-14 8.00E-14 2.06E-15 8.00E-14 8.00E-14
CGSOVL 4.71E-15 3.00E-14 3.00E-14 3.00E-14 7.71E-16 3.00E-14 3.00E-14
CGDOVL 4.71E-15 3.00E-14 3.00E-14 3.00E-14 7.71E-16 3.00E-14 3.00E-14
CGBOVL 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00
CGS 3.61E-14 2.30E-13 2.30E-13 2.30E-13 5.92E-15 2.30E-13 2.30E-13
CGD 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00
CGB 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00 0.00E+00
```

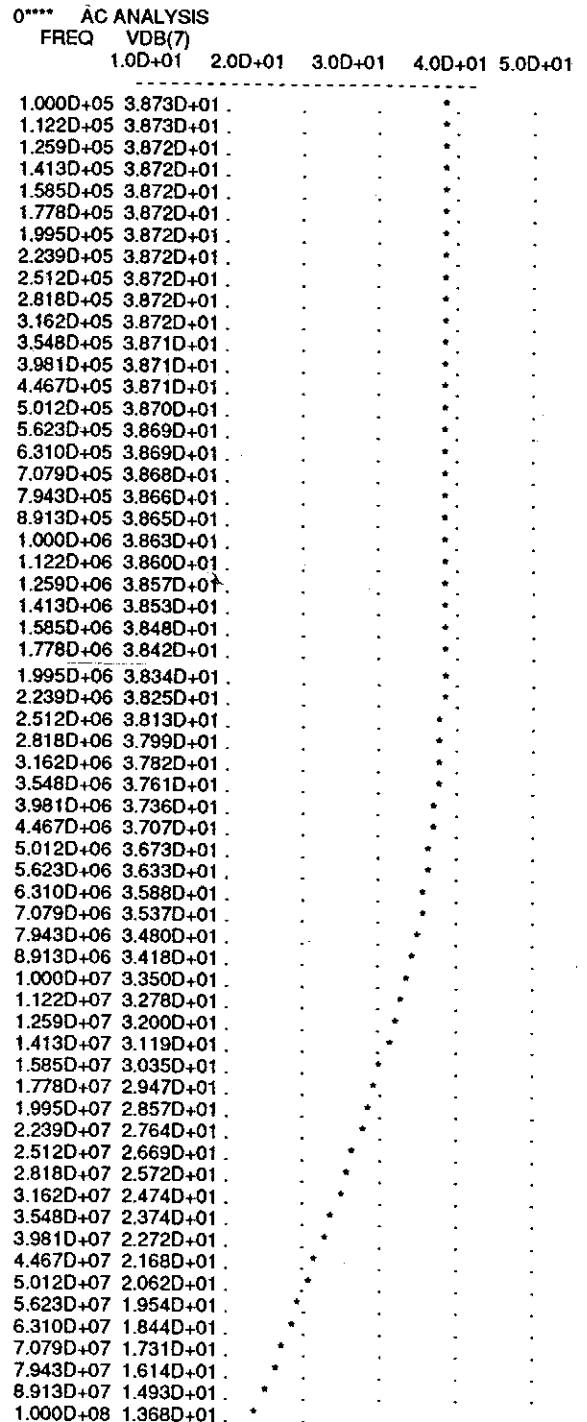

-3DB FREQUENCY = 6.31 MEGAHERTZ