

### Homework Assignment No. 7 -Solutions

#### Problem 1 - (10 points)

Find the low frequency PSRR and all roots of the positive and negative power supply rejection ratio performance for the two-stage op amp of Fig. P6.3-9.

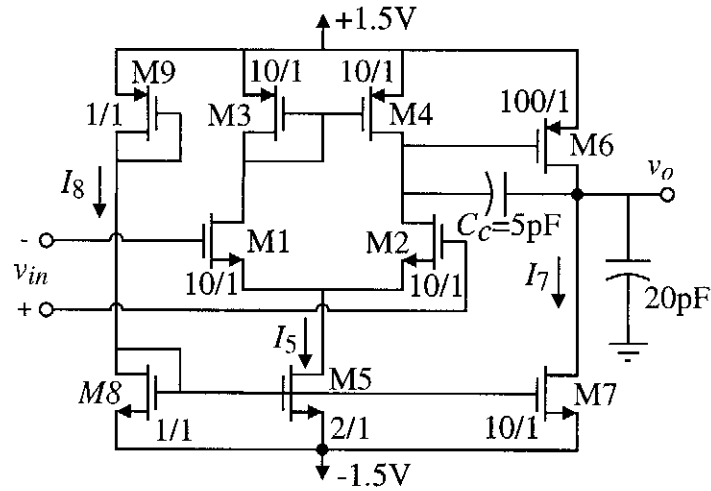


Figure P6.3-10

#### Solution

Referring to the figure

$$V_{DD} - V_{SS} = V_{T8} + V_{T9} + \sqrt{\frac{2I_8}{K_N (W/L)_8}} + \sqrt{\frac{2I_8}{K_P (W/L)_9}}$$

or,  $I_8 = 60 \mu A$

Now,

$$g_{m1} = 363.3 \mu S, g_{ds2} = 2.4 \mu S, g_{ds4} = 3 \mu S, g_{m6} = 774.6 \mu S, g_{ds6} = 30 \mu S$$

and  $g_{ds7} = 24 \mu S$

$$\therefore A_{v1} = 67.3 \text{ and } A_{v2} = 14.3$$

For the positive PSRR, the low frequency PSRR is

$$PSRR^+ = \frac{A_v(0)G_{II}}{g_{ds6}} = 1737$$

and poles and zeros are

$$p_1 = \frac{(GB)g_{ds6}}{A_v(0)G_{II}} = 6.66 \text{ KHz}, z_1 = GB = 11.6 \text{ MHz. and } z_2 = p_2 = 6.2 \text{ MHz.}$$

For the negative PSRR, the low frequency PSRR is given by

$$PSRR^- = \frac{A_v(0)G_{II}}{g_{ds7}} = 2171$$

and the poles and zeros are

$$p_1 = \frac{(GB)G_{II}}{g_{m1}} = 172.4 \text{ KHz}, z_1 = GB = 11.6 \text{ MHz and } z_2 = p_2 = 6.2 \text{ MHz.}$$

**Problem 2 – (10 points)**

A CMOS op amp that uses a 5V power supply is shown. All transistor lengths are 1μm and operate in the saturation region. Design all of the W values of every transistor of this op amp to meet the following specifications: Slew rate = ±10V/μs,  $V_{out(max)} = 4V$ ,  $V_{out(min)} = 1V$ ,  $V_{ic(min)} = 1.5V$ ,  $V_{ic(max)} = 4V$  and GB = 10MHz.

Your design should meet or exceed these specifications. Ignore bulk effects and summarize your W values to the nearest micron, the bias current,  $I_5(\mu A)$ , the power dissipation, the differential voltage gain,  $A_{vd}$ , and  $V_{BP}$  and  $V_{BN}$  in the table shown.

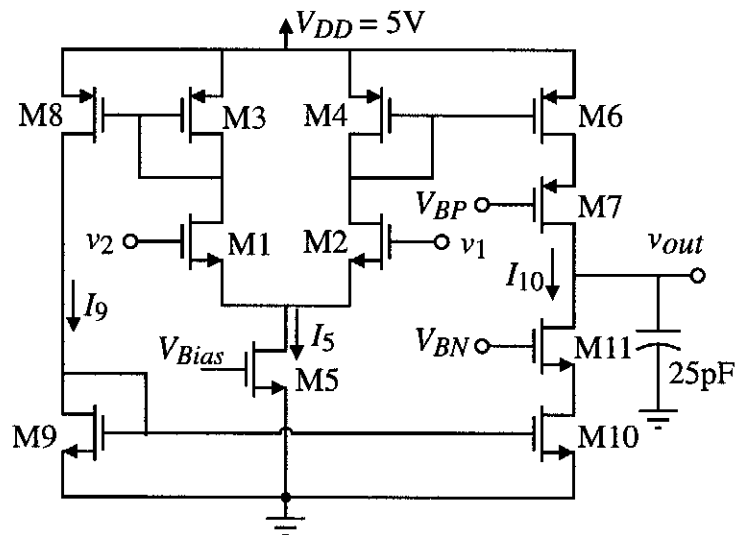


Figure P6.5-13

**Solution**

- 1.)  $I_5 = C_L \cdot SR = 250\mu A$
- 2.)  $g_{m1} = GB \cdot C_L = 20\pi \times 106 \cdot 25pF = 1,570.8\mu S \Rightarrow \frac{W_1}{L_1} = \frac{(1.570 \times 10^{-3})^2}{2 \cdot 110 \cdot 125 \times 10^{-6}} = 90$
- 3.)  $W_3=W_4=W_6=W_7=W_8 = \frac{2I_D}{K'(V_{DS(sat)})^2} = \frac{2 \cdot 250}{50 \cdot 0.25} = 40$  (assumed  $I_D$  of 250μA worst case)
- 4.)  $W_9=W_{10}=W_{11} = \frac{2I_D}{K'(V_{DS(sat)})^2} = \frac{2 \cdot 250}{110 \cdot 0.25} = 18$  (assumed  $I_D$  of 250μA worst case)
- 5.)  $V_{icm(min)} = V_{DS5(sat)} + V_{GS1} \rightarrow V_{DS5(sat)} = 1.5 - (0.159 + 0.7) = 0.6411V$   
 $\therefore W_5 = \frac{2I_D}{K'(V_{DS(sat)})^2} = \frac{2 \cdot 250}{110 \cdot 0.6411^2} = 11$
- 6.)  $A_{vd} = g_{m1}R_{out}$      $g_{mN} = 704\mu S$ ,  $r_{dsN} = 0.2M\Omega$ ,  $g_{mP} = 707\mu S$ ,  $r_{dsP} = 0.16M\Omega$   
 $R_{out} \approx g_{mN} \cdot r_{dsN}^2 \parallel g_{mP} \cdot r_{dsP}^2 = 28.14M\Omega \parallel 18.1M\Omega = 11M\Omega$   
 $\therefore A_{vd} = 1.57mS \cdot 11M\Omega = 17,329V/V$
- 7.)  $V_{BP} = 5 - V_{DSP(sat)} + V_{GSP(sat)} = 5 - 0.5 + 0.5 + 0.7 = 3.3V$   
 $V_{BN} = V_{DSP(sat)} + V_{GSP(sat)} = 0.5 + 0.5 + 0.7 = 1.7V$
- 8.)  $P_{diss} = 5(250\mu A + 250\mu A) = 2.5mW$

W1=W2	W3=W4=W6 =W7=W8	W9=W10 =W11	W5	$I_5(\mu A)$	$A_{vd}$	$V_{BP}$	$V_{BN}$	$P_{diss}$
90μm	40μm	18μm	11μm	250μA	17,329 V/V	3.3V	1.7V	2.5mW

Problem 3 - (10 points)

6.15

$$200 \mu\text{A} = |I_{D_8}| = |I_{D_5}| = |I_{D_7}| = I_{D_6}$$

$$100 \mu\text{A} = I_{D_1} = I_{D_2} = I_{D_3} = I_{D_4}$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.9 (8.85 \times 10^{-14} \text{ F/cm})}{80 \text{ \AA}}$$

$$= 431 \text{ nF/cm}^2$$

$$\mu_n C_{ox} = 450 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \cdot 431 \frac{\text{nF}}{\text{cm}^2}$$

$$= 194 \mu\text{A/V}^2$$

$$k'_n = 194 \mu\text{A/V}^2$$

$$k'_p = 64.7 \mu\text{A/V}^2$$

$$\frac{v_o}{v_i} = -g_{m_2} (r_{o_2} \parallel r_{o_4}) g_{m_6} (r_{o_6} \parallel r_{o_7})$$

$$\frac{1}{r_{o_2}} = \frac{I_{D_2}}{L_{eff}} \frac{dX_d}{dV_{D_5}} = \frac{100 \mu\text{A}}{0.72 \mu\text{m}} = 5.56 \mu\text{A}$$

$$r_{o_2} = 180 \text{ k}\Omega = r_{o_4}$$

$$r_{o_6} = 90 \text{ k}\Omega = r_{o_7}$$

$$L_{eff} = L - X_d - 2L_d$$

$$= 1 - 0.1 - 2(0.09)$$

$$= 0.72 \mu\text{m}$$

$$g_{m_2} = \sqrt{2 k'_p \frac{W}{L_{eff}} I_{D_2}}$$

$$= \sqrt{2 (64.7 \mu\text{A/V}^2) \left(\frac{150}{0.72}\right) (100 \mu\text{A})}$$

$$= 1640 \mu\text{A/V}$$

$$g_{m_6} = \sqrt{2 (194 \mu\text{A/V}^2) \left(\frac{100}{0.72}\right) (200 \mu\text{A})}$$

$$= 3280 \mu\text{A/V}$$

$$\frac{v_o}{v_i} = -(1.64 \text{ m}) (90 \text{ k}) (3.28 \text{ m}) (45 \text{ k})$$

$$= -2.18 \times 10^4$$

common mode range:

From (6.75),

$$V_{ic} > V_{t_1} + V_{t_3} + V_{ov_3} - V_{SS}$$

$$V_{ov_3} = \sqrt{\frac{2(100)}{194 (50/0.72)}} = 0.12 \text{ V}$$

$$V_{ic} > -0.8 + 0.6 + 0.12 - 1.5$$

$$V_{ic} > -1.58 \text{ V}$$

From (6.77),

$$V_{ic} < V_{t_1} + V_{ov_1} + V_{ov_5} + V_{DD}$$

$$V_{ov_5} = -\sqrt{\frac{2(200)}{64.7 (150/0.72)}} = -0.17 \text{ V}$$

$$V_{ov_1} = -\sqrt{\frac{2(100)}{64.7 (150/0.72)}} = -0.12 \text{ V}$$

$$V_{ic} < -0.8 - 0.12 - 0.17 + 1.5$$

$$V_{ic} < 0.41 \text{ V}$$

From (6.86),

$$\frac{v_o}{v_{dd}} \equiv 0$$

From (6.87),

$$\frac{v_o}{v_{SS}} = \frac{r_{o_7}}{r_{o_6} + r_{o_7}} = 0.5$$

## Problem 3 - Continued

```

TWO-STAGE CMOS AMPLIFIER
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PMOS W=150U L=1U
M2 8 6 4 4 PMOS W=150U L=1U
M3 7 7 200 200 NMOS W=50U L=1U
M4 8 7 200 200 NMOS W=50U L=1U
M5 4 3 100 100 PMOS W=150U L=1U
M6 9 8 200 200 NMOS W=100U L=1U
M7 9 3 100 100 PMOS W=150U L=1U
M8 3 3 100 100 PMOS W=150U L=1U
IBIAS 3 200 2000
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR
* TO SET THE OUTPUT TO ZERO.
V11 5 2 4.6U
V12 6 2 0
VIC 2 0 0
*LEFF = LDRAMB - 2LD -XD = 1 - 2(0.09) - 0.1 = 0.72 UM
*LAMBDA=(XHD/DVDS)/LEFF = 0.04U/0.72U = 0.0555
.MODEL NMOS NMOS LEVEL=1 KP=194U VTO=0.6 LAMBDA=0.0555
.MODEL PMOS PMOS LEVEL=1 KP=64.7U VTO=-0.8 LAMBDA=0.0555
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS VNTOL=1M ABSTOL=1F RELTOL=1U
.OFF
.TF V(9) V11
.END

**** OPERATING POINT INFORMATION TWCN= 27.000 TEMP= 27.000
      NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:2      = 0. 0:3      = 5.024E-01 0:4      = 9.357E-01
+0:5      = 4.600E-06 0:6      = 0. 0:7      = -7.609E-01
+0:8      = -7.602E-01 0:9      = 3.026E-04 0:100     = 1.500E+00
+0:200     = -1.500E+00

SUBCKT
ELEMENT 0:M1 0:M2 0:M3 0:M4
MODEL 0:PMOS 0:PMOS 0:NMOS 0:NMOS
ID -9.772E-05 -9.772E-05 9.772E-05 9.772E-05
IBS 0. 0. 0. 0.
IBD 1.697E-14 1.696E-14 -7.391E-15 -7.398E-15
VGS -9.357E-01 -9.357E-01 7.391E-01 7.391E-01
VDS -1.696E+00 -1.695E+00 7.391E-01 7.398E-01
VBS 0. 0. 0. 0.
VTH -8.000E-01 -8.000E-01 6.000E-01 6.000E-01
VDSAT -1.357E-01 -1.357E-01 1.391E-01 1.391E-01
BETA 1.062E-02 1.062E-02 1.010E-02 1.010E-02
GAM EFF 0. 0. 0. 0.
GM 1.441E-03 1.441E-03 1.405E-03 1.405E-03
GDS 4.957E-06 4.957E-06 5.210E-06 5.210E-06
GMS 0. 0. 0. 0.

SUBCKT
ELEMENT 0:M5 0:M6 0:M7 0:M8
MODEL 0:PMOS 0:NMOS 0:PMOS 0:PMOS
ID -1.354E-04 2.053E-04 -2.053E-04 -2.000E-04
IBS 0. 0. 0. 0.
IBD 5.643E-15 -1.500E-14 1.500E-14 9.976E-15
VGS -9.976E-01 7.398E-01 -9.976E-01 -9.976E-01
VDS -5.643E-01 1.500E+00 -1.499E+00 -9.976E-01
VBS 0. 0. 0. 0.
VTH -8.000E-01 6.000E-01 -8.000E-01 -8.000E-01
VDSAT -1.976E-01 1.398E-01 -1.976E-01 -1.976E-01
BETA 1.001E-02 2.102E-02 1.051E-02 1.024E-02
GAM EFF 0. 0. 0. 0.
GM 1.978E-03 2.937E-03 2.078E-03 2.024E-03
GDS 1.052E-05 1.052E-05 1.052E-05 1.052E-05
GMS 0. 0. 0. 0.

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V(9)/V11 = -1.975E+04
INPUT RESISTANCE AT V11 = 1.000E+20
OUTPUT RESISTANCE AT V(9) = 4.754E+04

```

```

TWO-STAGE CMOS AMPLIFIER (MAXIMUM COMMON-MODE INPUT VOLTAGE)
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PMOS W=150U L=1U
M2 8 6 4 4 PMOS W=150U L=1U
M3 7 7 200 200 NMOS W=50U L=1U
M4 8 7 200 200 NMOS W=50U L=1U
M5 4 3 100 100 PMOS W=150U L=1U
M6 9 8 200 200 NMOS W=100U L=1U
M7 9 3 100 100 PMOS W=150U L=1U
M8 3 3 100 100 PMOS W=150U L=1U
IBIAS 3 200 2000
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR
* TO SET THE OUTPUT TO ZERO.
V11 5 2 13.7U
V12 6 2 0
VIC 2 0 0.36
*LEFF = LDRAMB - 2LD -XD = 1 - 2(0.09) - 0.1 = 0.72 UM
*LAMBDA=(XHD/DVDS)/LEFF = 0.04U/0.72U = 0.0555
.MODEL NMOS NMOS LEVEL=1 KP=194U VTO=0.6 LAMBDA=0.0555
.MODEL PMOS PMOS LEVEL=1 KP=64.7U VTO=-0.8 LAMBDA=0.0555
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS VNTOL=1M ABSTOL=1F RELTOL=1U
.OFF
.TF V(9) V11
.END

**** OPERATING POINT INFORMATION TWCN= 27.000 TEMP= 27.000
      NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:2      = 3.600E-01 0:3      = 5.024E-01 0:4      = 1.293E+00
+0:5      = 3.600E-01 0:6      = 3.600E-01 0:7      = -7.622E-01
+0:8      = -7.602E-01 0:9      = 1.329E-04 0:100     = 1.500E+00
+0:200     = -1.500E+00

**** MOSFETS
SUBCKT
ELEMENT 0:M1 0:M2 0:M3 0:M4
MODEL 0:PMOS 0:PMOS 0:NMOS 0:NMOS
ID -9.584E-05 -9.585E-05 9.584E-05 9.585E-05
IBS 0. 0. 0. 0.
IBD 2.055E-14 2.053E-14 -7.378E-15 -7.398E-15
VGS -9.331E-01 -9.332E-01 7.378E-01 7.378E-01
VDS -2.055E+00 -2.053E+00 7.378E-01 7.398E-01
VBS 0. 0. 0. 0.
VTH -8.000E-01 -8.000E-01 6.000E-01 6.000E-01
VDSAT -1.331E-01 -1.332E-01 1.378E-01 1.378E-01
BETA 1.081E-02 1.081E-02 1.010E-02 1.010E-02
GAM EFF 0. 0. 0. 0.
GM 1.440E-03 1.440E-03 1.391E-03 1.391E-03
GDS 4.774E-06 4.775E-06 5.110E-06 5.110E-06
GMS 0. 0. 0. 0.

SUBCKT
ELEMENT 0:M5 0:M6 0:M7 0:M8
MODEL 0:PMOS 0:NMOS 0:PMOS 0:PMOS
ID -1.917E-04 2.053E-04 -2.053E-04 -2.000E-04
IBS 0. 0. 0. 0.
IBD 2.068E-15 -1.500E-14 1.500E-14 9.976E-15
VGS -9.976E-01 7.398E-01 -9.976E-01 -9.976E-01
VDS -2.068E-01 1.500E+00 -1.499E+00 -9.976E-01
VBS 0. 0. 0. 0.
VTH -8.000E-01 6.000E-01 -8.000E-01 -8.000E-01
VDSAT -1.976E-01 1.398E-01 -1.976E-01 -1.976E-01
BETA 9.816E-03 2.102E-02 1.051E-02 1.024E-02
GAM EFF 0. 0. 0. 0.
GM 1.940E-03 2.937E-03 2.078E-03 2.024E-03
GDS 1.052E-05 1.052E-05 1.052E-05 1.052E-05
GMS 0. 0. 0. 0.

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V(9)/V11 = -2.029E+04
INPUT RESISTANCE AT V11 = 1.000E+20
OUTPUT RESISTANCE AT V(9) = 4.753E+04

```

## Problem 3 - Continued

## TWO-STAGE CMOS AMPLIFIER (MINIMUM COMMON-MODE INPUT VOLTAGE)

```
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PMOS W=150U L=1U
M2 8 6 4 4 PMOS W=150U L=1U
M3 7 7 200 200 NMOS W=50U L=1U
M4 8 7 200 200 NMOS W=50U L=1U
M5 4 3 100 100 PMOS W=150U L=1U
M6 9 8 200 200 NMOS W=100U L=1U
M7 9 3 100 100 PMOS W=150U L=1U
M8 3 3 100 100 PMOS W=150U L=1U
IRIAS 3 200 200U
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR
* TO SET THE OUTPUT TO ZERO.
V11 5 2 -39.7U
V12 6 2 0
* THE MINIMUM VALUE OF VIC IS ADJUSTED BY TRIAL AND ERROR
* UNTIL M1 BARELY OPERATES IN THE ACTIVE REGION
* (WHERE |VDS| > |VDSAT| FOR M1)
VIC 2 0 -1.55
*LEFF = LDRAMN - 2LD -XD = 1 - 2(0.09) - 0.1 = 0.72 UM
*LAMBDA=(DD/DVDS)/LEFF = 0.04U/0.72U = 0.0555
.MODEL NMOS NMOS LEVEL=1 KP=194U VTO=0.6 LAMBDA=0.0555
.MODEL PMOS PMOS LEVEL=1 KP=64.7U VTO=-0.8 LAMBDA=0.0555
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS VNTOL=1N ABSTOL=1P RELTOL=1U
.OP
.TF V(9) V11
.END

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 27.000
      NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:2      = -1.550E+00 0:3      = 5.024E-01 0:4      = -6.030E-01
+0:5      = -1.550E+00 0:6      = -1.550E+00 0:7      = -7.552E-01
+0:8      = -7.602E-01 0:9      = 5.068E-04 0:100     = 1.500E+00
+0:200     = -1.500E+00

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V(9)/V11      = -1.647E-02
INPUT RESISTANCE AT VDD      = 4.723E+04
OUTPUT RESISTANCE AT V(9)    = 4.754E+04
```

## \*\*\*\* MOSFETS

## SUBCKT

```
ELEMENT 0:M1 0:M2 0:M3 0:M4
MODEL 0:PMOS 0:PMOS 0:NMOS 0:NMOS
ID -1.058E-04 -1.058E-04 1.058E-04 1.058E-04
IBS 0. 0. 0. 0.
IBD 1.523E-15 1.572E-15 -7.448E-15 -7.398E-15
VGS -9.471E-01 -9.470E-01 7.448E-02 7.448E-01
VDS -1.523E-01 -1.572E-01 7.448E-01 7.398E-01
VBS 0. 0. 0. 0.
VTH -8.000E-01 -8.000E-01 6.000E-01 6.000E-01
VDSAT -1.471E-01 -1.470E-01 1.448E-01 1.448E-01
BETA 9.797E-03 9.790E-03 1.010E-02 1.010E-02
GAM KFF 0. 0. 0. 0.
GM 1.439E-03 1.439E-03 1.462E-03 1.462E-03
GDS 5.824E-06 5.821E-06 5.640E-06 5.640E-06
GMB 0. 0. 0. 0.
```

## SUBCKT

```
ELEMENT 0:M5 0:M6 0:M7 0:M8
MODEL 0:PMOS 0:NMOS 0:PMOS 0:PMOS
ID -2.116E-04 2.053E-04 -2.053E-04 -2.000E-04
IBS 0. 0. 0. 0.
IBD 2.103E-14 -1.501E-14 1.499E-14 9.976E-15
VGS -9.976E-01 7.398E-01 -9.976E-01 -9.976E-01
VDS -2.103E+00 1.500E+00 -1.499E+00 -9.976E-01
VBS 0. 0. 0. 0.
VTH -8.000E-01 6.000E-01 -8.000E-01 -8.000E-01
VDSAT -1.976E-01 1.398E-01 -1.976E-01 -1.976E-01
BETA 1.044E-02 2.102E-02 1.051E-02 1.024E-02
GAM KFF 0. 0. 0. 0.
GM 2.142E-03 2.937E-03 2.077E-03 2.024E-03
GDS 1.052E-05 1.052E-05 1.052E-05 1.052E-05
GMB 0. 0. 0. 0.
```

## \*\*\*\* SMALL-SIGNAL TRANSFER CHARACTERISTICS

```
V(9)/V11      = -1.750E+04
INPUT RESISTANCE AT V11      = 1.000E+20
OUTPUT RESISTANCE AT V(9)    = 4.754E+04
```

## TWO-STAGE CMOS AMPLIFIER (GAIN FROM VDD)

```
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PMOS W=150U L=1U
M2 8 6 4 4 PMOS W=150U L=1U
M3 7 7 200 200 NMOS W=50U L=1U
M4 8 7 200 200 NMOS W=50U L=1U
M5 4 3 100 100 PMOS W=150U L=1U
M6 9 8 200 200 NMOS W=100U L=1U
M7 9 3 100 100 PMOS W=150U L=1U
M8 3 3 100 100 PMOS W=150U L=1U
IRIAS 3 200 200U
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR
* TO SET THE OUTPUT TO ZERO.
V11 5 2 4.6U
V12 6 2 0
VIC 2 0 0
*LEFF = LDRAMN - 2LD -XD = 1 - 2(0.09) - 0.1 = 0.72 UM
*LAMBDA=(DD/DVDS)/LEFF = 0.04U/0.72U = 0.0555
.MODEL NMOS NMOS LEVEL=1 KP=194U VTO=0.6 LAMBDA=0.0555
.MODEL PMOS PMOS LEVEL=1 KP=64.7U VTO=-0.8 LAMBDA=0.0555
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS VNTOL=1N ABSTOL=1P RELTOL=1U
.OP
.TF V(9) VDD
.END

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 27.000
      NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:2      = 0. 0:3      = 5.024E-01 0:4      = 9.357E-01
+0:5      = 4.600E-06 0:6      = 0. 0:7      = -7.609E-01
+0:8      = -7.602E-01 0:9      = 3.026E-04 0:100     = 1.500E+00
+0:200     = -1.500E+00

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V(9)/VDD      = -1.647E-02
INPUT RESISTANCE AT VDD      = 4.723E+04
OUTPUT RESISTANCE AT V(9)    = 4.754E+04
```


## TWO-STAGE CMOS AMPLIFIER (GAIN FROM VSS)

```
*****
VDD 100 0 1.5
VSS 200 0 -1.5
M1 7 5 4 4 PMOS W=150U L=1U
M2 8 6 4 4 PMOS W=150U L=1U
M3 7 7 200 200 NMOS W=50U L=1U
M4 8 7 200 200 NMOS W=50U L=1U
M5 4 3 100 100 PMOS W=150U L=1U
M6 9 8 200 200 NMOS W=100U L=1U
M7 9 3 100 100 PMOS W=150U L=1U
M8 3 3 100 100 PMOS W=150U L=1U
IRIAS 3 200 200U
* THE DC OFFSET IS ADJUSTED BY TRIAL AND ERROR
* TO SET THE OUTPUT TO ZERO.
V11 5 2 4.6U
V12 6 2 0
VIC 2 0 0
*LEFF = LDRAMN - 2LD -XD = 1 - 2(0.09) - 0.1 = 0.72 UM
*LAMBDA=(DD/DVDS)/LEFF = 0.04U/0.72U = 0.0555
.MODEL NMOS NMOS LEVEL=1 KP=194U VTO=0.6 LAMBDA=0.0555
.MODEL PMOS PMOS LEVEL=1 KP=64.7U VTO=-0.8 LAMBDA=0.0555
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS VNTOL=1N ABSTOL=1P RELTOL=1U
.OP
.TF V(9) VSS
.END

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 27.000
      NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:2      = 0. 0:3      = 5.024E-01 0:4      = 9.357E-01
+0:5      = 4.600E-06 0:6      = 0. 0:7      = -7.609E-01
+0:8      = -7.602E-01 0:9      = 3.026E-04 0:100     = 1.500E+00
+0:200     = -1.500E+00

**** SMALL-SIGNAL TRANSFER CHARACTERISTICS
V(9)/VSS      = 5.063E-01
INPUT RESISTANCE AT VSS      = 1.865E+05
OUTPUT RESISTANCE AT V(9)    = 4.754E+04
```


Problem 4 - (10 points)

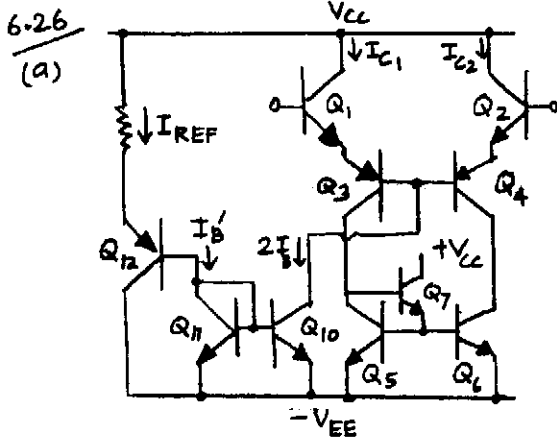

$$I_{C1} = I_{C2} = 10 \mu A \quad \beta_{PNP} = 50$$

$$I_B = \frac{I_{C1}}{1 + \beta_{PNP}} \quad \therefore 2I_B = 0.39 \mu A \approx I_B'$$
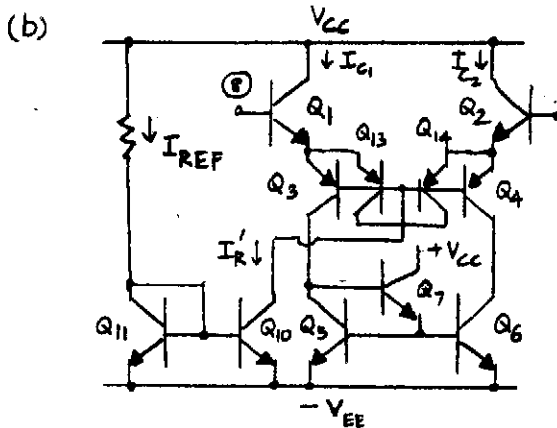
$$\therefore I_{REF} = (1 + \beta_{PNP}) I_B' = 20 \mu A$$



$$I_{C1} = I_{C2} = 10 \mu A$$

$$I_{E3} = I_{E13} = I_{E14} = I_{E4} \approx \frac{I_{C1}}{2} = 5 \mu A$$

$$I_{R'} = 2|I_{C3}| + 4|I_{B13}|$$

$$= 2 \left( \frac{5 \mu A}{1+50} \right) + 4 \cdot \left( \frac{5 \mu A}{1+50} \right)$$

$$= 10.2 \mu A = I_{REF}$$

741 INPUT BIAS SCHEME (A)

```
*****
VCC 100 0 15
VEE 200 0 -15
IREF 100 3 200
Q1 100 8 10 NPN
Q2 100 9 11 NPN
Q3 12 6 10 PNP
Q4 16 6 11 PNP
Q5 12 13 200 NPN
Q6 16 13 200 NPN
Q7 100 12 13 NPN
Q10 6 6 200 NPN
Q11 6 4 200 NPN
Q12 200 4 3 PNP
```

```
* WITH VIC = -12.6 V,
* VCE10 = VIC - VBE1 - |VBE3| - (-VEE)
* = -12.6 - 0.6 - 0.6 + 15 = 1.2 V
* THIS IS ENOUGH TO OPERATE Q10 IN THE FORWARD-ACTIVE REGION.
V11 8 0 -12.6
V12 9 0 -12.6 AC 1
```

```
.MODEL NPN NPN BF=250 IS=5E-15
.MODEL PNP PNP BF=50 IS=2E-15
.OPTIONS NOBACK NOMOD
.WIDTH OUT=40
.OP
```

```
* VOUT IS USED TO MEASURE THE AC SHORT CIRCUIT OUTPUT
* CURRENT TO FIND GM.
* THE DC VALUE OF VOUT WAS GIVEN IN THE PROBLEM STATEMENT.
VOUT 16 200 1.6
```

```
.AC DEC 1 1 10
.PRINT AC IM(VOUT) IP(VOUT)
```

```
* THE TRANSCONDUCTANCE CAN ALSO BE MEASURED BY ELIMINATING
* THE VOLTAGE SOURCE CONNECTED AT THE OUTPUT AND THE
* AC ANALYSIS ABOVE, FINDING THE VOLTAGE GAIN AND OUTPUT
* RESISTANCE WITH A .TF STATEMENT AS SHOWN BELOW,
* AND CALCULATING GM = (VOLTAGE GAIN)/(OUTPUT RESISTANCE)
* THE RESULT IS GM = 1.736E6/9.237E7 = 1.88E-6 A/V
.TF V(16) V12
.END
```

```
**** OPERATING POINT INFORMATION TNCM= 27.000 TEMP= 27.000
```

NODE	=VOLTAGE	NODE	=VOLTAGE	NODE	=VOLTAGE
+0:3	-1.392E+01 0:4	-1.453E+01 0:6	-1.373E+01		
+0:8	-1.260E+01 0:9	-1.260E+01 0:10	-1.315E+01		
+0:11	-1.315E+01 0:12	-1.401E+01 0:13	-1.444E+01		
+0:16	-1.340E+01 0:100	1.500E+01 0:200	-1.500E+01		

\*\*\*\* BIPOLAR JUNCTION TRANSISTORS

SUBJECT	0:Q1	0:Q2	0:Q3	0:Q4	0:Q5
ELEMENT	0:NPN	0:NPN	0:PNP	0:PNP	0:NPN
MODEL	0:NPN	0:NPN	0:PNP	0:PNP	0:NPN
IB	3.945E-08	3.945E-08	-1.942E-07	-1.949E-07	3.883E-08
IC	9.863E-06	9.863E-06	-9.708E-06	-9.707E-06	9.708E-06
VBE	5.536E-01	5.536E-01	-5.769E-01	-5.769E-01	5.532E-01
VCE	2.815E+01	2.815E+01	-8.651E-01	-2.464E-01	9.813E-01
VBC	-2.740E+01	-2.750E+01	2.883E-01	-3.304E-01	-4.282E-01
VS	-1.500E+01	-1.500E+01	1.373E+01	1.373E+01	1.401E+01
POWER	2.777E-04	2.777E-04	8.511E-06	2.505E-06	9.544E-06
BETA	2.500E+02	2.500E+02	5.000E+01	4.981E+01	2.500E+02
GM	3.813E-04	3.813E-04	3.756E-04	3.753E-04	3.753E-04
RPI	6.555E+05	6.556E+05	1.332E+05	1.332E+05	6.660E+05
RX	0.	0.	0.	0.	0.
RO	5.520E+15	5.520E+15	1.441E+14	1.661E+07	8.563E+13
BETAAC	2.500E+02	2.500E+02	5.000E+01	4.999E+01	2.500E+02

## Problem 4 - Continued

```

SUBCKT
ELEMENT 0:Q6 0:Q7 0:Q10 0:Q11 0:Q12
MODEL 0:NPN 0:NPN 0:NPN 0:NPN 0:PMP
IB 3.893E-08 3.094E-10 1.556E-09 1.556E-09 -3.922E-07
IC 9.708E-06 7.735E-08 3.890E-07 3.890E-07 -1.961E-05
VBE 5.532E-01 4.282E-01 4.699E-01 4.699E-01 -5.950E-01
VCE 1.600E+00 2.844E+01 1.269E+00 4.699E-01 -1.065E+00
VBC -1.046E+00 -2.901E+01 -7.996E-01 0. 4.699E-01
VS 1.340E+01 -1.500E+01 1.373E+01 1.453E+01 1.453E+01
POWER 1.555E-05 2.278E-06 4.947E-07 1.836E-07 2.112E-05
BETA0 2.500E+02 2.500E+02 2.500E+02 2.500E+02 5.000E+01
GM 3.753E-04 2.991E-06 1.504E-05 1.504E-05 7.581E-04
RPI 6.660E+05 8.359E+07 1.662E+07 1.662E+07 6.595E+04
XX 0. 0. 0. 0. 0.
NO 2.093E+14 5.803E+15 1.599E+14 5.172E+12 2.349E+14
BETAAC 2.500E+02 2.500E+02 2.500E+02 2.500E+02 5.000E+01

```

```

***** AC ANALYSIS THOM= 27.000 TEMP= 27.000
FREQ I MAG I PHASE VOUT VOUT
1.0000E+00 1.877E-04 4.174E-23
1.0000E+01 1.877E-04 4.174E-22

```

## 741 INPUT BIAS SCHEME (B)

\*\*\*\*\*

```

VCC 100 0 15
VEE 200 0 -15
IREF 100 4 10.2U
Q1 100 8 10 NPN
Q2 100 9 11 NPN
Q3 12 6 10 PMP
Q4 15 6 11 PMP
Q5 12 13 200 NPN
Q6 15 13 200 NPN
Q7 100 12 13 NPN
Q10 6 4 200 NPN
Q11 4 4 200 NPN

```

\* REMOVE Q12 FROM THE CIRCUIT.

\* IT WAS ONLY NEEDED FOR PART (A).

```

Q12 200 200 200 PMP
Q13 6 6 10 PMP
Q14 6 6 11 PMP

```

\* WITH VIC = -12.6 V,

\* VCE10 = VIC - VBE1 - |VBE3| - (-VEE)

\* = -12.6 - 0.6 - 0.6 + 15 = 1.2 V

\* THIS IS ENOUGH TO OPERATE Q10 IN THE FORWARD-ACTIVE REGION.

```

V1 8 0 -12.6
V12 9 0 -12.6 AC 1

```

.MODEL NPN NPN BF=250 IS=5E-15

.MODEL PMP PMP BF=50 IS=2E-15

.OPTIONS NOPAGE NOMOD

.WIDTH OUT=40

.OP

\* VOUT IS USED TO MEASURE THE AC SHORT CIRCUIT OUTPUT

\* CURRENT TO FIND GM.

\* THE DC VALUE OF VOUT WAS GIVEN IN THE PROBLEM STATEMENT.

```

VOUT 16 200 1.6

```

.AC DEC 1 1 10

.PRINT AC IM(VOUT) IP(VOUT)

\* THE TRANSCONDUCTANCE CAN ALSO BE MEASURED BY ELIMINATING

\* THE VOLTAGE SOURCE CONNECTED AT THE OUTPUT AND THE

\* AC ANALYSIS ABOVE, FINDING THE VOLTAGE GAIN AND OUTPUT

\* RESISTANCE WITH A .TF STATEMENT AS SHOWN BELOW,

\* AND CALCULATING GM = (VOLTAGE GAIN)/(OUTPUT RESISTANCE)

\* THE RESULT IS GM = 1.942E6/2.065E8 = 94E-6 A/V

\* THE TRANSCONDUCTANCE IS REDUCED HERE COMPARED

\* TO THE TRANSCONDUCTANCE IN PART (A) BECAUSE

\* THE COLLECTOR CURRENT OF Q13 AND Q14 HERE FLOWS

\* IN Q10 AND DOES NOT CONTRIBUTE TO THE STAGE OUTPUT.

\* .TF V(16) V12

.END

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 27.000
MODE =VOLTAGE MODE =VOLTAGE MODE =VOLTAGE
+0:3 = 0. 0:4 =-1.444E+01 0:6 =-1.371E+01
+0:8 =-1.260E+01 0:9 =-1.260E+01 0:10 =-1.315E+01
+0:11 =-1.315E+01 0:12 =-1.405E+01 0:13 =-1.446E+01
+0:16 =-1.340E+01 0:100 = 1.500E+01 0:200 =-1.500E+01

```

## \*\*\*\* BIPOLAR JUNCTION TRANSISTORS

```

SUBCKT
ELEMENT 0:Q1 0:Q2 0:Q3 0:Q4 0:Q5
MODEL 0:NPN 0:NPN 0:PMP 0:PMP 0:NPN
IB 3.954E-08 3.954E-08 -9.729E-08 -9.765E-08 1.946E-08
IC 1.884E-06 9.884E-06 -4.865E-06 -4.864E-06 4.865E-06
VBE 5.536E-01 5.536E-01 -5.590E-01 -5.590E-01 5.533E-01
VCE 2.815E+01 2.815E+01 -9.000E-01 -2.464E-01 9.450E-01
VBC -2.760E+01 -2.760E+01 3.418E-01 -3.126E-01 -4.103E-01
VS -1.500E+01 -1.500E+01 1.371E+01 1.371E+01 1.405E+01
POWER 2.783E-04 2.783E-04 4.437E-06 1.253E-06 4.610E-06
BETA0 2.500E+02 2.500E+02 5.000E+01 4.981E+01 2.500E+02
GM 3.822E-04 3.822E-04 1.881E-04 1.881E-04 3.881E-04
RPI 6.541E+05 6.541E+05 2.658E+05 2.658E+05 1.329E+06
XX 0. 0. 0. 0. 0.
NO 5.520E+15 5.520E+15 1.709E+14 7.292E+07 8.205E+13
BETAAC 2.500E+02 2.500E+02 5.000E+01 4.999E+01 2.500E+02

```

```

SUBCKT
ELEMENT 0:Q6 0:Q7 0:Q10 0:Q11 0:Q12
MODEL 0:NPN 0:NPN 0:NPN 0:NPN 0:PMP
IB 1.946E-08 1.550E-10 4.048E-08 4.048E-08 0.
IC 4.865E-06 3.876E-08 1.012E-05 1.012E-05 0.
VBE 5.535E-01 4.103E-01 5.542E-01 5.542E-01 0.
VCE 1.600E+00 2.946E+01 1.287E+00 5.542E-01 0.
VBC -1.064E+00 -2.905E+01 -7.332E-01 0. 0.
VS 1.340E+01 -1.500E+01 1.371E+01 1.444E+01 1.500E+01
POWER 7.794E-06 1.142E-06 1.305E-05 5.631E-06 0.
BETA0 2.500E+02 2.500E+02 2.500E+02 2.500E+02 0.
GM 1.881E-04 1.499E-06 3.912E-04 3.912E-04 0.
RPI 1.329E+06 1.668E+08 6.390E+05 6.390E+05 6.466E+14
XX 0. 0. 0. 0. 0.
NO 2.129E+14 5.810E+15 1.466E+14 5.172E+12 1.293E+13
BETAAC 2.500E+02 2.500E+02 2.500E+02 2.500E+02 0.

```

```

SUBCKT
ELEMENT 0:Q13 0:Q14
MODEL 0:PMP 0:PMP
IB -9.729E-08 -9.730E-08
IC -4.865E-06 -4.865E-06
VBE -5.590E-01 -5.590E-01
VCE -5.590E-01 -5.590E-01
VBC 0. 0.
VS 1.371E+01 1.371E+01
POWER 2.774E-06 2.774E-06
BETA0 5.000E+01 5.000E+01
GM 1.881E-04 1.881E-04
RPI 2.658E+05 2.658E+05
XX 0. 0.
NO 1.293E+13 1.293E+13
BETAAC 5.000E+01 5.000E+01


```

```

***** AC ANALYSIS THOM= 27.000 TEMP= 27.000
FREQ I MAG I PHASE VOUT VOUT
1.0000E+00 9.405E-05 8.873E-23
1.0000E+01 9.405E-05 8.873E-22

```

## Problem 5 -- (10 points)

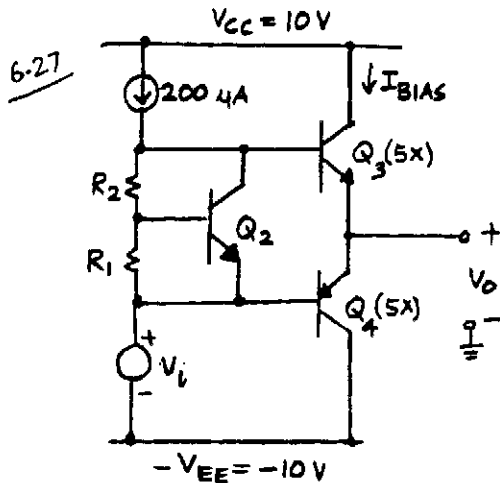

Neglect current flow through  $R_1$  and  $R_2$  from  $200 \mu\text{A}$  source.

$$\therefore I_{C2} = 200 \mu\text{A}, V_{BE2} = V_T \ln \frac{I_{C2}}{I_{S2}}$$

$$\begin{aligned} V_{BE4} + V_{BE3} &= V_{BE2} + \frac{V_{BE2}}{R_1} \times R_2 \\ &= \frac{V_T}{R_1} (R_1 + R_2) \ln \frac{I_{C2}}{I_{S2}} \\ &= V_T \ln \left( \frac{I_{C3} | I_{C4}|}{I_{S3} I_{S4}} \right) \end{aligned}$$

Areas of  $Q_3, Q_4$  are 5 times of  $Q_1$  and  $Q_2$ . Therefore,

$$I_{S1} = I_{S2} = 10^{-15} \text{ A} = I_S$$

$$I_{S3} = I_{S4} = 5 \times 10^{-15} \text{ A} = 5 I_S$$

$$V_T \ln \left( \frac{I_{BIAS}^2}{25 I_S^2} \right) = V_T \left( 1 + \frac{R_2}{R_1} \right) \ln \left( \frac{I_{C2}}{I_S} \right)$$

$$\begin{aligned} \therefore I_{BIAS} &= 5 I_S \left( \frac{I_{C2}}{I_S} \right)^{\frac{1}{2} \left( 1 + \frac{R_2}{R_1} \right)} \\ &= 5 \left( I_{C2} \right)^{\frac{1}{2} \left( 1 + \frac{R_2}{R_1} \right)} \left( I_S \right)^{\frac{1}{2} \left( 1 - \frac{R_2}{R_1} \right)} \end{aligned} \rightarrow \textcircled{1}$$

$$\frac{R_2}{R_1} = \frac{2 \ln \left( \frac{I_{BIAS}}{5 I_S} \right)}{\ln \left( \frac{I_{C2}}{I_S} \right)} - 1$$

$$I_{BIAS} = 50 \mu\text{A}, I_S = 10^{-15} \text{ A}, I_{C2} = 200 \mu\text{A}$$

$$\therefore \frac{R_2}{R_1} = 0.77$$

From  $\textcircled{1}$ , If we choose  $\frac{R_2}{R_1} = 1$

$$\begin{aligned} \text{then } I_{BIAS} &= 5 \left( I_{C2} \right)^{\frac{1}{2} \left( 1 + \frac{R_2}{R_1} \right)} \\ &= 1000 \mu\text{A} = 1 \text{ mA} \end{aligned}$$

and  $I_{BIAS}$  is independent of temperature. In general, if  $\frac{R_2}{R_1} \neq 1$  then  $I_{BIAS}$  is dependent on temperature because  $I_S$  depends on temperature.



## Problem 5 – Continued

```

741 OUTPUT-STAGE BIAS SCHEME
* CHANGE TO CHECK HAND CALCULATIONS
*****
VCC 100 0 10
VEE 200 0 -10
INKEF 100 3 200U
Q2 3 4 5 NPN
Q3 100 3 6 NPN 5
Q4 200 5 6 PNP 5
R1 4 5 100K
R2 3 4 77K
VI 5 200 9.404
.MODEL NPN NPN BF=10000 IS=1E-15
.MODEL PNP PNP BF=10000 IS=1E-15
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=40
.OP
.END

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 27.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 5.952E-01 0:4 = 7.614E-02 0:5 =-5.960E-01
+0:6 =-6.124E-04 0:100 = 1.000E+01 0:200 =-1.000E+01
**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 1.933E-04 5.000E-09 -5.000E-09
IC 1.933E-04 5.000E-05 -5.000E-05
VBE 6.721E-01 5.952E-01 -5.952E-01
VCE 1.191E+00 1.000E+01 -9.999E+00
BETA 1.000E+04 1.000E+04 1.000E+04

```

```

741 OUTPUT-STAGE BIAS SCHEME
* SET BF TO NOMINAL VALUES AND NOM TEMPERATURE SWEEP
*****
VCC 100 0 10
VEE 200 0 -10
INKEF 100 3 200U
Q2 3 4 5 NPN
Q3 100 3 6 NPN 5
Q4 200 5 6 PNP 5
R1 4 5 100K
R2 3 4 77K
VI 5 200 9.404
.MODEL NPN NPN BF=250 IS=1E-15
.MODEL PNP PNP BF=50 IS=1E-15
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OP
.TEMP -55 -35 -15 5 25 45 65 85 105 125
.END

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= -55.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 4.957E-01 0:4 = 2.135E-01 0:5 =-5.960E-01
+0:6 = 1.497E-01 0:100 = 1.000E+01 0:200 =-1.000E+01
**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.640E-07 1.301E-07 -6.403E-07
IC 1.910E-04 3.253E-05 -3.202E-05
VBE 8.095E-01 7.460E-01 -7.457E-01
VCE 1.491E+00 9.850E+00 -1.015E+01
BETA 2.500E+02 2.500E+02 5.000E+01

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= -35.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 4.375E-01 0:4 = 1.806E-01 0:5 =-5.960E-01
+0:6 = 1.206E-01 0:100 = 1.000E+01 0:200 =-1.000E+01
**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.650E-07 2.086E-07 -1.027E-06
IC 1.913E-04 5.215E-05 -5.134E-05
VBE 7.766E-01 7.169E-01 -7.166E-01
VCE 1.433E+00 9.879E+00 -1.012E+01
BETA 2.500E+02 2.500E+02 5.000E+01

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= -15.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 7.786E-01 0:4 = 1.473E-01 0:5 =-5.960E-01
+0:6 = 9.110E-02 0:100 = 1.000E+01 0:200 =-1.000E+01

```

```

**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.660E-07 3.116E-07 -1.533E-06
IC 1.915E-04 7.790E-05 -7.667E-05
VBE 7.432E-01 6.875E-01 -6.871E-01
VCE 1.374E+00 9.908E+00 -1.009E+01
BETA 2.500E+02 2.500E+02 5.000E+01

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 5.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 7.189E-01 0:4 = 1.135E-01 0:5 =-5.960E-01
+0:6 = 6.125E-02 0:100 = 1.000E+01 0:200 =-1.000E+01

```

```

**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.668E-07 4.401E-07 -2.166E-06
IC 1.917E-04 1.100E-04 -1.083E-04
VBE 7.095E-01 6.576E-01 -6.573E-01
VCE 1.314E+00 9.938E+00 -1.006E+01
BETA 2.500E+02 2.500E+02 5.000E+01

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 25.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 6.582E-01 0:4 = 7.939E-02 0:5 =-5.960E-01
+0:6 = 3.107E-02 0:100 = 1.000E+01 0:200 =-1.000E+01

```

```

**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.675E-07 5.946E-07 -2.925E-06
IC 1.919E-04 1.486E-04 -1.463E-04
VBE 6.754E-01 6.275E-01 -6.271E-01
VCE 1.254E+00 9.968E+00 -1.003E+01
BETA 2.500E+02 2.500E+02 5.000E+01

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 45.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 5.976E-01 0:4 = 4.492E-02 0:5 =-5.960E-01
+0:6 = 5.725E-04 0:100 = 1.000E+01 0:200 =-1.000E+01

```

```

**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.682E-07 7.741E-07 -3.810E-06
IC 1.920E-04 1.935E-04 -1.905E-04
VBE 6.409E-01 5.970E-01 -5.964E-01
VCE 1.193E+00 9.999E+00 -1.000E+01
BETA 2.500E+02 2.500E+02 5.000E+01

```

```

**** OPERATING POINT INFORMATION THOM= 27.000 TEMP= 65.000
NODE =VOLTAGE NODE =VOLTAGE NODE =VOLTAGE
+0:3 = 5.360E-01 0:4 = 1.012E-02 0:5 =-5.960E-01
+0:6 =-3.021E-02 0:100 = 1.000E+01 0:200 =-1.000E+01

```

```

**** BIPOLAR JUNCTION TRANSISTORS
SUBCKT
ELEMENT 0:Q2 0:Q3 0:Q4
MODEL 0:NPN 0:NPN 0:PNP
IB 7.688E-07 9.782E-07 -4.814E-06
IC 1.922E-04 2.446E-04 -2.407E-04
VBE 6.061E-01 5.662E-01 -5.658E-01
VCE 1.132E+00 1.003E+01 -9.969E+00
BETA 2.500E+02 2.500E+02 5.000E+01

```

Problem 5 – Continued

```

**** OPERATING POINT INFORMATION      THOM= 27.000 TEMP= 65.000
NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:3      = 4.739E-01 0:4      =-2.498E-02 0:5      =-5.960E-01
+0:6      =-6.127E-02 0:100     = 1.000E+01 0:200     =-1.000E+01
    
```

```

**** BIPOLAR JUNCTION TRANSISTORS
SUBCIRY
ELEMENT 0:Q2      0:Q3      0:Q4
MODEL   0:NPN     0:NPN     0:PNP
IB      7.693E-07 1.205E-06 -5.933E-06
IC      1.923E-04 3.014E-04 -2.966E-04
VBE     5.710E-01 5.352E-01 -5.347E-01
VCE     1.069E+00 1.006E+01 -9.938E+00
BTAD    2.500E+02 2.500E+02 5.000E+01
    
```

```

**** OPERATING POINT INFORMATION      THOM= 27.000 TEMP= 105.000
NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:3      = 4.113E-01 0:4      =-6.037E-02 0:5      =-5.960E-01
+0:6      =-9.259E-02 0:100     = 1.000E+01 0:200     =-1.000E+01
    
```

```


**** BIPOLAR JUNCTION TRANSISTORS
SUBCIRY
ELEMENT 0:Q2      0:Q3      0:Q4
MODEL   0:NPN     0:NPN     0:PNP
IB      7.697E-07 1.454E-06 -7.158E-06
IC      1.924E-04 3.636E-04 -3.579E-04
VBE     5.356E-01 5.039E-01 -5.034E-01
VCE     1.007E+00 1.009E+01 -9.907E+00
BTAD    2.500E+02 2.500E+02 5.000E+01
    
```

```

**** OPERATING POINT INFORMATION      THOM= 27.000 TEMP= 125.000
NODE      =VOLTAGE      NODE      =VOLTAGE      NODE      =VOLTAGE
+0:3      = 3.482E-01 0:4      =-9.604E-02 0:5      =-5.960E-01
+0:6      =-1.242E-01 0:100     = 1.000E+01 0:200     =-1.000E+01
    
```

```

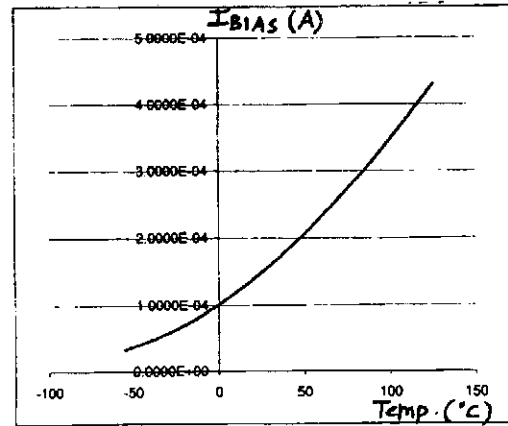**** BIPOLAR JUNCTION TRANSISTORS
SUBCIRY
ELEMENT 0:Q2      0:Q3      0:Q4
MODEL   0:NPN     0:NPN     0:PNP
IB      7.699E-07 1.723E-05 -8.480E-06
IC      1.925E-04 4.308E-04 -4.240E-04
VBE     5.000E-01 4.724E-01 -4.718E-01
VCE     9.442E-01 1.012E+01 -9.875E+00
BTAD    2.500E+02 2.500E+02 5.000E+01
    
```



TEMP (DEG C)	IC3 = IBIAS (A)	TEMP	IC3 = IBIAS (A)
-55	3.253E-05	45	1.935E-04
-35	5.215E-05	65	2.445E-04
-15	7.790E-05	85	3.014E-04
5	1.100E-04	105	3.636E-04
25	1.486E-04	125	4.308E-04