

Homework Assignment No. 12 - Solutions

Problem 1 - (10 points) - Problem 7.3-7 of Allen and Holberg, 2nd edition

(a.) If all transistors in Fig. 7.3-12 have a dc current of $50\mu\text{A}$ and a W/L of $10\mu\text{m}/1\mu\text{m}$, find the gain of the common mode feedback loop. (b.) If the output of this amplifier is cascoded, then repeat part (a.).

Solution

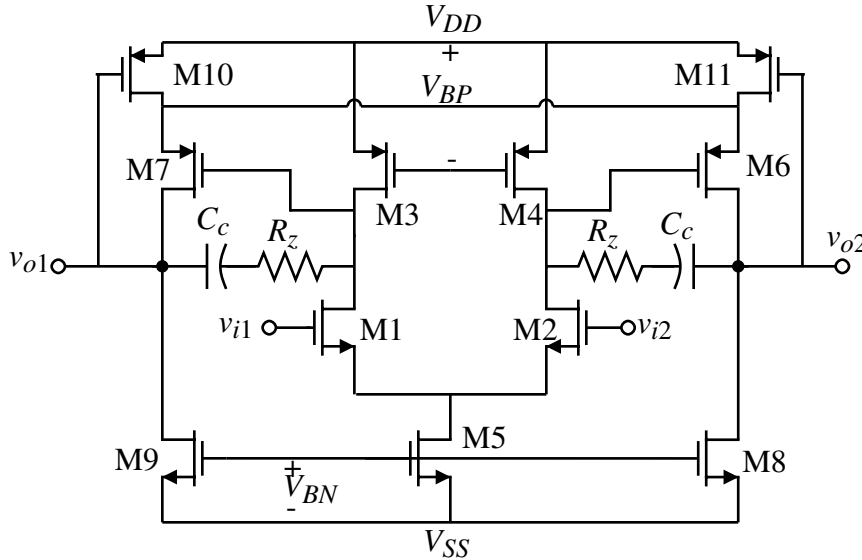


Figure 7.3-12 Two-stage, Miller, differential-in, differential-out op amp with common-mode stabilization.

The loop gain of the common-mode feedback loop is,

$$\text{CMFB Loop gain} \approx -\frac{g_{m10}}{g_{ds9}} = -g_{m10}r_{ds9} \quad \text{or} \quad -\frac{g_{m11}}{g_{ds8}} = -g_{m11}r_{ds8}$$

$$\text{With } I_D = 50\mu\text{A} \text{ and } W/L = 10\mu\text{m}/1\mu\text{m}, g_{m10} = \sqrt{\frac{2K_P'WI_D}{L}} = \sqrt{2 \cdot 50 \cdot 10 \cdot 50}$$

$$= 223.6\mu\text{S},$$

$$r_{dsN} = \frac{1}{\lambda_N I_D} = \frac{25}{50\mu\text{A}} = 0.5\text{M}\Omega \quad \text{and} \quad r_{dsP} = \frac{1}{\lambda_P I_D} = \frac{20}{50\mu\text{A}} = 0.4\text{M}\Omega$$

$$\therefore \boxed{\text{CMFB Loop gain} \approx -g_{m10}r_{ds9} = -223.6(0.5) = -111.8\text{V/V}}$$

If the output is cascoded, the gain becomes,

$$\text{CMFB Loop gain with cascoding} \approx -\frac{g_{m10}}{g_{ds9}} g_m(\text{cascode})r_{ds}(\text{cascode})$$

$$= -g_{m10}\{[r_{ds9} g_m(\text{cascode})r_{ds}(\text{cascode})] \parallel [g_{m7}r_{ds7} (r_{ds10} \parallel r_{ds10})]\}$$

$$g_{mP} = \sqrt{\frac{2K_N'WI_D}{L}} = \sqrt{2 \cdot 110 \cdot 10 \cdot 50} = 331.67\mu\text{S}$$

$$= -(223.6)[(0.5 \cdot 331.67 \cdot 0.5) \parallel (223.6)(0.4)(0.2)] = 223.6(14.7) = -3,290 \text{ V/V}$$

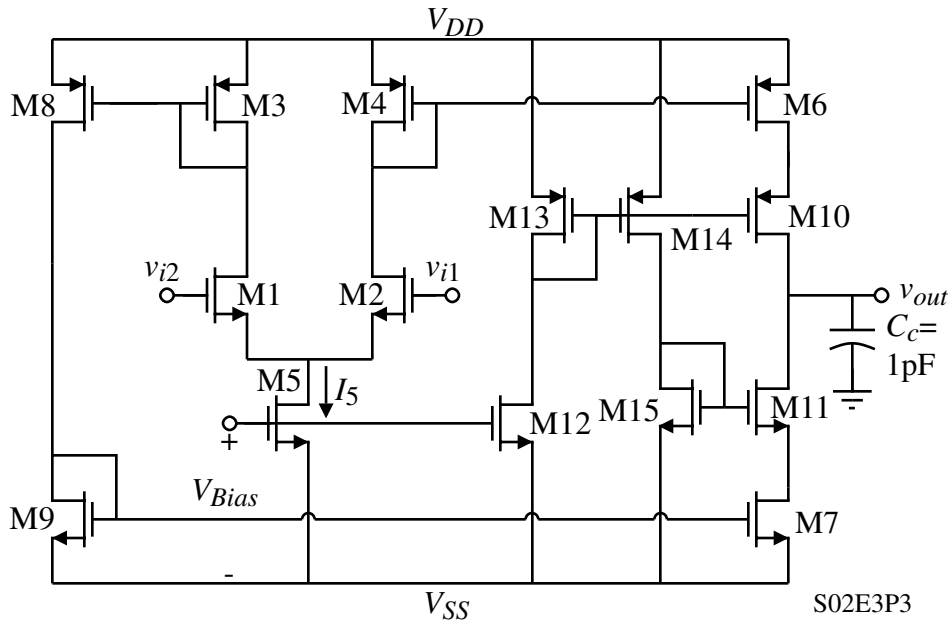
$$\therefore \boxed{\text{CMFB Loop gain with cascoding} \approx -3.290\text{V/V}}$$

Problem 2 – (10 points)

Calculate the small-signal voltage gain, the SR ($C_L = 1\text{pF}$), and the P_{diss} for the op amp shown where $I_5 = 100\text{nA}$ and all transistors M1-M11 have a W/L of $10\mu\text{m}/1\mu\text{m}$ and $V_{DD} = -V_{SS} = 1.5\text{V}$. If the minimum voltage across the drain-source of M6 and M7 are to be 0.1V , design the W/L ratios of M12-M15 that give the maximum plus and minus output voltage swing assuming that transistors M12 and M15 have a current of 50nA . The transistors are working in weak inversion and are modeled by the large signal model of

$$i_D = \frac{W}{L} I_{D0} \exp\left(\frac{v_{GS}}{nV_t}\right)$$

where $I_{D0} = 2\text{nA}$ for PMOS and NMOS and $n_P = 2.5$ and $n_N = 1.5$. Assume $V_t = 26\text{mV}$ and $\lambda_N = 0.4\text{V}^{-1}$ and $\lambda_P = 0.5\text{V}^{-1}$.

**Solution**

The small-signal voltage gain, A_v , is $g_{m1}R_{out}$ (see end of solution) where,

$$R_{out} = (r_{ds6}g_{m10}r_{ds10}) \parallel (r_{ds7}g_{m11}r_{ds11})$$

With the currents and W/L ratios of transistors M1 through M11 known, we get

$$g_{m1} = g_{m11} = \frac{50\text{nA}}{1.5 \cdot 26\text{mV}} = 1.282\mu\text{S} \quad \text{and} \quad r_{ds7} = r_{ds11} = \frac{10^9}{0.04 \cdot 50} = 0.5 \times 10^9 \Omega$$

$$g_{m10} = \frac{50\text{nA}}{2.5 \cdot 26\text{mV}} = 0.769\mu\text{S} \quad \text{and} \quad r_{ds6} = r_{ds10} = \frac{10^9}{0.05 \cdot 50} = 0.4 \times 10^9 \Omega$$

$$R_{out} = (0.4 \times 10^9 \cdot 1.282 \times 10^{-6} \cdot 0.4 \times 10^9) \parallel (0.5 \times 10^9 \cdot 0.769 \times 10^{-6} \cdot 0.5 \times 10^9) = 9.924 \times 10^{10} \Omega$$

$$\therefore A_v = 1.282 \times 10^{-6} \cdot 9.924 \times 10^{10} = \underline{\underline{127,726 \text{ V/V}}}$$

$$SR = \frac{100\text{nA}}{1\text{pF}} = \underline{\underline{0.1\text{V}/\mu\text{s}}}$$

$$P_{diss} = 3\text{V}(50\text{nA} \cdot 6) = \underline{\underline{0.9\mu\text{W}}}$$

Problem 2 - Continued

Design of the W/L 's of M12 through M15:

To get 50nA in M12 means the $W_{12}/L_{12} = 0.5(W_5/L_5) = \underline{5\mu\text{m}/1\mu\text{m}}$

M15:

$$V_{GS11} = n_N V_t \ln\left(\frac{I_D}{I_{DO}(W/L)}\right) = 1.5 \cdot 0.026 \ln\left(\frac{50}{2 \cdot 10}\right) = 0.0357\text{V}$$

$$\therefore V_{GS15} = 0.1 + 0.0357 = 0.1357\text{V} \rightarrow \frac{W_{15}}{L_{15}} = \frac{50\text{nA}}{2\text{nA} \cdot \exp\left(\frac{135.7}{1.5 \cdot 26}\right)} = \underline{0.77\mu\text{m}/1\mu\text{m}}$$

M13 and M14:

$$V_{SG10} = n_P V_t \ln\left(\frac{I_D}{I_{DO}(W/L)}\right) = 2.5 \cdot 0.026 \ln\left(\frac{50}{2 \cdot 10}\right) = 0.0596\text{V}$$

$$\therefore V_{GS13} = 0.1 + 0.0596 = 0.1596\text{V} \rightarrow \frac{W_{13}}{L_{13}} = \frac{50\text{nA}}{2\text{nA} \cdot \exp\left(\frac{159.6}{1.5 \cdot 26}\right)} =$$

2.146 $\mu\text{m}/1\mu\text{m}$

Thus

$$\frac{W_{13}}{L_{13}} = \frac{W_{14}}{L_{14}} = \underline{2.146\mu\text{m}/1\mu\text{m}}$$

Comments on the small-signal gain:

It is much easier to use the expression $g_{m1}R_{out}$ for the small-signal voltage gain. However, some prefer the following expression,

$$v_{out} = \left(\frac{g_{m1} \cdot g_{m8} \cdot g_{m7}}{2g_{m3} \cdot g_{m9}} + \frac{g_{m2} \cdot g_{m6}}{2g_{m4}} \right) R_{out}$$

which is equivalent since $g_{m3}=g_{m8}$, $g_{m7}=g_{m9}$, $g_{m4}=g_{m6}$, and $g_{m1}=g_{m2}$.

Problem 3 – (10 points) - Problem 7.4-3 of Allen and Holberg, 2nd edition

Derive Eq. (17). If $A = 2$, at what value of v_{in}/nV_t will $i_{out} = 5I_5$ or $5I_b$ if $b=1$?

Solution

Start with the following relationships:

$$i_1 + i_2 = I_5 + A(i_2 - i_1) \quad \text{Eq. (15)}$$

and $\frac{i_2}{i_1} = \exp\left(\frac{v_{in}}{nV_t}\right)$ Eq. (16)

Defining $i_{out} = b(i_2 - i_1)$ solve for i_2 and I_1 .

$$i_1 + i_1 \exp\left(\frac{v_{in}}{nV_t}\right) = I_5 + Ai_1 \exp\left(\frac{v_{in}}{nV_t}\right) - Ai_1$$

or $i_1[(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)] = I_5 \quad \rightarrow \quad i_1 = \frac{I_5}{(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)}$

Similarly for i_2 ,

$$i_2 = \frac{I_5 \exp\left(\frac{v_{in}}{nV_t}\right)}{(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)}$$

$$\therefore i_{out} = b(i_2 - I_1) = i_{out} = (i_2 - I_1) = \frac{I_5 \left(\exp\left(\frac{v_{in}}{nV_t}\right) - 1 \right)}{(1+A) + (1-A) \exp\left(\frac{v_{in}}{nV_t}\right)} \quad \text{Eq. (17)}$$


Setting $i_{out} = 5I_5$ and solving for $\frac{v_{in}}{nV_t}$ gives,

$$5[3 - \exp\left(\frac{v_{in}}{nV_t}\right)] = \exp\left(\frac{v_{in}}{nV_t}\right) - 1 \quad \rightarrow \quad 16 = 6 \exp\left(\frac{v_{in}}{nV_t}\right) \quad \rightarrow \quad \exp\left(\frac{v_{in}}{nV_t}\right) = 2.667$$

$$\therefore \frac{v_{in}}{nV_t} = \ln(2.667) = \underline{\underline{0.9808}}$$

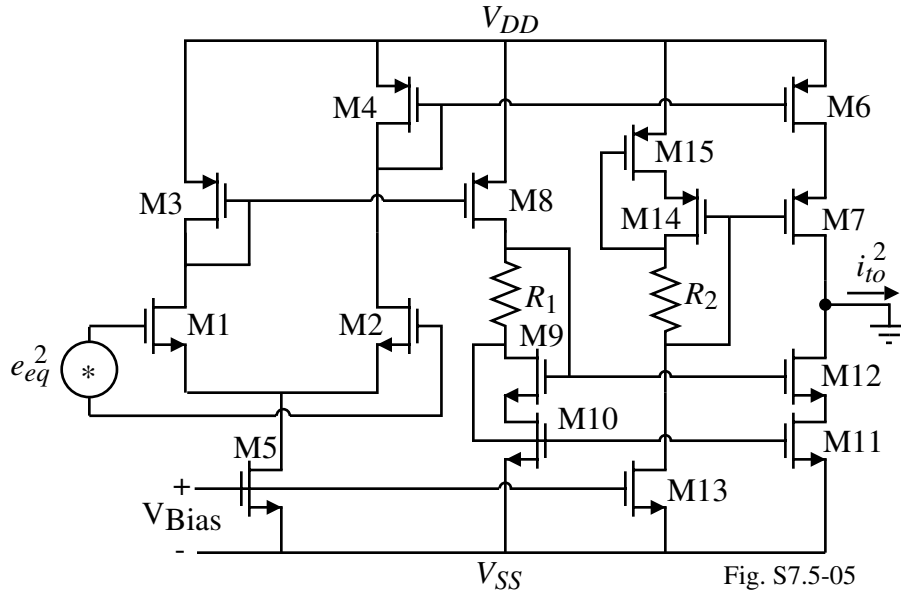Problem 4 - (10 points) - Problem 7.5-5 of Allen and Holberg, 2nd edition

Find the equivalent rms noise voltage of the op amp designed in Example 6.5-2 over a bandwidth of 1Hz to 100kHz. Use the values for KF of Example 7.5-1.



Solution

The circuit for this amplifier is shown.

The W/L ratios in microns are:

$$\begin{aligned}
 S_1 &= S_2 = 12/1 \\
 S_3 &= S_4 = 16/1 \\
 S_5 &= 7/1 \\
 S_5 &= 8.75/1 \\
 S_6 &= S_7 = S_8 = S_{14} = S_{15} = 40/1 \\
 S_9 &= S_{10} = S_{11} = S_{12} = 18.2/1
 \end{aligned}$$

Find the short circuit noise current at the output, i_{to}^2 , due to each noise-contributing transistor in the circuit (we will not include M7, M9, M12 and M14 because they are cascodes and their effective g_m is small. The result is,

$$i_{to}^2 = 2g_{m1}^2 e_{n1}^2 \left(\frac{g_{m8}^2}{g_{m3}^2} \right) + 2g_{m8}^2 e_{n3}^2 + 2g_{m8}^2 e_{n8}^2 + 2g_{m11}^2 e_{n10}^2$$

where we have assumed that $g_{m1}=g_{m2}$, $g_{m3}=g_{m4}$, $g_{m6}=g_{m8}$, and $g_{m10}=g_{m11}$ and $e_{n1}=e_{n2}$, $e_{n3}=e_{n4}$, $e_{n6}=e_{n8}$, and $e_{n10}=e_{n11}$. Dividing i_{to}^2 by the transconductance gain gives

$$e_{eq}^2 = \frac{i_{to}^2}{g_{m1}^2 g_{m8}^2 / g_{m3}^2} = 2e_{n1}^2 + 2 \left(\frac{g_{m3}^2}{g_{m1}^2} \right) e_{n3}^2 + 2 \left(\frac{g_{m3}^2}{g_{m1}^2} \right) e_{n8}^2 + 2 \left(\frac{g_{m3}^2 g_{m11}^2}{g_{m1}^2 g_{m8}^2} \right) e_{n10}^2$$

The values of the various parameters are:

$$g_{m1} = 251\mu S, g_{m3} = 282.5\mu S, g_{m8} = 707\mu S, \text{ and } g_{m11} = 707\mu S.$$

Problem 4 - Problem 7.5-05 of Allen and Holberg, 2nd edition – Continued

$$\therefore e_{eq}^2 = 2e_{n1}^2 \left[1 + 1.266 \left(\frac{e_{n3}^2}{e_{n1}^2} + \frac{e_{n8}^2}{e_{n1}^2} + \frac{e_{n10}^2}{e_{n1}^2} \right) \right]$$

1/f Noise:

Using the results of Ex. 7.5-1 we get $B_N = 7.36 \times 10^{-22} (\text{V}\cdot\text{m})^2$ and $B_P = 2.02 \times 10^{-22} (\text{V}\cdot\text{m})^2$

$$e_{n1}^2 = \frac{B_N}{fW_1L_1} = \frac{7.36 \times 10^{-22}}{f \cdot 12 \times 10^{-12}} = \frac{6.133 \times 10^{-11}}{f} \text{ V}^2/\text{Hz}$$

$$\frac{e_{n3}^2}{e_{n1}^2} = \frac{B_P \cdot f \cdot W_1L_1}{B_N \cdot f \cdot W_3L_3} = \frac{B_P \cdot W_1L_1}{B_N \cdot W_3L_3} = \frac{2.02 \cdot 12}{7.36 \cdot 16} = 0.2058$$

$$\frac{e_{n8}^2}{e_{n1}^2} = \frac{B_P \cdot f \cdot W_1L_1}{B_N \cdot f \cdot W_8L_3} = \frac{B_P \cdot W_1L_1}{B_N \cdot W_3L_3} = \frac{2.02 \cdot 12}{7.36 \cdot 40} = 0.0823$$

$$\frac{e_{n10}^2}{e_{n1}^2} = \frac{B_N \cdot f \cdot W_1L_1}{B_N \cdot f \cdot W_{10}L_{10}} = \frac{B_P \cdot W_1L_1}{B_N \cdot W_3L_3} = \frac{12}{18.2} = 0.6593$$

$$e_{eq}^2 = 2 \frac{6.133 \times 10^{-11}}{f} [1 + 1.266(0.2058 + 0.0823 + 0.6593)] = 2 \frac{6.133 \times 10^{-11}}{f} \cdot 2.1995$$

$$e_{eq}^2 = \frac{2.1995 \times 10^{-10}}{f} \text{ V}^2/\text{Hz}$$

Thermal noise:

$$e_{n1}^2 = \frac{8kT}{3g_{m1}} = \frac{8 \cdot 1.38 \times 10^{-23} \cdot 300}{3 \cdot 251 \times 10^{-6}} = 4.398 \times 10^{-17} \text{ V}^2/\text{Hz}$$

$$\frac{e_{n3}^2}{e_{n1}^2} = \frac{g_{m1}}{g_{m3}} = \frac{251}{282.4} = 0.8888 \quad \text{and} \quad \frac{e_{n8}^2}{e_{n1}^2} = \frac{e_{n10}^2}{e_{n1}^2} = \frac{g_{m1}}{g_{m8}} = \frac{251}{707} = 0.355$$

The corner frequency is $f_c = 2.698 \times 10^{-10} / 2.66 \times 10^{-16} = 1.01 \times 10^6$ Hz. Therefore in a 1Hz to 100kHz band, the noise is 1/f. Solving for the *rms* value gives,


$$V_{eq}^2(\text{rms}) = \int_1^{100,000} \frac{2.698 \times 10^{-10}}{f} df = 2.698 \times 10^{-10} [\ln(100,000) - \ln(1)] = 3.1062 \times 10^{-9} \text{ V}^2(\text{rms})$$

$$V_{eq}(\text{rms}) = \underline{\underline{55.73 \mu\text{V}(\text{rms})}}$$

Problem 5 - (10 points)

A CMOS op amp capable of operating from 1.5V power supply is shown. All device lengths are 1 μ m and are to operate in the saturation region. Design all of the W values of every transistor of this op amp to meet the following specifications.

Slew rate = $\pm 10\text{V}/\mu\text{s}$	$V_{\text{out(max)}} = 1.25\text{V}$	$V_{\text{out(min)}} = 0.75\text{V}$
$V_{\text{ic(min)}} = 1\text{V}$	$V_{\text{ic(max)}} = 2\text{V}$	$\text{GB} = 10\text{MHz}$
Phase margin = 60° when the output pole = 2GB and the RHP zero = 10GB. Keep the mirror pole $\geq 10\text{GB}$ ($C_{\text{ox}} = 0.5\text{fF}/\mu\text{m}^2$).		

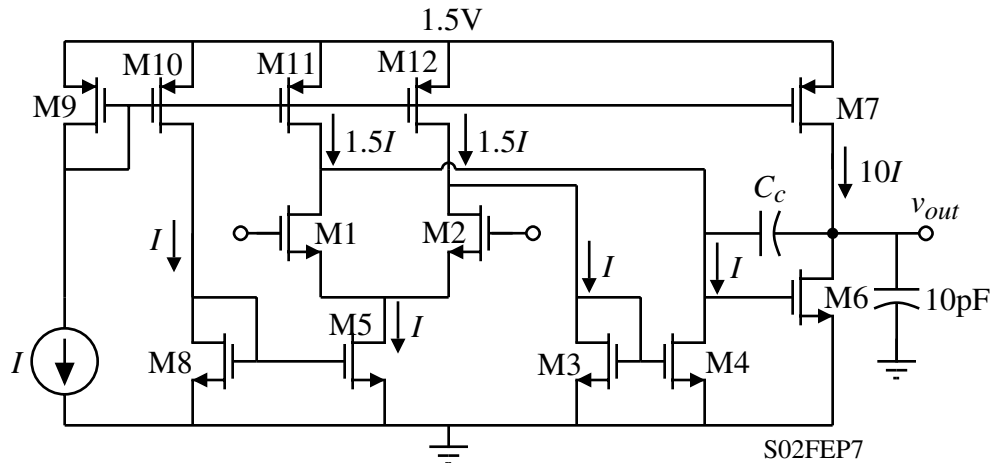

Your design should meet or exceed these specifications. Ignore bulk effects in this problem and summarize your W values to the nearest micron, the value of C_c (pF), and I (μA) in the following table. Use the following model parameters: $K_N' = 24\mu\text{A}/\text{V}^2$, $K_P' = 8\mu\text{A}/\text{V}^2$, $V_{TN} = -V_{TP} = 0.75\text{V}$, $\lambda_N = 0.01\text{V}^{-1}$ and $\lambda_P = 0.02\text{V}^{-1}$.

Solution

$$1.) p_2 = 2\text{GB} \Rightarrow g_{m6}/C_L = 2g_{m1}/C_c \text{ and } z = 10\text{GB} \Rightarrow g_{m6} = 10g_{m1}. \therefore \boxed{C_c = C_L/5 = 2\text{pF}}$$

$$2.) I = C_c \cdot \text{SR} = (2 \times 10^{-12}) \cdot 10^7 = 20\mu\text{A} \quad \therefore \boxed{I = 20\mu\text{A}}$$

$$3.) \text{GB} = g_{m1}/C_c \Rightarrow g_{m1} = 20\pi \times 10^6 \cdot 2 \times 10^{-12} = 40\pi \times 10^{-6} = 125.67\mu\text{S}$$

$$\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{g_{m1}^2}{2K_N(I/2)} = \frac{(125.67 \times 10^{-6})^2}{2 \cdot 24 \times 10^{-6} \cdot 10 \times 10^{-6}} = 32.9 \Rightarrow \boxed{W_1 = W_2 = 33\mu\text{m}}$$

$$4.) V_{\text{ic(min)}} = V_{\text{DS5(sat)}} + V_{\text{GS1}}(10\mu\text{A}) = 1\text{V} \rightarrow V_{\text{DS5(sat)}} = 1 - \sqrt{\frac{2 \cdot 10}{24 \cdot 33}} - 0.75 = 0.0908$$

$$V_{\text{DS5(sat)}} = 0.0908 = \sqrt{\frac{2 \cdot I}{K_N S_5}} \rightarrow W_5 = \frac{2 \cdot 20}{24 \cdot (0.0908)^2} = 201.9\mu\text{m} \quad \boxed{W_5 = 202\mu\text{m}}$$

$$5.) V_{\text{ic(max)}} = V_{\text{DD}} - V_{\text{SD11(sat)}} + V_{\text{TN}} = 1.5 - V_{\text{SD11(sat)}} + 0.75 = 2\text{V} \rightarrow V_{\text{SD11(sat)}} = 0.25\text{V}$$

$$V_{\text{SD11(sat)}} \leq \sqrt{\frac{2 \cdot 1.5I}{K_P \cdot S_{11}}} \rightarrow S_{11} = W_{11} \geq \frac{2 \cdot 30}{(0.25)^2 \cdot 8} = 120 \rightarrow \underline{\underline{W_{11} = W_{12} \geq 120\mu\text{m}}}$$

Problem 5 - Continued

6.) Choose $S_3(S_4)$ by satisfying $V_{ic}(\max)$ specification then check mirror pole.

$$V_{ic}(\max) \geq V_{GS3}(20\mu A) + V_{TN} \rightarrow V_{GS3}(20\mu A) = 1.25V \geq \sqrt{\frac{2 \cdot I}{K_N \cdot S_3}} + 0.75V$$

$$S_3 = S_4 = \frac{2 \cdot 20}{(0.5)^2 \cdot 24} = 6.67 \Rightarrow \boxed{W_3 = W_4 = 7\mu m}$$

7.) Check mirror pole ($p_3 = g_{m3}/C_{Mirror}$).

$$p_3 = \frac{g_{m3}}{C_{Mirror}} = \frac{g_{m3}}{2 \cdot 0.667 \cdot W_3 \cdot L_3 \cdot C_{ox}} = \frac{\sqrt{2 \cdot 24 \cdot 6.67 \cdot 20 \times 10^{-6}}}{2 \cdot 0.667 \cdot 6.67 \cdot 0.5 \times 10^{-15}} = 17.98 \times 10^9$$

which is much greater than 10GB (0.0628×10^9). Therefore, W_3 and W_4 are OK.

8.) $g_{m6} = 10g_{m1} = 1256.7\mu S$

$$a.) g_{m6} = \sqrt{2K_N S_6 I_6} \Rightarrow W_6 = 164.5\mu m$$

$$b.) V_{out}(\min) = 0.5 \Rightarrow V_{DS6}(\text{sat}) = 0.5 = \sqrt{\frac{2 \cdot I_6}{K_N S_6}} \Rightarrow W_6 = 66.67\mu m$$

Therefore, use $\boxed{W_6 = 165\mu m}$

Note: For proper mirroring, $S_4 = \frac{I_4}{I_6} S_6 = 8.25\mu m$ which is close enough to $7\mu m$.

9.) Use the $V_{out}(\max)$ specification to design W_7 .

$$V_{out}(\max) = 0.25V \geq V_{DS7}(\text{sat}) = \sqrt{\frac{2 \cdot 200\mu A}{8 \times 10^{-6} \cdot S_7}}$$

$$\therefore S_7 \geq \frac{400\mu A}{8 \times 10^{-6} (0.25)^2} \Rightarrow \boxed{W_7 = 800\mu m}$$

10.) Now to achieve the proper currents from the current source I gives,

$$S_9 = S_{10} = \frac{S_7}{10} = 80 \rightarrow \boxed{W_9 = W_{10} = 80\mu m}$$

and

$S_{11} = S_{12} = \frac{1.5 \cdot S_7}{10} = 120 \rightarrow W_{11} = W_{12} = 120\mu m$. We saw in step 5 that W_{11} and W_{12} had to be greater than $120\mu m$ to satisfy $V_{ic}(\max)$. $\therefore \boxed{W_{11} = W_{12} = 120\mu m}$

11.) $P_{diss} = 15I \cdot 1.5V = 300\mu A \cdot 1.5V = 450\mu W$

C_c	I	$W_1=W_2$	$W_3=W_4$	$W_5=W_8$	W_6	W_7	$W_9=W_{10}$	$W_{11}=W_{12}$	P_{diss}
2pF	20 μ A	33 μ m	7 μ m	202 μ m	165 μ m	800 μ m	80 μ m	120 μ m	450 μ W