



## Output Voltage Swing of the Follower - Continued

The previous results do not include the bulk effect on  $V_{T1}$  of  $V_{GS1}$ .

Therefore,

$$V_{T1} = V_{T01} + \gamma \sqrt{2|\phi_F| - v_{BS}} - \sqrt{2|\phi_F|} \approx V_{T01} + \gamma \sqrt{v_{SB}} = V_{T01} + \gamma_1 \sqrt{v_{OUT(\max)} - V_{SS}}$$

$$\therefore v_{OUT(\max)} - V_{SS} \approx V_{DD} - V_{SS} - V_{ON1} - V_{T1} = V_{DD} - V_{SS} - V_{T01} - \gamma_1 \sqrt{v_{OUT(\max)} - V_{SS}}$$

Define  $v_{OUT(\max)} - V_{SS} = v_{OUT(\max)}$

which gives the quadratic,

$$v_{OUT(\max)} + \gamma_1 \sqrt{v_{OUT(\max)}} - (V_{DD} - V_{SS} - V_{ON1} - V_{T01}) = 0$$

Solving the quadratic gives,

$$v_{OUT(\max)} \approx \frac{\gamma_1^2}{4} - \frac{\gamma_1}{2} \sqrt{\gamma_1^2 + 4(V_{DD} - V_{SS} - V_{ON1} - V_{T01})} + \frac{\gamma_1^2 + 4(V_{DD} - V_{SS} - V_{ON1} - V_{T01})}{4}$$

If  $V_{DD} = 2.5\text{V}$ ,  $\gamma_N = 0.4\text{V}^{1/2}$ ,  $V_{TN1} = 0.7\text{V}$ , and  $V_{ON1} = 0.2\text{V}$ , then  $v_{OUT(\max)} = 3.661\text{V}$  and

$$v_{OUT(\max)} = 3.661 - 2.5 = 0.8661\text{V}$$

## Maximum Sourcing and Sinking Currents for the Source Follower

Maximum Sourcing Current (into a short circuit):

We assume that the transistors are in saturation and  $V_{DD} = -V_{SS} = 2.5\text{V}$ , thus

$$I_{OUT(\text{sourcing})} = \frac{K'_1 W_1}{2L_1} [V_{DD} - v_{OUT} - V_{T1}]^2 - I_Q$$

where  $v_{IN}$  is assumed to be equal to  $V_{DD}$ .

If  $W_1/L_1 = 10$  and if  $v_{OUT} = 0\text{V}$ , then

$$V_{T1} = 1.08\text{V} \Rightarrow I_{OUT} \text{ equal to } 1.11 \text{ mA.}$$

However, as  $v_{OUT}$  increases above  $0\text{V}$ , the current rapidly decreases.

Maximum Sinking Current:

For the current sink load, the sinking current is whatever the sink is biased to provide.

$$I_{OUT(\text{sinking})} = I_Q$$

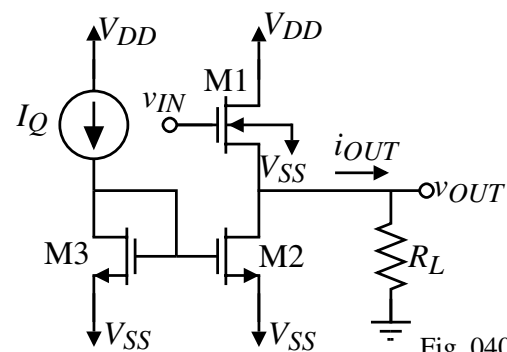


Fig. 040-01

### Efficiency of the Source Follower

Assume that the source follower can swing to power supply:

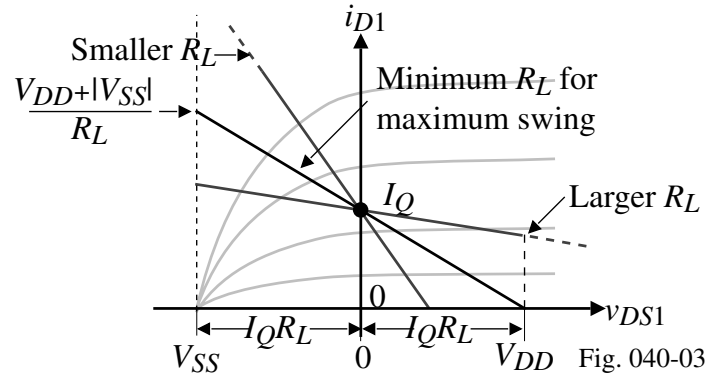


Fig. 040-03

$$\text{Efficiency} = \frac{P_{RL}}{P_{Supply}} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{DD} - V_{SS})I_Q} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{DD} - V_{SS})\left(\frac{V_{DD} - V_{SS}}{2R_L}\right)} = \left(\frac{v_{OUT(\text{peak})}}{V_{DD} - V_{SS}}\right)^2$$

Maximum efficiency occurs when  $v_{OUT(\text{peak})} = V_{DD} = |V_{SS}|$  which gives 25%.

Comments:

- Maximum efficiency occurs for the minimum value of  $R_L$  which gives maximum swing.
- Other values of  $R_L$  result in less efficiency (and smaller signal swings before clipping)
- We have ignored the fact that the dynamic  $Q$  point cannot travel along the full length of the load line because of minimum and maximum voltage limits.

### Small Signal Performance of the Source Follower

Small-signal model:

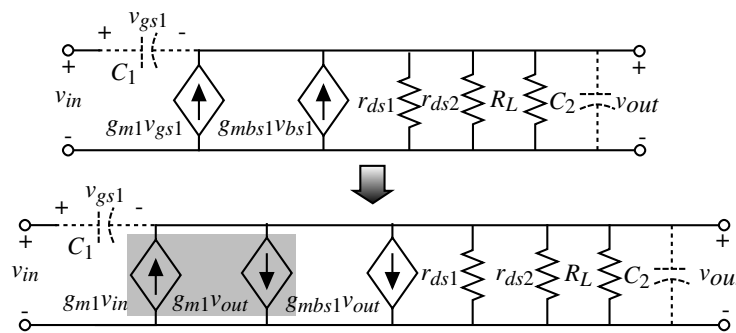


Fig. 040-04

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{ds1} + g_{ds2} + g_{m1} + g_{mbs1} + G_L} \cong \frac{g_{m1}}{g_{m1} + g_{mbs1} + G_L} \cong \frac{g_{m1}R_L}{1 + g_{m1}R_L}$$

If  $V_{DD} = -V_{SS} = 2.5V$ ,  $V_{out} = 0V$ ,  $W_1/L_1 = 10\mu\text{m}/1\mu\text{m}$ ,  $W_2/L_2 = 1\mu\text{m}/1\mu\text{m}$ , and  $I_D = 500\mu\text{A}$ , then

For the current sink load follower ( $R_L = \infty$ ):

$$\frac{V_{out}}{V_{in}} = 0.869V/V, \text{ if the bulk effect were ignored, then } \frac{V_{out}}{V_{in}} = 0.963V/V$$

For a finite load,  $R_L = 1000\Omega$ :

$$\frac{V_{out}}{V_{in}} = 0.512V/V$$

## Small Signal Performance of the Source Follower - Continued

The output resistance is:

$$R_{out} = \frac{1}{g_{m1} + g_{mbs1} + g_{ds1} + g_{ds2} + G_L}$$

For the current sink load follower:

$$R_{out} = 830\Omega$$

The frequency response of the source follower:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(g_{m1} + sC_1)}{g_{ds1} + g_{ds2} + g_{m1} + g_{mbs1} + G_L + s(C_1 + C_2)}$$

where

$C_1$  = capacitances connected between the input and output  $\approx C_{GS1}$

$C_2 = C_{bs1} + C_{bd2} + C_{gd2}$  (or  $C_{gs2}$ ) +  $C_L$

$$z = -\frac{g_{m1}}{C_1} \quad \text{and} \quad p \approx -\frac{g_{m1} + G_L}{C_1 + C_2}$$

The presence of a LHP zero leads to the possibility that in most cases the pole and zero will provide some degree of cancellation leading to a broadband response.

## EMITTER FOLLOWER

### Voltage Transfer Characteristic

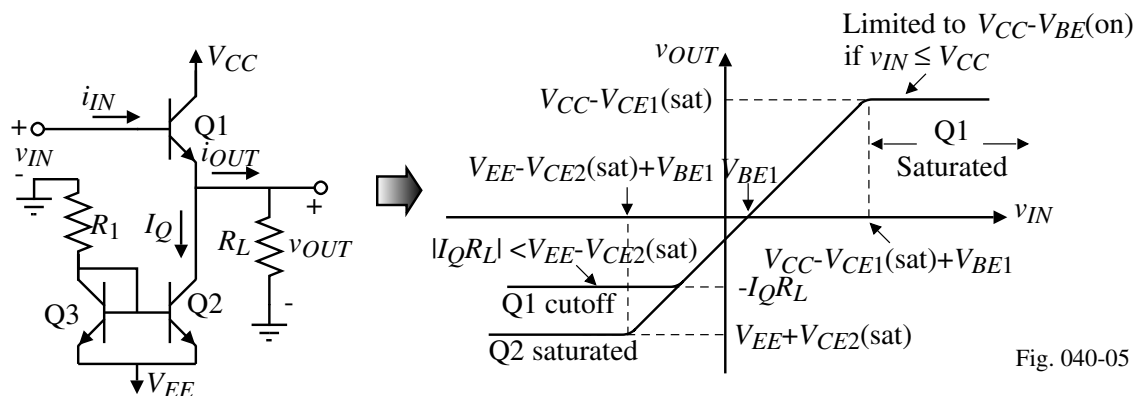


Fig. 040-05

Maximum signal swings:


- $v_{OUT(max)} = V_{CC} - V_{CE1(sat)}$  or  $V_{CC} - V_{BE1}$  if  $v_{IN(max)} \leq V_{CC}$

(The circuit driving the emitter follower must provide a current of  $\frac{V_{CC} - V_{CE1(sat)}}{\beta_F R_L}$  )

- $v_{OUT(min)} = V_{EE} - V_{CE2(sat)}$  or  $v_{OUT(min)} = -I_Q R_L$  (if  $|I_Q R_L| < V_{EE} - V_{CE2(sat)}$ )
- $i_{OUT(source)} = \beta_F i_{IN}$
- $i_{OUT(sink)} = I_Q$
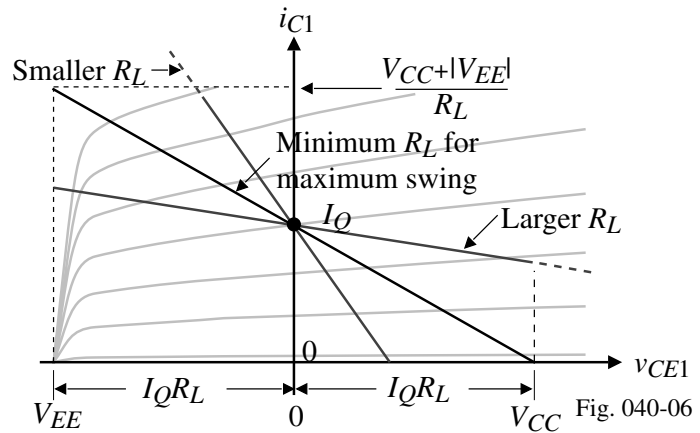
## Efficiency of the Emitter Follower

Assume that the emitter follower can swing to power supply:



$$\text{Efficiency} = \frac{P_{RL}}{P_{Supply}} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{CC} - V_{EE})I_Q} = \frac{\frac{v_{OUT(\text{peak})}^2}{2R_L}}{(V_{CC} - V_{EE})\left(\frac{(V_{CC} - V_{EE})}{2R_L}\right)} = \left(\frac{v_{OUT(\text{peak})}}{V_{CC} - V_{EE}}\right)^2$$


Maximum efficiency occurs when  $v_{OUT(\text{peak})} = V_{CC} = |V_{EE}|$  which gives 25%.

Comments:

- Maximum efficiency occurs for the minimum value of  $R_L$  which gives maximum swing.
- Other values of  $R_L$  will result in less efficiency (smaller signal swings before clipping)
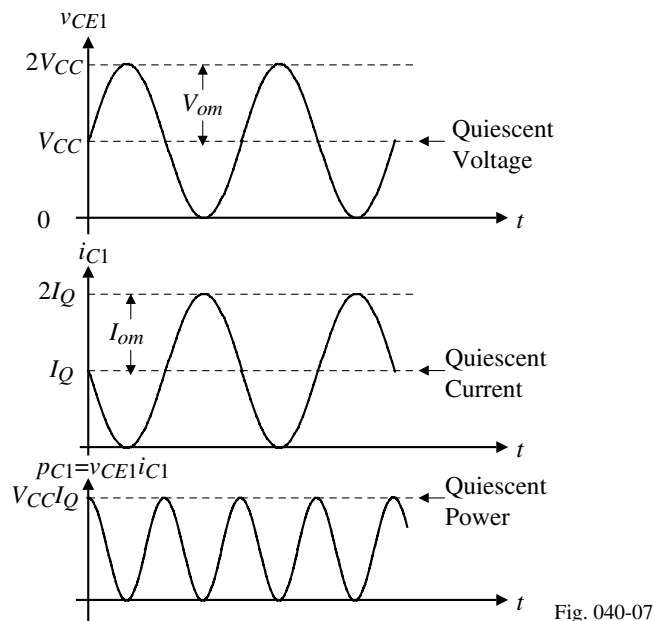
## Power Considerations of the Emitter Follower


Waveforms of the transistor variables for maximum efficiency.



$$p_{C1} = v_{CE1} i_{C1} = [V_{CC}(1 + \sin \omega t)][I_Q(1 - \sin \omega t)] = V_{CC} I_Q (1 - \sin^2 \omega t) = \frac{V_{CC} I_Q}{2} (1 + \cos 2\omega t)$$

## Power Considerations of the Emitter Follower - Continued

Parabolas of constant power:

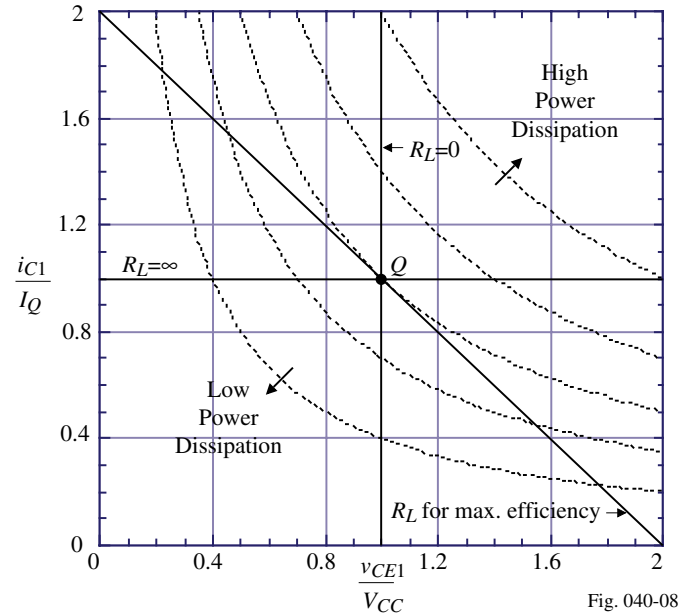

Comments:

- Maximum power dissipation occurs at the  $Q$  point for the  $R_L$  corresponding to maximum efficiency.
- For smaller values of  $R_L$  the power dissipation can become very large.

### Example - Design of an Emitter Follower for Maximum Efficiency

The emitter follower shown has  $V_{CC} = -V_{EE} = 5V$ ,  $R_1 = 2.15k\Omega$ , and  $V_{CE(sat)} = 0.2V$ . Find the value of  $R_L$  for maximum efficiency and find the value of this efficiency.

Solution

The  $R_L$  for maximum efficiency is found as,

$$R_L = \frac{V_{CC} - V_{CE(sat)}}{I_Q}$$

$$I_Q = \frac{-V_{EE} - V_{BE}}{R_1} = \frac{5 - 0.7}{2.15k\Omega} = 2mA$$


$$\therefore R_L = \frac{5 - 0.2}{2mA} = 2.4k\Omega$$

The efficiency can be found by calculating the power to the load and from the sources.

$$P_{L(max)} = \left( \frac{V_{CC} - V_{CE(sat)}}{\sqrt{2}} \right) \left( \frac{I_Q}{\sqrt{2}} \right) = 0.5(4.8V)(2mA) = 4.8mW$$

$$P_{supply} = 2V_{CC}I_Q = 2(5)(2mA) = 20mW$$
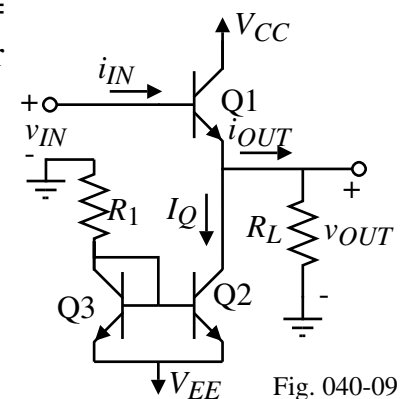
$$\therefore \eta = \frac{P_{L(max)}}{P_{supply}} = \frac{4.8}{20} = 0.24 \text{ or } 24\% \text{ which is close to the theoretical maximum.}$$



## Emitter Follower - Small Signal Performance

The small signal model of the emitter follower is:

$$R_{in} = R_S + r_{\pi} + (1 + \beta_F)R_L$$

$$R_{out} \approx 1/g_m \text{ (excluding } R_L)$$

$$v_{out} = (g_m + g_{\pi})v_1 R_L = (g_m + g_{\pi})(i_{in} r_{\pi})R_L$$

$$= (g_m + g_{\pi}) r_{\pi} R_L \left( \frac{v_{in}}{R_{in}} \right)$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{(g_m + g_{\pi}) r_{\pi} R_L}{R_S + r_{\pi} + (1 + \beta_F)R_L} \approx \frac{R_L}{R_L + \frac{1}{g_m} + \frac{R_S}{\beta_F}}$$

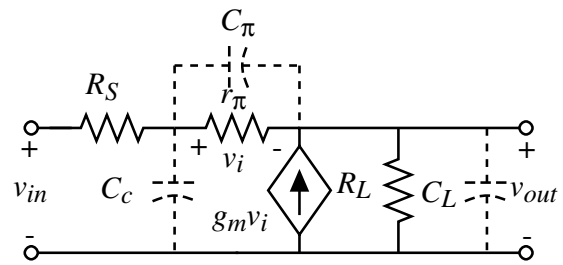


Fig. 040-10

If  $\beta_F = 100$ ,  $g_m = 20\text{mA/V}$ ,  $R_L = R_S = 1\text{k}\Omega$ ,  $C_{\pi} = 5\text{pF}$  and  $C_L = 10\text{pF}$ , we get

$$R_{in} = 1\text{k}\Omega + 5\text{k}\Omega + 101\text{k}\Omega = 107\text{k}\Omega, \quad R_{out} = 50\Omega, \quad \frac{v_{out}}{v_{in}} = \frac{1\text{k}\Omega}{1\text{k}\Omega + 50\Omega + 9.9\Omega} = 0.943\text{V/V}$$

The transfer function assuming  $R_S = 0$ , is given as,

$$\frac{V_{out}}{V_{in}} = \frac{g_m + g_{\pi} + sC_{\pi}}{g_m + g_{\pi} + G_L + sC_{\pi} + sC_L} \Rightarrow \text{Zero} \approx -\frac{g_m}{C_{\pi}} \quad \text{and} \quad \text{Pole} \approx -\frac{g_m + G_L}{C_{\pi} + C_L}$$

$$\text{Zero} = -4 \times 10^9 \text{ rads./sec.} \quad \text{and} \quad \text{Pole} = -1.4 \times 10^9 \text{ rads./sec.}$$

## SUMMARY

### Requirements of Output Stages

- The objectives are to provide output power in form of voltage and/or current.
- In addition, the output amplifier should be linear and be efficient.
- Low output resistance is required to provide power efficiently to a small load resistance.
- High source/sink currents are required to provide sufficient output voltage rate due to large load capacitances.
- Types of output stages considered:
  - Source and emitter follower (Class A)
- Did not consider the distortion analysis of GHLM, Sec. 5.3.2