

# LECTURE 060 – PUSH-PULL OUTPUT STAGES

## (READING: GHLM – 362-384, AH – 226-229)

### Objective

The objective of this presentation is:

Show how to design stages that

- 1.) Provide sufficient output power in the form of voltage or current.
- 2.) Avoid signal distortion.
- 3.) Be efficient
- 4.) Provide protection from abnormal conditions (short circuit, over temperature, etc.)


### Outline

- Push-Pull MOS (Class B)
- Push-Pull BJT (Class B)
- Summary

## PUSH-PULL MOS OUTPUT STAGES (Class AB and B)
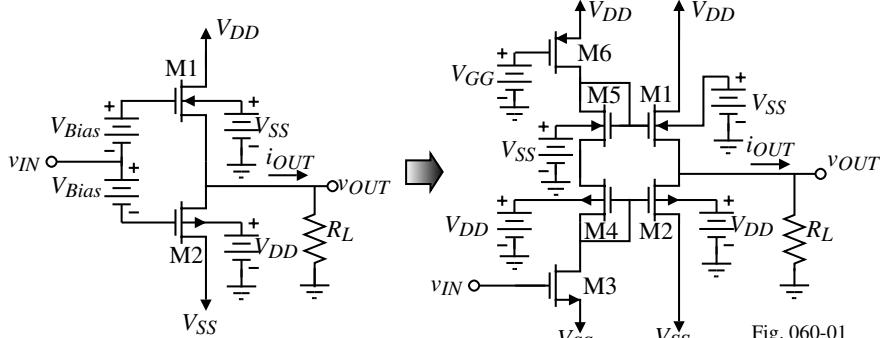
### Push-Pull Source Follower

Can both sink and source current and provide a slightly lower output resistance.



Efficiency:

Depends on how the transistors are biased.

- Class B - one transistor has current flow for only  $180^\circ$  of the sinusoid (half period)


$$\therefore \text{Efficiency} = \frac{P_{RL}}{P_{VDD}} = \frac{\frac{v_{OUT}(\text{peak})^2}{2R_L}}{(V_{DD} - V_{SS}) \left( \frac{1}{2} \right) \left( \frac{2v_{OUT}(\text{peak})}{\pi R_L} \right)} = \frac{\pi}{2} \frac{v_{OUT}(\text{peak})^2}{V_{DD} - V_{SS}}$$

Maximum efficiency occurs when  $v_{OUT}(\text{peak}) = V_{DD}$  and is 78.5%

- Class AB - each transistor has current flow for more than  $180^\circ$  of the sinusoid. Maximum efficiency is between 25% and 78.5%
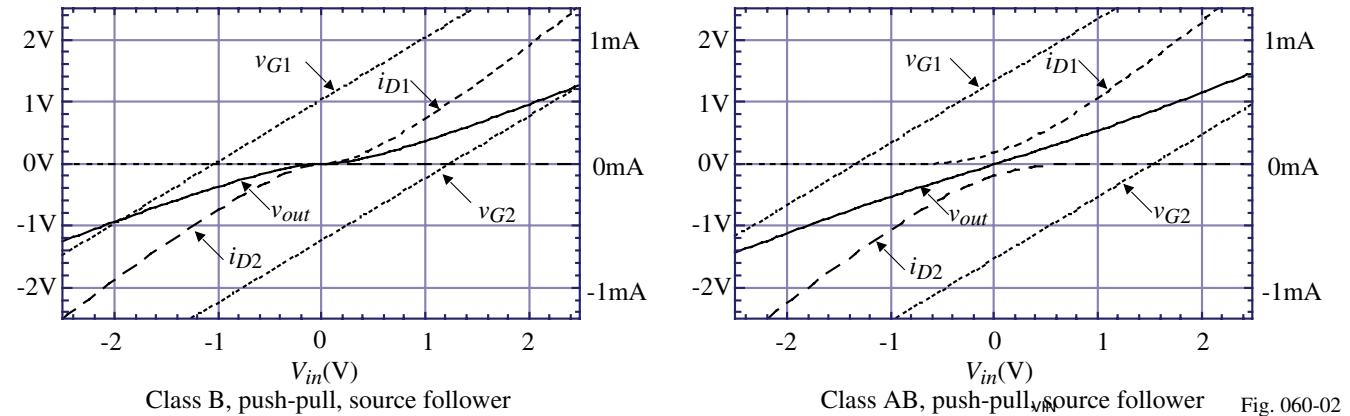
## Illustration of Class B and Class AB Push-Pull, Source Follower

Output current and voltage characteristics of the push-pull, source follower ( $R_L = 1\text{k}\Omega$ ):




Comments:

- Note that  $v_{OUT}$  cannot reach the extreme values of  $V_{DD}$  and  $V_{SS}$
- $I_{OUT}^+(\text{max})$  and  $I_{OUT}^-(\text{max})$  is always less than  $V_{DD}/R_L$  or  $V_{SS}/R_L$
- For  $v_{OUT}=0\text{V}$ , there is quiescent current flowing in M1 and M2 for Class AB
- Note that there is significant distortion at  $v_{IN}=0\text{V}$  for the Class B push-pull follower

## Small-Signal Performance of the Push-Pull Follower

Model:

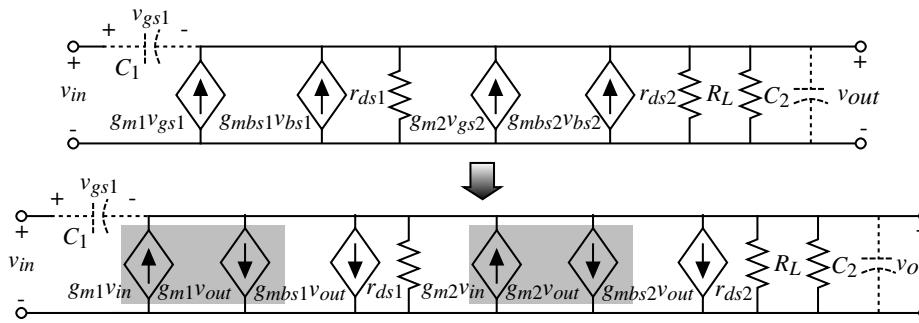

$$\frac{v_{out}}{v_{in}} = \frac{g_m + g_{m2}}{g_{ds1} + g_{ds2} + g_m + g_{mbs1} + g_{m2} + g_{mbs2} + G_L}$$

$$R_{out} = \frac{1}{g_{ds1} + g_{ds2} + g_m + g_{mbs1} + g_{m2} + g_{mbs2}} \quad (\text{does not include } R_L)$$

If  $V_{DD} = -V_{SS} = 2.5\text{V}$ ,  $V_{out} = 0\text{V}$ ,  $I_{D1} = I_{D2} = 500\mu\text{A}$ , and  $\text{W/L} = 20\mu\text{m}/2\mu\text{m}$ ,  $A_v = 0.787$  ( $R_L = \infty$ ) and  $R_{out} = 448\Omega$ .

A zero and pole are located at

$$z = \frac{-(g_m + g_{m2})}{C_1} \quad p = \frac{-(g_{ds1} + g_{ds2} + g_m + g_{mbs1} + g_{m2} + g_{mbs2} + G_L)}{C_1 + C_2}.$$

These roots will be high-frequency because the associated resistances are small.

## Push-Pull, Common Source Amplifiers

Similar to the class A but can operate as class B providing higher efficiency.

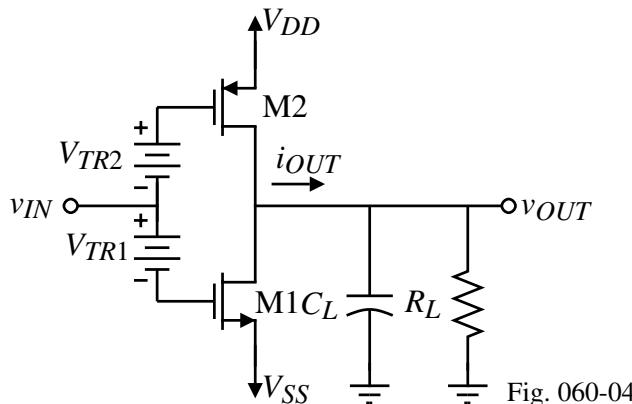


Fig. 060-04

Comments:

- The batteries  $V_{TR1}$  and  $V_{TR2}$  are necessary to control the bias current in M1 and M2.
- The efficiency is the same as the push-pull, source follower.

## Practical Implementation of the Push-Pull, Common Source Amplifier

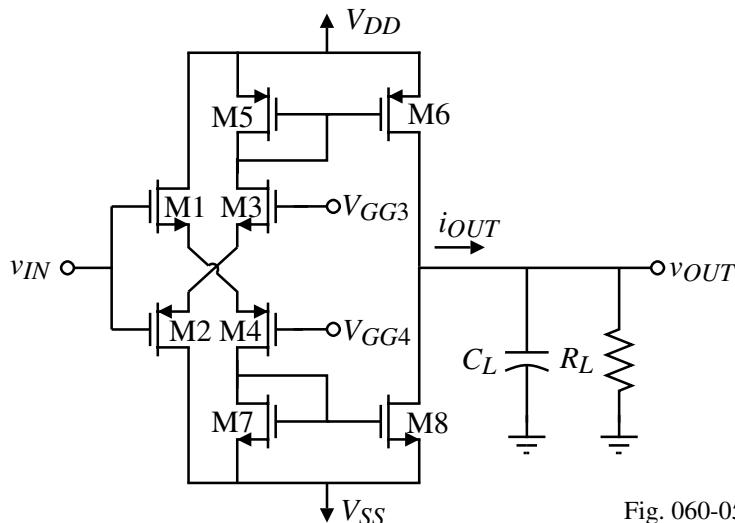



Fig. 060-05

$V_{GG3}$  and  $V_{GG4}$  can be used to bias this amplifier in class AB or class B operation.


Note, that the bias current in M6 and M8 is not dependent upon  $V_{DD}$  or  $V_{SS}$  (assuming  $V_{GG3}$  and  $V_{GG4}$  are not dependent on  $V_{DD}$  and  $V_{SS}$ ).
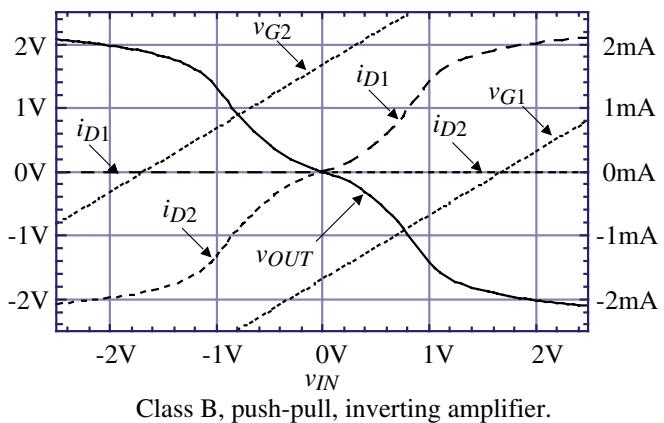
## Illustration of Class B and Class AB Push-Pull, Inverting Amplifier

Output current and voltage characteristics of the push-pull, inverting amplifier ( $R_L = 1\text{k}\Omega$ ):



Class B, push-pull, inverting amplifier.

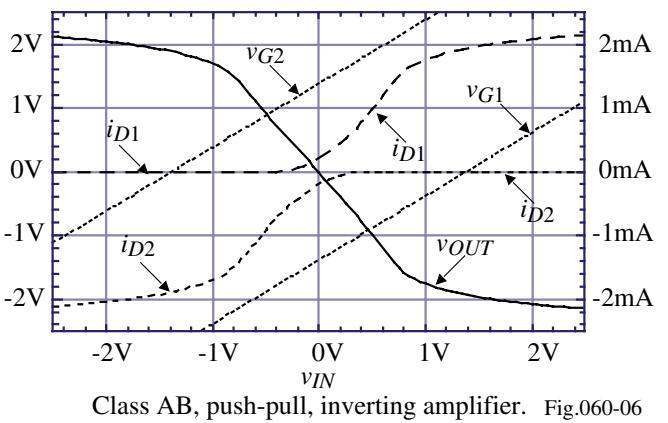

Class AB, push-pull, inverting amplifier. Fig.060-06

Comments:

- Note that there is significant distortion at  $v_{IN} = 0\text{V}$  for the Class B inverter
- Note that  $v_{OUT}$  cannot reach the extreme values of  $V_{DD}$  and  $V_{SS}$
- $I_{OUT}^+(\text{max})$  and  $I_{OUT}^-(\text{max})$  is always less than  $V_{DD}/R_L$  or  $V_{SS}/R_L$
- For  $v_{OUT} = 0\text{V}$ , there is quiescent current flowing in M1 and M2 for Class AB

## Use of Negative, Shunt Feedback to Reduce the Output Resistance

Concept:

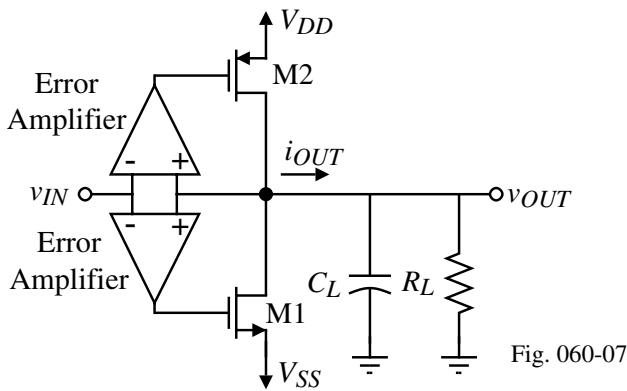


Fig. 060-07

$$R_{out} = \frac{r_{ds1} \| r_{ds2}}{1 + \text{Loop Gain}}$$

Comments:

- Can achieve output resistances as low as  $10\Omega$ .
- If the error amplifiers are not balanced, it is difficult to control the quiescent current in M1 and M2
- Great linearity because of the strong feedback
- Can be efficient if operated in class B or class AB

## Simple Implementation of Neg., Shunt Feedback to Reduce the Output Resistance

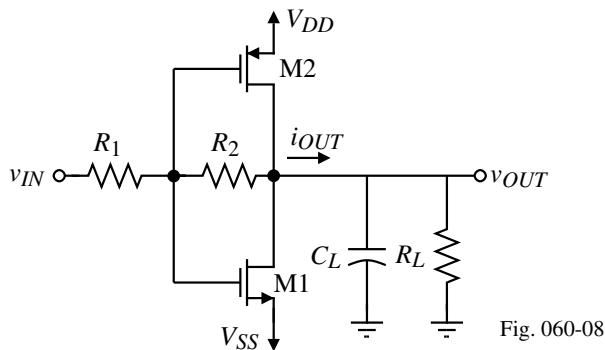


Fig. 060-08

$$\text{Loop gain} \approx \left( \frac{R_1}{R_1 + R_2} \right) \left( \frac{g_{m1} + g_{m2}}{g_{ds1} + g_{ds2} + G_L} \right)$$

$$\therefore R_{out} = \frac{r_{ds1} \| r_{ds2}}{1 + \left( \frac{R_1}{R_1 + R_2} \right) \left( \frac{g_{m1} + g_{m2}}{g_{ds1} + g_{ds2} + G_L} \right)}$$

Let  $R_1 = R_2$ ,  $R_L = \infty$ ,  $I_{Bias} = 500\mu\text{A}$ ,  $W_1/L_1 = 100\mu\text{m}/1\mu\text{m}$  and  $W_2/L_2 = 200\mu\text{m}/1\mu\text{m}$ .

Thus,  $g_{m1} = 3.316\text{mS}$ ,  $g_{m2} = 3.162\text{mS}$ ,  $r_{ds1} = 50\text{k}\Omega$  and  $r_{ds2} = 40\text{k}\Omega$ .

$$\therefore R_{out} = \frac{50\text{k}\Omega \| 40\text{k}\Omega}{1 + 0.5 \left( \frac{3316 + 3162}{25 + 20} \right)} = \frac{22.22\text{k}\Omega}{1 + 0.5(143.9)} = 304\Omega \quad (R_{out} = 5.42\text{k}\Omega \text{ if } R_L = 1\text{k}\Omega)$$

## What about the use of BJTs in CMOS Technology?

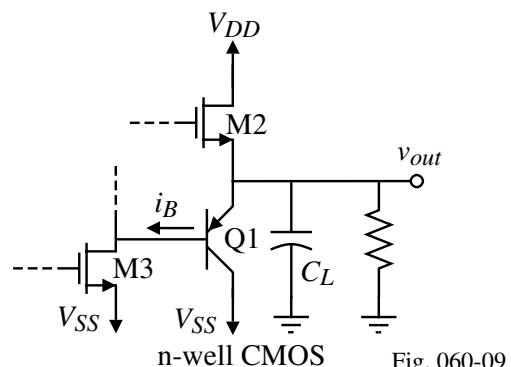
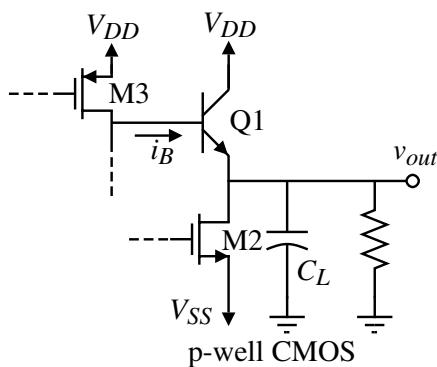


Fig. 060-09

Comments:

- Can use either substrate or lateral BJTs.
- Small-signal output resistance is  $1/g_m$  which can easily be less than  $100\Omega$ .
- Unfortunately, only PNP or NPN BJTs are available but not both on a standard CMOS technology.
- In order for the BJT to sink (or source) large currents, the base current,  $i_B$ , must be large. Providing large currents as the voltage gets to extreme values is difficult for MOSFET circuits to accomplish.
- If one considers the MOSFET driver, the emitter can only pull to within  $v_{BE} + V_{ON}$  of the power supply rails. This value can be 1V or more.

## PUSH-PULL BJT OUTPUT STAGES (Class AB and B)

### Simple Class B Output Stage

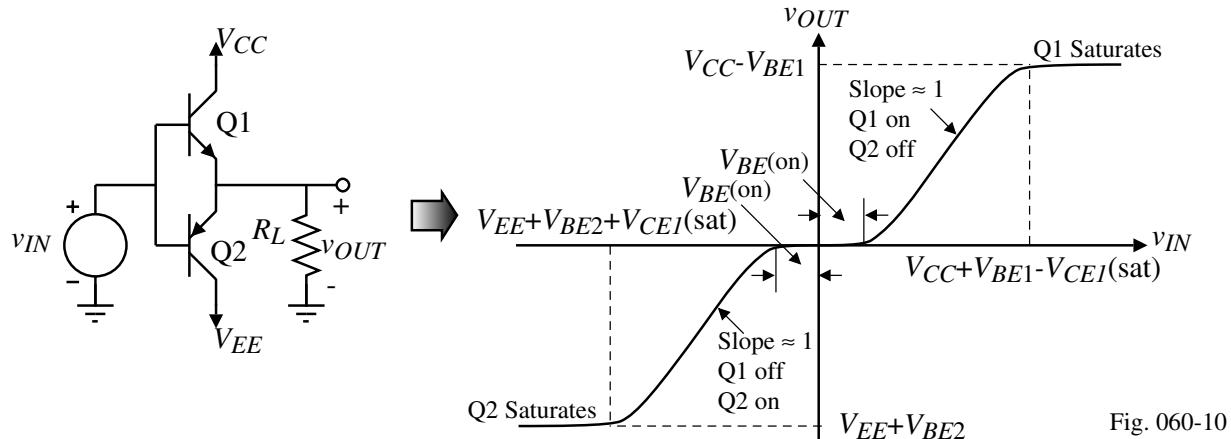


Fig. 060-10

Class B operation: Two active devices are used to deliver the power instead of one. Each device conducts for alternate half cycles.

Efficiency can approach 78.5%

Can suffer from crossover distortion - the transition from one device to the other.

### Class AB Output Stage

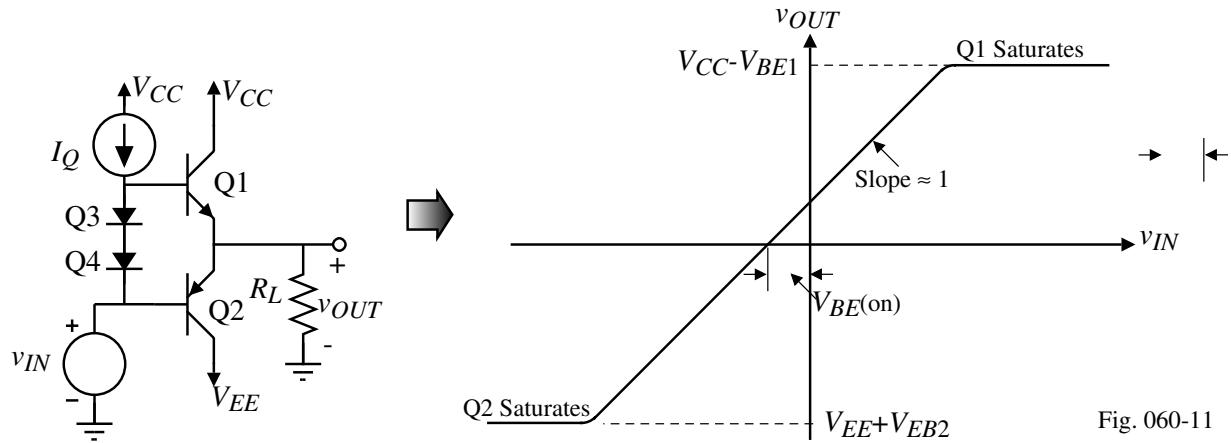


Fig. 060-11

$I_Q$  sets up the bias current in Q1 and Q2 when there is no input signal.

Each transistor is biased so that there is a region in the middle where both are on (Class AB)

## Power Considerations in the Class B Output Stage

Voltage and current waveforms for a Class B amplifier:

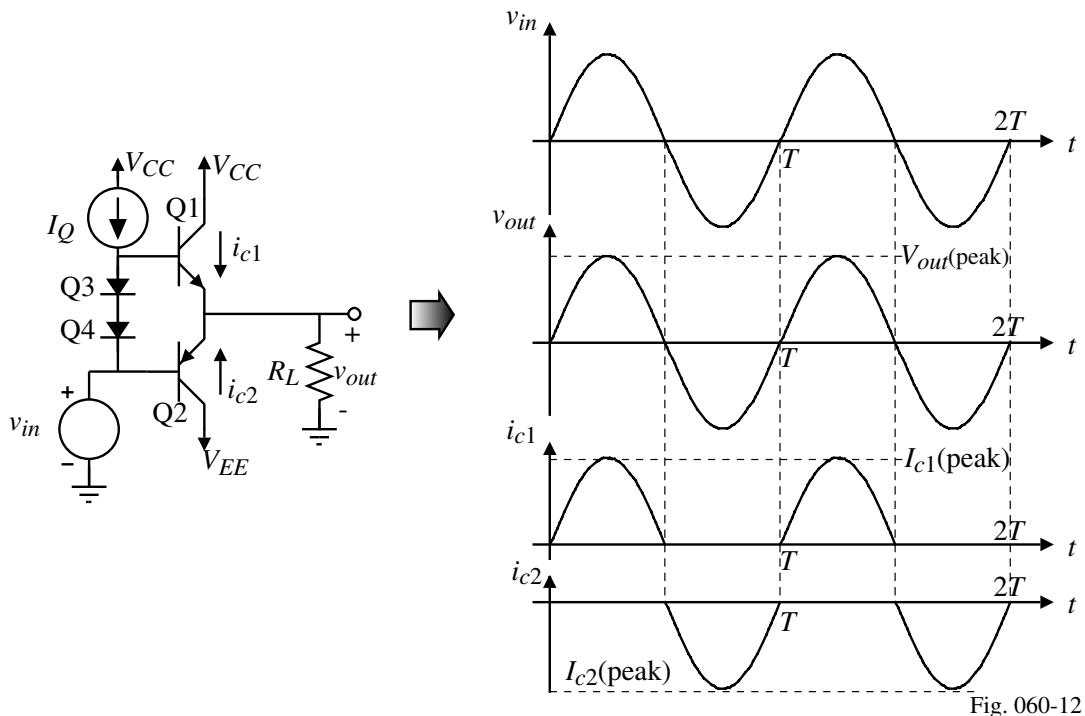


Fig. 060-12

## Efficiency Considerations of the Class-B Push-Pull Output Stage

Load line for one device in a class-B stage:

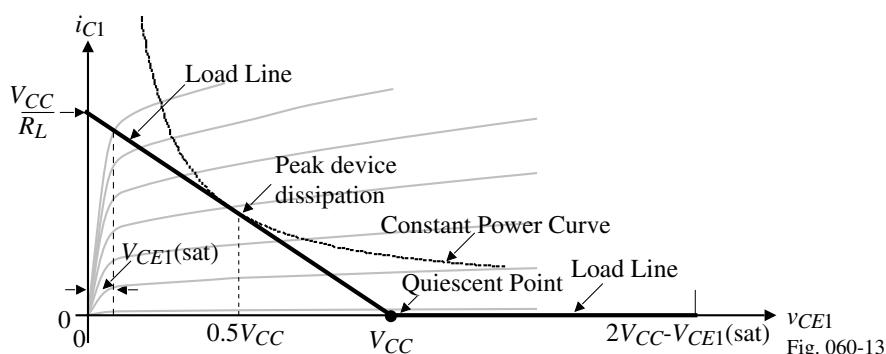


Fig. 060-13

Efficiency:

$$P_L = \frac{1}{2} \frac{[V_{out}(peak)]^2}{R_L}$$

and  $P_{\text{supply}} = 2V_{CC}I_{\text{supply}} = 2V_{CC} \left( \frac{1}{T} \int_0^T i_C(t) dt \right) = 2V_{CC} \left( \frac{I_c(\text{peak})}{\pi} \right) = \frac{2}{\pi} \frac{V_{CC}}{R_L} V_{out}(\text{peak})$

$$\therefore \eta = \frac{P_L}{P_{\text{supply}}} = \frac{\pi}{4} \frac{V_{out}(\text{peak})}{V_{CC}} \Rightarrow \eta_{\max} = \frac{\pi}{4} = 78.6\%$$

Max. efficiency for the above class-B push-pull output stage is  $\eta_{\max} = \frac{\pi}{4} \frac{V_{CC} - V_{CE}(\text{sat})}{V_{CC}}$

## 709 Output Stage


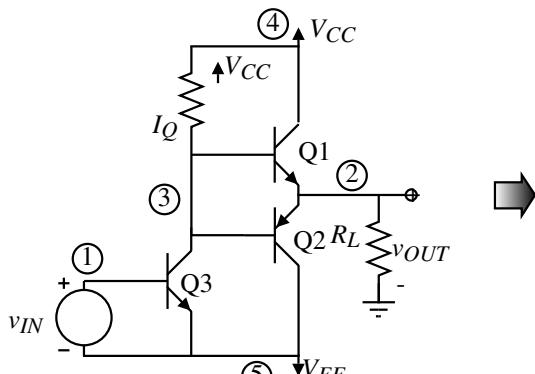


Fig. 060-14

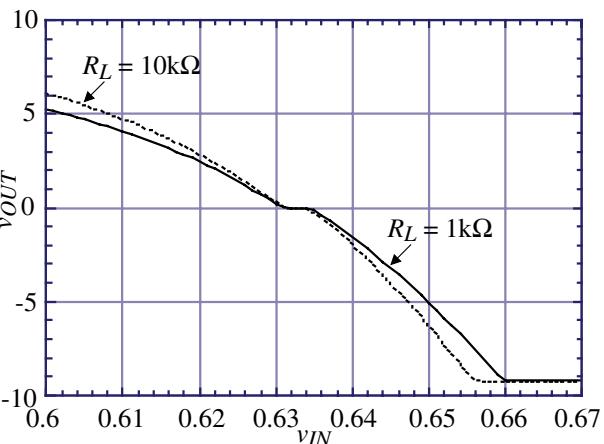

### 709 Output Stage Voltage Transfer Function

```
.MODEL BJTN NPN IS=1E-14 BF=100 VAF=50
.MODEL BJTP PNP IS=1E-14 BF=50 VAF=50
Q1 4 3 2 BJTN
Q2 5 3 2 BJTP
Q3 3 1 5 BJTN
VCC 4 0 DC 10V
VEE 5 0 DC -10V
```

### VIN 1 5

```
RL 2 0 1KILOHM
R1 4 3 20KILOHM
.DC VIN 0.60 0.67 0.001
.PRINT DC V(2)
.PROBE
.END
```

This stage assumes that feedback will be used around the amplifier which will linearize the nonlinearity of the output stage.

## 741 Output Stage


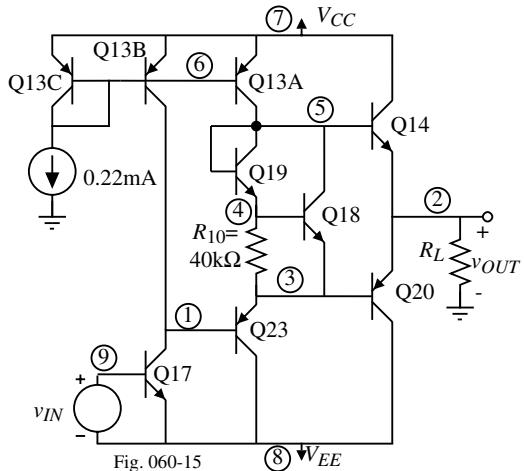


Fig. 060-15

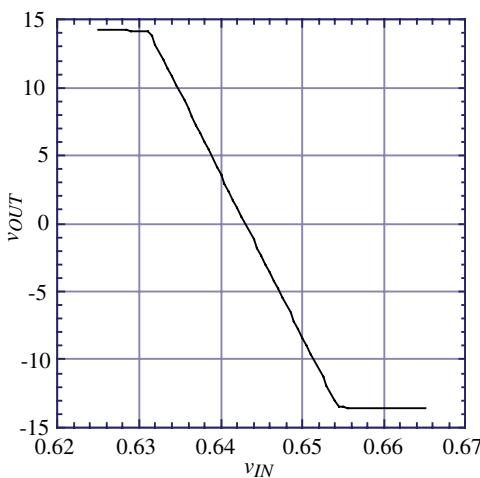

### 741 Output Stage Voltage Transfer Function - RL = 1Kilohm

```
.MODEL BJTN NPN IS=1E-14 BF=100 VAF=50
.MODEL BJTP PNP IS=1E-14 BF=50 VAF=50
Q23 8 1 3 BJTP
Q20 8 3 2 BJTP
Q14 7 5 2 BJTN
Q17 1 9 8 BJTN
Q18 5 4 3 BJTN
Q19 5 5 4 BJTN
Q13A 5 6 7 BJTP
Q13B 1 6 7 BJTP 3.0
```

### Q13C 6 6 7 BJTP

```
VCC 7 0 DC 15V
VEE 8 0 DC -15V
IBIAS 6 0 220UA
VIN 9 8 DC 0.645
R10 4 3 40KILOHM
RL 2 0 1KILOHM
.DC VIN 0.625 0.665 0.0005
.PRINT DC V(2)
.PROBE
.END
```

## Quasi-Complementary Output Stages

Quasi-complementary connections are used to improve the performance of the PNP or PMOS transistor.

Composite connections:

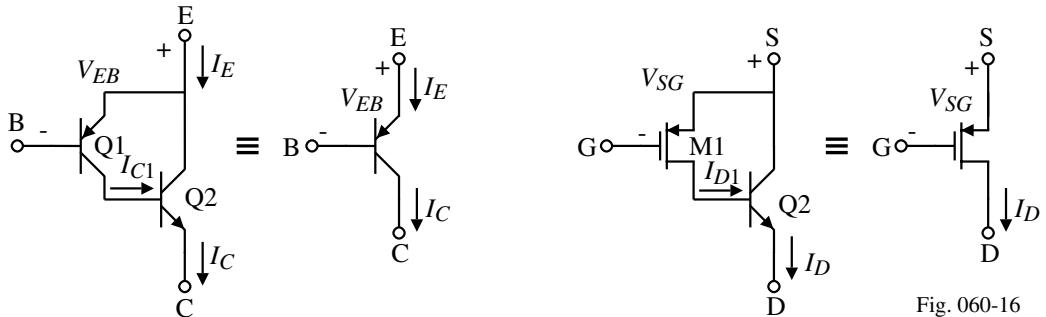


Fig. 060-16

PNP Equivalent:

$$I_C = (1 + \beta_2) I_{C1} = (1 + \beta_2) I_s \exp\left(\frac{V_{EB}}{V_t}\right) \quad I_D = (1 + \beta_2) I_{D1} = (1 + \beta_2) \left(\frac{K_P' W_1}{2 L_1}\right) (V_{GS} - V_T)^2$$

∴ The composite has the beta of an NPN


PMOS Equivalent:

∴ The composite has an enhanced  $K'$

## Overload Protection

For circuits that can provide large amounts of output current, it is necessary to provide short-circuit current protection.

Example:

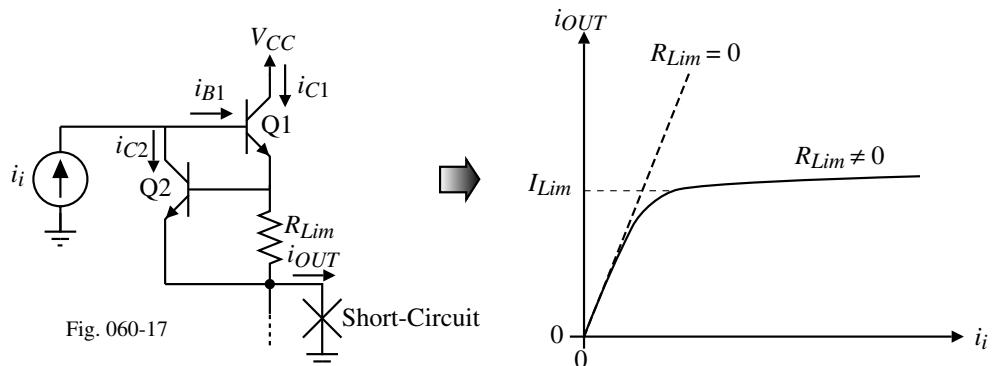

$$i_{OUT} = i_{C1} + i_{C2} \approx i_{C1} \quad \therefore \quad i_{OUT} = \beta_1 i_{B1} = \beta_1 (i_i - i_{C2})$$

$$\text{But } i_{C2} \approx I_s 2 \exp\left(\frac{v_{BE2}}{V_t}\right) \approx I_s 2 \exp\left(\frac{i_{C1} R_{Lim}}{V_t}\right)$$

$$\therefore \quad i_{OUT} = \beta_1 i_i - I_s 2 \exp\left(\frac{i_{C1} R_{Lim}}{V_t}\right)$$

As  $i_{OUT}$  increases, Q2 turns on and pulls base current away from Q1 limiting the output current.

## **SUMMARY**

### Requirements of Output Stages

- The objectives are to provide output power in form of voltage and/or current.
- In addition, the output amplifier should be linear and be efficient.
- Low output resistance is required to provide power efficiently to a small load resistance.
- High source/sink currents are required to provide sufficient output voltage rate due to large load capacitances.

### Types of output stages considered:

Class B or AB stage with push-pull (maximum efficiency was 78.6%)

- Quasi-complementary devices help improve the performance of the p-type devices
- Protection circuits prevent large currents from flowing in the output devices
- For large load capacitors all that is required from an output stage is large current, the output resistance does not have to be small