

# LECTURE 290 – FEEDBACK CIRCUIT ANALYSIS USING RETURN RATIO

(READING: GHLM – 599-613)

## Objective

The objective of this presentation is:

- 1.) Illustrate the method of using return ratio to analyze feedback circuits
- 2.) Demonstrate using examples

## Outline

- Concept of return ratio
- Closed-loop gain using return ratio
- Closed-loop impedance using return ratio
- Summary

## Concept of Return Ratio

Instead of using two-port analysis, return ratio takes advantage of signal flow graphs (theory).

The return ratio for a dependent source in a feedback loop is found as follows:

- 1.) Set all independent sources to zero.
- 2.) Change the dependent source to an independent source and define the controlling variable as  $s_r$ , and the source variable as  $s_t$ .
- 3.) Calculate the return ratio designated as  $RR = -s_r/s_t$ .


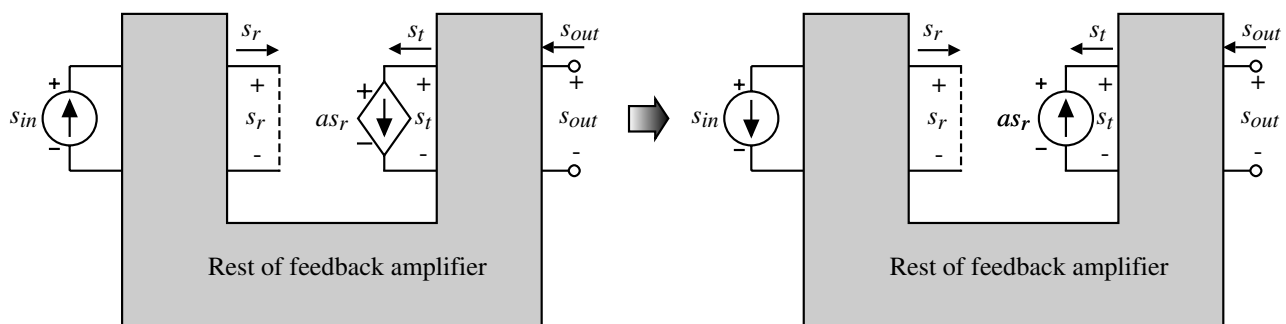


Fig. 290-01
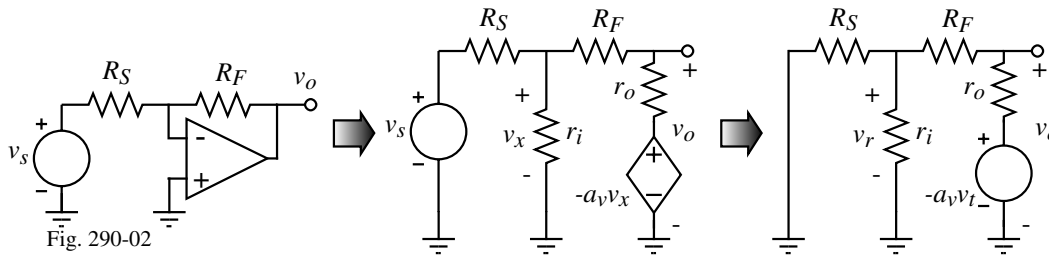
### Example 1 – Calculation of Return Ratio

Find the return ratio of the op amp with feedback shown if the input resistance of the op amp is  $r_i$ , the output resistance is  $r_o$ , and the voltage gain is  $a_v$ .



**Solution**

$$v_r = \frac{(-a_v v_t) R_S \parallel r_i}{r_o + R_F + R_S \parallel r_i} \quad \rightarrow \quad RR = -\frac{v_r}{v_t} = \frac{(a_v v_t) R_S \parallel r_i}{r_o + R_F + R_S \parallel r_i}$$

### Closed-Loop Gain Using Return Ratio

Consider the following general feedback amplifier:

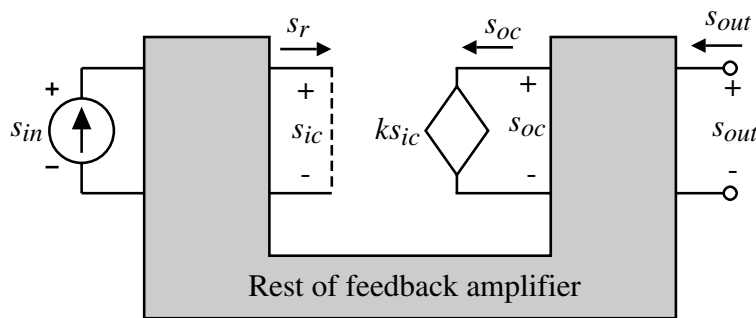


Fig. 290-03

Note that  $s_{oc} = ks_{ic}$ .

Assume the amplifier is linear and express  $s_{ic}$  and  $s_{out}$  as linear functions of the two sources,  $s_{in}$  and  $s_{oc}$ .

$$s_{ic} = B_1 s_{in} - H s_{oc}$$

$$s_{out} = d s_{in} + B_2 s_{oc}$$

where  $B_1$ ,  $B_2$ , and  $H$  are defined as

$$B_1 = \left. \frac{s_{ic}}{s_{oc}} \right|_{s_{oc}=0} = \left. \frac{s_{ic}}{s_{oc}} \right|_{k=0}, \quad B_2 = \left. \frac{s_{out}}{s_{oc}} \right|_{s_{in}=0}, \quad \text{and} \quad H = - \left. \frac{s_{ic}}{s_{oc}} \right|_{s_{in}=0}$$

## Closed-Loop Gain Using Return Ratio – Continued

Interpretation:

$B_1$  is the transfer function from the input to the controlling signal with  $k = 0$ .

$B_2$  is the transfer function from the controlling signal to the output with  $s_{in} = 0$ .

$H$  is the transfer function from the output of the dependent source to the controlling signal with  $s_{in} = 0$  and multiplied times a  $-1$ .

$d$  is defined as,

$$d = \left. \frac{s_{out}}{s_{in}} \right|_{s_{oc}=0} = \left. \frac{s_{out}}{s_{in}} \right|_{k=0}$$

$d$  is the direct signal feedthrough when the controlled source in  $A$  is set to zero ( $k=0$ )

Closed-loop gain ( $s_{out}/s_{in}$ ) can be found as,

$$s_{ic} = B_1 s_{in} - H s_{oc} = B_1 s_{in} - kH s_{ic} \quad \rightarrow \quad \frac{s_{ic}}{s_{in}} = \frac{B_1}{1 + kH}$$

$$s_{out} = d s_{in} + B_2 s_{oc} = d s_{in} + kB_2 s_{ic} = d s_{in} + \frac{B_1 kB_2}{1 + kH} s_{in}$$

$$2.) \quad A = \frac{s_{out}}{s_{in}} = \frac{B_1 kB_2}{1 + kH} + d = \frac{B_1 kB_2}{1 + RR} + d = \frac{g}{1 + RR} + d$$

where  $RR = kH$  and  $g = B_1 kB_2$  (gain from  $s_{in}$  to  $s_{out}$  if  $H = 0$  and  $k = 0$ )

## Closed-Loop Gain Using Return Ratio – Continued

Further simplification:

$$A = \frac{g}{1 + RR} + d = \frac{g + d(1 + RR)}{1 + RR} = \frac{g + d \cdot RR}{1 + RR} + \frac{d}{1 + RR} = \frac{\left(\frac{g}{RR} + d\right)RR}{1 + RR} + \frac{d}{1 + RR}$$

Define

$$A_\infty = \frac{g}{RR} + d$$

$$3.) \quad A = A_\infty \frac{RR}{1 + RR} + \frac{d}{1 + RR}$$

Note that as  $RR \rightarrow \infty$ , that  $A = A_\infty$ .

$A_\infty$  is the closed-loop gain when the feedback circuit is ideal (i.e.,  $RR \rightarrow \infty$  or  $k \rightarrow \infty$ ).

Block diagram of the new formulation:

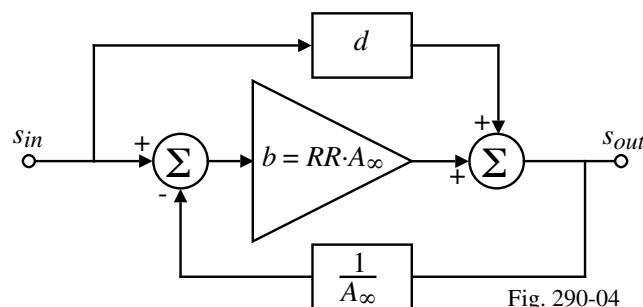


Fig. 290-04



Note that  $b = RR \cdot A_\infty$  is called the effective gain of the feedback amplifier.

### Example 2 – Use of Return Ratio Approach to Calculate the Closed-Loop Gain

Find the closed-loop gain and the effective gain of the transistor feedback amplifier shown using the previous formulas. Assume that the BJT  $g_m = 40\text{mS}$ ,  $r_\pi = 5\text{k}\Omega$ , and  $r_o = 1\text{M}\Omega$ .
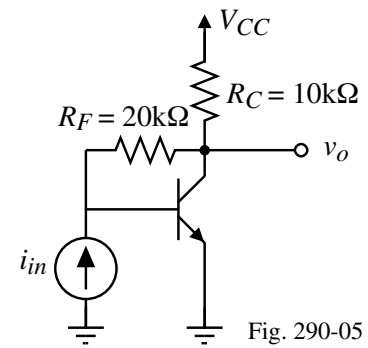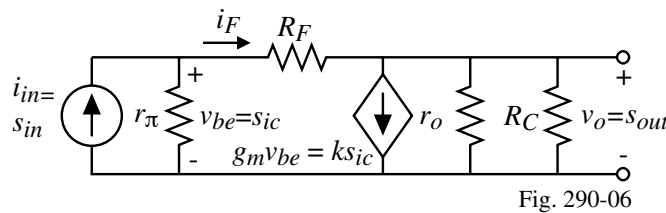
#### Solution

The small-signal model suitable for calculating  $A_\infty$  and  $d$  is shown.



$$A_\infty = \left. \frac{s_{out}}{s_{in}} \right|_{k=\infty} = \left. \frac{v_o}{i_{in} g_{m=\infty}} \right|_{k=\infty} = ? \quad \text{Remember that } A = \frac{a}{1+af} \rightarrow \frac{1}{f} \text{ as } a \rightarrow \infty.$$


$$f = \left. \frac{v_o}{i_F} \right|_{v_{in}=0} = \frac{-1}{R_F} \quad \text{Therefore, } A_\infty = -R_F = -20\text{k}\Omega$$

$$d = \left. \frac{s_{out}}{s_{in}} \right|_{k=0} = \left. \frac{v_o}{i_{in} g_{m=0}} \right|_{k=0} = \frac{r_\pi}{r_\pi + R_F + (r_o \parallel R_C)} (r_o \parallel R_C)$$

$$= \frac{5\text{k}\Omega}{5\text{k}\Omega + 20\text{k}\Omega + 1\text{M}\Omega \parallel 10\text{k}\Omega} (1\text{M}\Omega \parallel 10\text{k}\Omega) = 1.42\text{k}\Omega$$
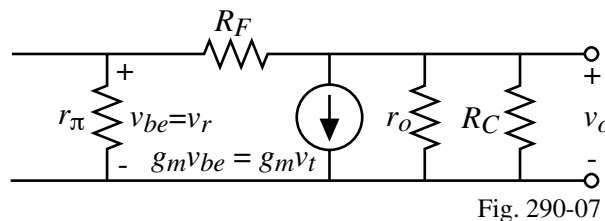
### Example 2 – Continued

What is left is to calculate the  $RR$ . A small-signal model for this is shown below.



$$v_r = (-g_m v_t) \left( \frac{r_o \parallel R_C}{r_\pi + R_F + r_o \parallel R_C} \right) r_\pi \quad \rightarrow \quad \frac{v_r}{v_t} = (-g_m r_\pi) \left( \frac{r_o \parallel R_C}{r_\pi + R_F + r_o \parallel R_C} \right)$$

$$RR = -\frac{v_r}{v_t} = (g_m r_\pi) \left( \frac{r_o \parallel R_C}{r_\pi + R_F + r_o \parallel R_C} \right) = (200) \left( \frac{1\text{M}\Omega \parallel 10\text{k}\Omega}{5\text{k}\Omega + 20\text{k}\Omega + 1\text{M}\Omega \parallel 10\text{k}\Omega} \right) = 56.74$$

Now, the closed loop gain is found to be,

$$A = A_\infty \frac{RR}{1 + RR} + \frac{d}{1 + RR} = (-20\text{k}\Omega) \left( \frac{56.74}{1 + 56.74} \right) + \left( \frac{1.4\text{k}\Omega}{1 + 56.74} \right) = -19.63\text{k}\Omega$$

The effective gain is given as,

$$b = RR \cdot A_\infty = 56.74(-20\text{k}\Omega) = -1135\text{k}\Omega$$

### Closed-Loop Impedance Formula using the Return Ratio (Blackman's Formula)

Consider the following linear feedback circuit where the impedance at port X is to be calculated.

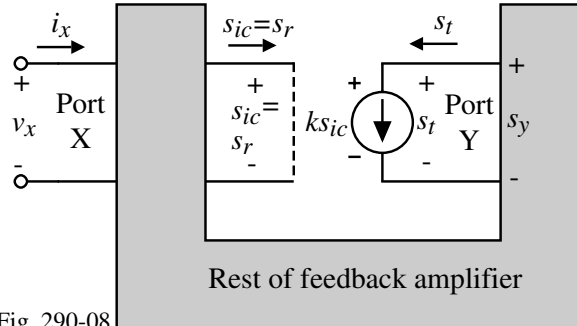


Fig. 290-08

Expressing the signals,  $v_x$  and  $s_{ic}$  as linear functions of the signals  $i_x$  and  $s_y$  gives,

$$v_x = a_1 i_x + a_2 s_y$$

$$s_{ic} = a_3 i_x + a_4 s_y$$

The impedance looking into port X when  $k = 0$  is,

$$Z_{port}(k=0) = \left. \frac{v_x}{i_x} \right|_{k=0} = \left. \frac{v_x}{i_x} \right|_{s_y=0}$$

### Closed-Loop Impedance Formula using the Return Ratio – Continued

Next, compute the  $RR$  for the controlled source,  $k$ , under two different conditions.

1.) The first condition is when port X is open ( $i_x = 0$ ).

$$s_{ic} = a_4 s_y = a_4 s_t$$

Also,

$$s_r = k s_{ic} \quad \rightarrow \quad s_r = k a_4 s_t \quad \rightarrow \quad RR(\text{port open}) = -\frac{s_r}{s_t} = -k a_4$$

2.) The second condition is when port X is shorted ( $v_x = 0$ ).

$$i_x = -\frac{a_2}{a_1} s_y = -\frac{a_2}{a_1} s_t$$

$$\therefore s_{ic} = a_3 i_x + a_4 s_y = \left( a_4 - \frac{a_2 a_3}{a_1} \right) s_t$$

The return signal is

$$s_r = k s_{ic} = k \left( a_4 - \frac{a_2 a_3}{a_1} \right) s_t \quad \rightarrow \quad RR(\text{port shorted}) = -\frac{s_r}{s_t} = -k \left( a_4 - \frac{a_2 a_3}{a_1} \right)$$

3.) The port impedance can be found as (Blackman's formula),

$$4.) \quad Z_{port} = \frac{v_x}{i_x} = a_1 \left( \frac{1 - k \left( a_4 - \frac{a_2 a_3}{a_1} \right)}{1 - a_4} \right) \Rightarrow \boxed{Z_{port} = Z_{port}(k=0) \left[ \frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right]}$$

### Example 3 – Application of Blackman’s Formula

Use Blackman’s formula to calculate the output resistance of Example 2.

#### Solution

We must calculate three quantities. They are  $R_{out}(g_m=0)$ ,  $RR(\text{output port shorted})$ , and  $RR(\text{output port open})$ . Use the following model for calculations:

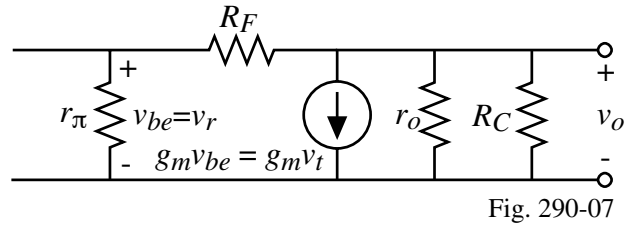


Fig. 290-07

$$R_{out}(g_m=0) = r_o \parallel R_C \parallel (r_\pi + R_F) = 7.09\text{k}\Omega$$

$$RR(\text{output port shorted}) = 0 \text{ because } v_t = 0.$$

$$RR(\text{output port open}) = RR \text{ of Example 2} = 56.74$$

$$\therefore R_{out} = R_{out}(g_m=0) \left[ \frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right] = 7.09\text{k}\Omega \left( \frac{1}{1+56.74} \right) = 129\Omega$$

### Example 4 – Output Resistance of a Super-Source Follower

Find an expression for the small-signal output resistance of the circuit shown.

#### Solution

The appropriate small-signal model is shown where  $g_{m2} = k$ .

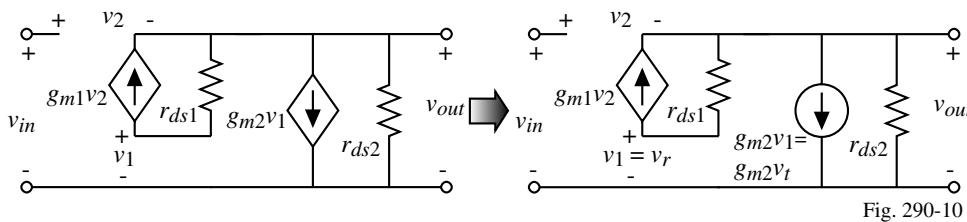


Fig. 290-10

$$R_{out}(g_{m2}=0) = r_{ds2} \quad \text{and} \quad RR(\text{output port shorted}) = 0 \text{ because } v_t = 0.$$

$$RR(\text{output port open}) = -\frac{s_r}{s_t} = -\frac{v_r}{v_t}$$

$$v_r = v_{out} - (g_{m1}v_2)r_{ds1} = v_{out} - g_{m1}r_{ds1}(-v_{out}) = v_{out}(1 + g_{m1}r_{ds1})$$

$$v_{out} = -g_{m2}r_{ds2}v_t \quad \rightarrow \quad v_r = -(1 + g_{m1}r_{ds1})g_{m2}r_{ds2}v_t$$

$$RR(\text{output port open}) = -\frac{v_r}{v_t} = (1 + g_{m1}r_{ds1})g_{m2}r_{ds2}$$

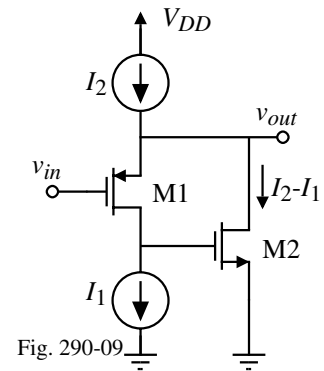


Fig. 290-09

$$\therefore R_{out} = R_{out}(g_{m2}=0) \left[ \frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right] = r_{ds2} \left( \frac{1+0}{1+(1+g_{m1}r_{ds1})g_{m2}r_{ds2}} \right) \approx \frac{1}{g_{m1}r_{ds1}g_{m2}}$$

### SUMMARY

- Return ratio is associated with a dependent source. If the dependent source is converted to an independent source, then the return ratio is the gain from the dependent source variable to the previously controlling variable.
- The closed-loop gain of a linear, negative feedback system can be expressed as

$$A = A_{\infty} \frac{RR}{1 + RR} + \frac{d}{1 + RR}$$

where

$A_{\infty}$  = the closed-loop gain when the loop gain is infinite

$RR$  = the return ratio

$d$  = the closed-loop gain when the amplifier gain is zero

- The resistance at a port can be found from Blackman's formula which is

$$Z_{\text{port}} = Z_{\text{port}}(k=0) \left[ \frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right]$$

where  $k$  is the gain of the dependent source chosen for the return ratio calculation

- This stuff is all great but of *little use as far as calculations are concerned*.

Small-signal analysis is generally quicker and easier than the two-port approach or the return ratio approach.

- Why study feedback? Because it is a great tool for understanding a circuit and for design.