

EXAMINATION NO. 3
(Average score = 74/100)

Problem 1 - (25 points)

Referring to the feedback circuit shown on the right, answer and/or fill in the blanks of the following questions:

a. What kind of mixing is being employed?

Series $\rightarrow (V_{in} - V_{out})$

b. What kind of sampling is being employed?

Shunt $\rightarrow (V_{out}$ via *mn1's CG gain stage*)

c. What type of amplifier is the feedback circuit?

$V_{out} / V_{in} \rightarrow$ Voltage Amplifier

d. $R_{in} = R_{in_open_loop} * \underline{\underline{(1 + LoopGain)}}$


e. $R_{out} = R_{out_open_loop} * \underline{\underline{1 \div (1 + LoopGain)}}$

f. Calculate the loop gain of this circuit (assume $r_{ds} \rightarrow \infty$ and derive the relationship as a function of small-signal parameters, R, and A_v) –hint: break the loop somewhere and compute the transfer function–.

Opening the loop at the gate of mn2:

$$LG = (v_{d2} / v_{g2}) (v_{d1} / v_{s1}) (v_{g2}' / v_{d1}) = (CS \text{ gain}) (CG \text{ gain}) (A_v)$$

$$= (-g_{m2} / g_{m1}) (g_{m1} R) (A_v) = -g_{m2} R A_v$$

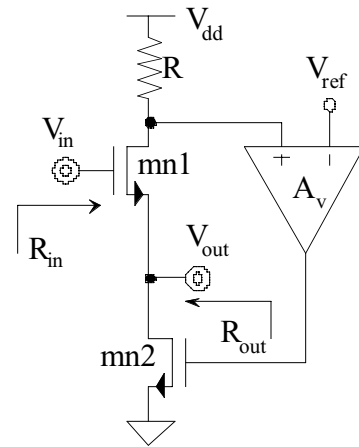

Problem 2 - (25 points)

Referring to the circuit shown, determine the closed-loop output resistance R_{out} using Return-Ratio (RR) and Blackman's formula:

$$R_{out} = \frac{R_{out-(\text{Controlled Source Gain}=0)} * (1 + RR_{\text{output port shorted}})}{(1 + RR_{\text{output port open}})}$$

(Assume $r_{ds} \rightarrow \infty$, R_i , R_o , and A_v are the input resistance, the output resistance, and the gain of the differential amplifier. Derive the relationship as a function of small-signal parameters, R_1 , R_2 , and A_v .)

Solution

For RR (Loop Gain), break the loop at the gate of mn1:

$RR_{\text{output port shorted}} = 0$ (amplifier A_v amplifies a "0" signal)

$RR_{\text{output port open}} = (v_{s1} / v_{g1}) (v_- / v_{s1}) (v_{g1}' / v_-) = (\text{CD gain}) (\text{Voltage divider}) (A_v)$


$$= \frac{g_{m1} (R_1 \parallel [R_i + R_2])}{1 + g_{m1} (R_1 \parallel [R_i + R_2])} \cdot \frac{R_i}{R_i + R_2} \cdot A_v$$

$$R_{out-(\text{Controlled Source Gain}=0)} = (1/g_{m1}) \parallel R_1 \parallel (R_2 + R_1)$$

$$= R_{out_open_loop} \text{ (open loop at gate of mn1)}$$


Thus:

$$R_{out} = \frac{(1/g_{m1}) \parallel R_1 \parallel (R_2 + R_1)}{1 + \frac{g_{m1} (R_1 \parallel [R_i + R_2])}{1 + g_{m1} (R_1 \parallel [R_i + R_2])} \cdot \frac{R_i}{R_i + R_2} \cdot A_v}$$

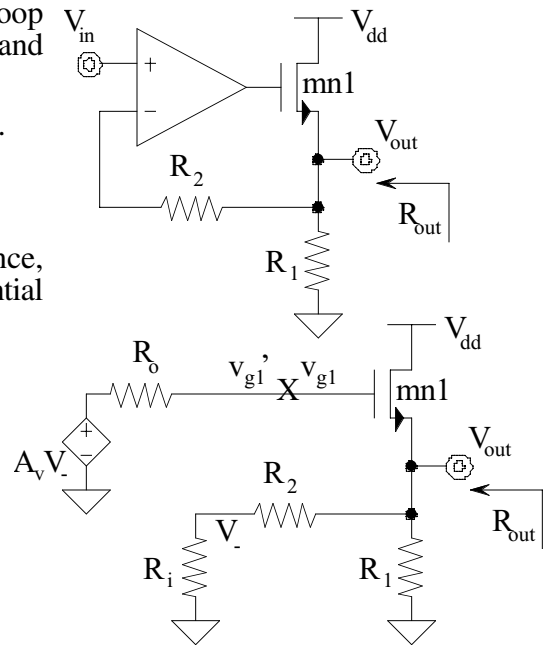

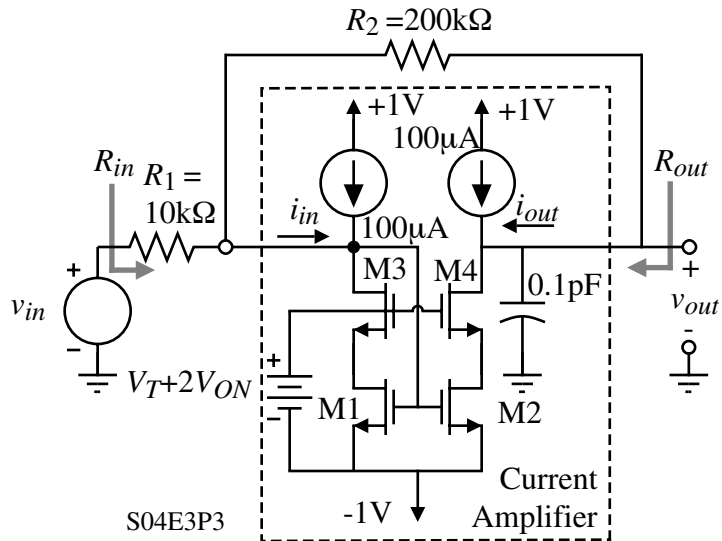Problem 3 - (25 points)

A voltage amplifier using feedback around a current amplifier is shown. In this problem assume all of the NMOS transistors are identical. Assume that R_1 is greater than the transistor transconductance and find the input resistance, R_{in} , the output resistance, R_{out} , the voltage gain, v_{out}/v_{in} , and the gainbandwidth (GB) in Hz. Assume that the output resistance connected to this voltage amplifier is large.



Solution

$$R_{in} \approx R_1 = \underline{10k\Omega}$$

$$R_{out} = \frac{v_t}{i_t}, \quad i_t = 2 \frac{v_{out}}{R_2} = 2 \frac{v_t}{R_2} \rightarrow R_{out} = \frac{v_t}{i_t} = \frac{200k\Omega}{2} = \underline{100k\Omega}$$

$$i_{in} \approx \frac{v_{in}}{R_1} + \frac{v_{out}}{R_2} \quad \text{and} \quad i_{out} \approx - \frac{v_{out}}{R_2}$$

Since $i_{in} = i_{out}$, we get

$$\frac{v_{in}}{R_1} + \frac{v_{out}}{R_2} = - \frac{v_{out}}{R_2} \rightarrow \frac{v_{in}}{R_1} = - 2 \frac{v_{out}}{R_2} \rightarrow \frac{v_{out}}{v_{in}} = - \frac{R_2}{2R_1} = \underline{-10V/V}$$

The dominant pole is found as,

$$P_{dominant} = \frac{1}{R_{out}C_{out}} = \frac{1}{100k\Omega \cdot 0.1pF} = 100 \times 10^6 \text{ rads/sec.}$$

$$\therefore GB = 10 \cdot 100 \times 10^6 \text{ rads/sec.} = 1000 \times 10^6 \text{ rads/sec.} \rightarrow GB = \underline{159.15MHz}$$

Note: Many tried to work this problem as a feedback problem (which it is) so the results would be achieved from a shunt-shunt feedback network as follows.

The feedback factor would be $f = -1/R_2$ and the amplifier gain would be

$$a = \frac{v_{out}}{i_{in}} = -R_2 \quad (\text{loop gain is } 1)$$

Therefore the closed loop gain would be

$$\frac{v_{out}}{i_{in}} = \frac{a}{1+af} = \frac{-R_2}{2}$$


The desired voltage gain would be

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{i_{in}} \frac{1}{R_{in}} = - \frac{R_2}{2R_1} = \underline{-10V/V}$$

The input resistance of the current amplifier is approximately zero, so feedback would give the correct input and output resistances calculated above.

Problem 4 - (25 points)

A differential CMOS amplifier using depletion mode input devices is shown. Assume that the normal MOSFETs parameters are $K_N' = 110\text{V}/\mu\text{A}^2$, $V_{TN} = 0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$ and for the PMOS transistors are $K_P' = 110\text{V}/\mu\text{A}^2$, $V_{TP} = 0.7\text{V}$, $\lambda_P = 0.04\text{V}^{-1}$. For the depletion mode NMOS transistors, the parameters are the same as the normal NMOS except that $V_{TN} = -0.5\text{V}$. (a.) What is the maximum input common-mode voltage, $V_{icm}^+(\text{max})$? (b.) What is the minimum input common-mode voltage, $V_{icm}^-(\text{min})$? (c.) What value of V_{DD} gives an $ICMR = 0.5V_{DD}$?

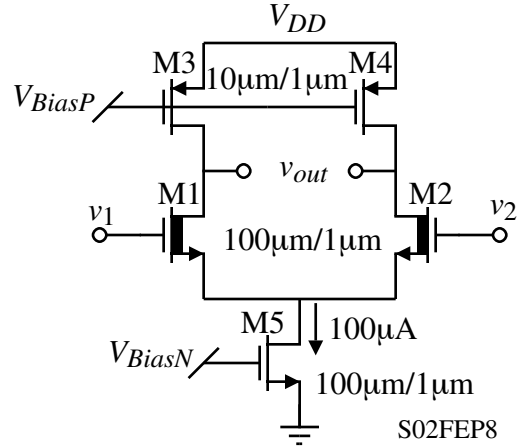Solution

$$(a.) \quad V_{icm}^+(\text{max}) = V_{DD} - V_{SD3}(\text{sat}) - V_{DS1}(\text{sat}) + V_{GS1}(50\mu\text{A})$$

$$i_D = \frac{\beta}{2} (V_{GS1} - V_{T1})^2 \rightarrow V_{GS1} = \sqrt{\frac{2i_D}{\beta}} + V_{T1} = V_{DS1}(\text{sat}) + V_{T1}$$

$$\therefore V_{icm}^+(\text{max}) = V_{DD} - V_{SD3}(\text{sat}) + V_{T1} = V_{DD} - \sqrt{\frac{2I_{D3}}{\beta_3}} + V_{T1}$$

$$V_{icm}^+(\text{max}) = V_{DD} - 0.3015 - 0.5 = \underline{\underline{V_{DD} - 0.8015}}$$

$$(b.) \quad V_{icm}^-(\text{min}) = V_{DS5}(\text{sat}) + V_{GS1}(50\mu\text{A}) = V_{DS5}(\text{sat}) + V_{DS1}(\text{sat}) + V_{T1}$$

$$V_{icm}^-(\text{min}) = \sqrt{\frac{2I_{D5}}{\beta_5}} + \sqrt{\frac{2I_{D1}}{\beta_1}} + V_{T1} = 0.1348 + 0.0953 - 0.5 = \underline{\underline{-0.2698\text{V}}}$$

$$(c.) \quad ICMR = V_{icm}^+(\text{max}) - V_{icm}^-(\text{min}) = V_{DD} - 0.8015 + 0.2698 = V_{DD} - 0.5317$$

$$\therefore V_{DD} - 0.5317 = 0.5V_{DD} \rightarrow V_{DD} = 2(0.5317) = \underline{\underline{1.063\text{V}}}$$